

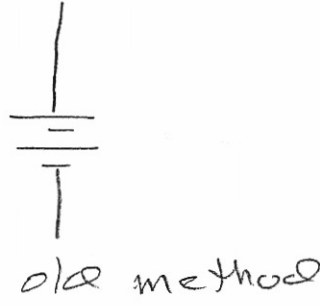
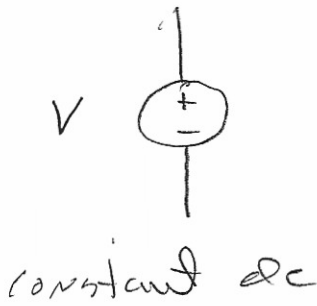


Ideal Voltage Sources


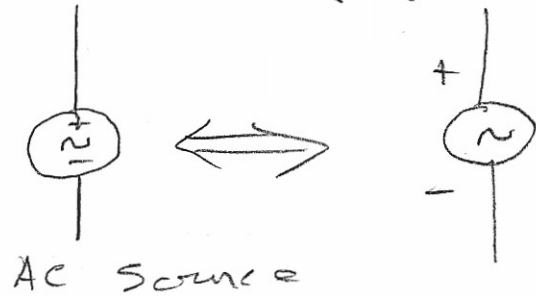
An ideal voltage source is one that would have no internal resistance. We denote such a source by



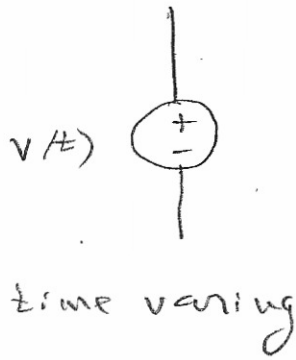How do you know the low resistance can use you with a dc battery?



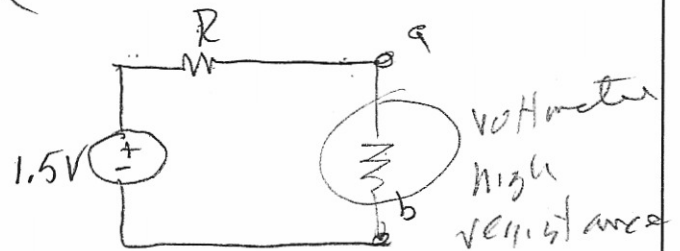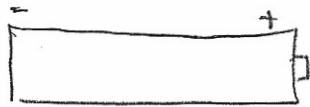A "fresh" battery, say a size D, AA, AAA would have very low internal resistance





R goes up as the battery ages.

An ideal voltage source can put out infinite current / power


Ideal current sources

These are harder to come by.

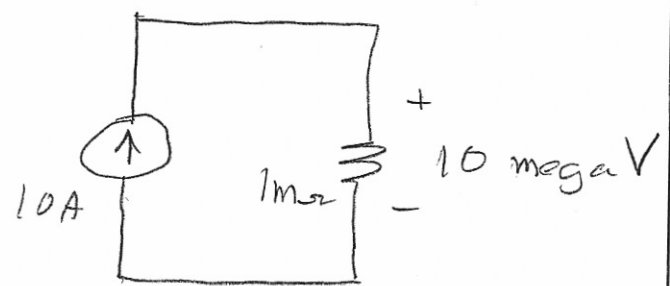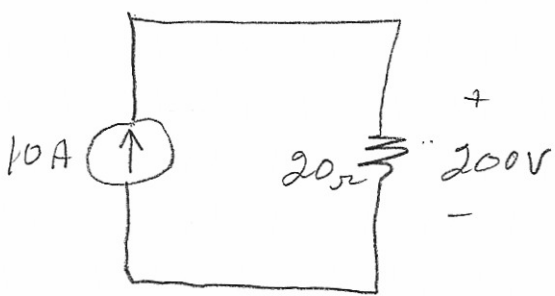

won't happen in reality.

What happens;

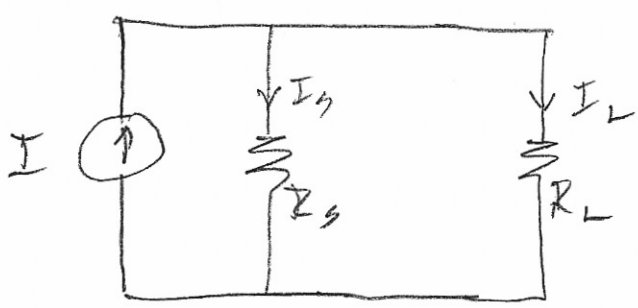


$$I_L = \frac{I \times R_s}{R_L + R_s} = \frac{I}{\frac{R_L}{R_s} + 1}$$

If $R_s \rightarrow \infty$, then $I_L = I$

Dependent (controlled) sources

These become important in electronics.

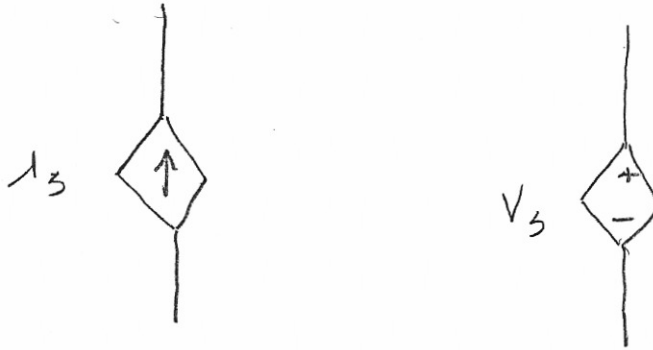


(always a diamond)

* The current source can be controlled by either a voltage or current somewhere else in the circuit.

The voltage source can be controlled by a current or voltage somewhere else in the circuit.

To illustrate:

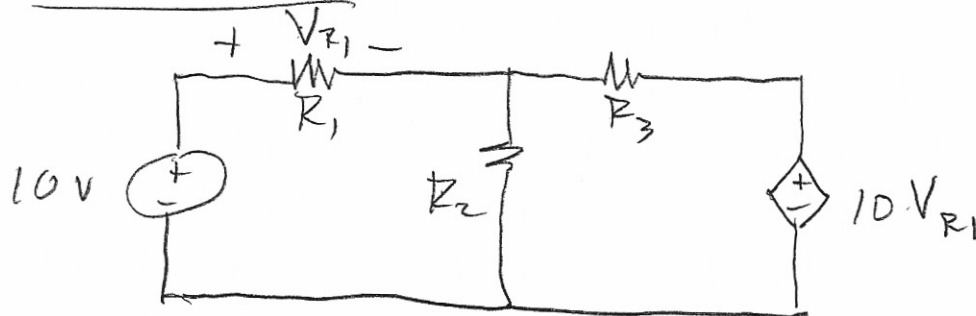

As categories

[Voltage controlled voltage source	VCVS	$V_s = k_1 V_x$
	Current controlled voltage	CCVS	$V_s = k_2 i_x$
[Current controlled current source	CCCS	$I_s = k_3 i_x$
	Voltage controlled current source	VCCS	$I_s = k_3 V_x$

Some Definitions

- Branch
- Node
- Loop
- Mesh


Branch: A branch represents a single element such as a voltage source or resistor. (represents a two terminal element)

Node: A point of connection between two or more branches.

Loop: Any closed path of a circuit. (cannot cross a node more than once)

$b = l + n - 1$
independent

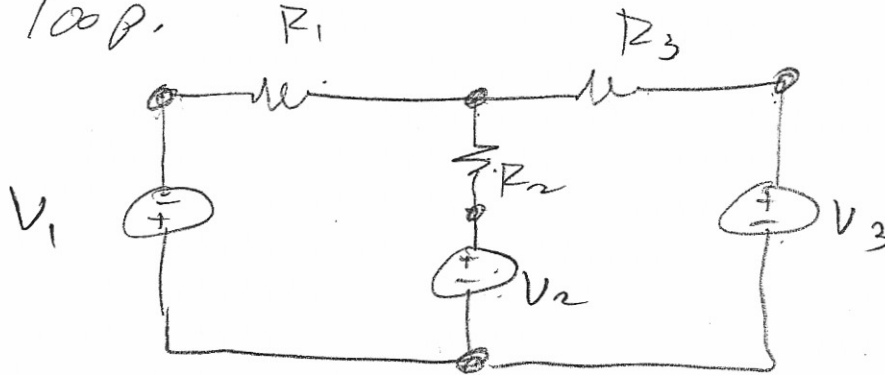A loop is independent if it contains at least one branch which is not a part of any other independent loop.



How many independent loops?

How many nodes?

How many branches?

$$b = l + n - 1$$

(l is independent loops)


Above: $l = 2$, $n = 5$

$$b = 2 + 5 - 1 = 6$$

Later, when we do nodal analysis,
I use essential node

If a part of a circuit has two or more elements in series we can usually treat this as a single branch.

Above;

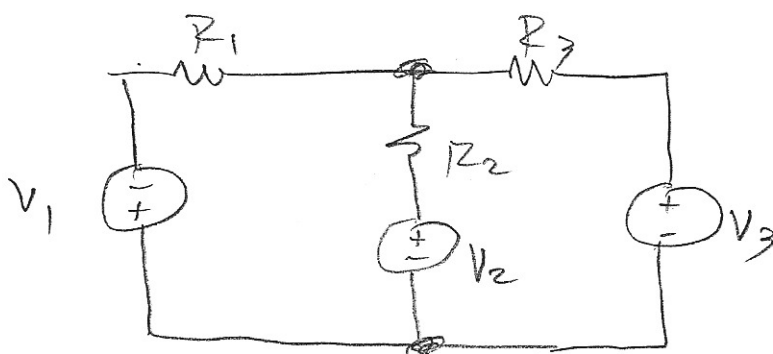

$$\# l = 2, \# n = 2$$

$$b = l + n - 1 = 2 + 2 - 1 = 3$$

Kirchhoff's LAWS

Three basic laws allow us to solve circuits.

- KCL
- KVL
- Ohm's Law


KCL:

Sum of currents (algebraic) entering a node = 0

Sum of currents (algebraic) leaving a node = 0

Sum of currents entering a node equal sum of currents leaving a node.

Find I_x, I_y, I_z, I_w

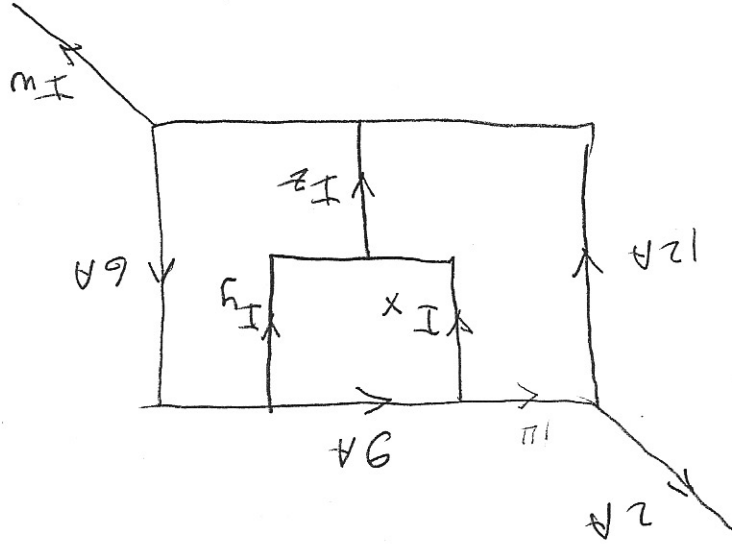

$$I_2 + I_4 = I_1 + I_3 + I_5$$


$$\sum \text{moments} = 0$$

$$I_2 + I_4 - I_1 - I_3 - I_5 = 0$$

$$\sum \text{moments} = 0$$

$$I_1 + I_3 + I_5 - I_2 - I_4 = 0$$

$$\sum \text{moments} = 0$$

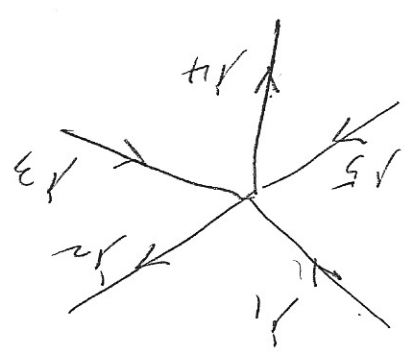

KVL

$$\sum_{m=1}^{m=N} V_m = 0$$


Sum of all voltage rises around a closed path = 0.

Sum of all voltage drops around a closed path = 0.

How do we define a voltage rise?

How do we define a voltage drop?

Consider

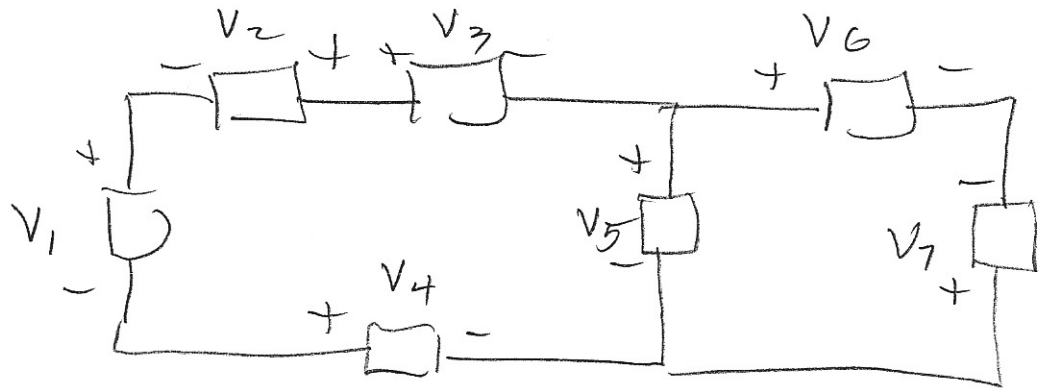

Write KVL around paths