

lecture 2

$i = \frac{\Delta q}{\Delta t}$ in the limit

$$i(t) = \frac{dq}{dt} \rightarrow \frac{\text{coulomb}}{\text{sec}}$$

$$v(t) = \frac{dw}{dq}$$

$$P = \frac{dw}{dt} = \frac{dw}{dq} \times \frac{dq}{dt} = v \times i$$

$$P = v \times i$$

W = P * t
KUL

Passive Sign Convention

If the assumed direction of the current enters the assumed positive polarity of a device, we say that the power absorbed is


$$P = +vi$$

abs

If the assumed direction of the current leaves the assumed positive polarity of a device we say that the power supplied is

$$P = -vi$$

sup

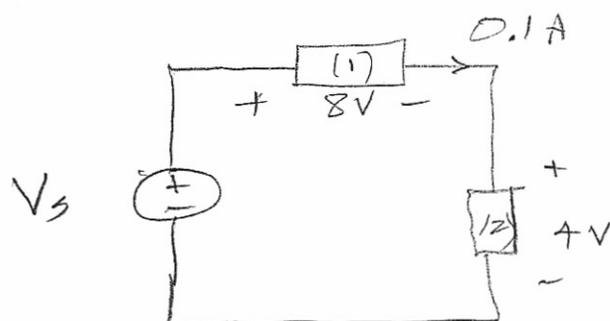EXAMPLE (c) 2.8

FIND the power absorbed by (1) & (2)
 FIND the power supplied by V_s .

We note

$$-V_s + 8 + 4 = 0$$

$$V_s = 12 \text{ V}$$

$$P_{\text{Abs (1)}} = 0.1 \times 8 = 0.8 \text{ W}$$


$$P_{\text{Abs (2)}} = 0.1 \times 4 = 0.4 \text{ W}$$

$$\Sigma P_{\text{Abs}} = 1.2 \text{ W}$$

$$P_{\text{Supp}} = 0.1 \times 12 = 1.2 \text{ W}$$

Example 2.9

GIVEN

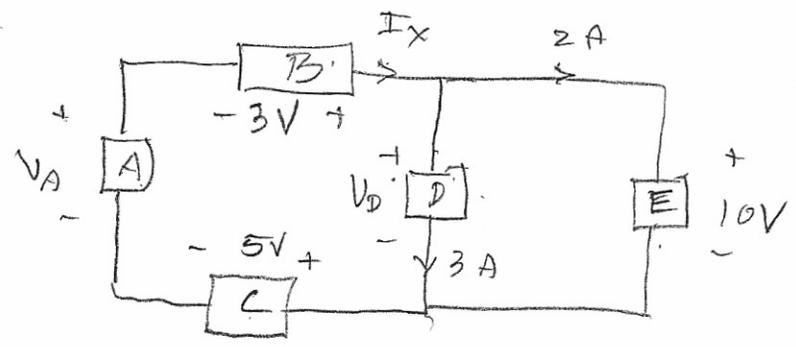

$$I_x = 5 \text{ A}$$

$$V_D = 10 \text{ V}$$

$$5 - V_A - 3 + 10 = 0$$

$$V_A = 12 \text{ V}$$

$P_{A \& B}$

(assume all are absorbing)
(A negative # means supplying)

$$P_A = -(5) \times (12) = -60 \text{ W}$$

$$P_B = (-3) \times (5) = -15 \text{ W}$$


supplied 75 W

$$P_C = 5 \times 5 = 25 \text{ W}$$

$$P_D = 3 \times 10 = 30 \text{ W}$$

$$P_E = 2 \times 10 = 20 \text{ W}$$

Absorbed 75 W

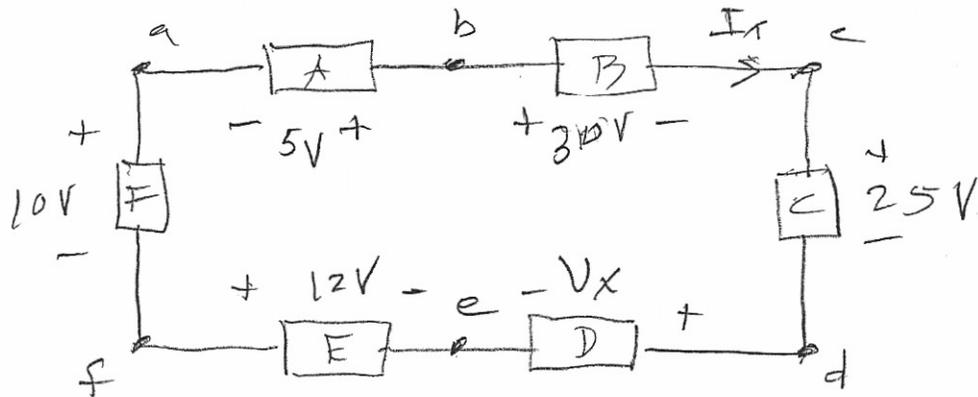Example

Given: power absorbed by c is 20 W.

(a) Find V_x

(b) Find I_x

(c) Find V_{ce}

$$\begin{array}{r} 55 \\ 27 \\ \hline 28 \end{array}$$

27

$$V_x - 12 - 10 - 5 + 30 + 25 = 0$$

$$V_x + 28 = 0$$

$$V_x = -28 \text{ V}$$





Since C absorbs,

$$P_c = 20 = I_x \cdot 25$$

$$I_x = 0.8 \text{ A}$$

We call V_{eb} double subscript notation. There are 3 common

ways we denote voltage

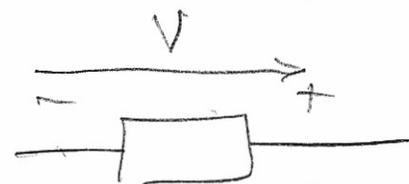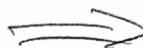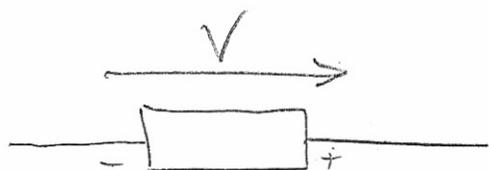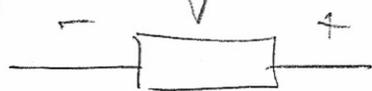

Now find V_{ce} .

We assume c is positive with respect to e .

We can write

$$+V_{ce} - V_{de} - V_{cd} = 0$$

$$V_{ce} = V_{de} + V_{cd} = -28V + 25 = -3V$$

$$V_{ce} = -3V$$

OR

$$V_{te} + V_{af} + V_{ba} + V_{cb} - V_{ce} = 0$$


$$V_{ce} = V_{te} + V_{af} + V_{ba} + V_{cb}$$

$$= 12 + 10 + 5 - 30$$


$$V_{ce} = -3V$$

check

Ohm's LAW

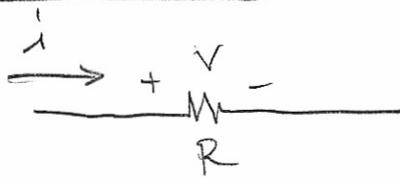


$$V = +iR$$

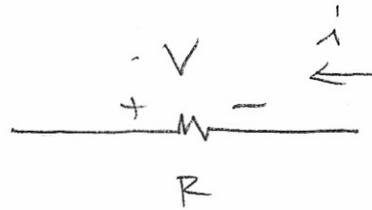

$$V = -iR$$

How does this work?

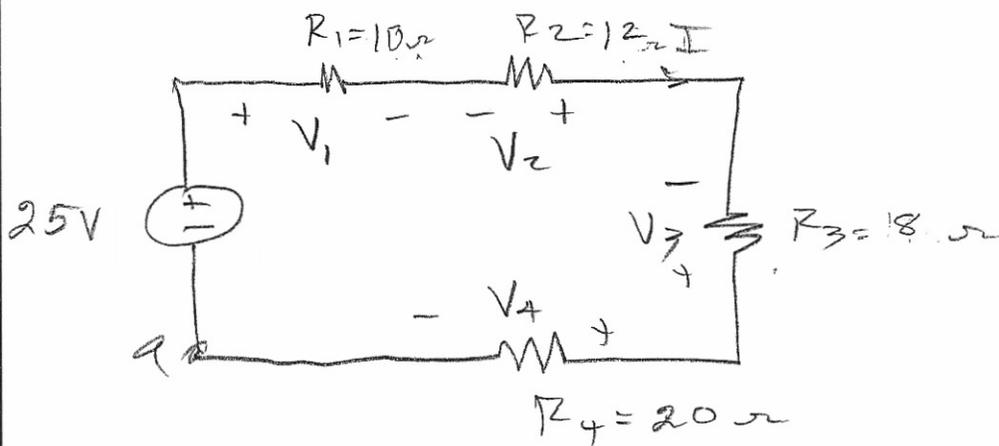

FIND I

FIND V_1, V_2, V_3, V_4

$\sum \Delta_{\text{drops}} = 0$, cw start at a

$$-25 + V_1 - V_2 - V_3 + V_4 = 0$$

$$-25 + 10I - (-12I) - (-8I) + 20I$$

$$(10 + 12 + 8 + 20)I = 25$$

$$50I = 25$$

$$I = 0.5 \text{ A}$$


Now we can calculate any of the voltages.

$$V_1 = +IR_1 = 0.5 \times 10 = 5V$$

$$V_2 = -12I = -12 \times 0.5 = -6V$$

What does this mean?

Default sign convention.

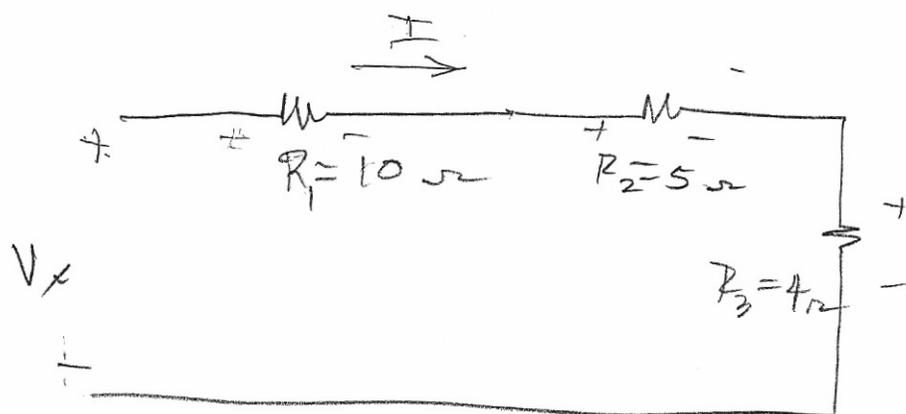

Says that you assume voltage is positive at the terminal where the current enters the element.

$$-V_x + 10I + 5I + 4I = 0$$

$$V_x = 19I$$