

Stepping Back And Looking At ThingsCurrent:

$$i = \frac{\Delta Q}{\Delta T} \rightarrow \frac{\text{coulombs}}{\text{second}}$$

$$i = \frac{dq}{dt}$$

Knows KCL and how to use

Voltage

$$V = \frac{\Delta W}{\Delta Q} \Rightarrow \frac{\text{Joules}}{\text{Coulomb}}$$

$$V = \frac{dW}{dq}$$

Power

$$P(t) = \frac{dW}{dt}$$

$$W = \int P dt$$

(This is how we pay)

Watt-Hours

KWH about 6¢


per KWH

$$P = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt}$$


$$P = Vi$$

We will come back to this shortly.

### Ohm's Law

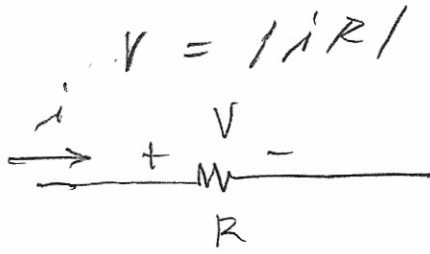

$$V = +iR$$

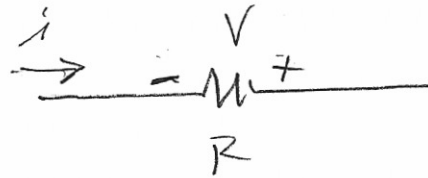

$$V = -iR$$

### Now Go Back To Power

$$P = Vi$$

$$\text{(let } V = iR)$$

$$= iRi$$

$$P = i^2 R$$

$$P = Vi \quad \text{(let } i = \frac{V}{R})$$

$$= V \cdot \frac{V}{R}$$

$$P = \frac{V^2}{R}$$


so;

$$P = Vi = i^2 R = \frac{V^2}{R}$$

Know how to use

The so-called Passive Sign Convention for power.

Consider any electrical circuit

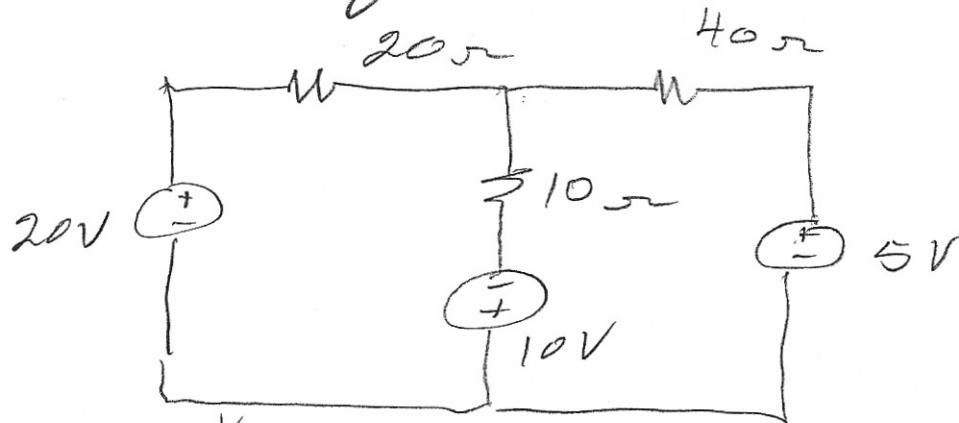

We are <sup>not</sup> quite ready to solve this circuit right now but what we can say is

$$\sum P_{\text{supplied}} = \sum P_{\text{absorbed}} \quad (1)$$

$$\text{OR} \quad \sum P_{\text{supplied}} = 0 \quad (2)$$


$$\sum P_{\text{absorbed}} = 0 \quad (3)$$

(2) & (3) must accommodate both  $\pm$  supplied and absorbed.

How is this done? Answer, by how we define each one.

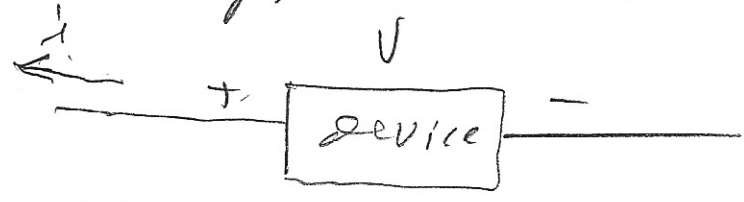
### • Power Supplied

Given a device and polarity assumptions as below



$$P_{sup} = +Vi$$


If either V or i is reversed:

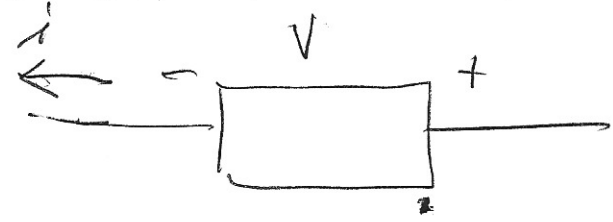


$$P_{sup} = -Vi$$

### • Power Absorbed

Same scenario;

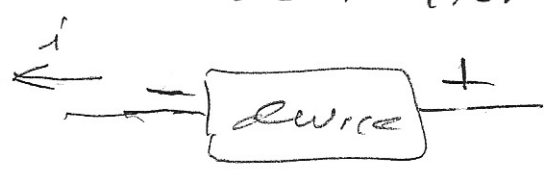


$$P_{abs} = +Vi'$$

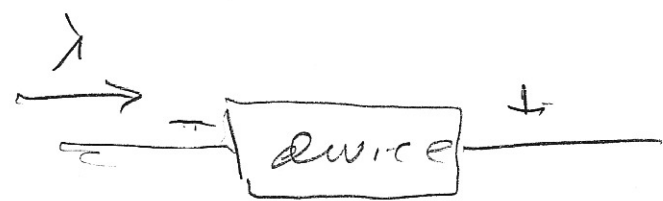

$$P_{abs} = -Vi'$$
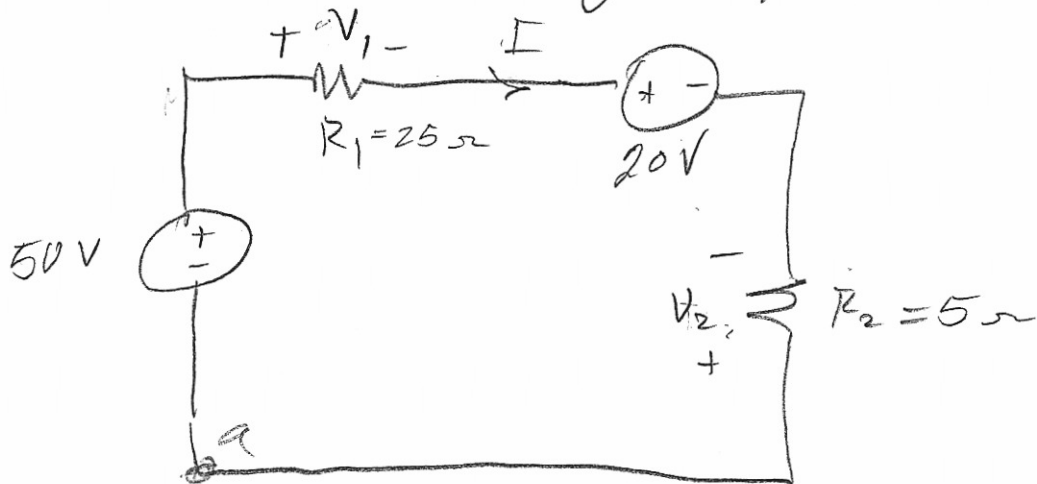
## Example

- Solve for  $V_1$ ,  $V_2$  below.
- Find  $P_{sup}$  by each source
- Find  $P_{abs}$  by  $R_1$ ,  $R_2$



$\Sigma \text{drops} = 0$ , start at "a", go cw.

$$\rightarrow 50 + V_1 + 20 - V_2 = 0 \quad \text{KVL}$$

but ohm's law

$$V_1 = 25I$$

$$V_2 = -5I$$

$$25I - (-5I) = 50 - 20$$

$$30I = 30$$

$$I = 1 \text{ Amp}$$

$$P_{\text{sup}}_{50} = 50I = 50W$$

$$P_{\text{sup}}_{20} = -20I = -20W$$

$$P_{\text{abs}}_{25} = I^2 R = 25W$$

$$P_{\text{abs}}_5 = 1 \times 5 = 5W$$

$$\Sigma P_{\text{sup}} = \Sigma P_{\text{abs}}$$


$$50 - 20 = 5 + 25 \quad \text{check}$$

### Resistance



$$G, \text{ conductance} = \frac{1}{R}, \text{ Sieman (S)}$$

CONV. CIR.

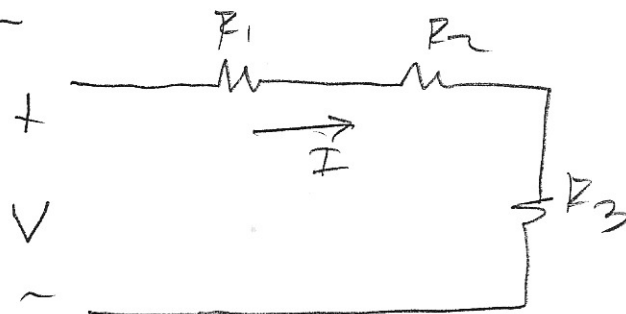


Default. Sign convention.

Assume  $V_R$  is + at the terminal where  $I$  enters; we have

$$-V + IR_1 + IR_2 + IR_3 = 0$$


$$\frac{V}{I} = R_1 + R_2 + R_3$$

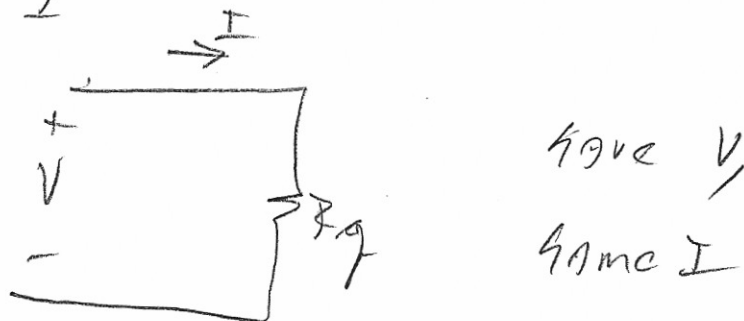

$$\frac{V}{I} = R_{eq} = R_1 + R_2 + R_3$$

Resistors in series add.

### Voltage Division Rule

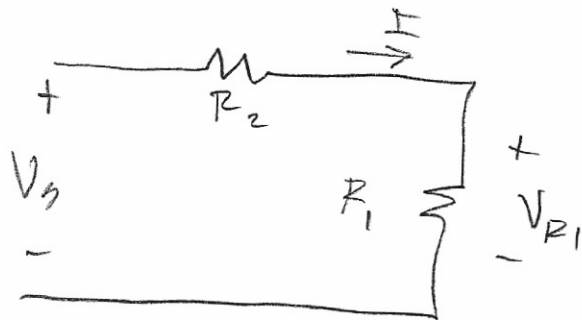

$$I = \frac{V_s}{R_1 + R_2}$$


$$V_{R1} = I R_1 = \frac{V_s R_1}{R_1 + R_2}$$

o The Rule in words



$V_{R_1}$  is equal to source voltage,  $V_s$ , times  $R_1$  divided by  $R_1 + R_2$ .

Simple Example,

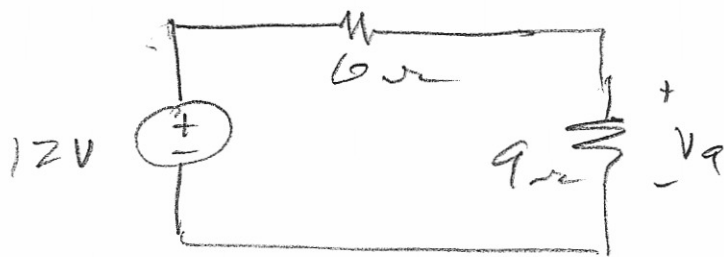


$$V_9 = \frac{12 \times 9}{9 + 6} = \frac{12 \times 9}{15} = 7.2 \text{ V}$$

$$V_6 = \frac{12 \times 6}{9 + 6} = 4.8$$


$$12 = V_6 + V_9 = 7.2 + 4.8 = 12 \text{ V}$$

You should observe the following:



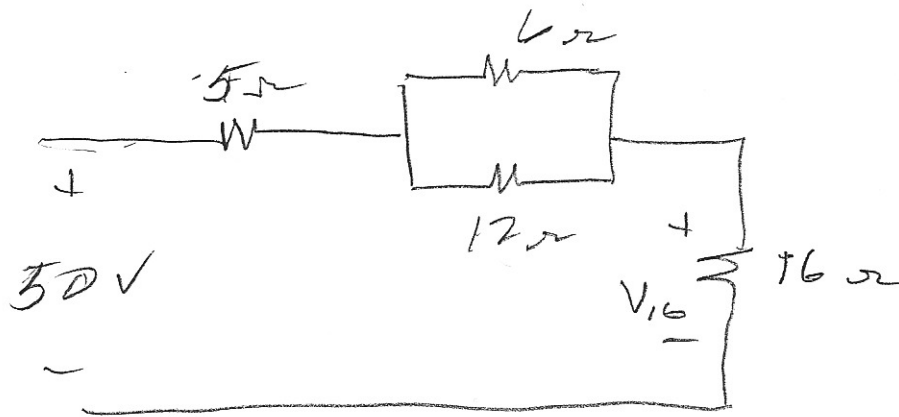

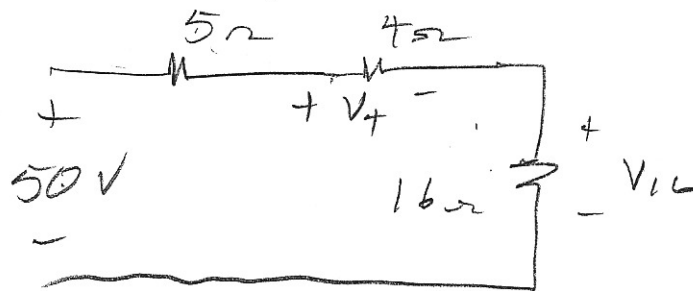Find  $V_{16}$  using Voltage division;  
change to;




$$V_{16} = \frac{50 \times 16}{25} = 32 \text{ V}$$

$$V_4 = \frac{50 \times 4}{25} = 8 \text{ V}$$

etc,

This is handy. Saves time.  
Used very often in circuits

# Resistors In Parallel

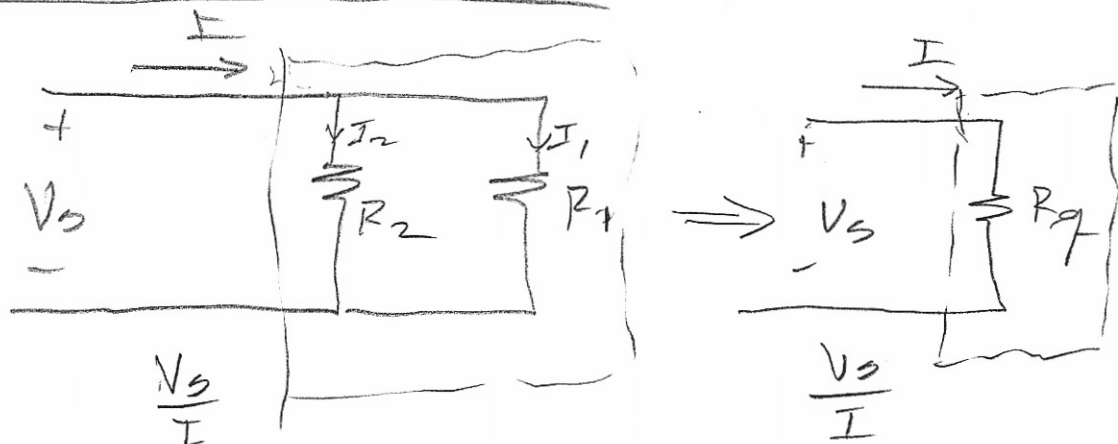

$$I_1 = \frac{V_s}{R_1} \quad , \quad I_2 = \frac{V_s}{R_2}$$

$$I = I_1 + I_2$$

$$I = V \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] \quad \cdot \quad I = V \left[ \frac{1}{R_{eq}} \right]$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (13)$$


$$G_{eq} = G_1 + G_2 \quad (14)$$

From 3

$$\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad (\text{Product divided by sum})$$

• Current splitting or current division,

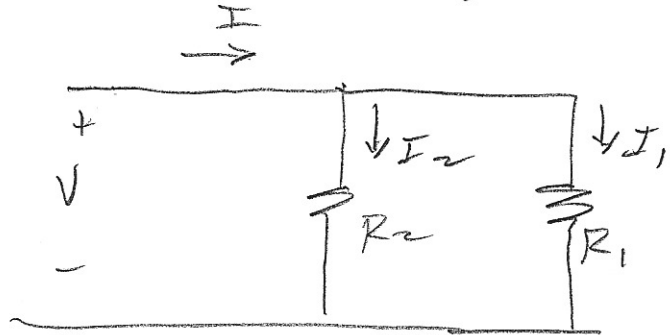

$$I_1 = \frac{V}{R_1} = \frac{I R_{eq}}{R_1} = \frac{I R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{I \times R_2}{R_1 + R_2}$$


Similarly we can show

$$I_2 = \frac{I \times R_1}{R_1 + R_2}$$

Words

$I_1$  equals incoming current multiplied by opposite resistor, divided by the sum of the resistance.

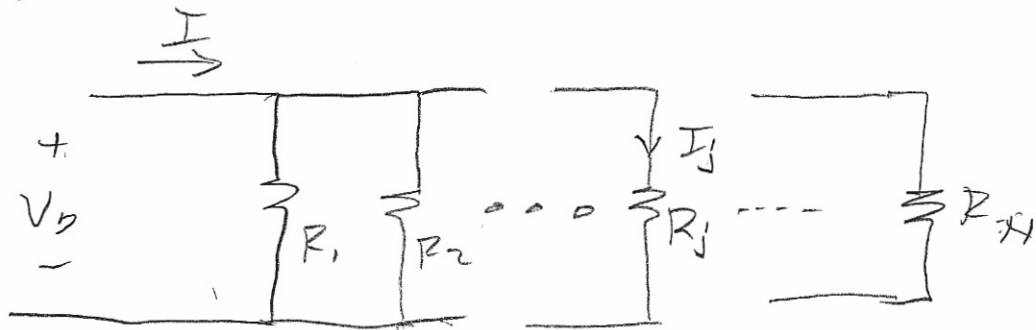
A general expression, any number of resistors,



$$I_j = \frac{I \times R_{eq}}{R_j}$$

Example

Find  $I_{12}$  below  
 $2A$

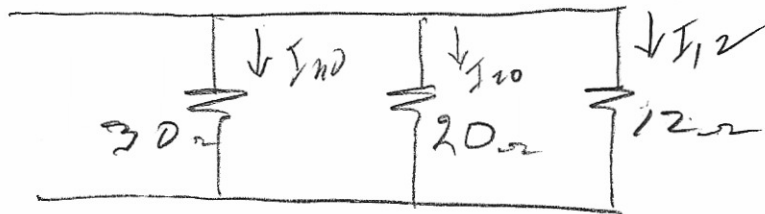

Find  $R_q$  ;

$$\frac{30 \times 20}{30 + 20} = \frac{600}{50} = 12\Omega$$

$$R_q = \frac{12 \times 12}{12 + 12} = 6\Omega$$

$$I_{12} = \frac{2 \times R_{eq}}{12} = \frac{R_{eq}}{6} = \frac{6}{6} = 1 \text{ A}$$

How much is  $I_{20}$ ,  $I_{30}$ ?


$$I_{20} = \frac{12 \text{ V}}{20} = \frac{6}{10} = 0.6 \text{ A}$$

$$I_{30} = \frac{12 \text{ V}}{30} = \frac{6}{15} = \frac{2}{5} = 0.4 \text{ A}$$

$$I_s = I_{10} + I_{20} + I_{30} = 1 + 0.6 + 0.4 = 2 \text{ A}$$


$2 \text{ A}$

### Combination of Resistance

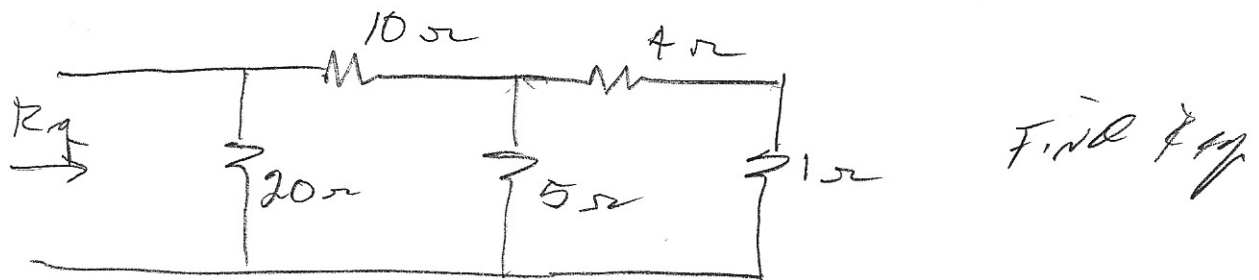

First a comment:

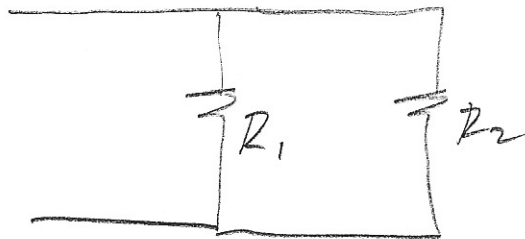The equivalent resistance of two resistors in parallel is always less than the smallest resistor.



Let  $R_2 < R_1$

$$R_2 = k R_1, \quad 0 < k < 1$$

$$R_q = \frac{R_1 R_2}{R_1 + R_2} = \frac{(R_1)(k R_1)}{R_1 + k R_1}$$

$$R_q = \frac{k R_1}{1 + k} = \frac{R_1}{1 + \frac{1}{k}}$$


$$1 + \frac{1}{k} > 1, \quad \text{so}$$

$$R_q < R_1 \quad (\text{smallest resistor})$$


What if  $R_1 = R_2$

$$R_q = \frac{R_1 R_1}{R_1 + R_1} = \frac{R_1}{2}$$

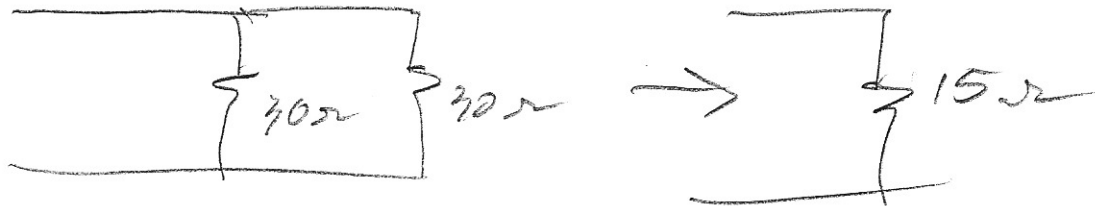$R_q$  for 2 resistors in parallel of the same value is half the resistor



For the previous problem

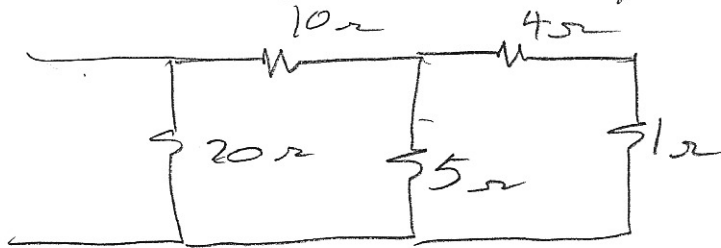

Generally, start at the right and work left.

$$5 \parallel 5 = 2.5$$


$$R_q = (10 + 2.5) \parallel 20$$

$$R_q = \frac{12.5 \times 20}{12.5 + 20}$$

$$R_q = 7.69 \Omega$$

Example 2.32

Given the following

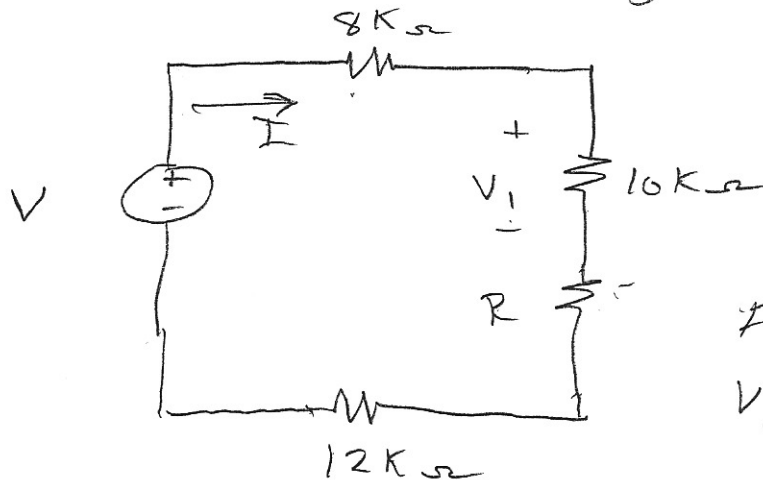

Find:

$V_1, V, R$

Given: Power supplied = 40 mW

$$V_1 = \frac{V}{11}$$

$$VI = 40 \times 10^{-3} \quad (a)$$

$$V_1 = \frac{V}{4} = 10 \times 10^{-3} I \quad (b)$$

no

$$V = 40 \times 10^{-3} I$$

subst. into (a)

$$40 \times 10^{-3} I^2 = 40 \times 10^{-3}$$

$$I = 1 \times 10^{-3} = 1 \text{ mA}$$

$$V = \frac{40 \times 10^{-3}}{1 \times 10^{-3}} = 40 \text{ V}$$

$$V_1 = \frac{V}{4} = 10 \text{ V}$$


$$V_1 = 10 \text{ V}$$

$$V_1 = RI = 1 \times 10^{-3} R = 10$$

$$R = \frac{10}{1 \times 10^{-3}} = 10 \text{ k}\Omega$$

$$R_1 = 10 \text{ k}\Omega$$

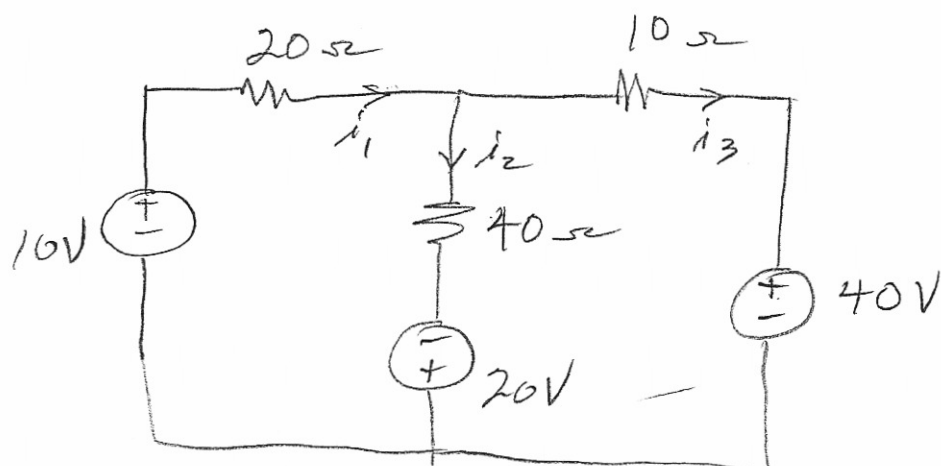

Example

FIND  $i_1$ ,  $i_2$ ,  $i_3$  IN THE CIRCUIT  
below.

using default convention.

$$-10 + 20i_1 + 40i_2 - 20 = 0$$

$$20i_1 + 40i_2 + 0i_3 = 30$$

$$20 - 40i_2 + 10i_3 + 40 = 0$$

$$0i_1 - 40i_2 + 10i_3 = -60$$

$$-i_1 + i_2 + i_3 = 0$$

$$\begin{bmatrix} 20 & 40 & 0 \\ 0 & -40 & 10 \\ -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 30 \\ -60 \\ 0 \end{bmatrix}$$

$$i_1 = -0.643 \text{ A} \quad i_2 = 1.0714 \text{ A}, \quad i_3 = -1.7143 \text{ A}$$

By mesh

$$\begin{bmatrix} 100 & -40 \\ -40 & 50 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 30 \\ -60 \end{bmatrix}$$

$$\overset{\uparrow}{i_1} = -0.643 \text{ A}, \quad \overset{\uparrow}{i_2} = i_3 = -1.7143 \text{ A}$$

OK.