

## Reverse recovery in a two-phase buck converter

Figure 1 shows a two-phase buck converter. The output capacitance  $C$  is large enough such that negligible ripple is present during operation. The input voltage  $V_g$  is 12 V and the output voltage  $V$  is 1 V. Both converters are operated with the same duty cycle,  $D$ , and switching frequency  $f_s$ . The two MOSFETs conduct for  $0 < t < DT_s$

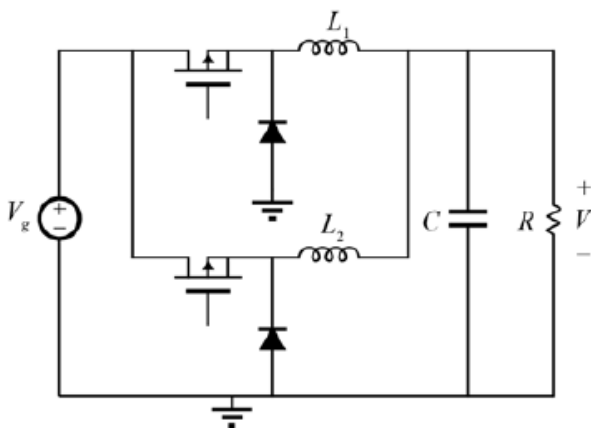


Figure 1: Two-phase buck converter

- (a) Assuming  $L_1$  and  $L_2$  are equal in value and are large enough such that small-ripple approximations apply, solve for the duty cycle of the converters,  $D$ .

For (c-d), both converters transfer 20 W of power each to the load resistor. The diodes are identical and are ideal except for their reverse recovery characteristics, which are shown in Figure 2. During MOSFET turn-on, the ramp rate of the diode current is found to be  $|di_F/dt| = 800 \text{ A}/\mu\text{s}$ .

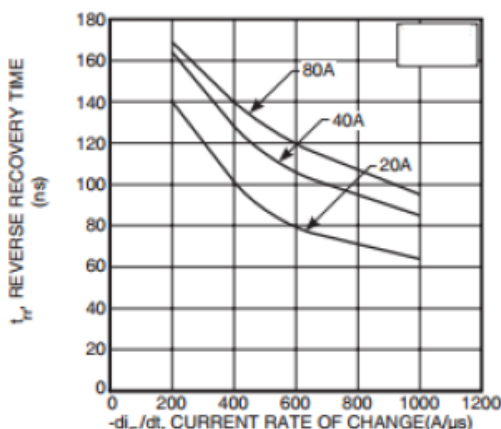


Figure 3. Reverse Recovery Time vs. Current Rate of Change

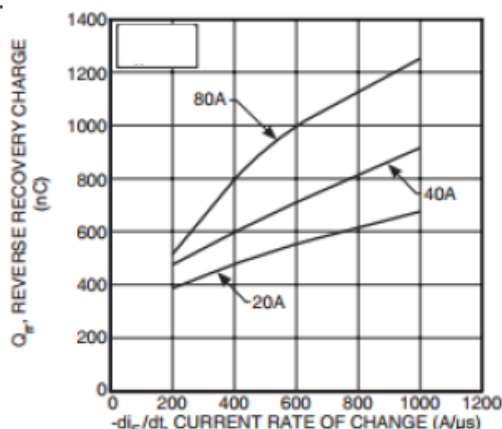


Figure 4. Reverse Recovery Charge vs. Current Rate of Change

Figure 2: Diode reverse recovery characteristics

- (b) Solve for energy loss of the two-phase converter during each switching period  
 (c) Select the maximum switching frequency of the converter  $f_s$  so that the converter efficiency is greater than 95%  
 (d) At the switching frequency solved in (c), find values for the inductances  $L_1 = L_2$  such that each inductor has 10% current ripple.