

### Switching Loss Estimation in a Buck-Boost Converter

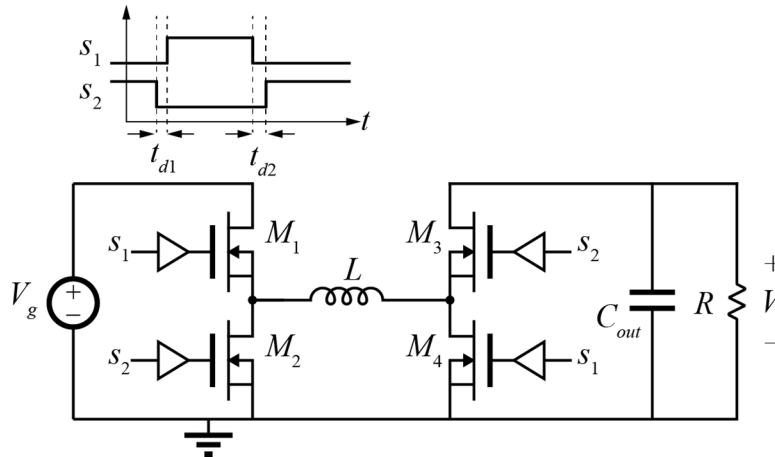


Figure 1: Noninverting Buck-Boost Converter

The noninverting buck-boost converter of Fig. 1 is switched using the given logic-level signals,  $s_1$  and  $s_2$ . The topology is used to design a power converter with the following characteristics

- Input voltage  $V_g = 400$  V
- Output voltage  $V = 200$  V
- Output resistance  $R = 40$
- Switching frequency  $f_s = 500$  kHz

All devices,  $M_1$ - $M_4$ , are implemented with a silicon MOSFET. Its parasitics are summarized in the attached datasheet. Note that, as with all datasheets, not all of the information contained is explicitly necessary for the calculations here. Consider a “slow” gate driver with  $V_{GS} = 10$  V and  $I_g = 1$  A. Both  $L$  and  $C_{out}$  are large. The dead times are longer than any switching transient dynamics, but you may assume that  $t_{d1} + t_{d2} \ll T_s$ .

- a) Neglecting all nonidealities and losses, solve for the converter duty cycle  $D$ , which is the portion of each switching period in which  $s_1$  is high.
- b) Solve for the conduction loss due to devices' on-resistance.
- c) Sketch the drain-to-source voltage, gate-to-source voltage, and drain current of the following MOSFETs during the specified transition. Label all salient features
  - i)  $M_1$  turn on
  - ii)  $M_3$  turn on
- d) Solve for the total switching loss due to (if applicable)
  - i) device output capacitance  $C_{oss}$
  - ii)  $v$ - $i$  overlap due to the gate drive
  - iii) gate switching
  - iv) reverse recovery of the devices' body diodes
- e) Solve for the total power dissipation of each individual device,  $M_1$ - $M_4$
- f) Estimate the power required from a 10 V auxiliary supply for this circuit.