

Steady-State Analysis of a Time-Invariant SRC

In this problem, consider the same time-invariant SRC from Homework #2, shown in Fig. 1 and Fig. 2. You may re-use your state space description from Homework #2, or use the model posted in the solutions. Note that **A** is non-singular.

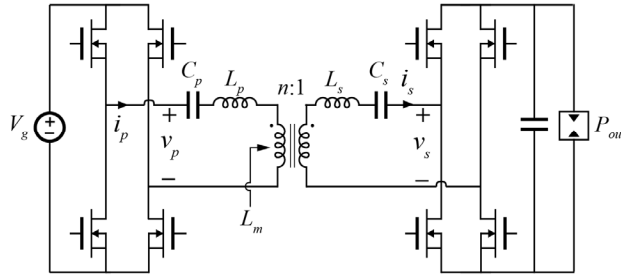


Fig. 1: Series Resonant Converter

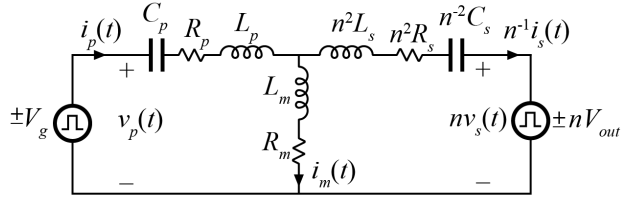


Fig. 2: Time-Invariant Circuit Model of SRC

Given an initial condition vector for the states at the beginning of a switching period $\mathbf{X}_0 = \mathbf{x}(t=0)$, the states $\mathbf{X}_\varphi = \mathbf{x}(t=t_\varphi)$ are given by

$$\mathbf{X}_\varphi = e^{A t_\varphi} \mathbf{X}_0 + \mathbf{A}^{-1} (e^{A t_\varphi} - \mathbf{I}) \mathbf{B} u_1$$

- Using the same approach, write an expression which uses an initial condition $\mathbf{X}_0 = \mathbf{x}(t=0)$ to solve the states at $t = T_s/2$
- Using results from (a), write a closed expression form expression for \mathbf{X}_0 in steady-state for any given t_φ
- Using the results from (b) and the knowledge that **A** is non-singular, write a closed-form (algebraic) expression for the average input and output dc power as a function of the results (a), (b), and \mathbf{X}_φ

Using the above analysis (and without employing `lsim()` or any other time-stepping integration), examine the following in MATLAB

- Generate a single plot of the output power and efficiency that the converter exhibits in steady state for $0 < t_\varphi < T_s/2$ for the following converter implementation (from Homework 2).

C_p	R_p	L_p	L_m	R_m	$n^2 L_s$	$n^2 R_s$	$n^2 C_s$	V_g	nV_{out}	f_s	t_φ^\dagger	n
30 nF	.2 Ω	10 μ H	10 μ H	.1 Ω	10 μ H	.2 Ω	30 nF	20 V	20 V	200 kHz	$T_s/4$	4

[†] See Fig. 3 for waveform timing definitions

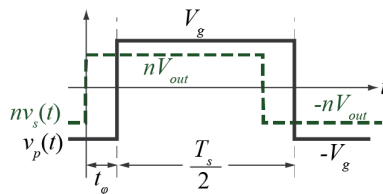


Fig. 3: Input waveform timing definitions