

### Small Signal Discrete Time Modeling of a DCM Buck Converter

In this problem, you will investigate the control-to-output transfer function of a 12-to-3 V Buck converter shown in Fig. 1

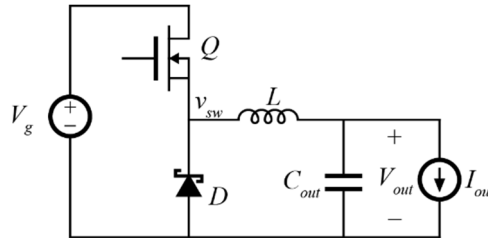


Fig. 1: Buck Converter

Table I: Converter design specification

$r_{on,Q}$	$r_{on,D}$	$f_s$	$L$	$V_g$	$I_{load}$	$C_{out}$
10 m $\Omega$	10 m $\Omega$	500 kHz	1 $\mu$ H	12 V	1 A	10 $\mu$ F

When conducting, the diode and MOSFET can be modeled as on-resistances of value  $r_{on,D}$  and  $r_{on,Q}$ , respectively. When not conducting, both can be modeled as ideal open-circuits.

Derive the control-to-output transfer function  $G_{vd}(z)$  from  $d(t)$  to  $V_{out}$ . An ADC samples the output voltage at the instant the MOSFET turns on, with zero conversion delay.

- Find the steady-state duty cycles  $D$  and  $D_2$  of the converter such that the output voltage is  $V_{out} = 3$  V and diode conduction is correctly modeled, where  $D$  is the duty cycle of MOSFET conduction and  $D_2$  is the duty cycle of diode conduction.
- Derive the traditional averaged model of the control-to-output transfer function  $G_{vd,avg}(s)$ .
- Derive a generalized state space model of the system of the form

$$\begin{aligned} x[k+1] &= f(x[k], u[k], D[k], w[k]) \\ 0 &= \sigma(x[k], u[k], D[k], w[k]) \end{aligned}$$

Give full realizations of both equations, and state explicitly what auxiliary variable(s) are included in  $w[k]$

- Solve the system in (c) to obtain a complete discrete time small-signal model of the DCM buck converter. Give expressions for each matrix/vector in terms of the state space models of the converter.
- On the same axes, produce a bode plot of the averaged model  $G_{vd,avg}(s)$  and your discrete time model  $G_{vd}(z)$ , using the built-in discrete time conversion in the `bode()` function. Comment on any differences.