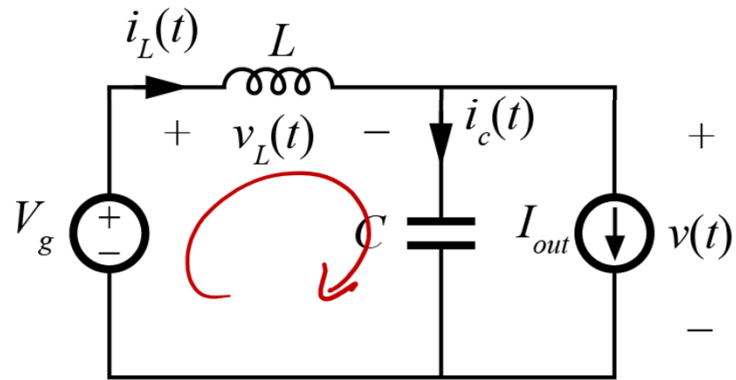


Example State Space Parsing



$$\begin{bmatrix} C & 0 \\ 0 & L \end{bmatrix} \frac{d}{dt} \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \cdot \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ I_{out} \end{bmatrix}$$

Simple case:


- ^ "well-formed" LTI circuit
- All C & L are states
- No resistors in the circuit

Goal: express

$$v_L = f(v_c, V_g) \rightarrow \text{KVL w/ } V_x, v_c \text{ \& } 1 \text{ other element}$$

$$i_c = f(i_L, I_{out}) \rightarrow \text{KCL w/ } I_x, i_L \text{ \& } 1 \text{ other element}$$

Component Partitioning

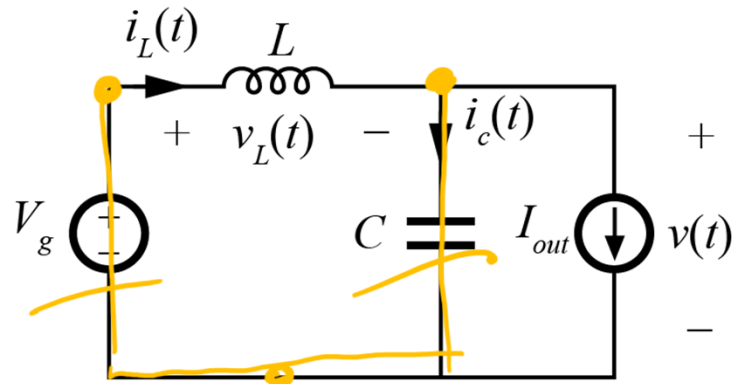


Graph / Network Theory

Tree: subset of all circuit elements ("branches") that includes every node but has no loops

co-Tree: All elements not in the tree ("links")
 - Tree + any one link forms a loop

→ If we form a tree with only V & C components
 can write every voltage on link element as $\sum V_x$ & V_c

Incidence Matrix

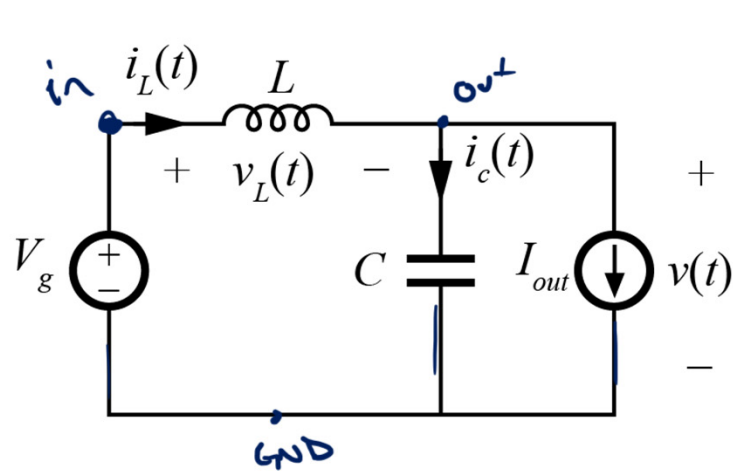

		Components		
		C	L	I _{out}
Nodes	in	∅	1	∅
	GND	-1	∅	-1
	out	∅	-1	1

→ Incidence Matrix A₀


Rows tell all of the components connected at each node, so

$$A_0 i = \phi$$

All KCL at each node

$$i = \begin{bmatrix} I_g \\ i_c \\ i_L \\ I_{out} \end{bmatrix}$$

Loop Matrix

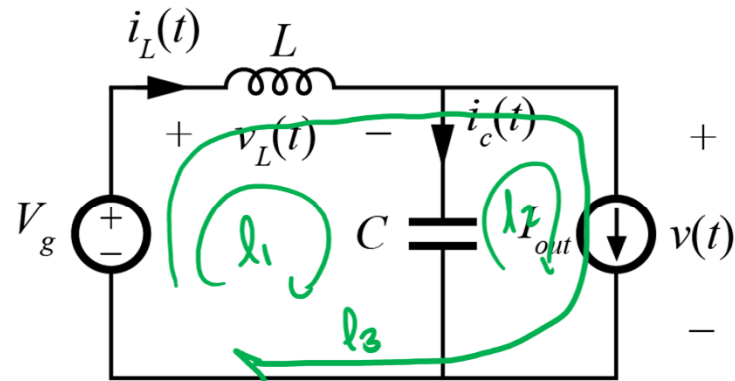

$$B_0 v = \phi$$


$$v = \begin{bmatrix} v_g \\ v_c \\ v_L \\ v_{out} \end{bmatrix}$$

components

loops

$$\begin{bmatrix} l_1 \\ l_2 \\ l_3 \end{bmatrix} \begin{bmatrix} v_g & c & L & I_{out} \\ -1 & 1 & 1 & \phi \\ 0 & -1 & 0 & 1 \\ -1 & \phi & 1 & 1 \end{bmatrix} = B_0$$

Selecting a Tree

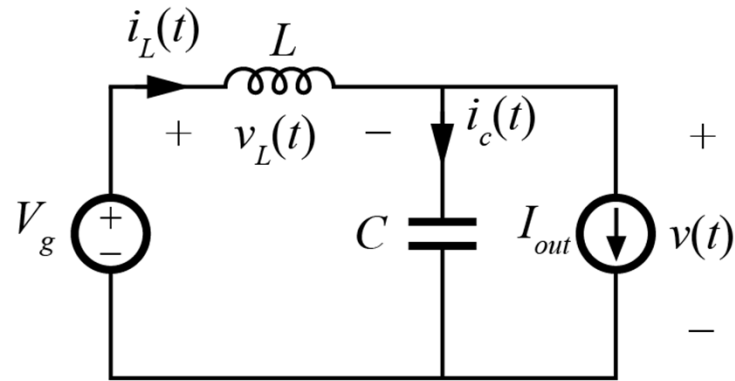

$$A_0 = \begin{matrix} \text{in} \\ \text{GND} \\ \text{out} \end{matrix} \begin{bmatrix} v_g & C & L & I_{out} \\ - & 0 & 1 & 0 \\ 0 & 1 & -1 & 1 \end{bmatrix}$$

Reduce A_0 to row echelon form

- In MATLAB `rref()`
- Apply elementary row operations to generate an upper triangular matrix with 1 for all pivots

Tree ←

$$A = \left[\begin{array}{cc|cc} v_g & C & L & I_{out} \\ 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 1 \end{array} \right]$$

Components (columns) associated are the tree

with first non-zero element in each row (pivots)

Partitioning

$$A = \begin{bmatrix} A_T & A_L \end{bmatrix}$$

tree co-Tree

$$B = \begin{bmatrix} B_T & B_L \end{bmatrix}$$

In simplest case:

$$A_T = I \rightarrow$$

get an equation for current through all tree components as a function of co-Tree currents

$$B_L = I \rightarrow$$

(flip columns before ref)

get equation for voltage on all co-Tree components as function of only tree voltages

$$(\text{Any row of } A) * (\text{Any row of } B)^T = \phi, \quad AB^T = \phi$$

if loop to node
don't share any elements

= zero ✓



$$AB^T = \phi$$

$$\begin{bmatrix} A_T & A_L \end{bmatrix} \begin{bmatrix} B_T^T \\ \vdots \\ B_L^T \end{bmatrix} = \phi$$

$$D = A_T^{-1} A$$


$$B = \begin{bmatrix} B_T & I \end{bmatrix}$$

$$= \begin{bmatrix} (-A_T^{-1} A_L)^T & I \end{bmatrix}$$


$$\begin{bmatrix} A_T & A_L \end{bmatrix} \begin{bmatrix} B_T^T \\ \vdots \\ I \end{bmatrix} = \phi = A_T B_T^T + A_L = \phi$$

$$B_T^T = -A_T^{-1} A_L$$

Loop and Cutset Matrices

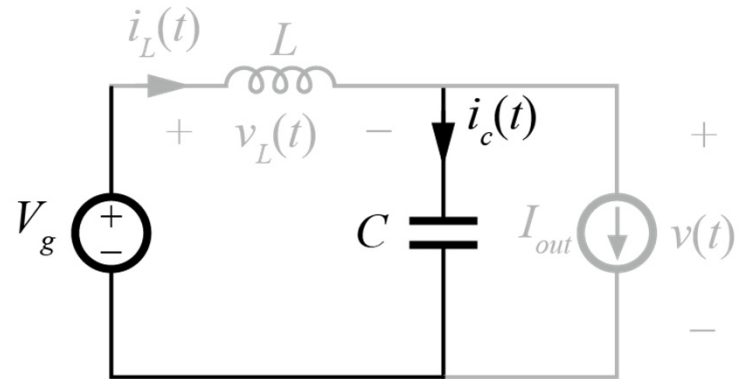

Final State Space

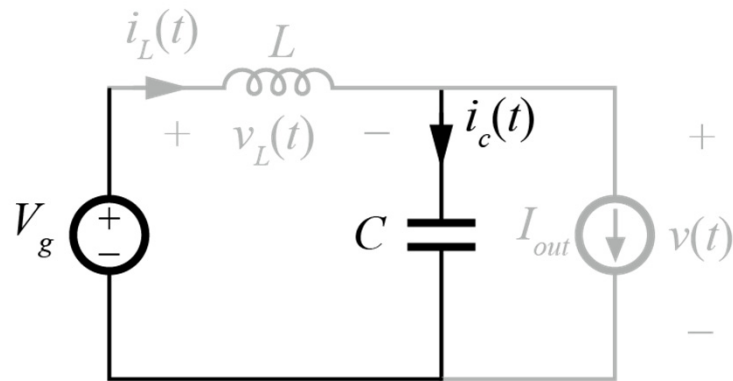

$$Bv = \phi$$

$$Di = \phi$$

$$B = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & -1 & 0 & 1 \end{bmatrix}$$


Components: V_g , C , L , I_{out}

$$D = \begin{bmatrix} 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 1 \end{bmatrix}$$

$$N_L + N_C - v_g = \phi \rightarrow v_L = L \frac{di_L}{dt} = v_g - v_C$$

$$i_C - i_L + I_{out} = \phi \rightarrow i_C = C \frac{dv}{dt} = -I_{out} + i_L$$

Including Resistances

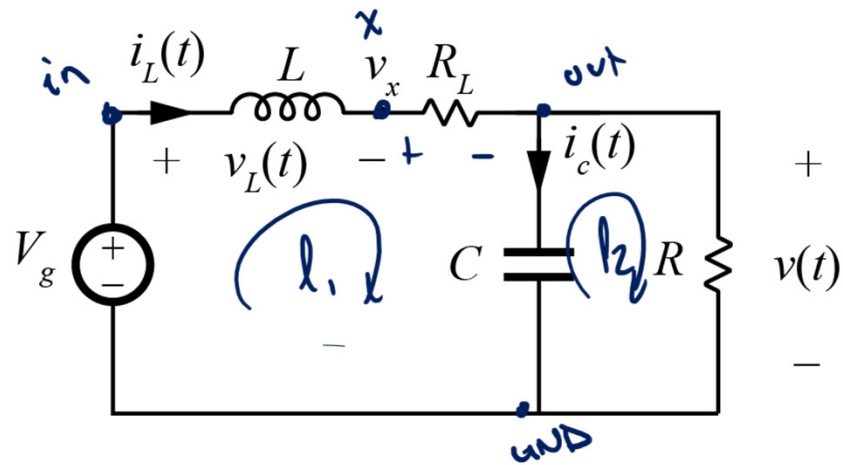

$$B = \begin{bmatrix} V_g & C & R_L & R & L \\ 0 & -1 & 0 & 1 & 0 \\ -1 & 1 & 1 & 0 & 1 \end{bmatrix} = [B_T \mid I]$$

Components: R , R_L

Nodes: in, x, out, gnd


$$\begin{bmatrix} V_g & C & R & R_L & L \\ 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & -1 & -1 \\ 0 & -1 & -1 & -1 & 0 \\ -1 & -1 & -1 & 0 & 0 \end{bmatrix} = A_0$$

REF

$$\begin{bmatrix} 1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 1 & -1 \end{bmatrix} \begin{matrix} \leftarrow 2 + 3 \\ \leftarrow 2 \end{matrix}$$

$$A = \begin{bmatrix} V_g & C & R_L & R & L \\ 1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & 1 & -1 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix} = [I \mid A_L]$$

Including Resistances

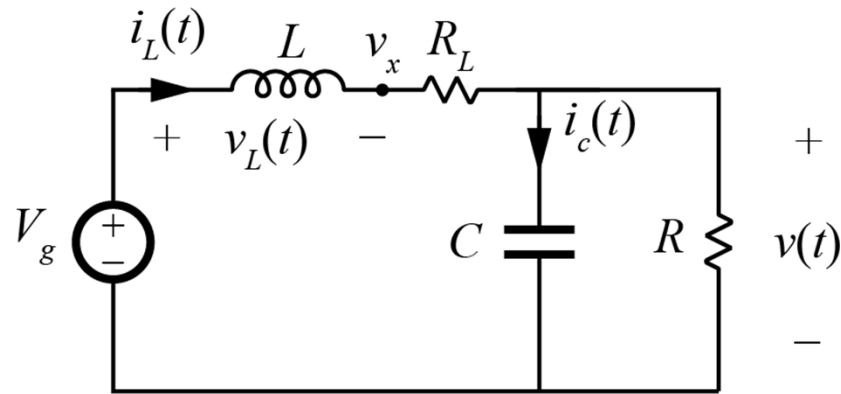

- Additional step to eliminate all resistor currents/voltages
 - solve voltage on tree resistors and current in link resistors

$$D = \begin{matrix} & V_g & C & RL & | & R & L \\ \begin{matrix} 1 \\ 0 \\ 0 \end{matrix} & \begin{matrix} 0 \\ 1 \\ 0 \end{matrix} & \begin{matrix} 0 \\ 1 \\ 0 \end{matrix} & \begin{matrix} 0 \\ 0 \\ 1 \end{matrix} & | & \begin{matrix} 0 \\ 1 \\ 0 \end{matrix} & \begin{matrix} 1 \\ -1 \\ -1 \end{matrix} \end{matrix} = [I \quad D_L]$$

$$D_L = \begin{bmatrix} D_{EG} & D_{EJ} \\ D_{RG} & D_{RJ} \end{bmatrix}$$



$$\begin{matrix} \downarrow \\ \uparrow \end{matrix} \begin{bmatrix} I_{V,C} \\ V_{I,L} \end{bmatrix} = \begin{bmatrix} -(D_{EG}Z^{-1}D_{EG}^T) & D_{EG}Z^{-1}D_{RG}^T Z_R D_{RJ} - D_{EJ} \\ D_{EJ}^T - D_{RJ}^T Y^{-1} D_{RG} Y_G D_{EG}^T & -(D_{RJ}^T Y^{-1} D_{RJ}) \end{bmatrix} \begin{matrix} \downarrow \\ \uparrow \end{matrix} \begin{bmatrix} V_{V,C} \\ I_{I,D} \end{bmatrix}$$



$$\begin{bmatrix} i_g(t) \\ i_c(t) \\ v_L(t) \end{bmatrix} = \begin{bmatrix} 0 & 0 & -1 \\ 0 & -\frac{1}{R} & 1 \\ 1 & -1 & -R_L \end{bmatrix} \begin{bmatrix} V_g \\ v_c(t) \\ i_L(t) \end{bmatrix}$$