
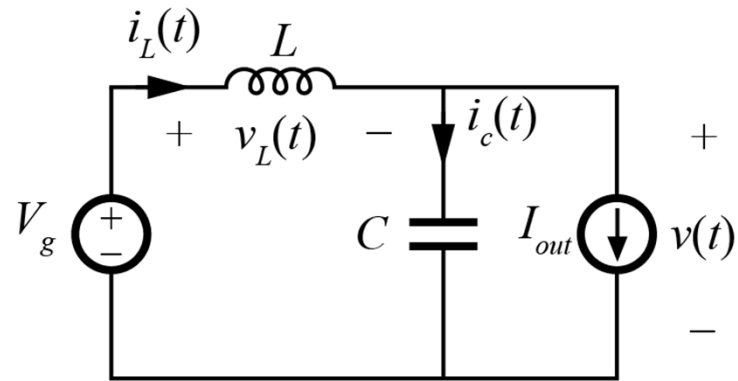


Example State Space Parsing

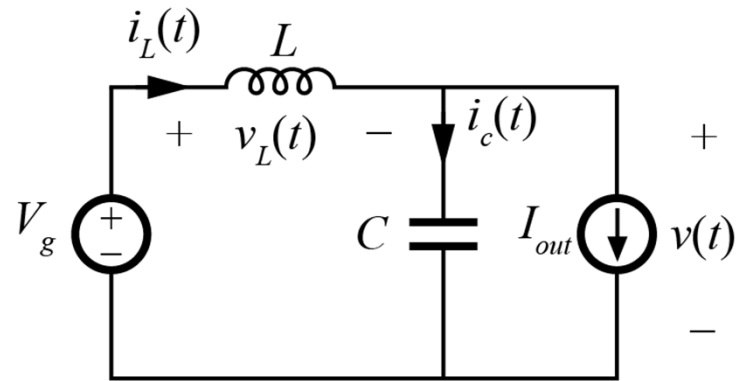


$$\frac{d}{dt} \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} = \begin{bmatrix} \quad \\ \quad \end{bmatrix} \cdot \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} \quad \\ \quad \end{bmatrix} [V_g \quad I_{out}]$$


Component Partitioning



Incidence Matrix

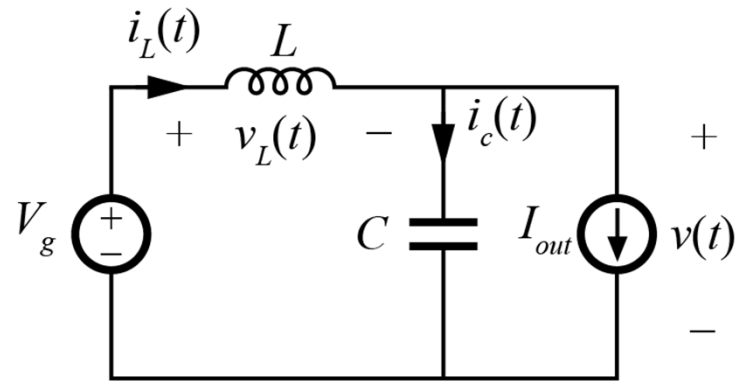


Loop Matrix

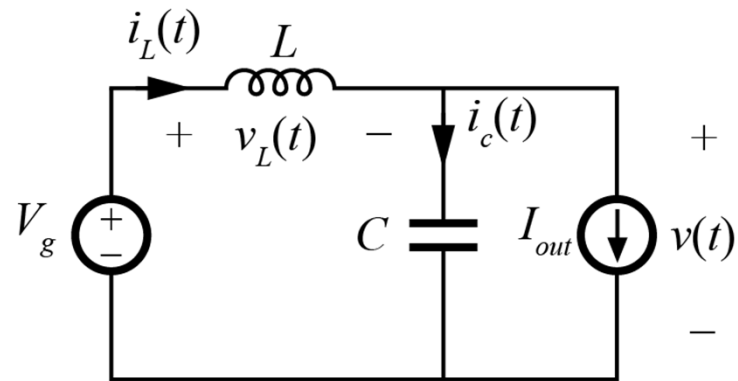


Partitioning


Selecting a Tree

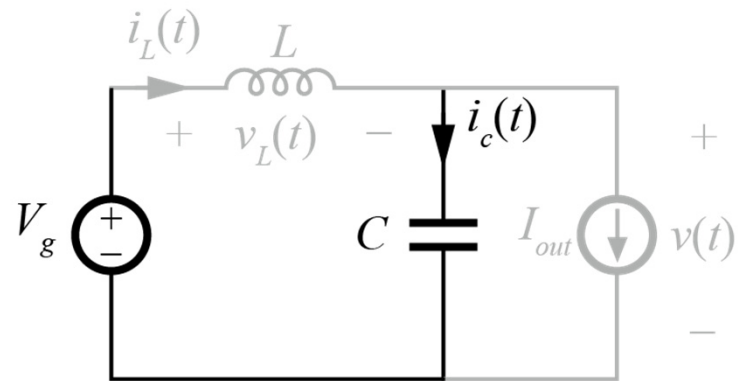



Loop and Cutset Matrices

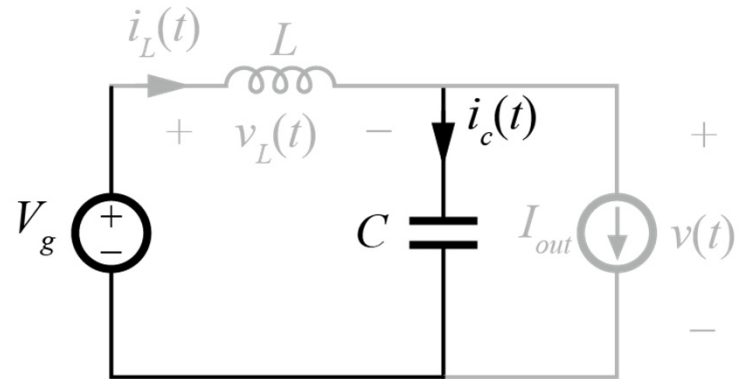


Final State Space

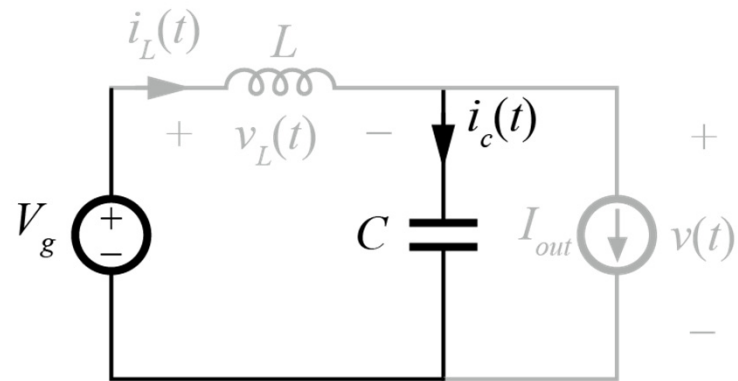

Including Resistances

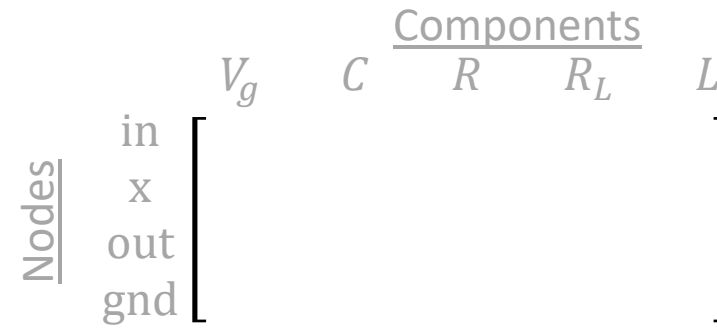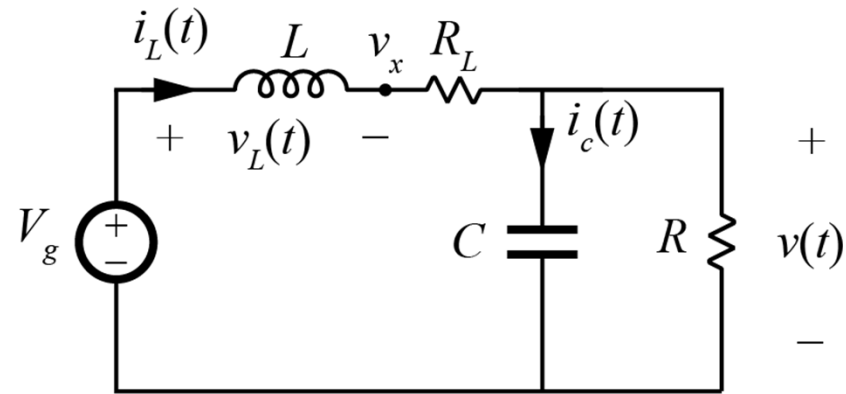

Including Resistances

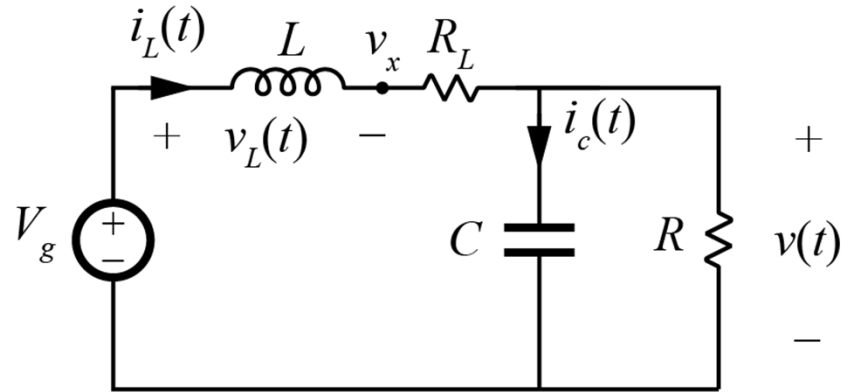

- Additional step to eliminate all resistor currents/voltages
 - solve voltage on tree resistors and current in link resistors

$$D = \begin{array}{c|ccc} & V_g & C & R_L \\ \hline & 1 & 0 & 0 \\ & 0 & 1 & 0 \\ & 0 & 0 & 1 \end{array} \begin{array}{c|cc} & R & L \\ \hline & 0 & 1 \\ & 1 & -1 \\ & 0 & -1 \end{array} = [I \mid D_L]$$

$$D_L = \begin{array}{c|cc} & D_{EG} & D_{EJ} \\ \hline & D_{RG} & D_{RJ} \end{array}$$



$$\begin{bmatrix} I_{V,C} \\ V_{I,L} \end{bmatrix} = \begin{bmatrix} -(D_{EG}Z^{-1}D_{EG}^T) & D_{EG}Z^{-1}D_{RG}^T Z_R D_{RJ} - D_{EJ} \\ D_{EJ}^T - D_{RJ}^T Y^{-1} D_{RG} Y_G D_{EG}^T & -(D_{RJ}^T Y^{-1} D_{RJ}) \end{bmatrix} \begin{bmatrix} V_{V,C} \\ I_{I,L} \end{bmatrix}$$



$$\begin{bmatrix} i_g(t) \\ i_c(t) \\ v_L(t) \end{bmatrix} = \begin{bmatrix} 0 & 0 & -1 \\ 0 & -\frac{1}{R} & 1 \\ 1 & -1 & -R_L \end{bmatrix} \begin{bmatrix} V_g \\ v_c(t) \\ i_L(t) \end{bmatrix}$$