


Midterm Project

- Select a (dc-dc) converter steady-state hardware design problem
- Detail
 - Application specification
 - Performance specification
 - should advance on SotA; near-optimal design
 - Design parameters
- Apply techniques from class
 - Design using MATLAB
 - Validate through simulation (PLECs/Spice) ←
- Should result in prototype-ready paper design
- Finalize scope by **October 4th**
 - 5 pts, text entry or pdf
 - Briefly describe application, performance spec, and design parameters
- Report Due **October 18th**
 - Narrative of analysis and results
 - Clear but minimally “wordy”
 - IEEE format (though incomplete content w.r.t. review and explanation)
- Class presentations thereafter

Symmetric Converters

Hw #3 solution
Applies symmetry

AC-link Topologies

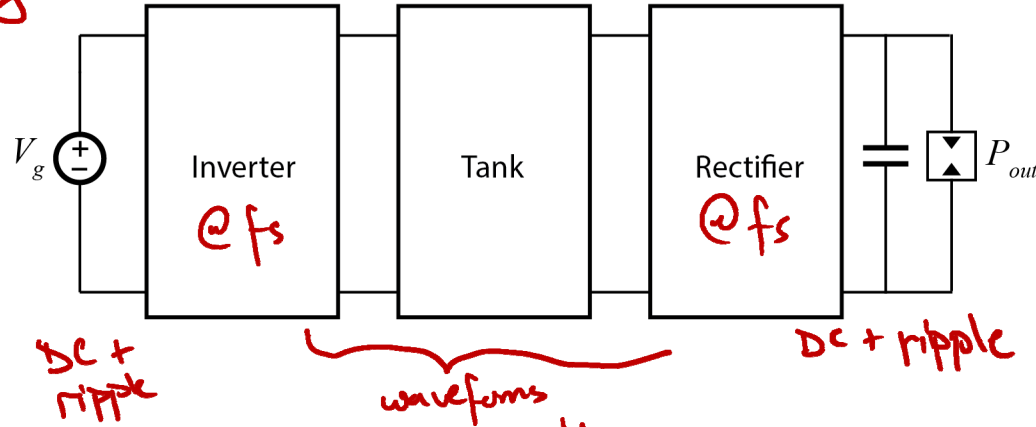

Converter waveforms exhibit defined symmetry

- All waveforms are periodic about f_s
- ac waveforms have half-period antisymmetry
- dc waveforms have half-period symmetry

n_i = number of switching intervals in one period

without symmetry, using Augmented SS

$$\tilde{X}(T_s) = \left(\prod_{i=1}^{n_i} e^{\hat{A}_i t_i} \right) \tilde{X}(0)$$

$$\tilde{X}_{ss} \rightarrow \text{null} \left(I - \prod_{i=1}^{n_i} e^{\hat{A}_i t_i} \right)$$


using symmetry arguments:

$$\tilde{X}(T_s/2) = \left(I_{Hc} \prod_{i=1}^{n_i/2} e^{\hat{A}_i t_i} \right) \tilde{X}(0)$$

$$x(t) = \begin{bmatrix} x_{dc} \\ x_{ac} \end{bmatrix} \rightarrow I_{Hc} = \begin{bmatrix} I & \emptyset \\ \emptyset & -I \end{bmatrix}$$


$$\tilde{X}_{ss} \rightarrow \text{null} \left(I - I_{Hc} \prod_{i=1}^{n_i/2} e^{\hat{A}_i t_i} \right)$$

DAB Example

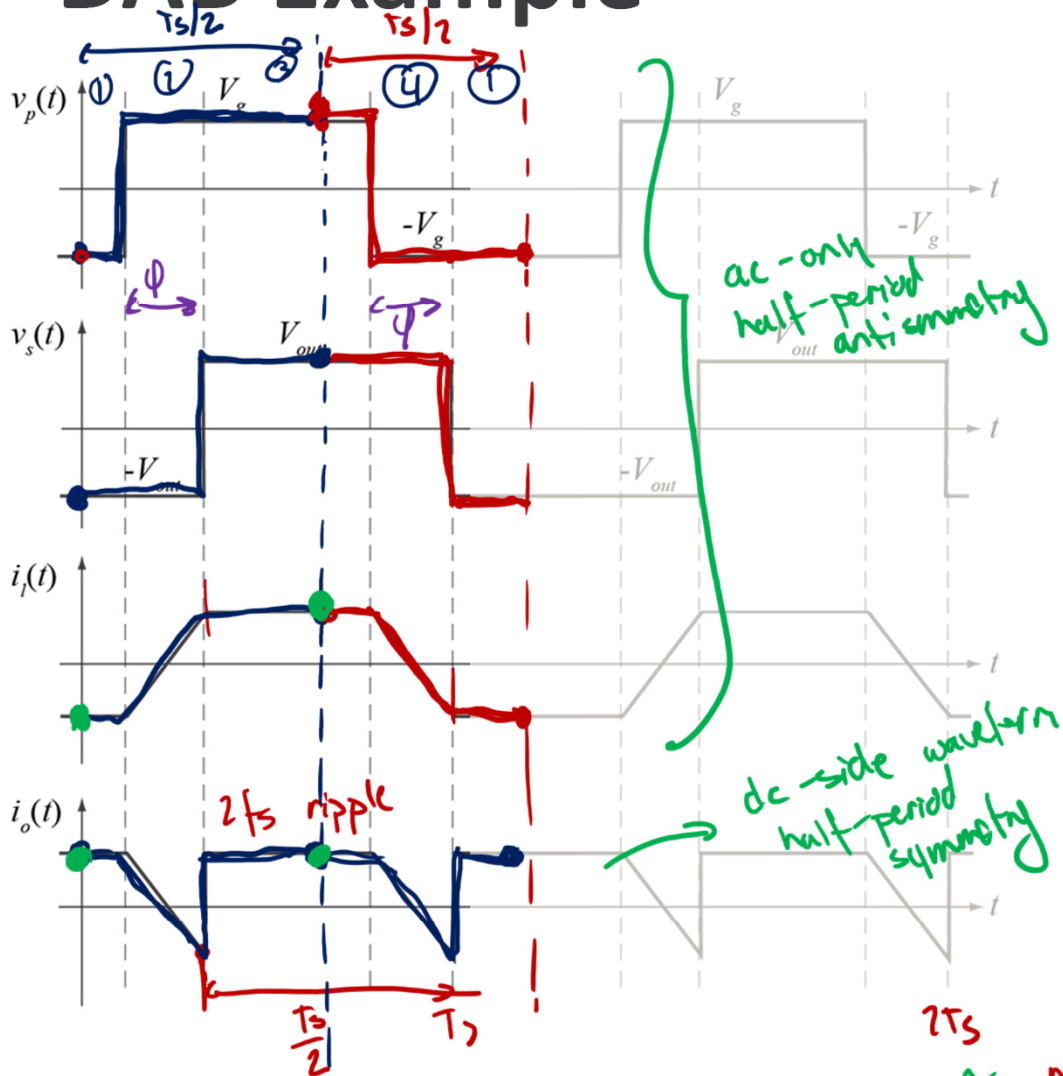

Note: this implies control possible about $2 \cdot f_s$
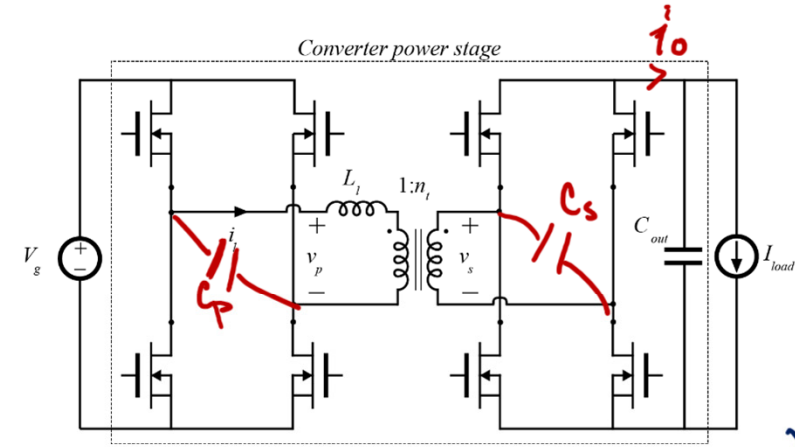
$$\tilde{A}_i = \begin{bmatrix} n_s & 1 \\ A_i & B_i \\ 0 & 0 \end{bmatrix}$$



for this DAB
without symmetry

$$\Phi = e^{\tilde{A}_1 t_1} e^{\tilde{A}_2 t_2} e^{\tilde{A}_3 t_3} e^{\tilde{A}_4 t_4}$$

$$x(T_s) = \Phi x(0)$$

$$x_{ss} \rightarrow \text{null}(\mathbf{I} - \Phi)$$

half-cycle symmetry


$$\Phi_H = e^{\tilde{A}_1 t_1} e^{\tilde{A}_1 t_1}$$

$$x_{ss} \rightarrow \text{null}(\mathbf{I} - \mathbf{I}_{Hc} \Phi_H)$$


$$\mathbf{I}_{Hc} = \begin{bmatrix} n_p & n_s & i_i & i_o \\ -1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & -1 \end{bmatrix}$$

State-dependent Switching

DEM Buck

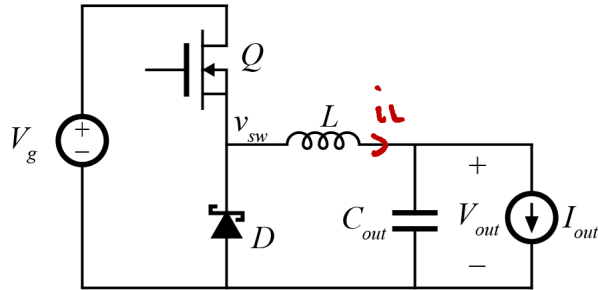

ZVS Buck

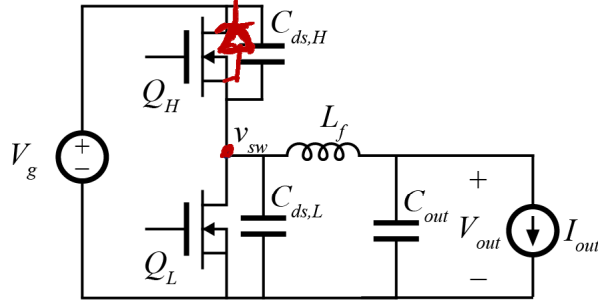

CPM Buck

