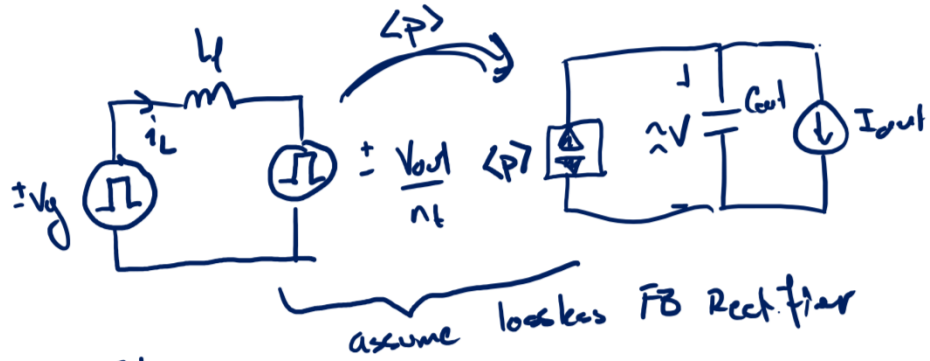


One Approach: Relaxing The Average





$$\langle P \rangle = \frac{2}{T_s} \int_0^{T_s/2} i_L(t) \cdot \frac{v_s(t)}{n_t} dt$$

$$= \frac{2}{T_s} \frac{1}{n_t} \left[(-V_{out}) \frac{-I_{pk} + I_1}{2} (t_\varphi) + \frac{I_1 + I_{pk}}{2} (V_{out}) \left(\frac{T_s}{2} - t_\varphi \right) \right]$$

$$= \frac{V_{out}}{n_t T_s} \left[(I_{pk} - I_1) t_\varphi + (I_1 + I_{pk}) \left(\frac{T_s}{2} - t_\varphi \right) \right]$$
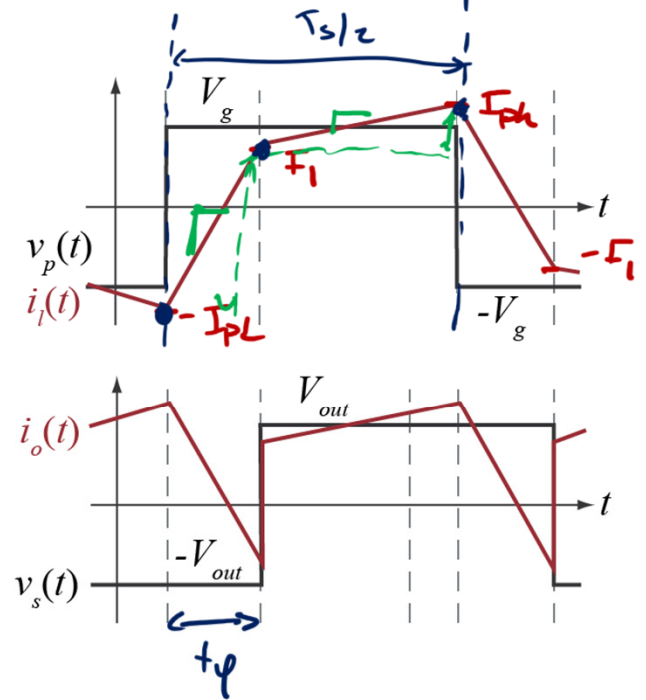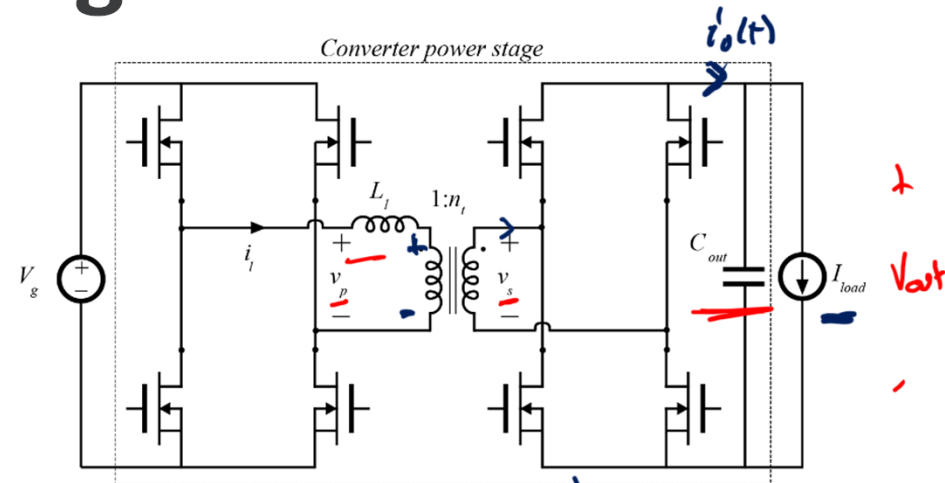
$$\left\{ \begin{aligned} I_{pk} - I_1 &= \frac{V_g - \frac{V_{out}}{n_t}}{L_e} \left(\frac{T_s}{2} - t_\varphi \right) \\ I_{pk} + I_1 &= \frac{(V_g + \frac{V_{out}}{n_t}) t_\varphi}{L_e} \end{aligned} \right.$$



$$\langle P \rangle = \frac{V_{out}}{\eta_f T_s} \left[\frac{V_g - \frac{V_{out}}{n}}{L_f} t_f \left(\frac{T_s}{2} - t_f \right) + \frac{V_g + \frac{V_{out}}{n}}{L_f} \left(\frac{T_s}{2} - t_f \right) t_f \right]$$


$$\langle P \rangle = \frac{V_{out}}{\eta_f T_s L_f} t_f \left(\frac{T_s}{2} - t_f \right) [2 V_g]$$

$$\langle P \rangle = \frac{V_{out} V_g}{\eta_f T_s L_f} (T_s t_f - 2 t_f^2)$$

$$\langle i_o \rangle = \frac{\langle P \rangle}{V_{out}} = \frac{V_g}{\eta_f T_s L_f} (T_s t_f - 2 t_f^2)$$

← $\langle i_o \rangle$ is independent of V_{out}
output looks like a current source

Output Power


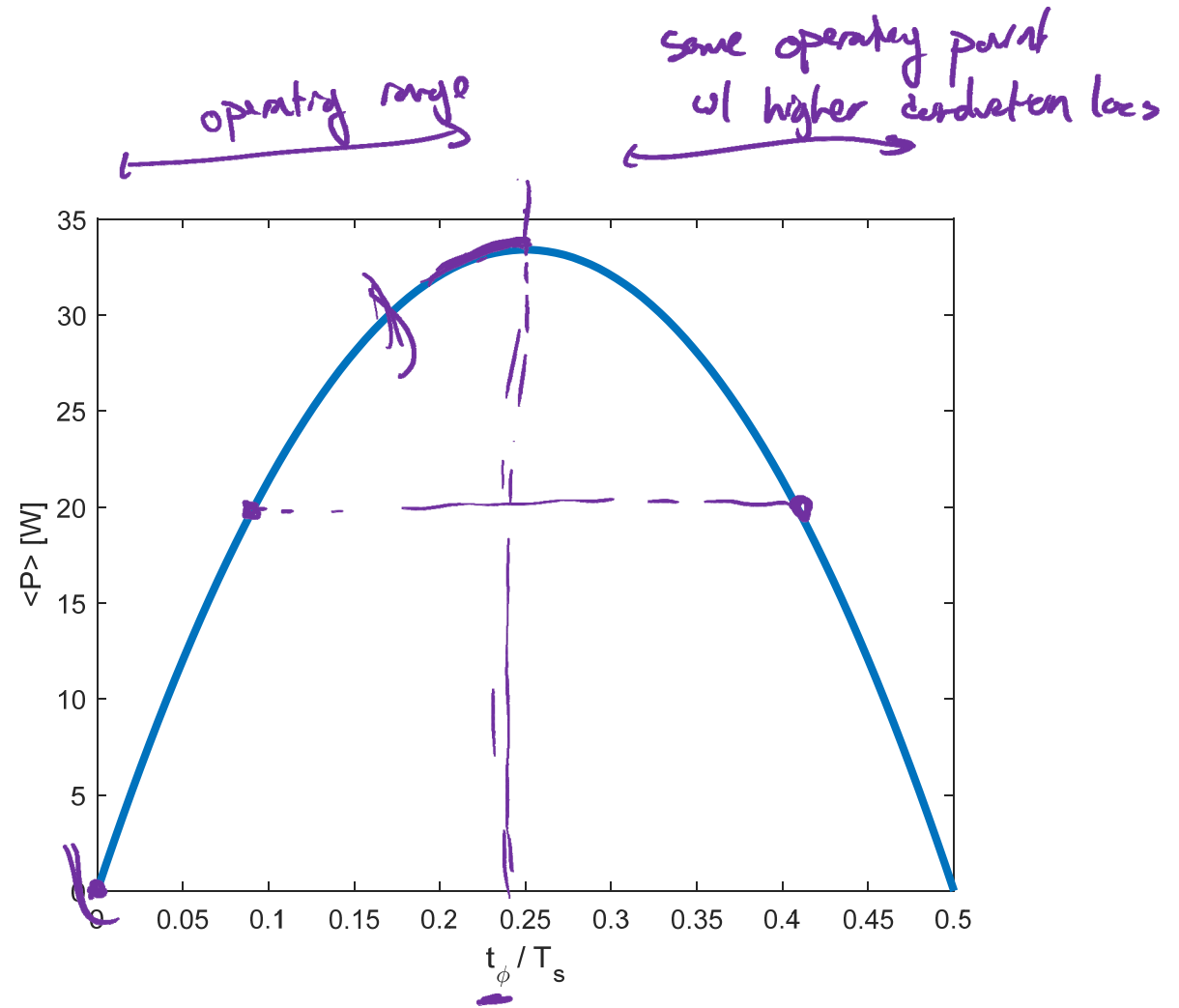


Including R_L

common in power electronics design

"high- η " approximation

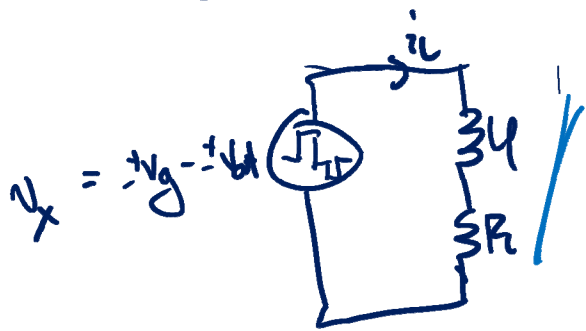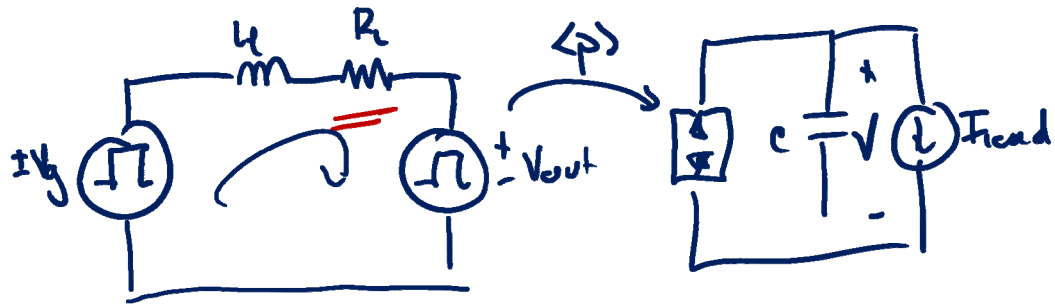Neglect all losses, solve converter, then calculate losses using your solution



$$v_x = L \frac{di_L}{dt} + i_L R_L$$

$$i_L(t) = \frac{v_x}{R_L} + C e^{-\frac{R_L}{L}t}$$

$$= f(v_x, I_{L0}, t)$$

for $i_L(t=0) = I_{L0}$


$$C = I_{L0} \cdot \frac{L}{R_L}$$

$$\left. \begin{aligned} I_{pk} &= f\left(v_g + \frac{v_{out}}{2}, I_1, \frac{T_s}{2} - t\right) \\ I_1 &= f\left(v_g - \frac{v_{out}}{2}, -I_{pk}, t\right) \end{aligned} \right\}$$



$$\langle p \rangle = \frac{2}{T_s} \left[\int_0^{t_p} \left(-\frac{v_{out}}{2}\right) f\left(v_g + \frac{v_{out}}{2}, -I_{pk}, \tau\right) d\tau + \int_0^{\frac{T_s}{2} - t_p} \frac{v_{out}}{2} f\left(v_g - \frac{v_{out}}{2}, I_1, \tau\right) d\tau \right]$$

Including Losses
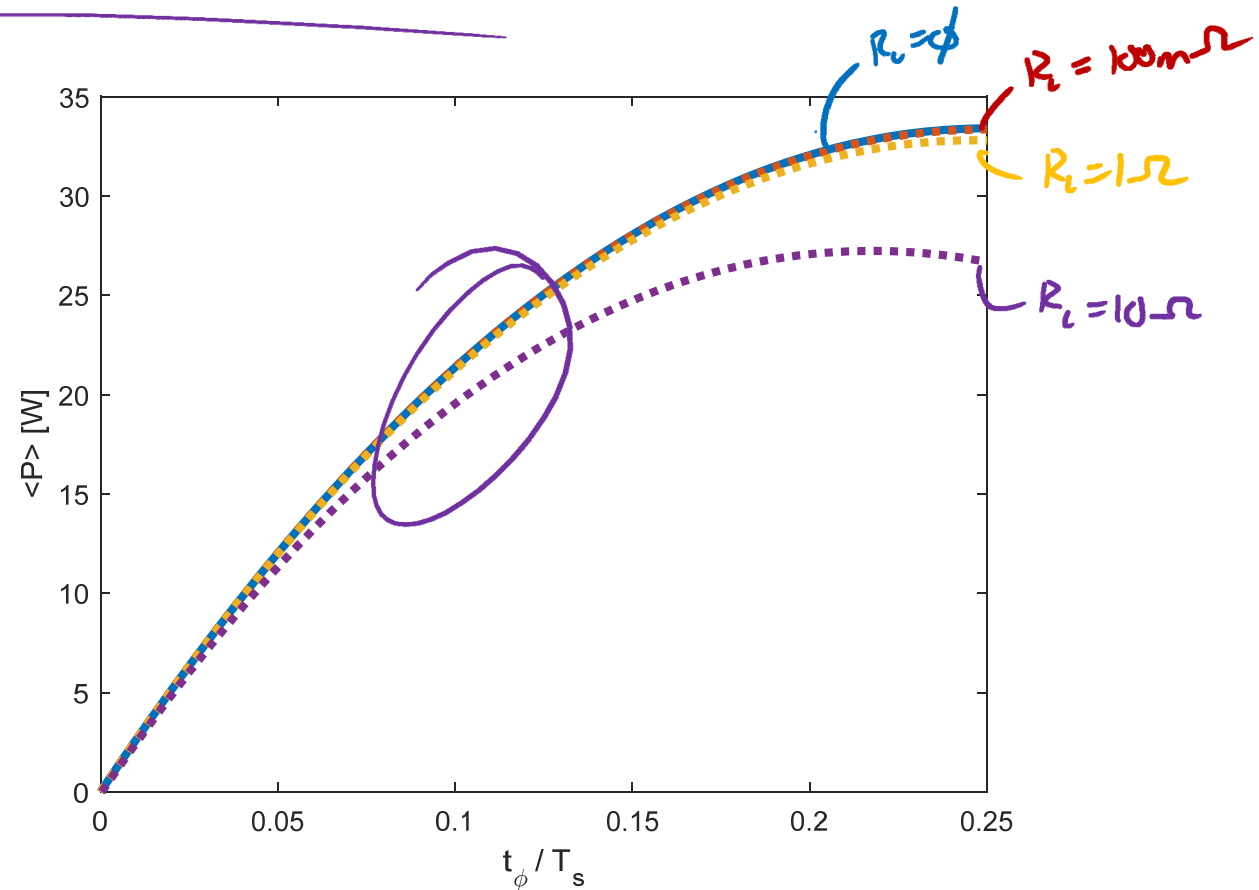
$$\langle P \rangle = \frac{nV}{R_L^2 T_s} \left(\frac{4L_l \left(\left(1 + e^{\frac{R_l T_s}{2L_l}} - 2e^{\frac{R_l(-2t_\phi + T_s)}{2L_l}} \right) V_g + \left(-1 + e^{\frac{R_l T_s}{2L_l}} \right) nV \right)}{1 + e^{\frac{R_l T_s}{2L_l}}} + R_L (-4t_\phi V_g + T_s (V_g - nV)) \right)$$



DAB Operated at High Frequency

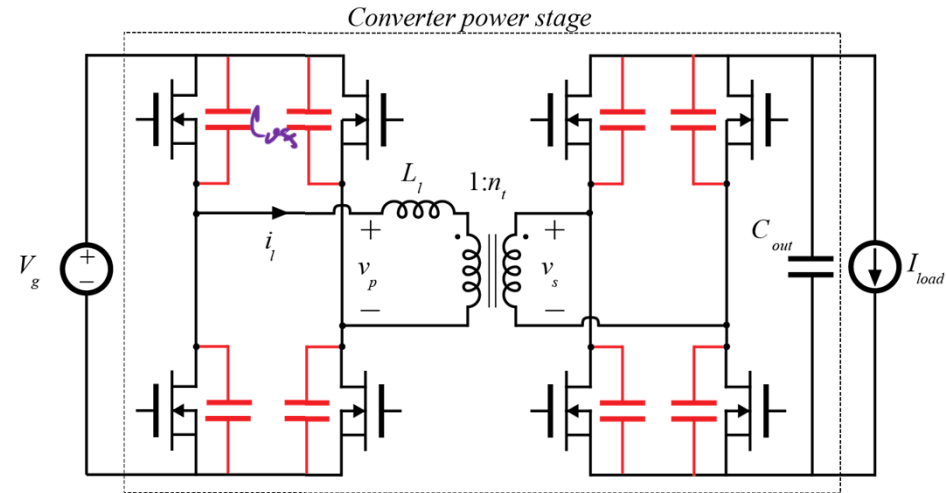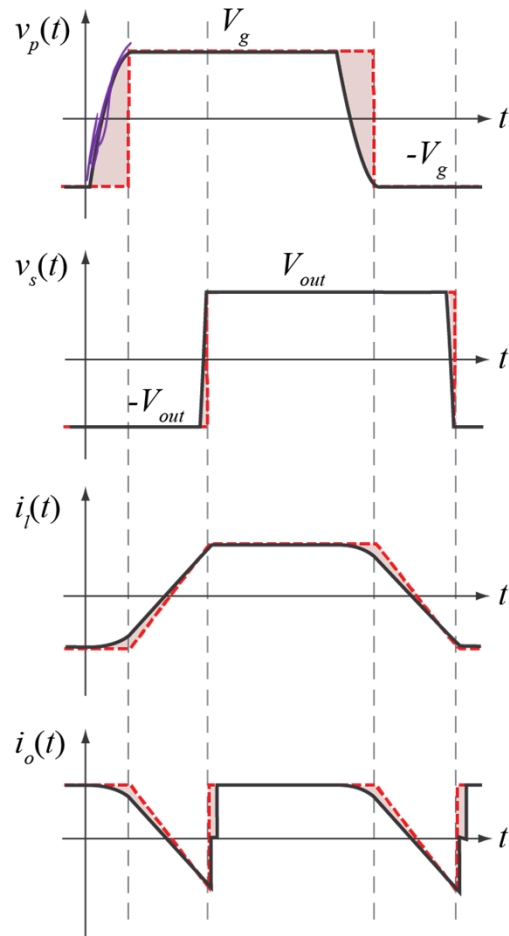

- At high switching frequency, resonant ZVS transitions become significant

State Plane Solution

Covered in ELE581

works for one resonance in any subinterval \neq a lossless converter

$$\alpha = \sin^{-1} \frac{2}{J_p}$$

$$\beta = \frac{1}{2}(J_2 + J_1)$$

$$\delta = n_t \sin^{-1} \frac{2n_t^2}{R_0' J_p} \sqrt{\frac{C_s}{C_p}}$$


$$\zeta = \frac{F}{\pi} - \alpha - \beta - \delta$$

$$J_1 = \sqrt{J_p^2 - 4}$$


$$J_2 = \frac{R_0}{R_0'} \sqrt{\left(J_p \frac{R_0'}{R_0} \right)^2 - (2n_t)^2}$$

$$J = \frac{F}{\pi} \left[2 + \frac{1}{4}(J_1^2 - J_2^2) + J_p \left(\frac{\pi}{F} - \alpha - \beta - \delta \right) \right]$$

Primary

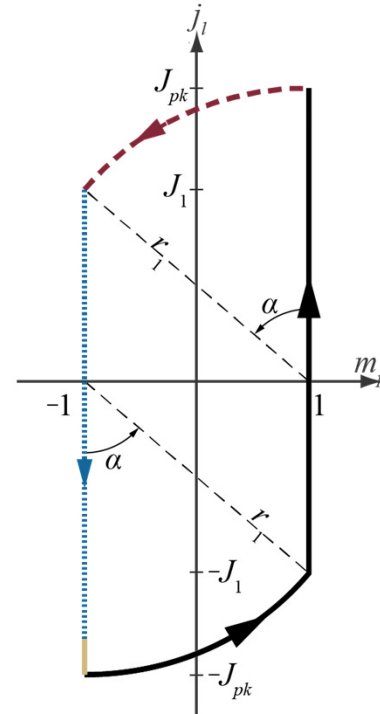


Secondary

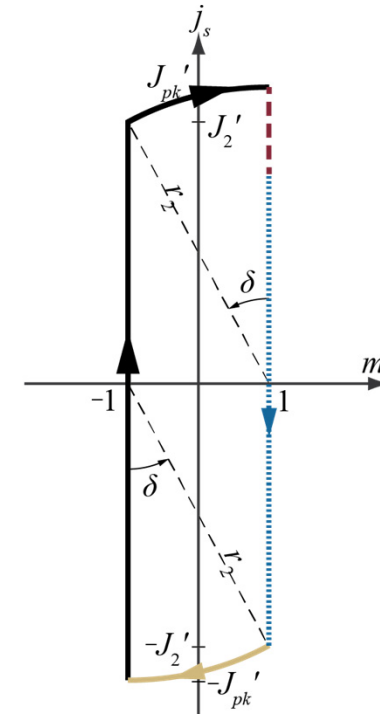

Different Operating Modes

Mode I

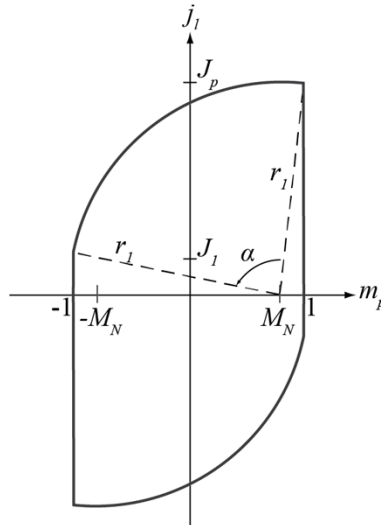

$$J_1 = \sqrt{J_p^2 - 4M_N}$$

$$\alpha = \cos^{-1} \left(1 - \frac{(J_p - J_1)^2 + 4}{2J_p^2 + 2(1 - M_N)^2} \right)$$


$$\beta = \frac{J_1 + J_2}{1 + M_N}$$

$$\zeta = \frac{J_p - J_2}{1 - M_N}$$

$$\frac{\pi}{F} = \alpha + \beta + \delta$$

$$J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left(2 + \frac{J_p + J_2}{2} \zeta + \frac{J_1 - J_2}{2} \beta \right)$$

Mode II

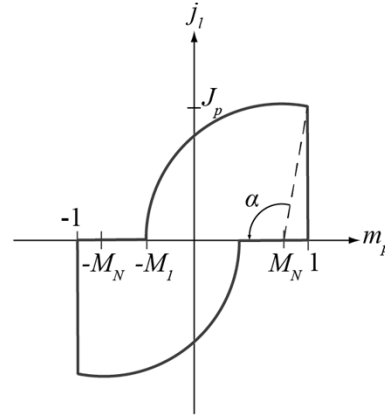

$$M_1 = \sqrt{J_p^2 + (1 - M_N)^2} - M_N$$

$$\alpha = \cos^{-1} \left(1 - \frac{J_p^2 + (1 + M_1)^2}{2(M_1 - M_N)^2} \right)$$


$$J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left(1 + M_1 + \frac{J_p + J_2}{2} \zeta - \frac{J_2}{2} \beta \right)$$

$$\beta = \frac{J_1 + J_2}{1 + M_N}$$

$$\zeta = \frac{J_p - J_2}{1 - M_N}$$

$$\frac{\pi}{F} = \alpha + \beta + \delta$$

Mode III

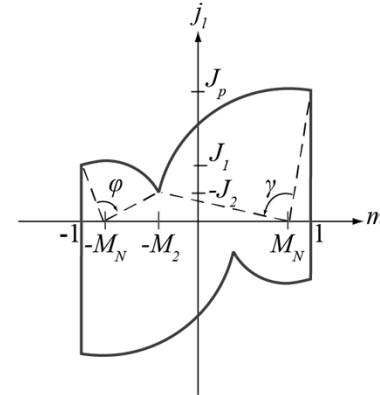

$$\gamma = \cos^{-1} \left(1 - \frac{(J_p + J_2)^2 + (1 + M_2)^2}{2(1 - M_N)^2 + 2J_p^2} \right)$$

$$\phi = \cos^{-1} \left(1 - \frac{(J_1 + J_2)^2 + (1 - M_2)^2}{2(M_N - M_2)^2 + 2J_2^2} \right)$$

$$J_2^2 = (1 - M_N)^2 + J_p^2 - (M_2 + M_N)^2$$


$$J_1^2 = -(1 - M_N)^2 + J_2^2 + (M_N - M_2)^2$$

$$\zeta = \frac{J_p + J_1}{1 - M_N}$$

$$\frac{\pi}{F} = \gamma + \phi + \zeta = \alpha + \zeta$$

$$J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left(2M_2 + \frac{J_p - J_1}{2} \zeta \right)$$

Mode IV

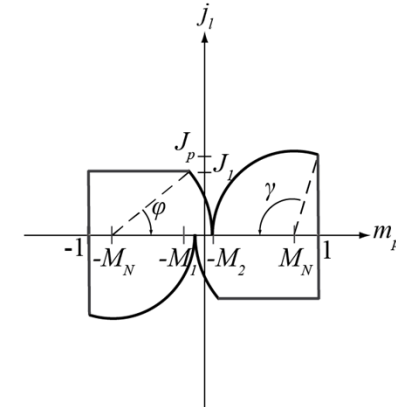

$$\phi = \cos^{-1} \left(1 - \frac{J_1^2 + (M_1 - M_2)^2}{2(M_N - M_2)^2} \right)$$

$$J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left(2M_2 + 1 - M_1 + \frac{J_p - J_1}{2} \zeta \right)$$

$$J_2^2 = (1 - M_N)^2 + J_p^2 - (M_2 + M_N)^2$$


$$J_1^2 = -(1 - M_N)^2 + J_2^2 + (M_N - M_2)^2$$

$$\zeta = \frac{J_p + J_1}{1 - M_N}$$


$$\frac{\pi}{F} = \gamma + \phi + \zeta = \alpha + \zeta$$

Different Topologies


PWM

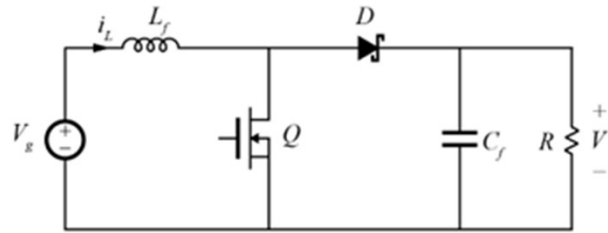


Switched-Capacitor

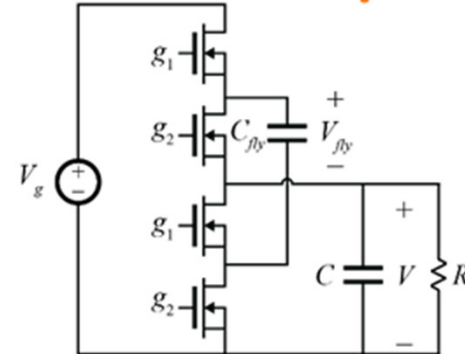


Quasi-Resonant

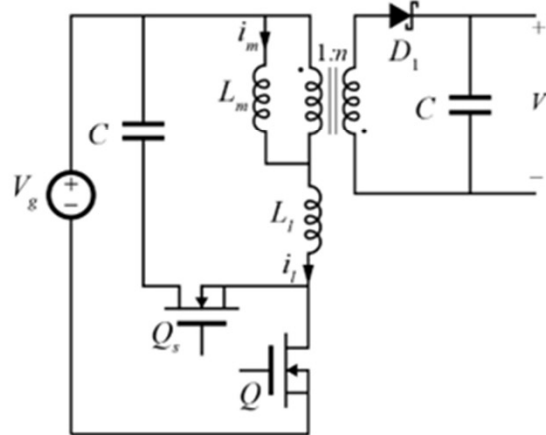


Multi-Resonant

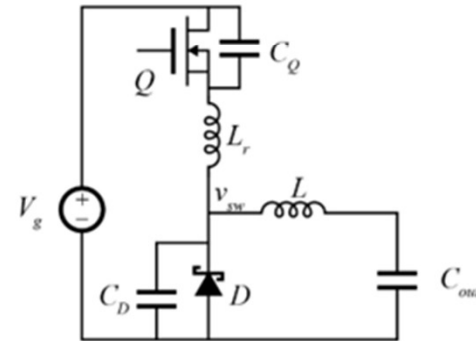

Hybrid Switched-Capacitor

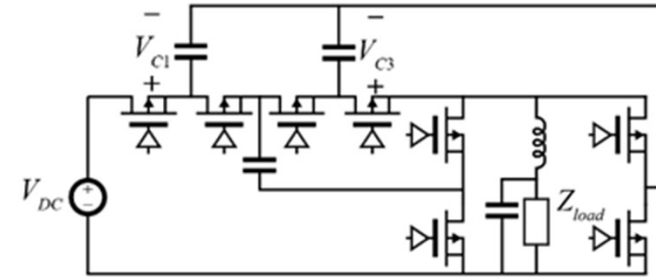


AC-Link

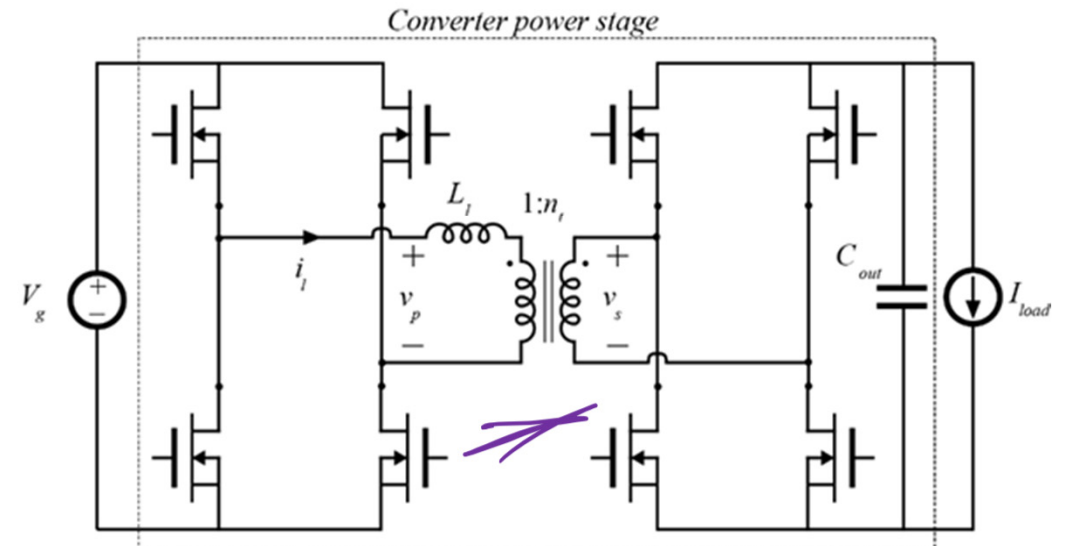


Converter Analysis

Resonant (AC-link)	Multi-Resonant	Z-source, matrix, others
QSW & QR Converters	Multilevel Resonant SC	MMC
PWM (small ripple)	Hybrid Switched Capacitor	Switched Capacitor


Converter Analysis

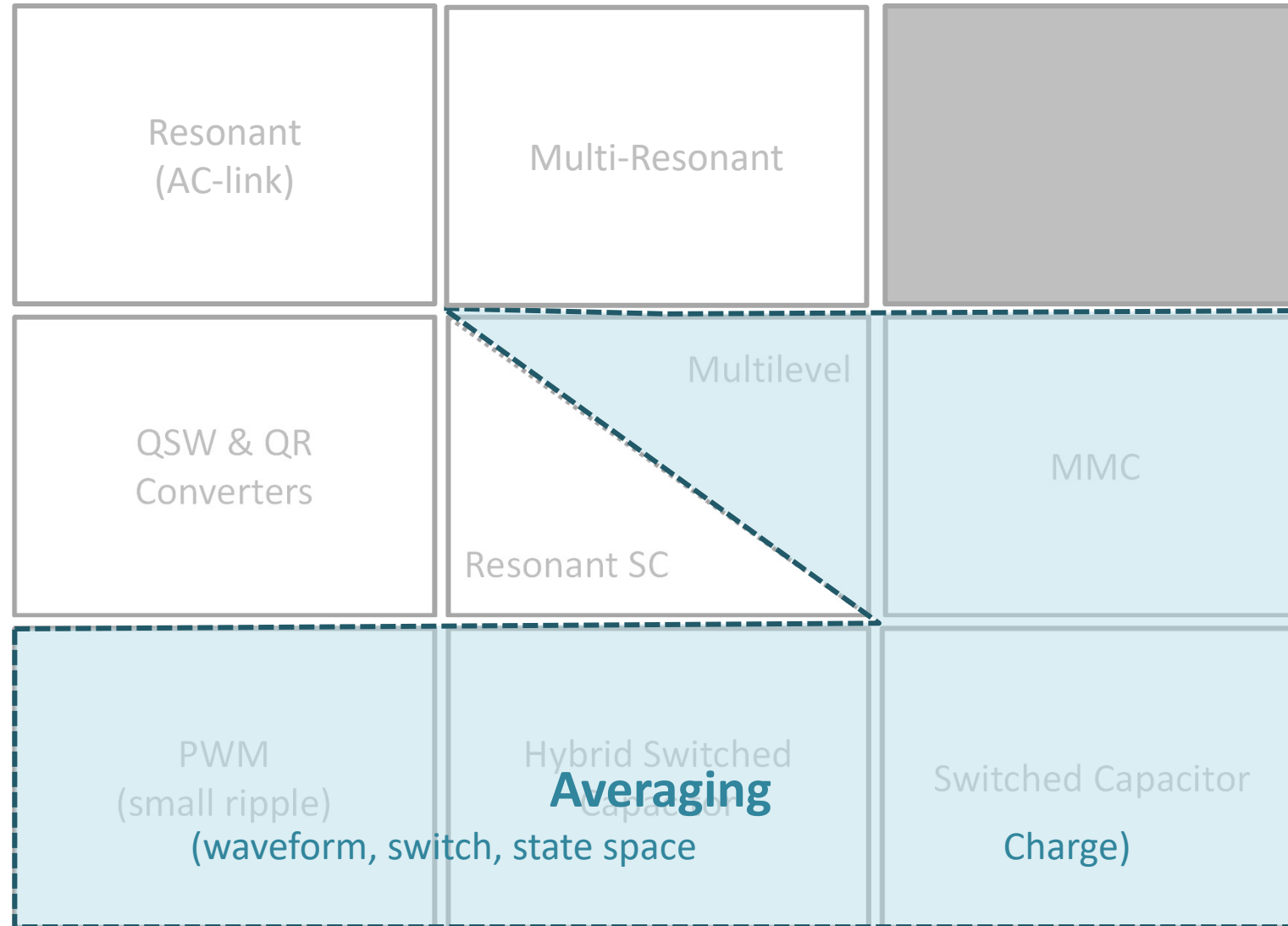


Converter Analysis

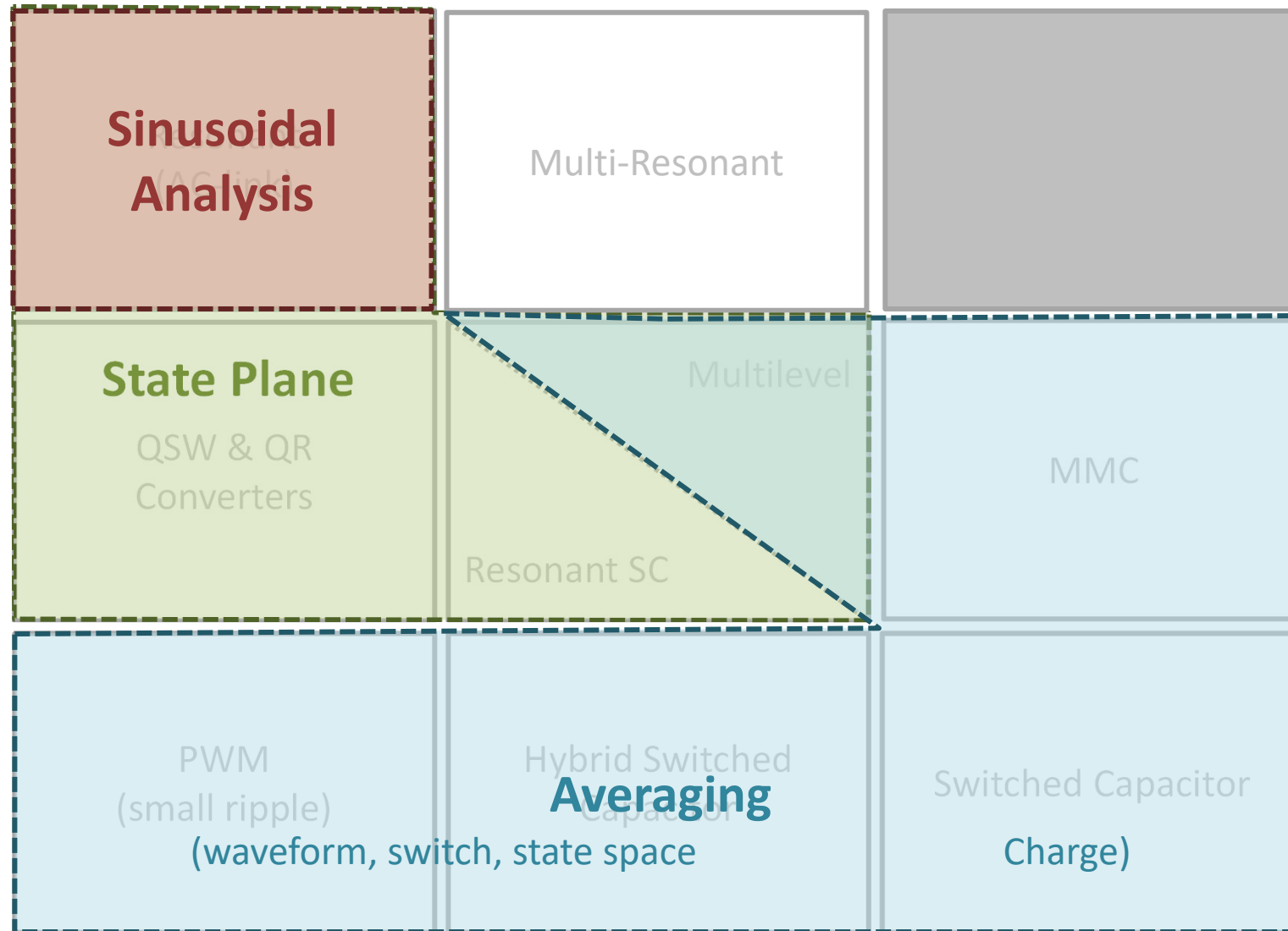

High-level View

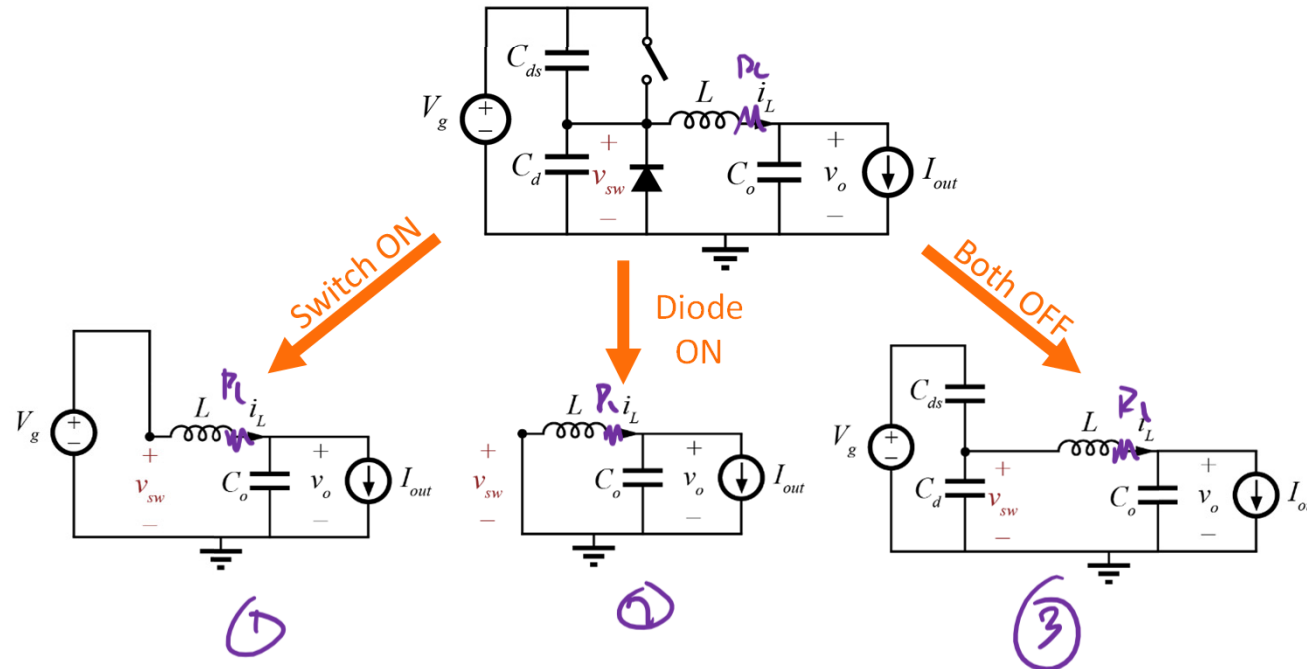

Purposes Of Analysis

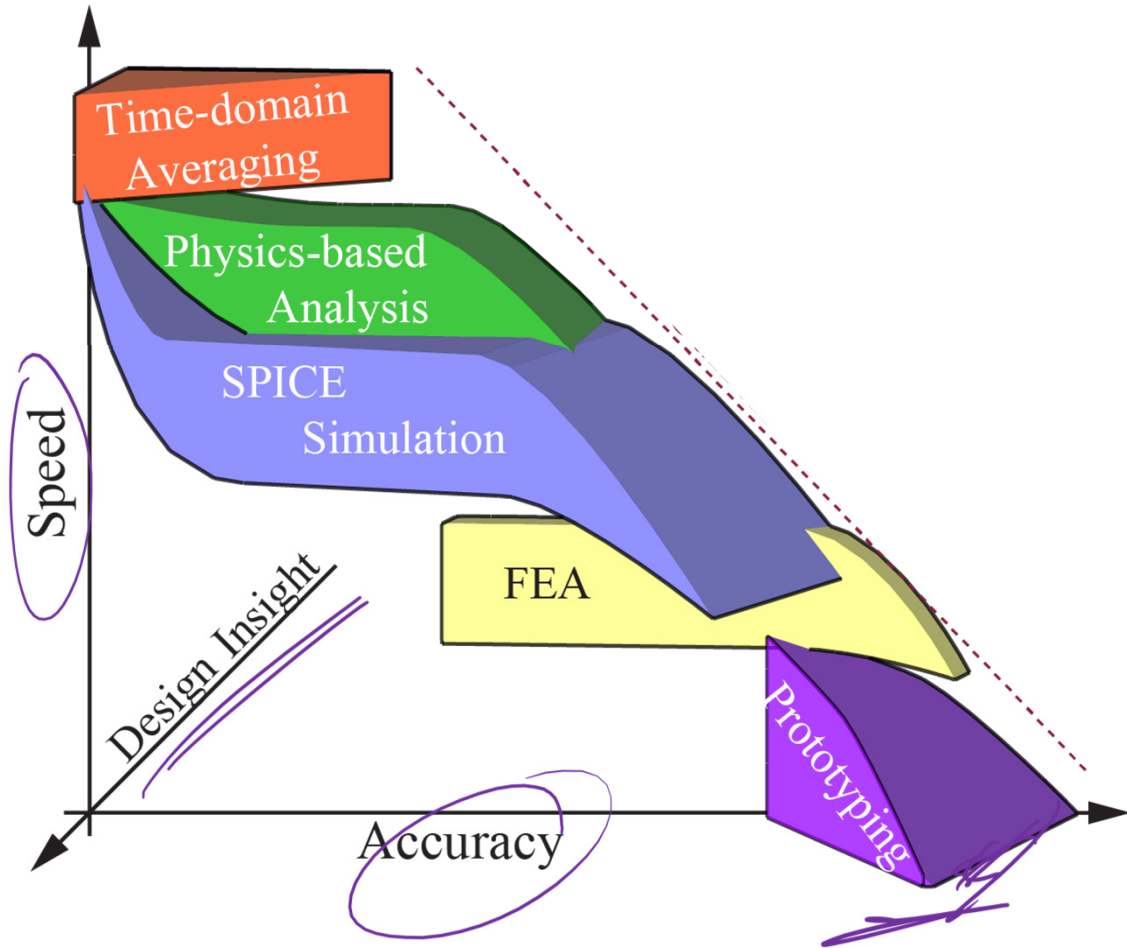

The Design "V"

