

Compensator Realizations (PID compensators)

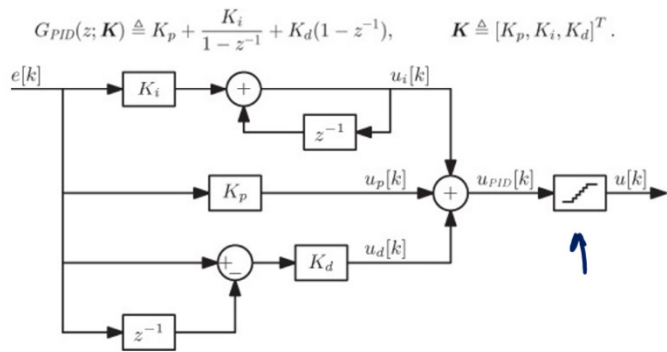


Figure 6.2 Parallel realization of a digital PID compensator.

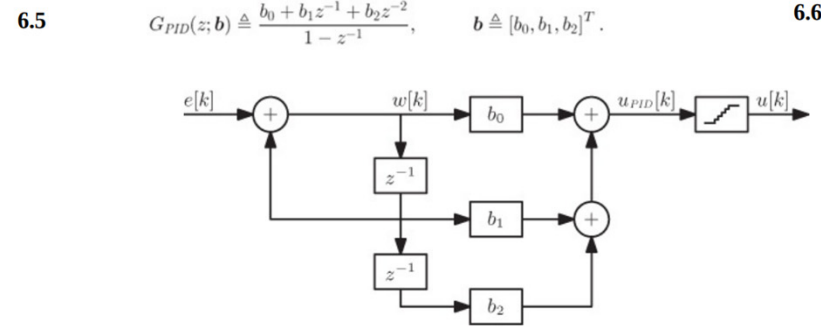


Figure 6.3 Direct realization of a digital PID compensator.

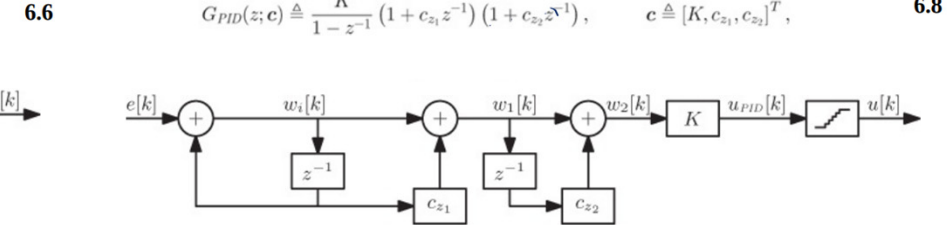


Figure 6.4 Cascade realization of a digital PID compensator.

Parallel Realization

$$\begin{aligned}
 u_p[k] &= K_p e[k], \\
 u_i[k] &= u_i[k-1] + K_i e[k], \\
 u_d[k] &= K_d (e[k] - e[k-1]), \\
 u[k] &= u_p[k] + u_i[k] + u_d[k].
 \end{aligned}$$

4.10

The compensator coefficients K_p , K_i , and K_d are the proportional, integral, and derivative gains, respectively.


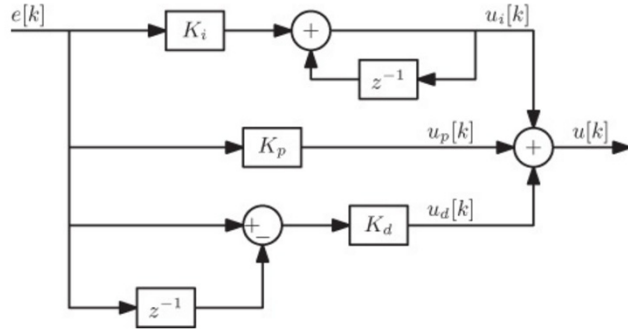


Figure 4.3 Block diagram of a digital PID compensator in the parallel form.

$$G_{PID}(z) = K_p + \frac{K_i}{1 - z^{-1}} + K_d(1 - z^{-1}).$$
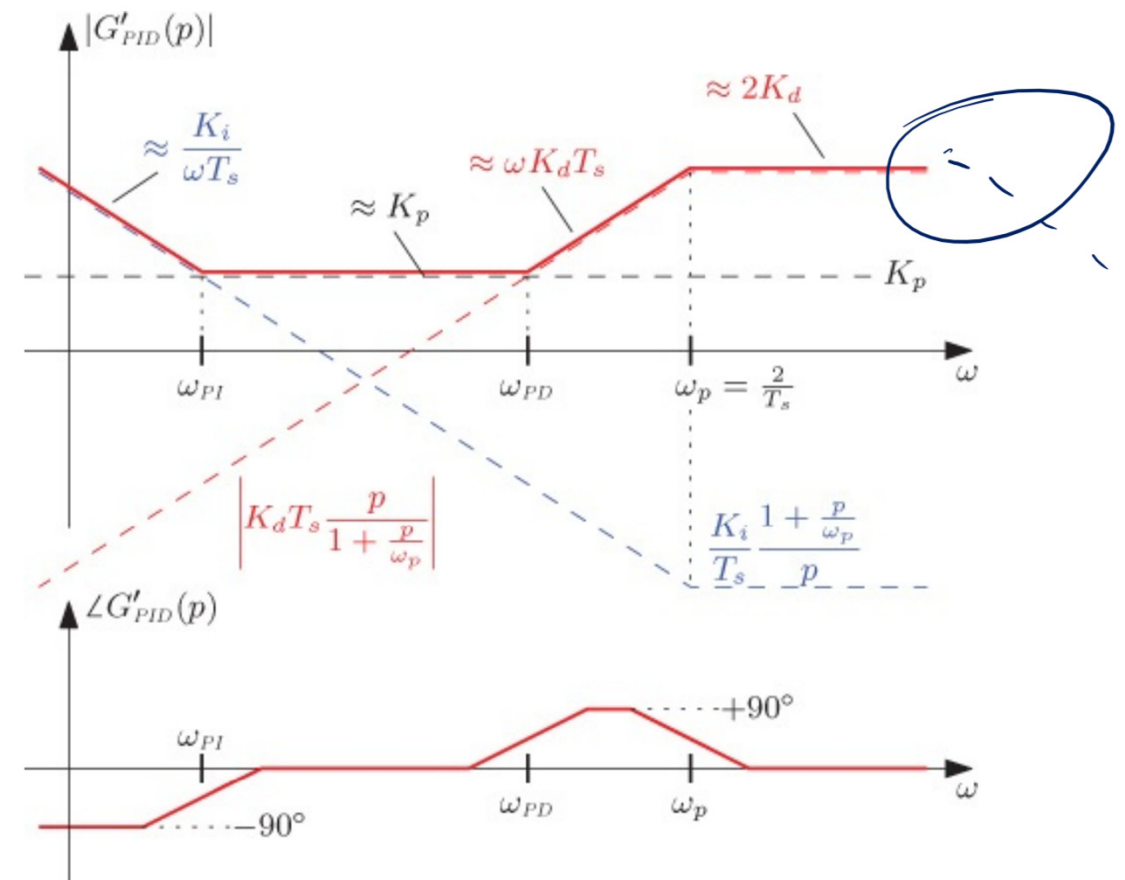
$$G'_{PID}(p) = \underbrace{K_p}_{\text{Proportional term}} + \underbrace{\frac{K_i}{T_s} \frac{1 + \frac{p}{\omega_p}}{p}}_{\text{Integral term}} + \underbrace{K_d T_s \frac{p}{1 + \frac{p}{\omega_p}}}_{\text{Derivative term}},$$





$$G'_{PID}(p) = \underbrace{G'_{PI\infty} \left(1 + \frac{\omega_{PI}}{p}\right)}_{PI} \underbrace{G'_{PD0} \frac{1 + \frac{p}{\omega_{PD}}}{1 + \frac{p}{\omega_p}}}_{PD},$$

$$K_p = G'_{PI\infty} G'_{PD0} \left(1 + \frac{\omega_{PI}}{\omega_{PD}} - \frac{2\omega_{PI}}{\omega_p}\right),$$


$$K_i = 2G'_{PI\infty} G'_{PD0} \frac{\omega_{PI}}{\omega_p},$$

$$K_d = \frac{G'_{PI\infty} G'_{PD0}}{2} \left(1 - \frac{\omega_{PI}}{\omega_p}\right) \left(\frac{\omega_p}{\omega_{PD}} - 1\right).$$

Simulation (Large Signal)

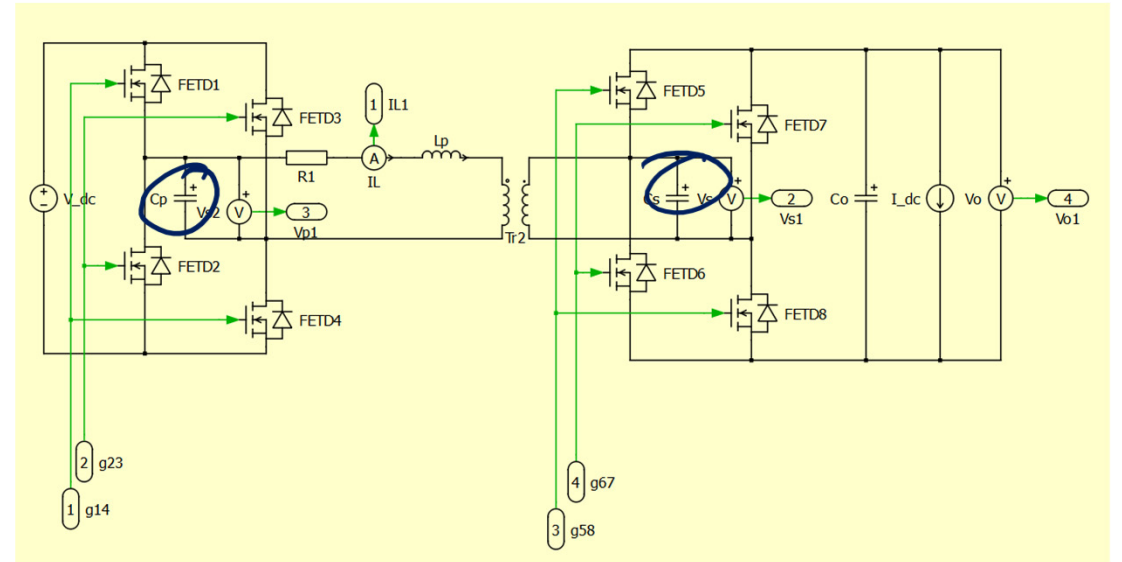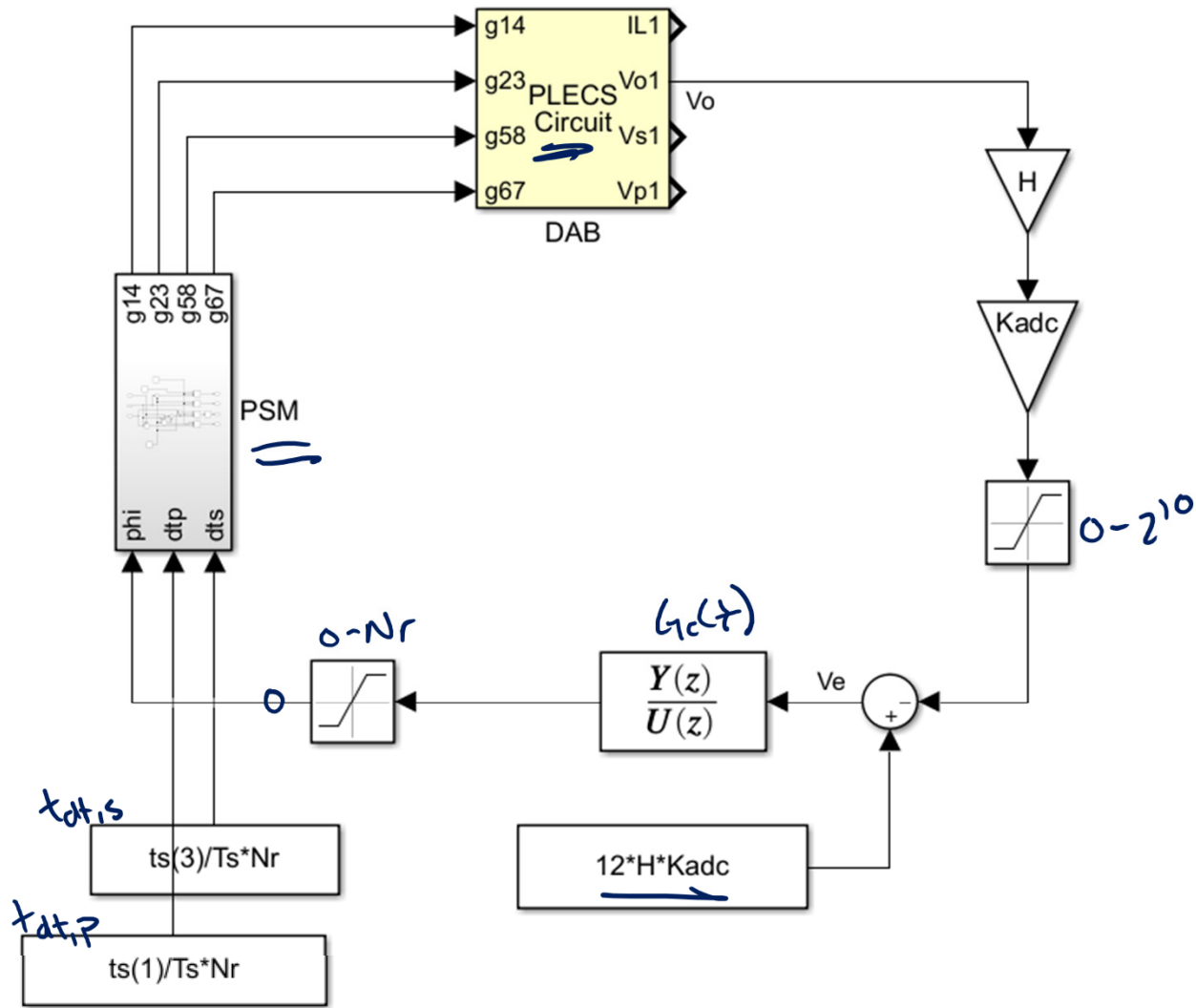


Simulation (Small Signal)

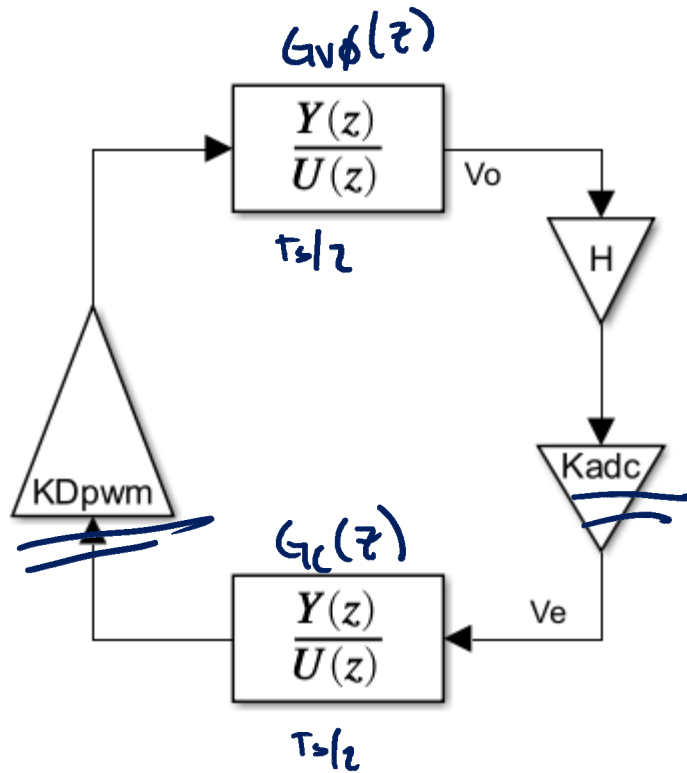


Simulation

0-Nr continuous sawtooth


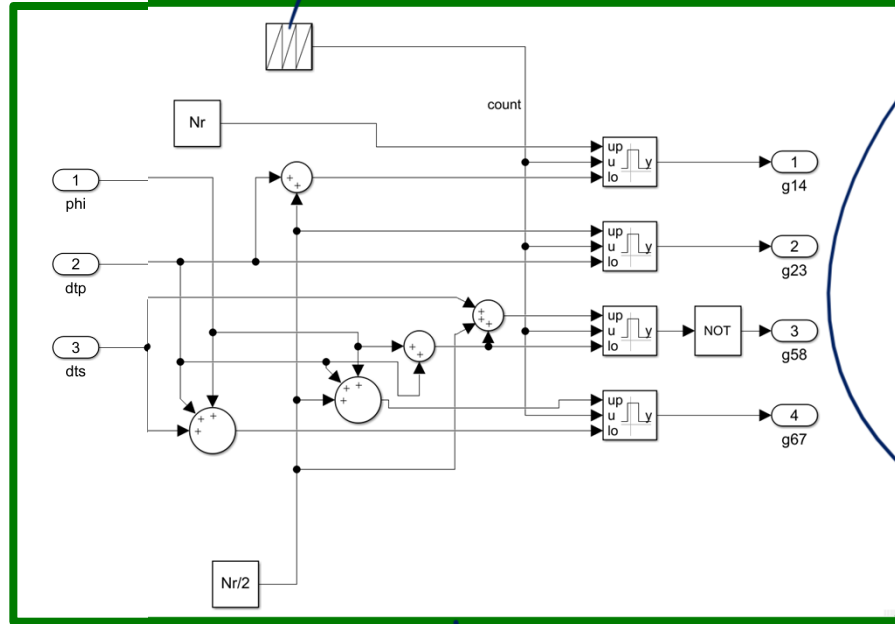


Phase shift modulator

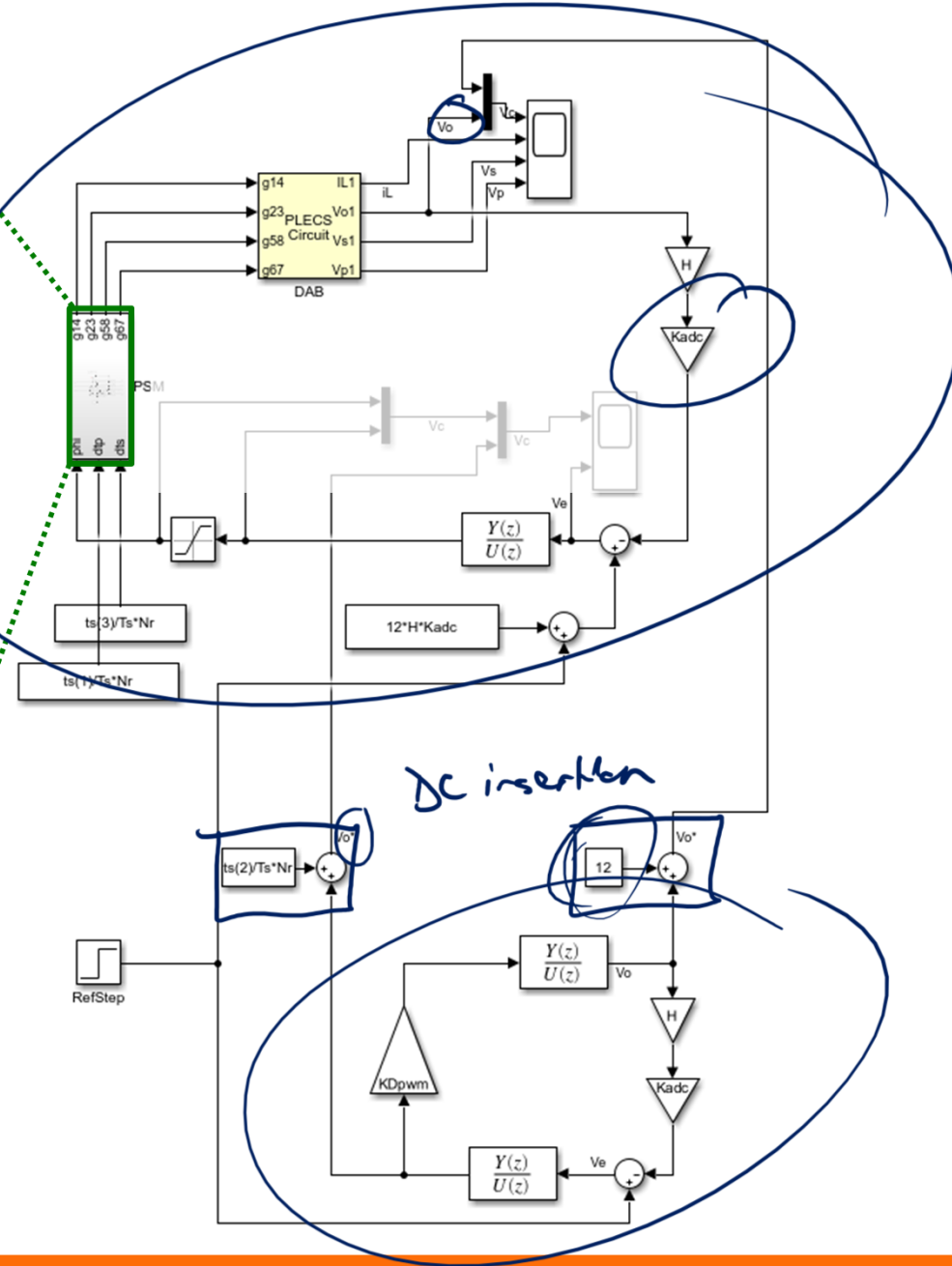



DC insertion

Large Signal, No Quantization

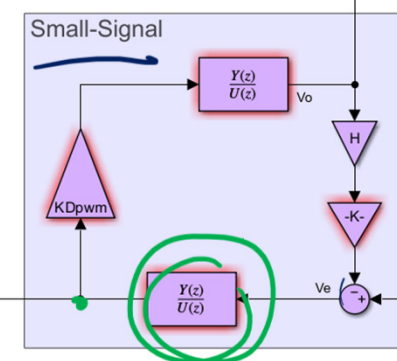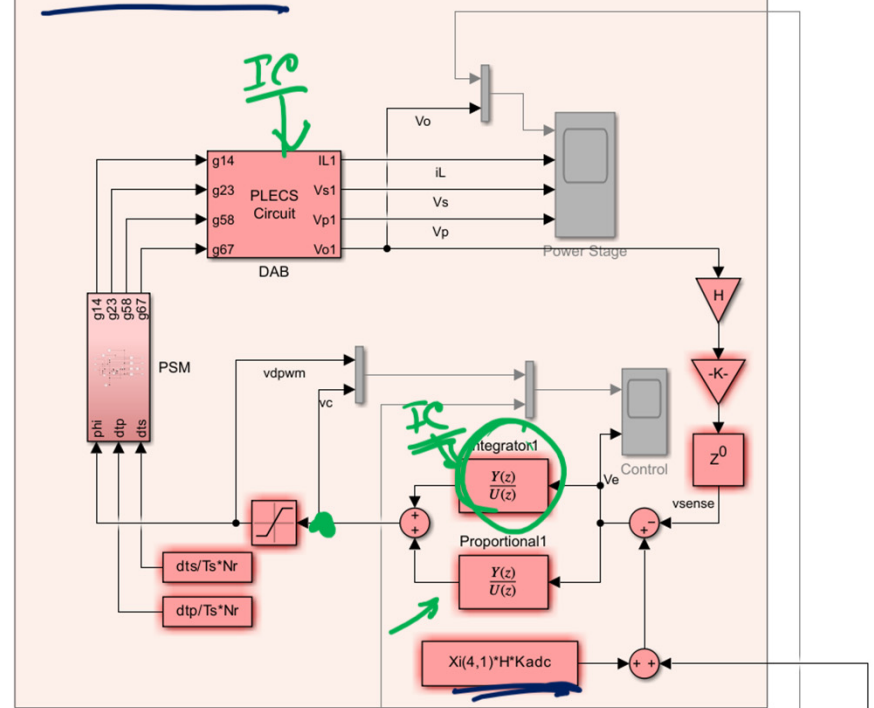


0.05V
RefStep
step
||

Simulation Results

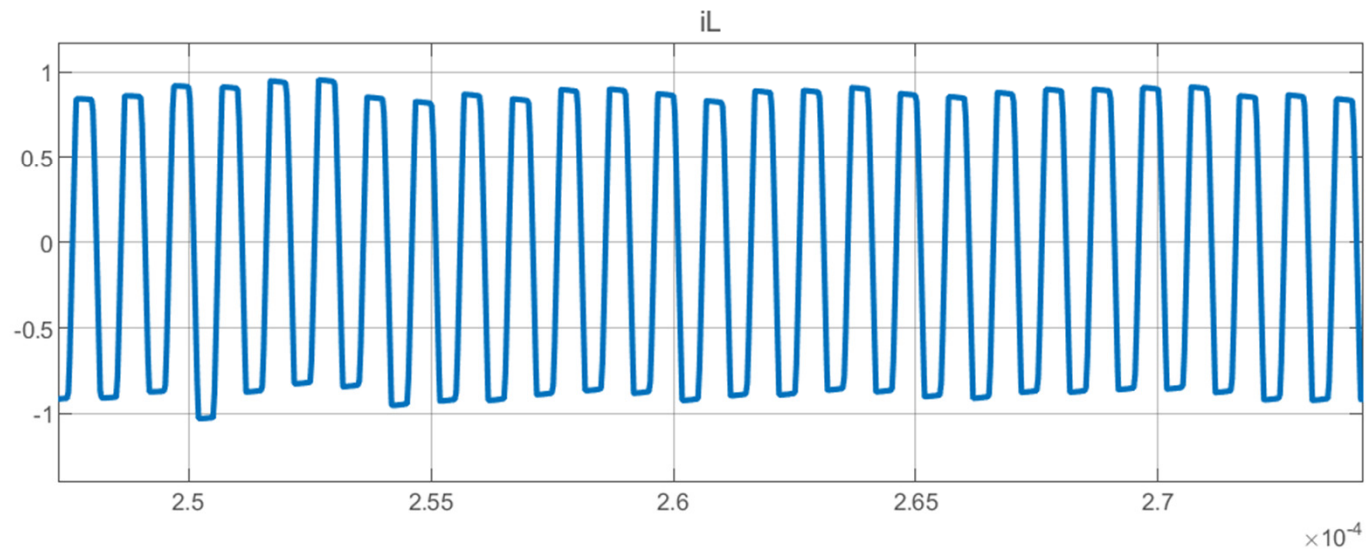
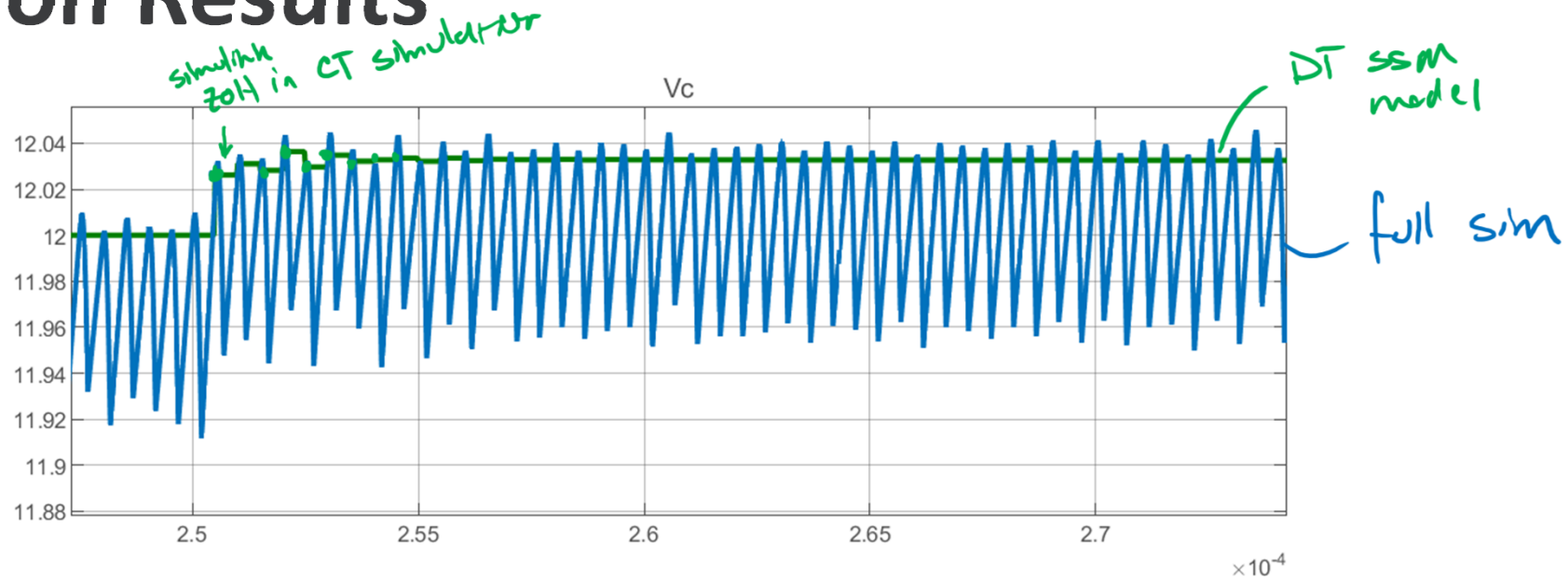


ac Waveform Comparison


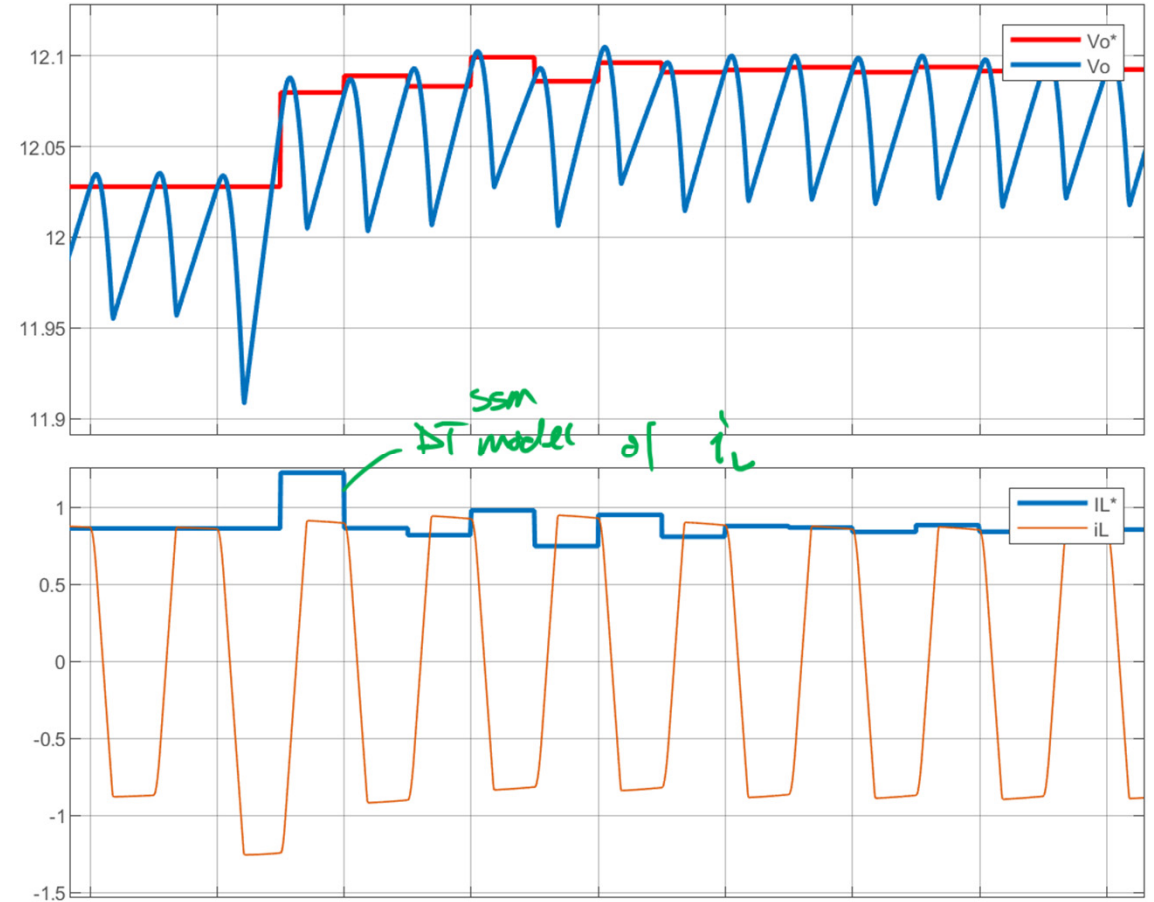


Half-cycle symmetric DAB model


Inverting ac waveform

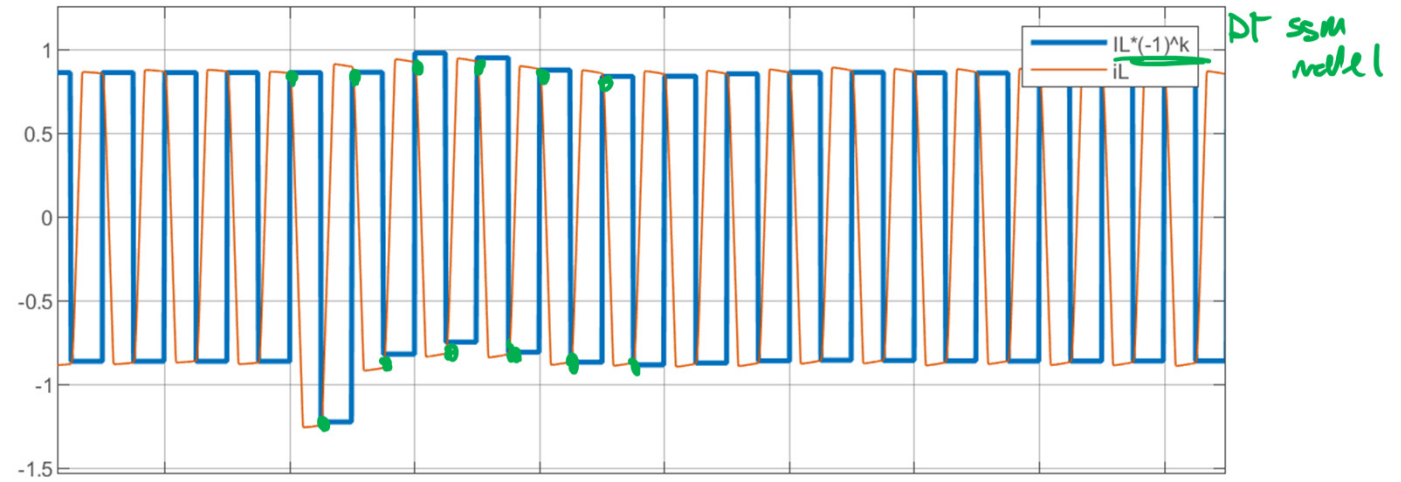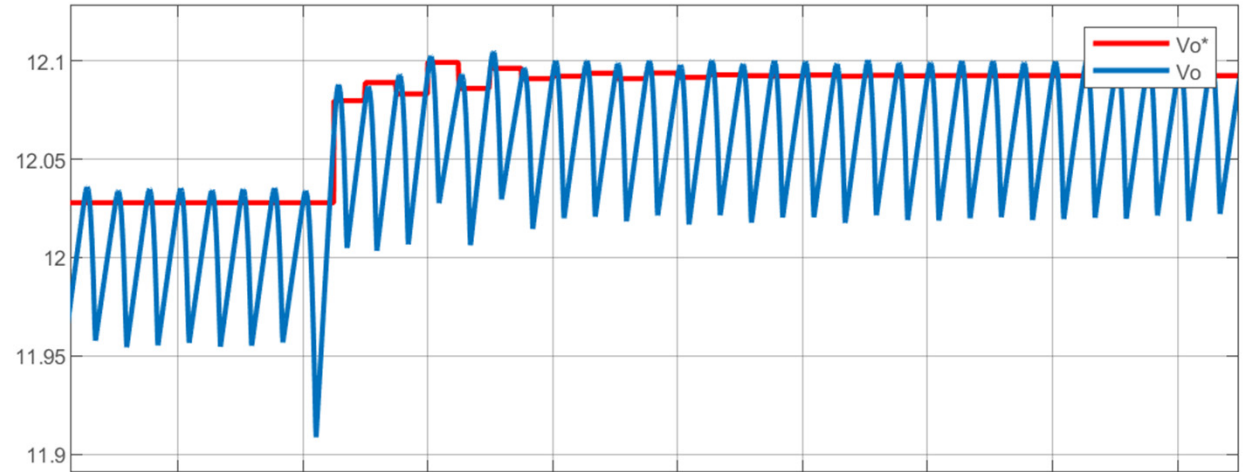

Simulation Results (cont)

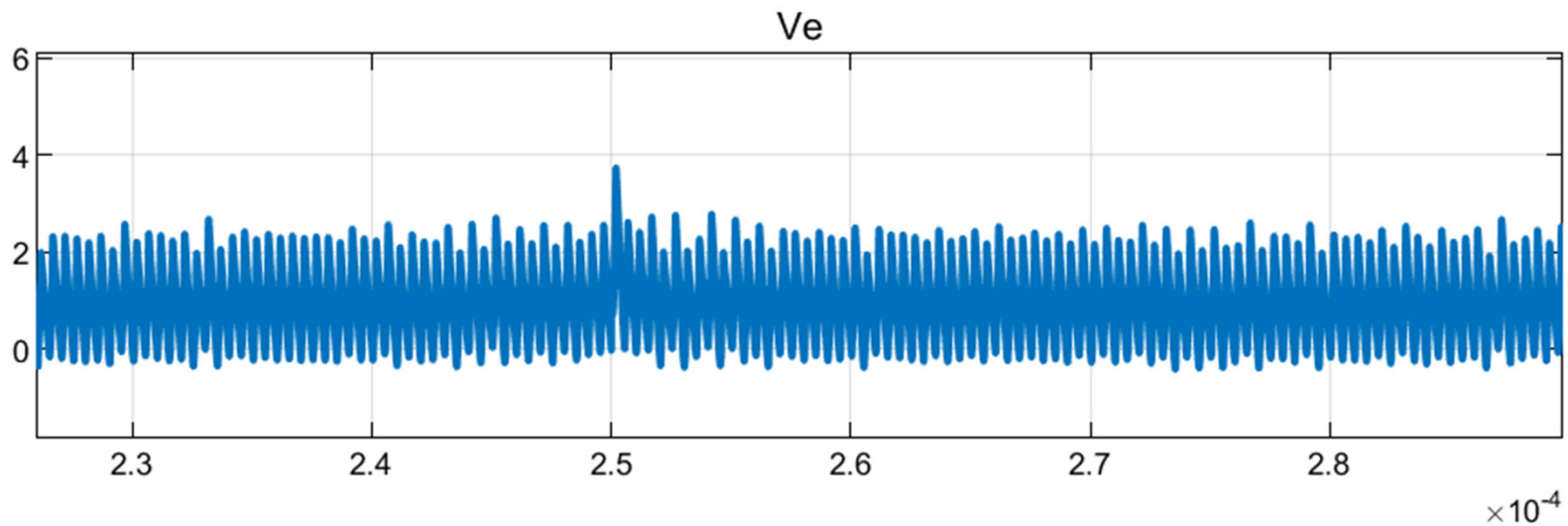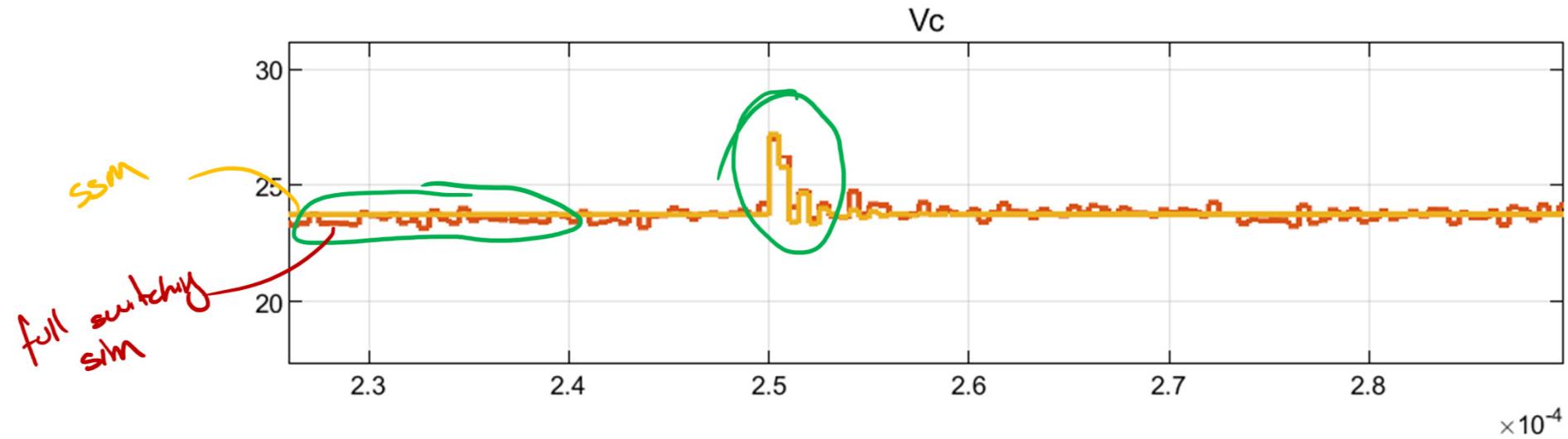


Simulation Results (max step 10ps)

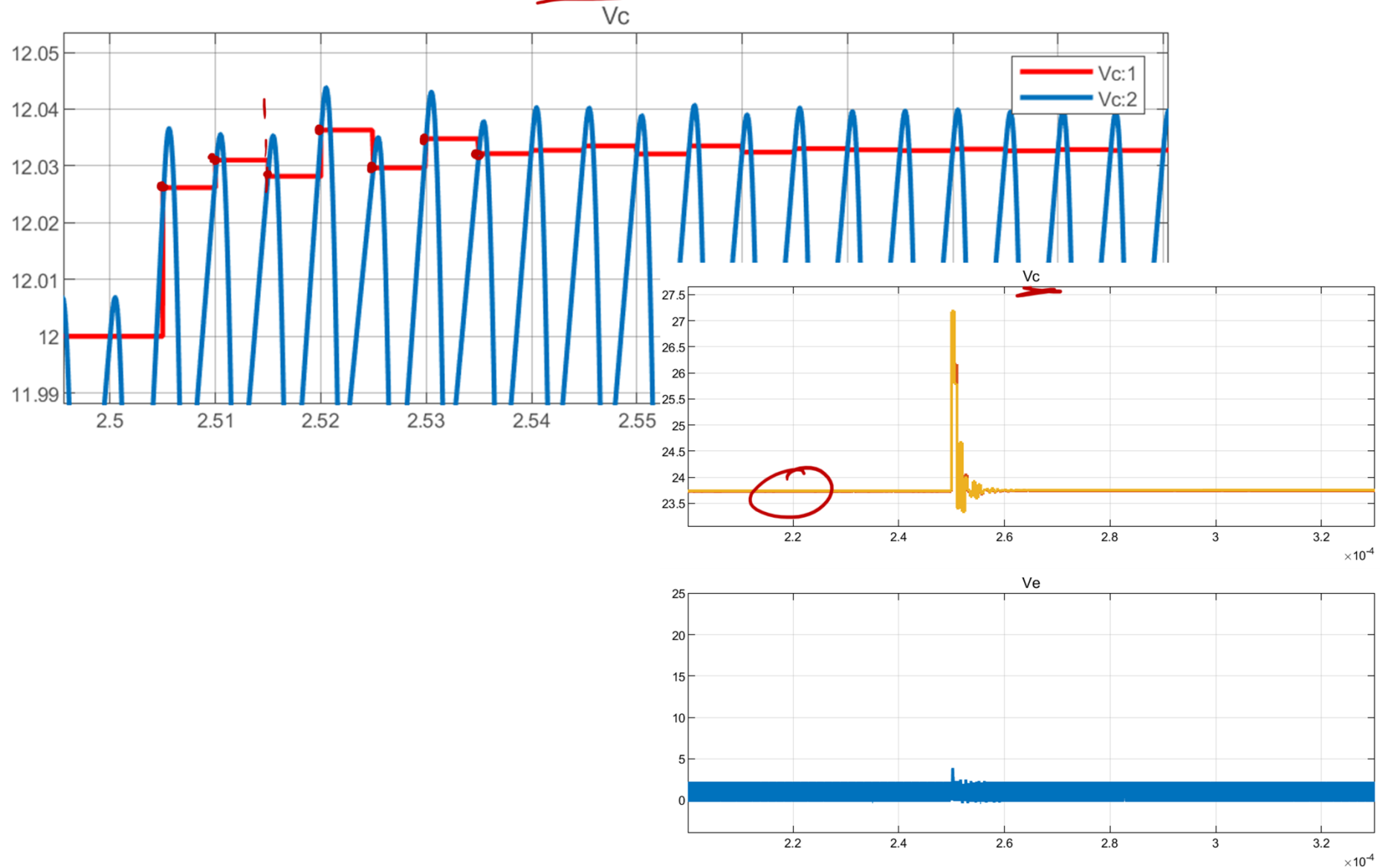




Quantization




0-Nr integer counter

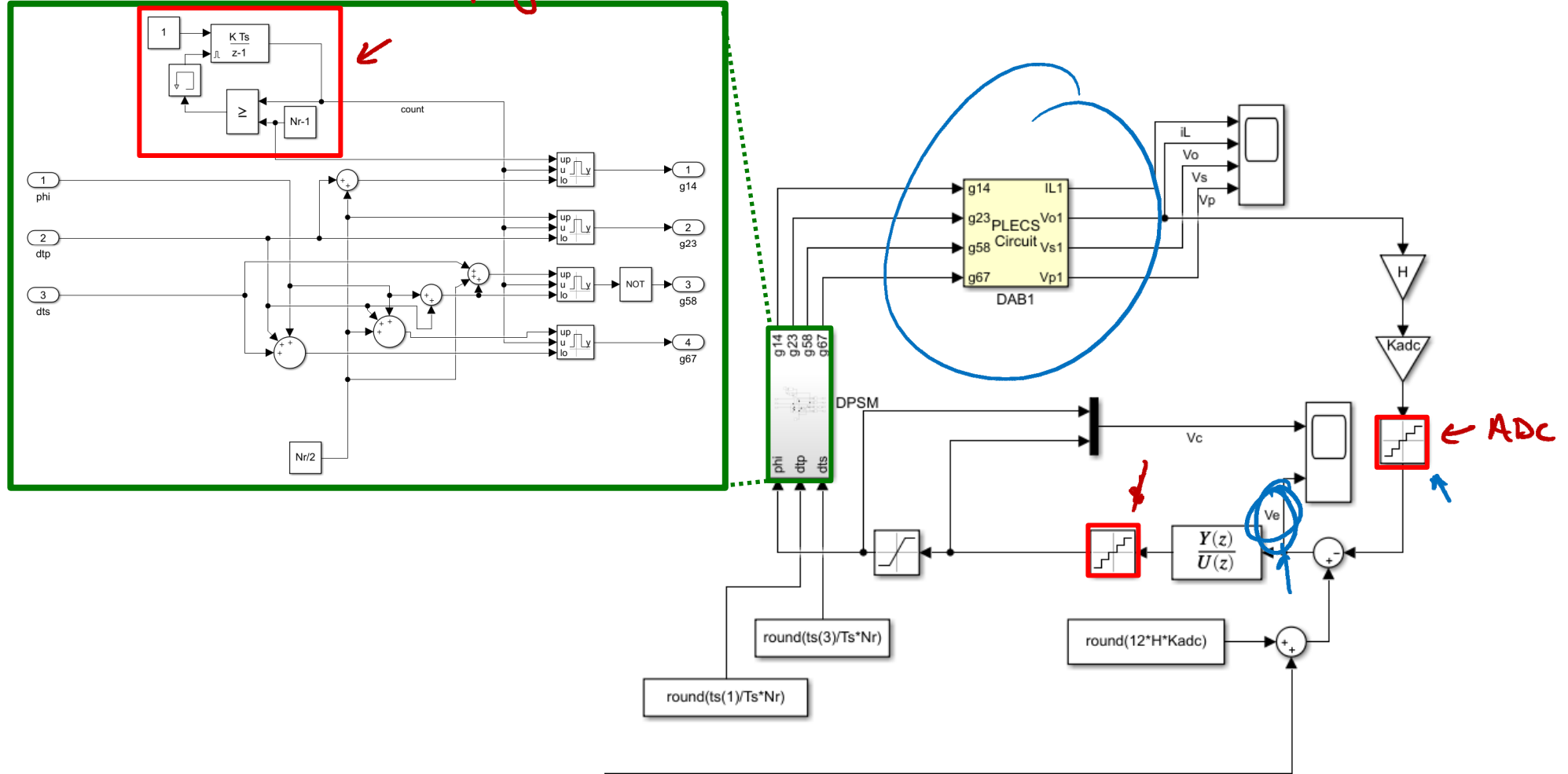


Comment out

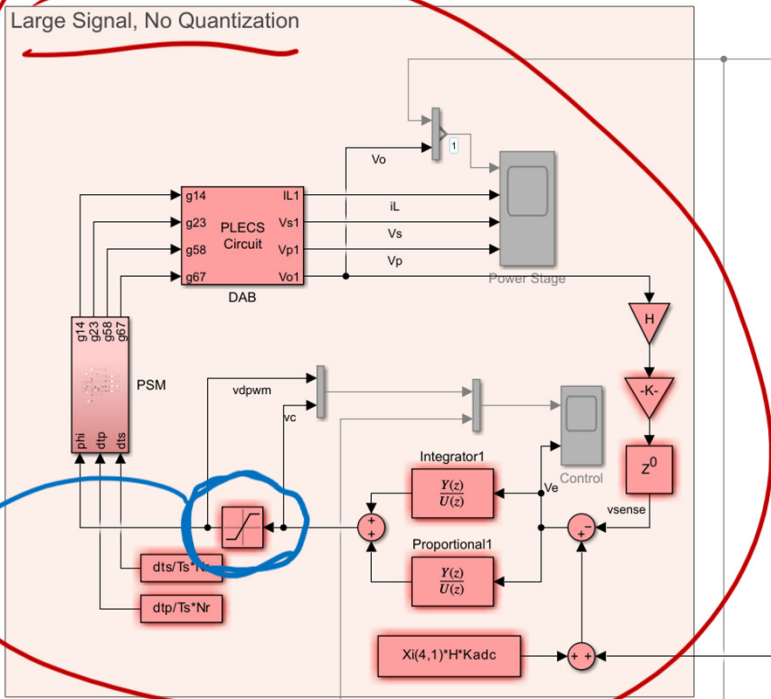

Limit $\varphi \approx \frac{\pi}{4}$

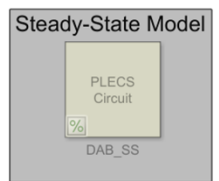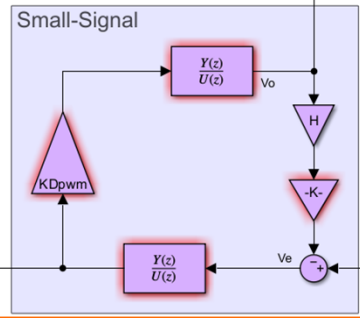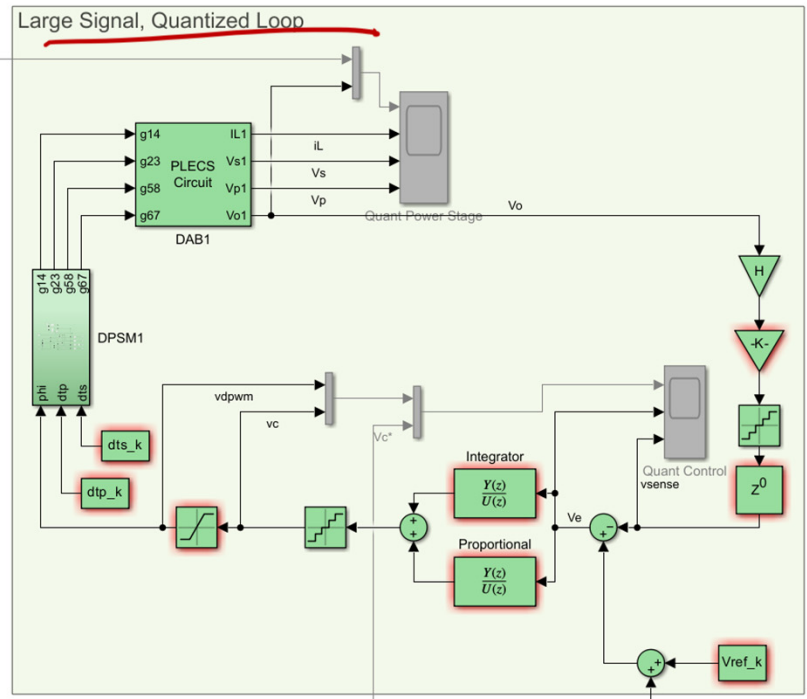

Simulation with Quantization

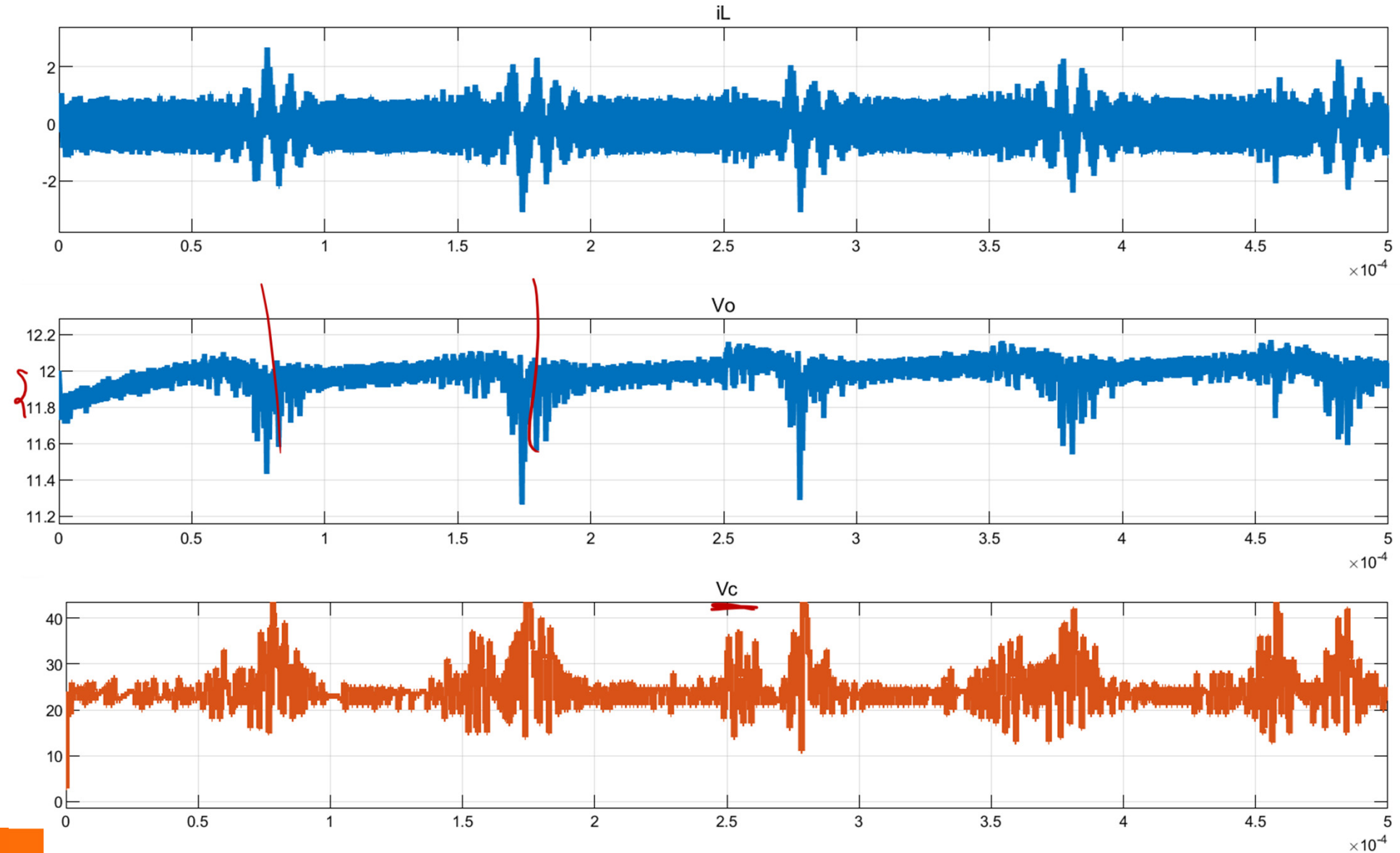

Quantization Impact


Caused Limit cycling

$$g_{Vo}^{ADC} = \frac{1}{K_{ADC}} \frac{1}{H} = \frac{V_{FS}}{2^{N_{ADC}}} \cdot 10 = \boxed{32mV} \text{ w/ 10-bit A/D}$$

$$g_{Vo}^{DPCM} = \frac{1}{N_r} \left(\frac{\partial M(\varphi)}{\partial \varphi} \bigg|_{\varphi_0} \right) \cdot V_g = \boxed{3.07V!}$$

@ $N_r = 200$

Note: DAB \approx

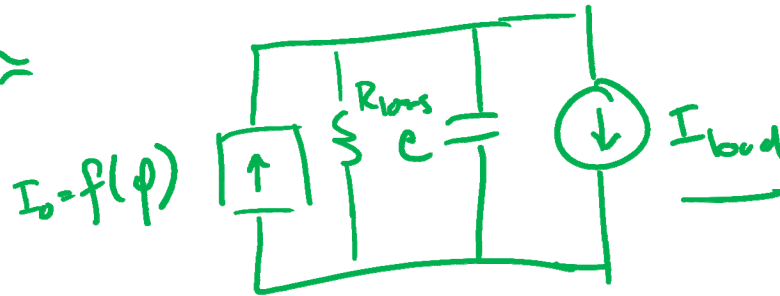

$g_{Vo}^{DPCM} \Rightarrow g_{Vo}^{ADC} \sim 100x$
 limit cycling will occur

Try to remove Limit cycling:

DPCM: Add 6-bits to resolution (e.g. by a hybrid DPCM)

$$N_r = 200 \cdot 2^6 = 200 \cdot 64 = 12800$$

ADC: Drop ADC resolution to 9 bits


$$g_{Vo}^{ADC} = 64mV$$

128x
 change in quantization
 comparison

New Compensator


OLD

Bode Diagram

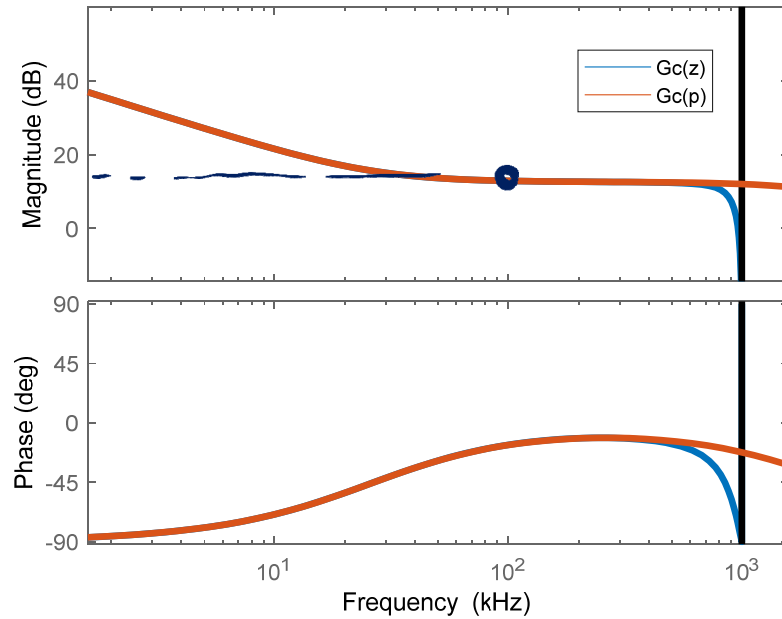

New

Bode Diagram

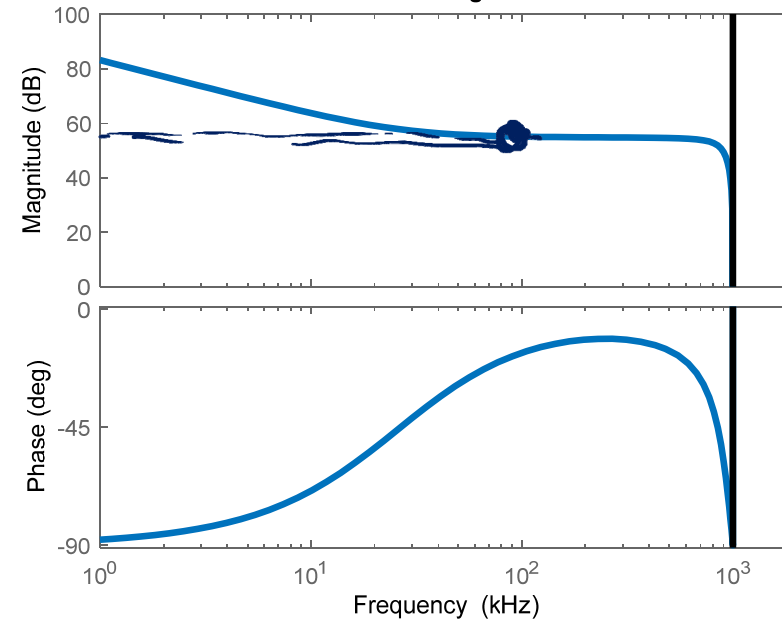


12x

$$\left\{ \begin{array}{l} k_i' = k_i \cdot 12x \\ k_p' = k_p \cdot 12x \end{array} \right. \left. \begin{array}{l} \downarrow \\ \text{new} \end{array} \right. \quad \left. \begin{array}{l} \downarrow \\ \text{old} \end{array} \right.$$

} $T(z)$ remains unchanged

High Res Modulator

still Limit Cycling!

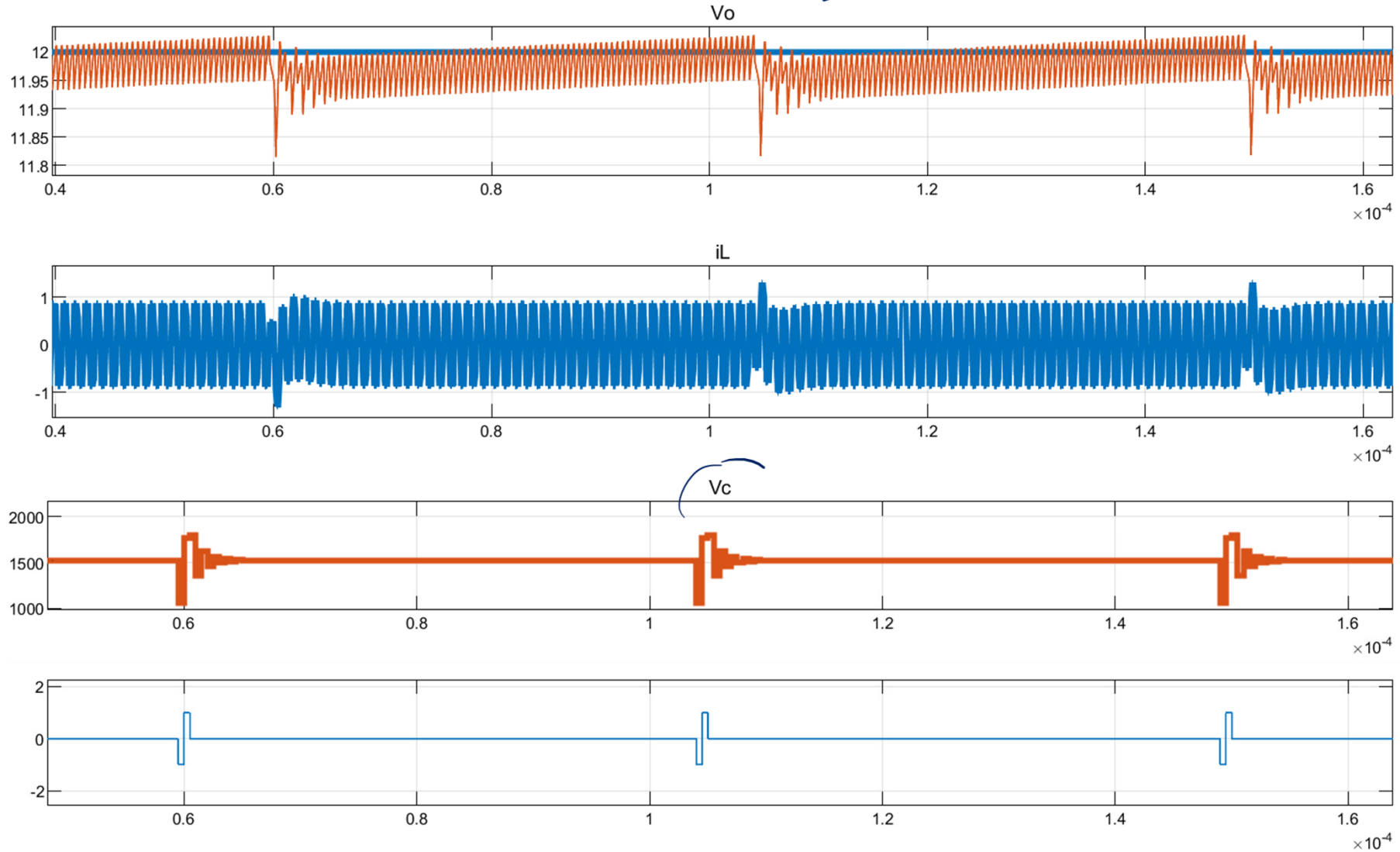

Integral Gain



$$k_i' = 22$$

$$t_p' = 435.5$$


because $k_i' > 1$, we can only get steady state $\tilde{\phi}$ values of $n \cdot 22$

Can drop k_i to 1

New Compensator

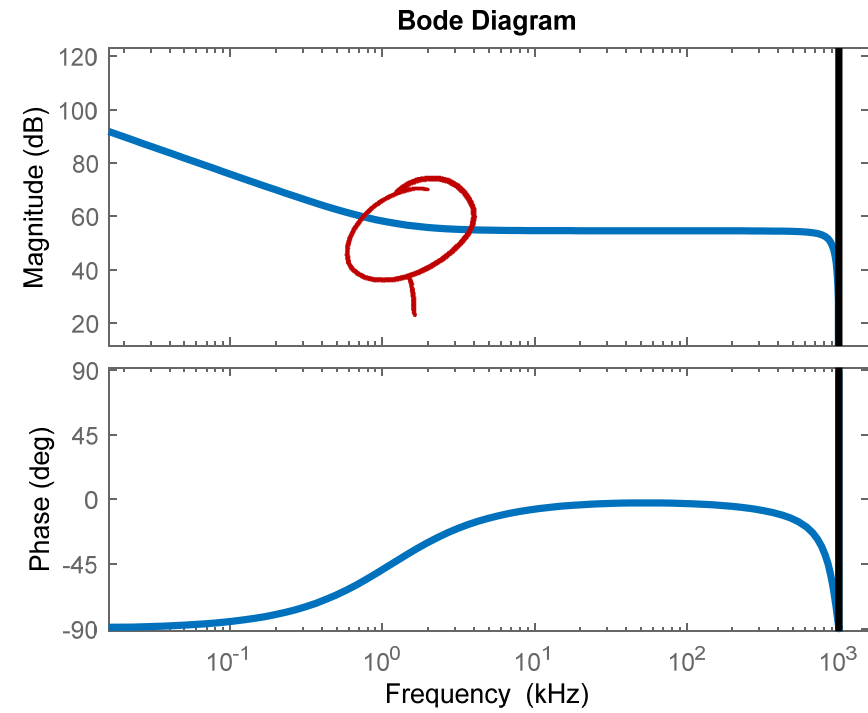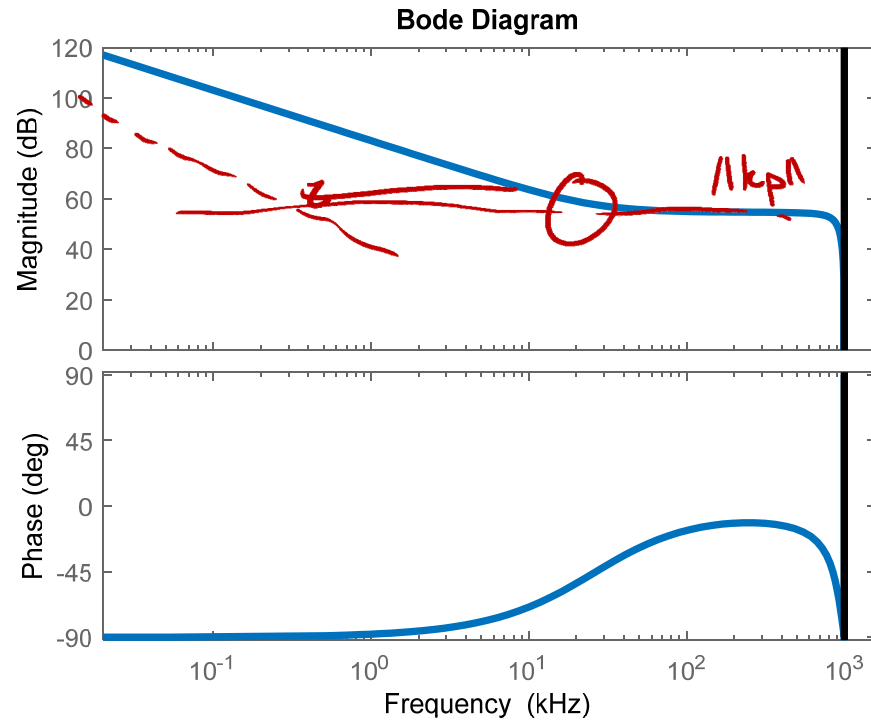

Low Ki


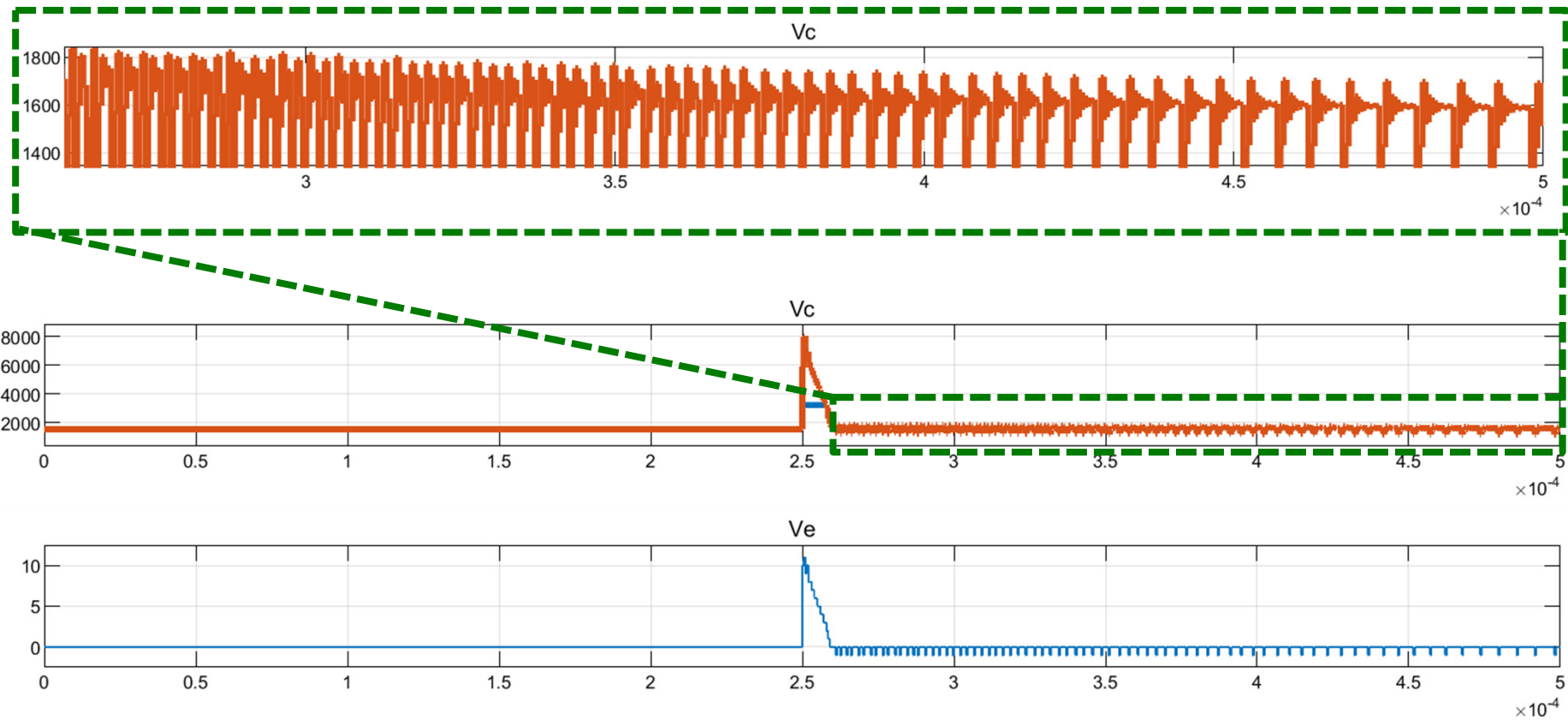


Anti-Windup



Not a problem in previous simulation

2nd transient to decrease integral term.

Integral compensator

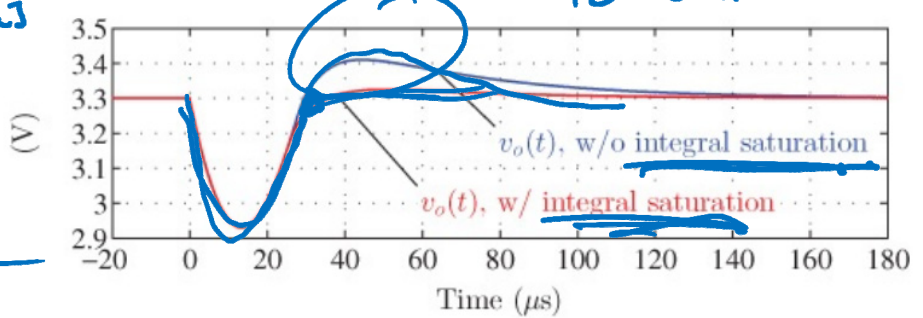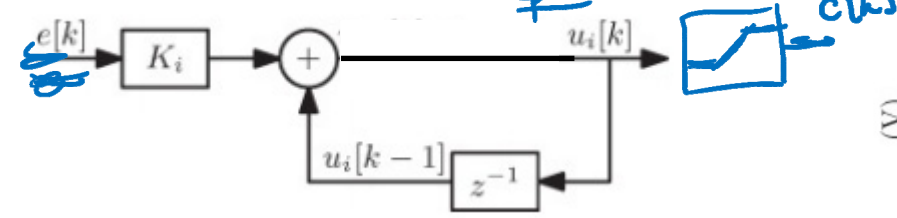

1st solution

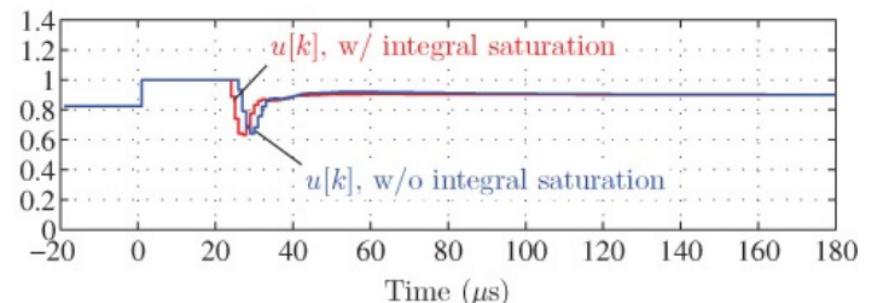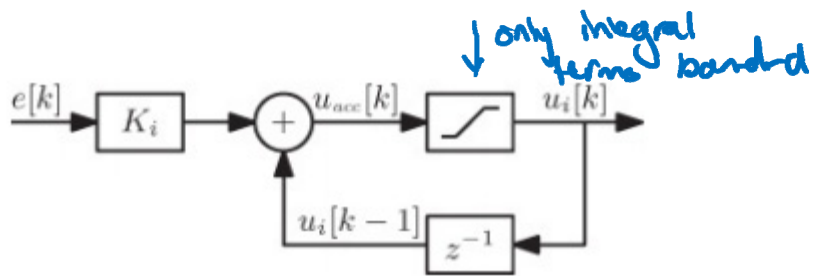

2nd solution (better)

