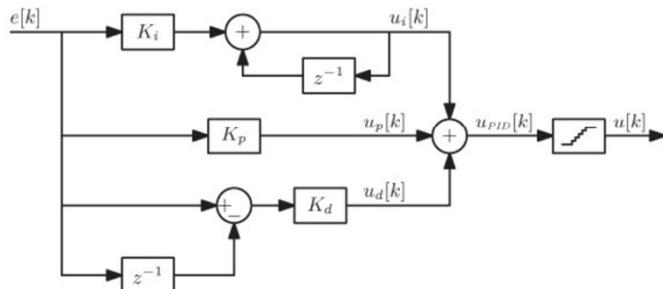


# Compensator Realizations

$$G_{PID}(z; \mathbf{K}) \triangleq K_p + \frac{K_i}{1-z^{-1}} + K_d(1-z^{-1}), \quad \mathbf{K} \triangleq [K_p, K_i, K_d]^T.$$



6.5

$$G_{PID}(z; \mathbf{b}) \triangleq \frac{b_0 + b_1 z^{-1} + b_2 z^{-2}}{1 - z^{-1}}, \quad \mathbf{b} \triangleq [b_0, b_1, b_2]^T.$$

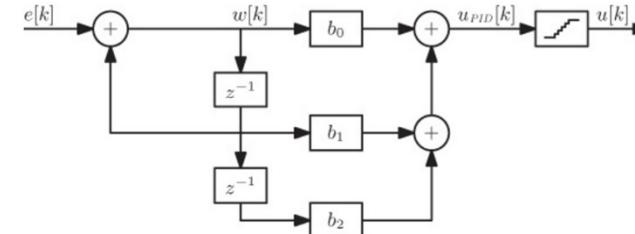


Figure 6.3 Direct realization of a digital PID compensator.

6.6

$$G_{PID}(z; \mathbf{c}) \triangleq \frac{K}{1-z^{-1}} (1 + c_{z_1} z^{-1}) (1 + c_{z_2} z^{-1}), \quad \mathbf{c} \triangleq [K, c_{z_1}, c_{z_2}]^T,$$

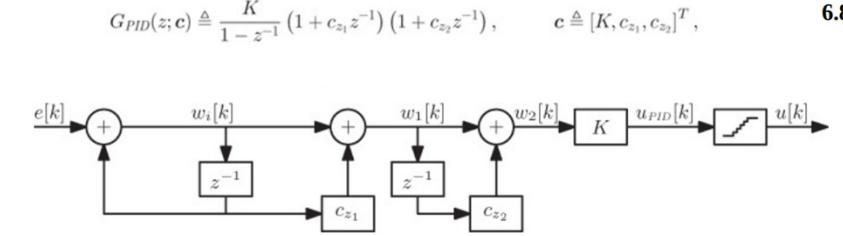


Figure 6.4 Cascade realization of a digital PID compensator.


Figure 6.2 Parallel realization of a digital PID compensator.

# Parallel Realization

$$\begin{aligned} u_p[k] &= K_p e[k], \\ u_i[k] &= u_i[k-1] + K_i e[k], \\ u_d[k] &= K_d(e[k] - e[k-1]), \\ u[k] &= u_p[k] + u_i[k] + u_d[k]. \end{aligned}$$

4.10


The compensator coefficients  $K_p$ ,  $K_i$ , and  $K_d$  are the proportional, integral, and derivative gains, respectively.

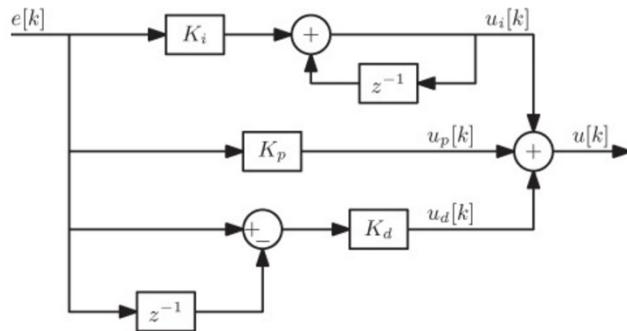

**Figure 4.3** Block diagram of a digital PID compensator in the parallel form.

$$G_{PID}(z) = K_p + \frac{K_i}{1-z^{-1}} + K_d(1-z^{-1}).$$
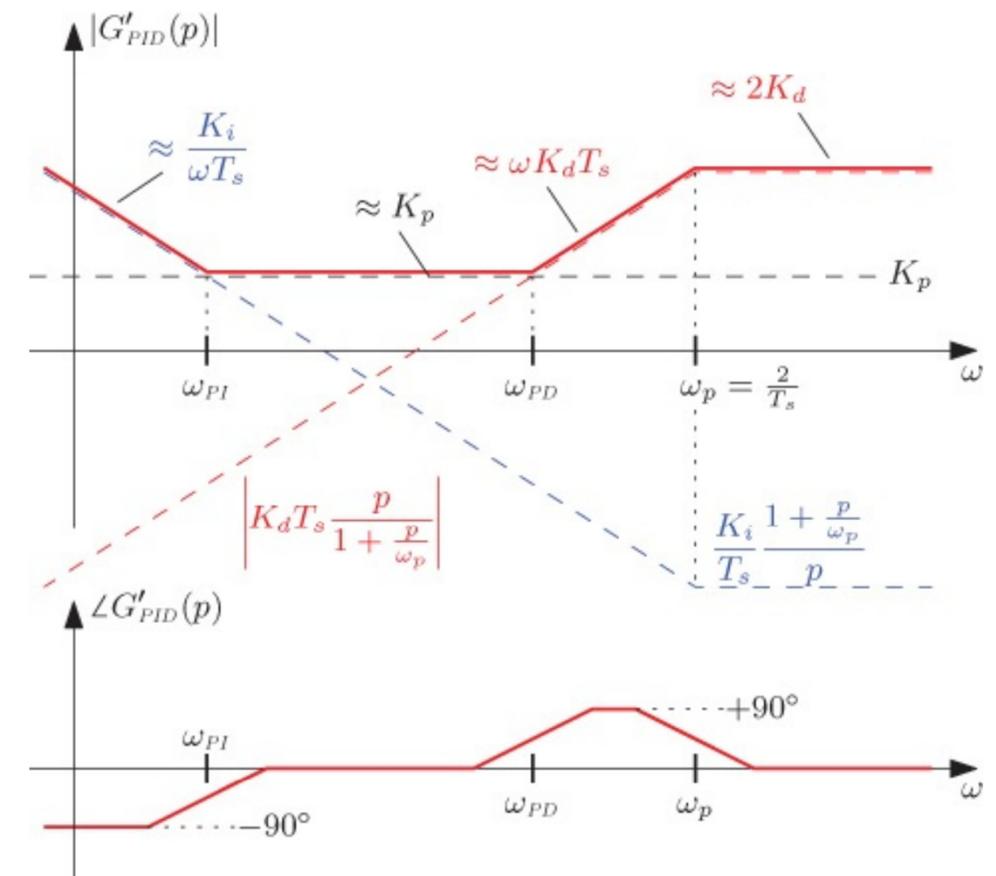
$$G'_{PID}(p) = \underbrace{K_p}_{\text{Proportional term}} + \underbrace{\frac{K_i}{T_s} \frac{1+\frac{p}{\omega_p}}{p}}_{\text{Integral term}} + \underbrace{K_d T_s \frac{p}{1+\frac{p}{\omega_p}}}_{\text{Derivative term}},$$





$$G'_{PID}(p) = G'_{PI\infty} \underbrace{\left(1 + \frac{\omega_{PI}}{p}\right)}_{PI} G'_{PD0} \underbrace{\frac{1 + \frac{p}{\omega_{PD}}}{1 + \frac{p}{\omega_p}}}_{PD},$$

$$K_p = G'_{PI\infty} G'_{PD0} \left(1 + \frac{\omega_{PI}}{\omega_{PD}} - \frac{2\omega_{PI}}{\omega_p}\right),$$


$$K_i = 2G'_{PI\infty} G'_{PD0} \frac{\omega_{PI}}{\omega_p},$$

$$K_d = \frac{G'_{PI\infty} G'_{PD0}}{2} \left(1 - \frac{\omega_{PI}}{\omega_p}\right) \left(\frac{\omega_p}{\omega_{PD}} - 1\right).$$

# Simulation (Large Signal)

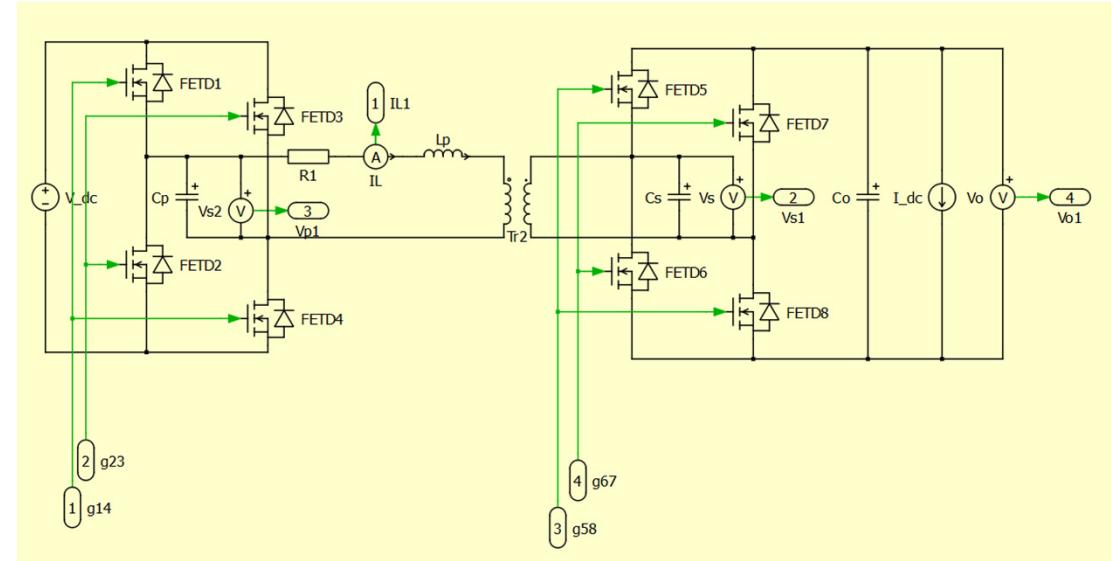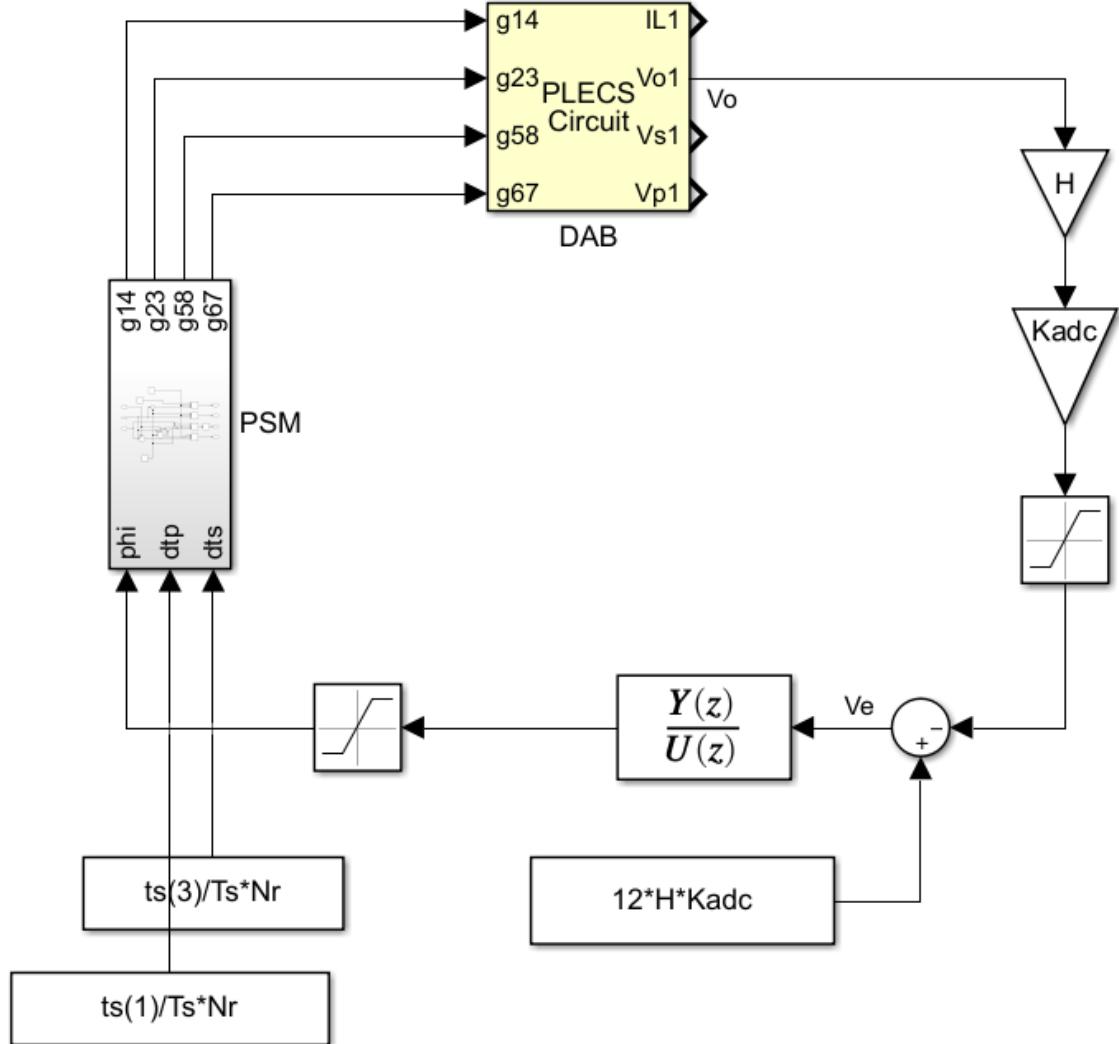


# Alternative Simulation (Large Signal)

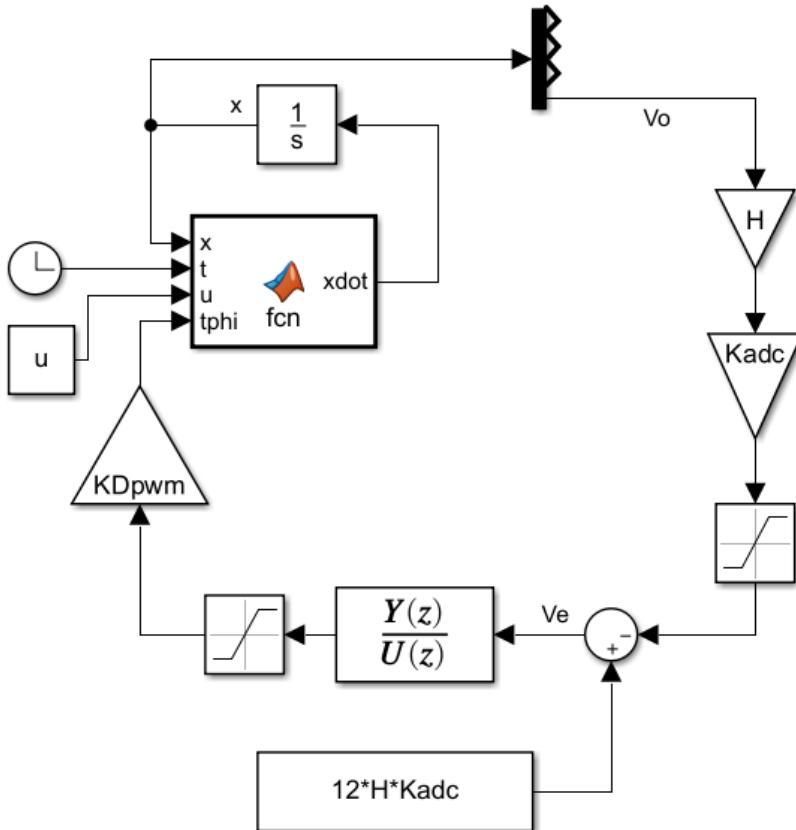


```
function xdot = fcn(x, t,  
u,tphi, A1, A2, B1, B2, Ts)  
  
tp = mod(t,Ts);  
  
if(tp<tphi)  
    xdot = A1*x + B1*u;  
else  
    xdot = A2*x+B2*u;  
end
```


# Simulation (Small Signal)

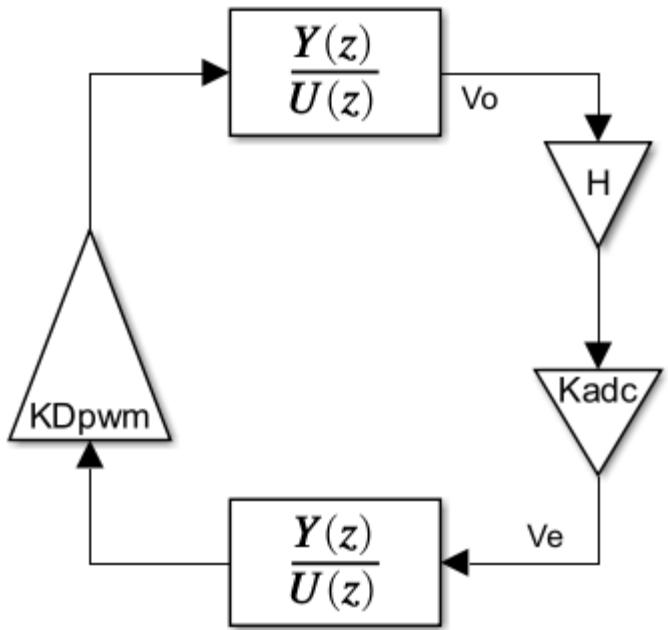


# Simulation

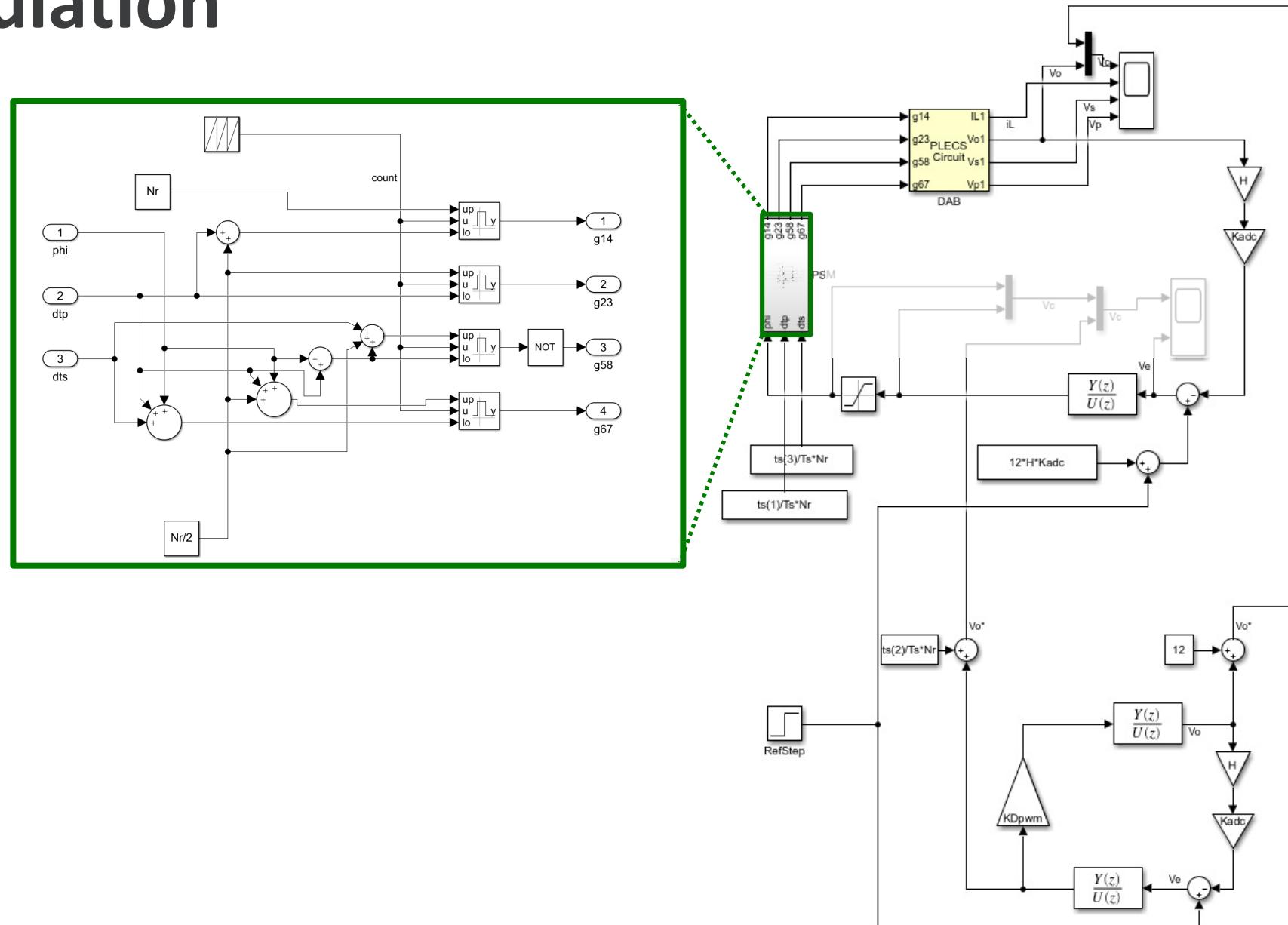


### Large Signal, No Quantization

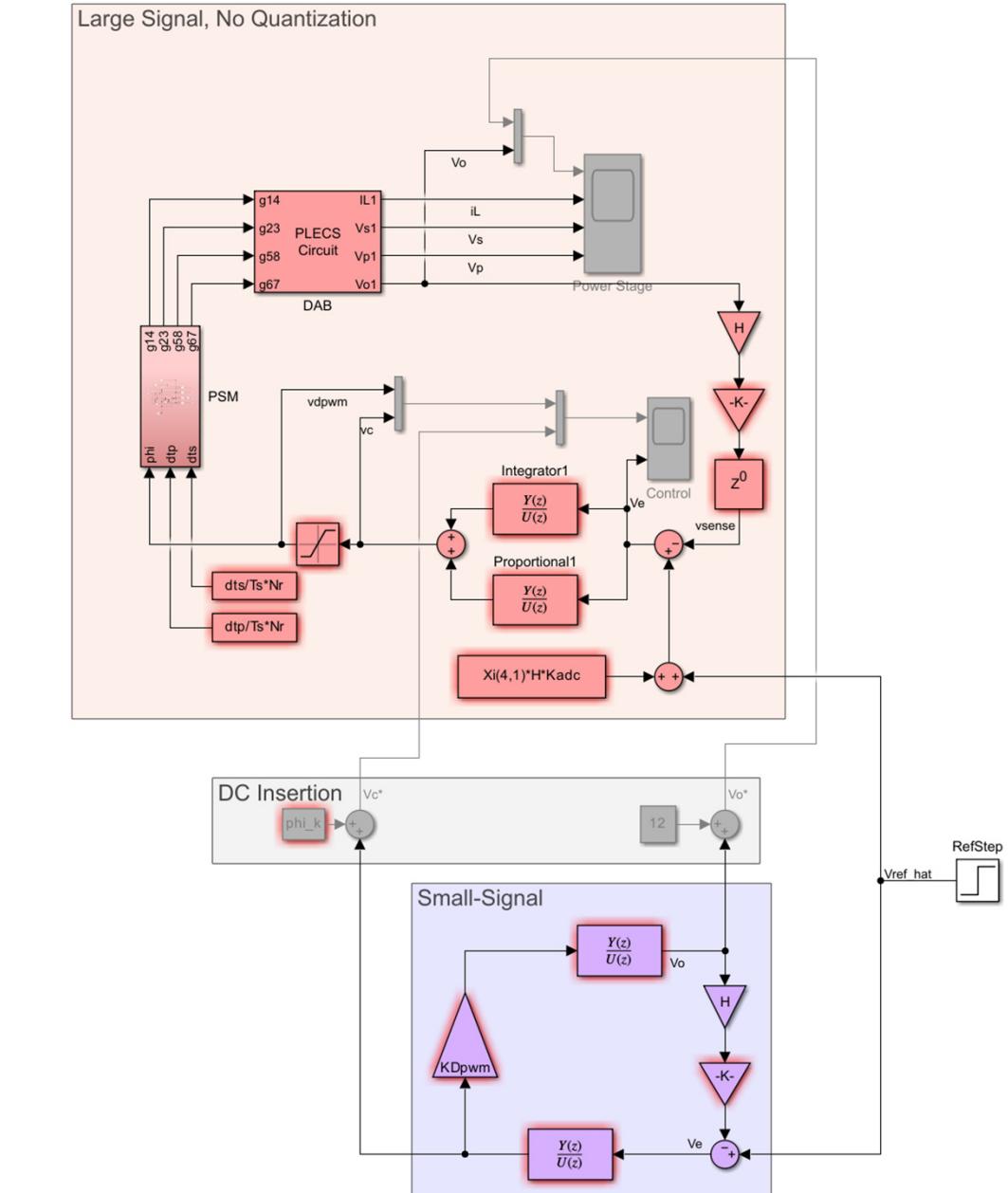


# Simulation Results

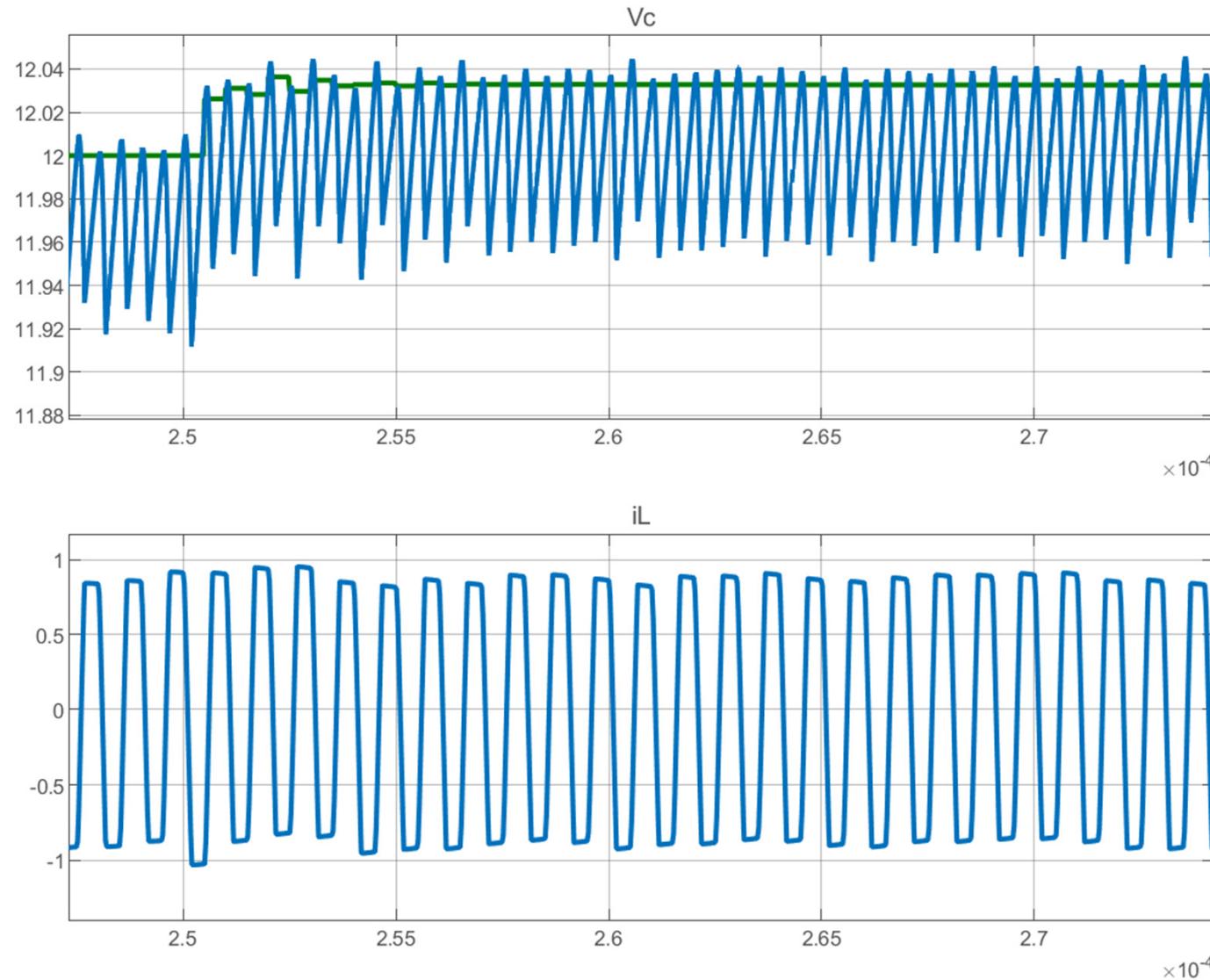

# Simulation Results (cont)

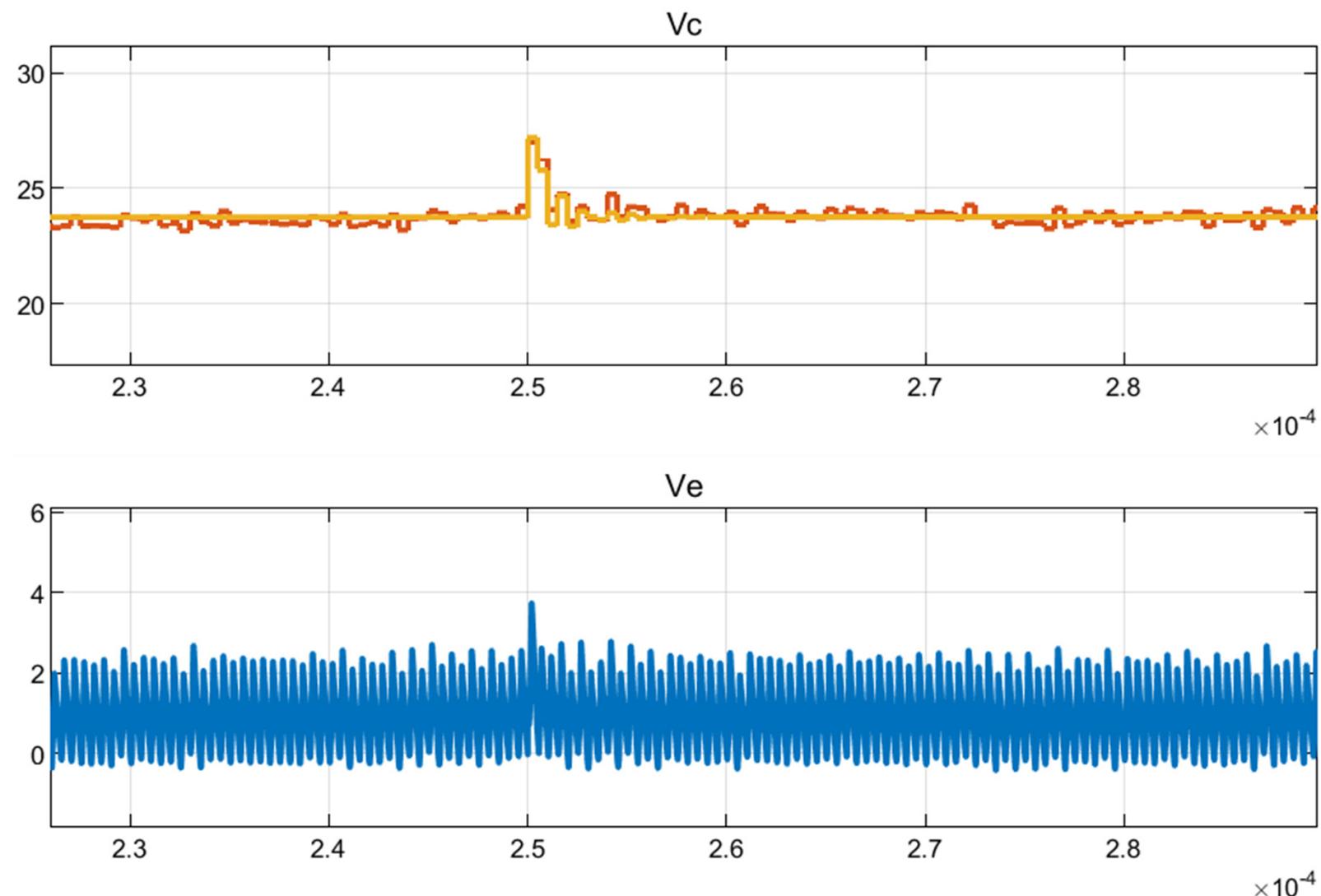



# Simulation Results (max step 10ps)

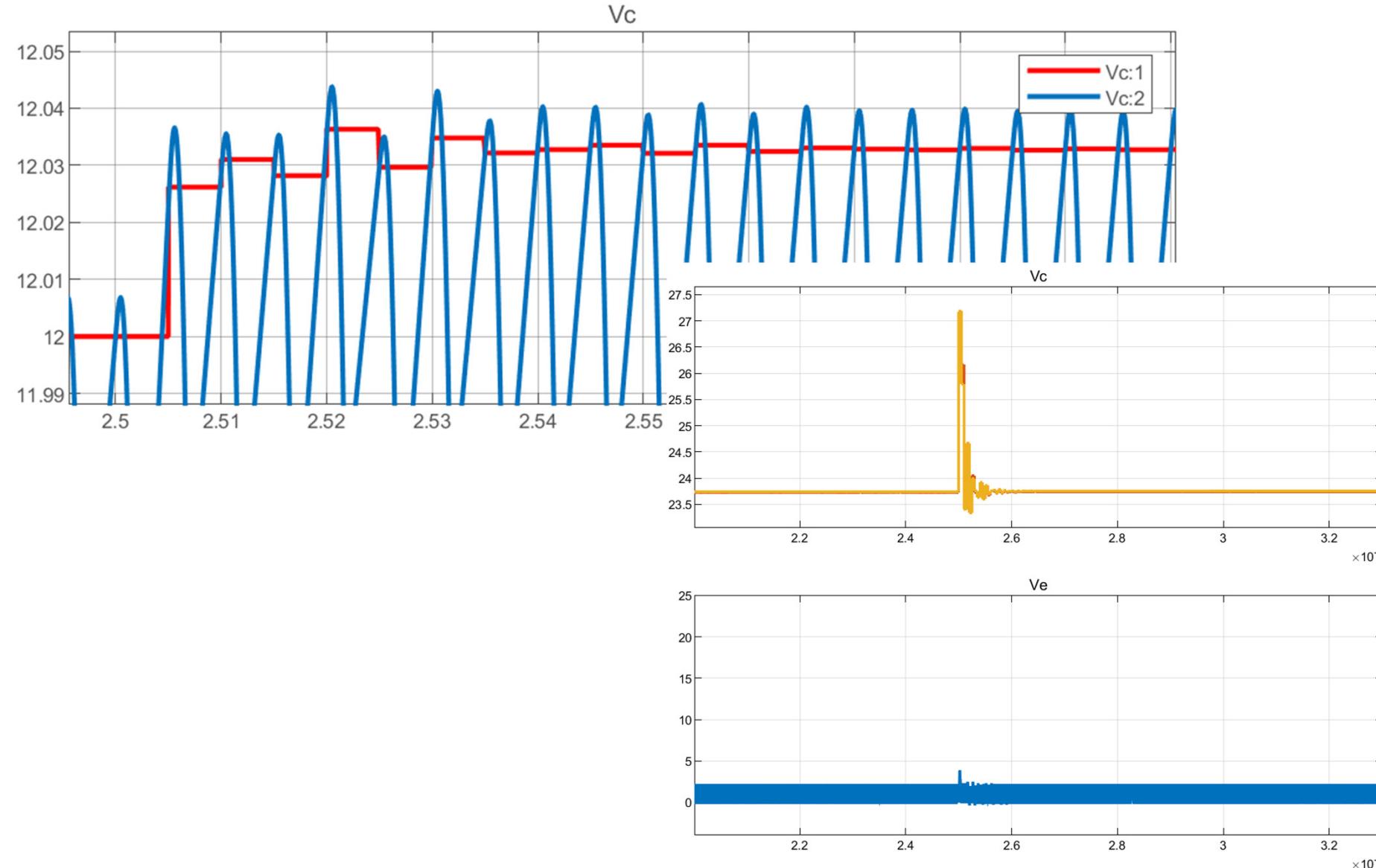




# Quantization

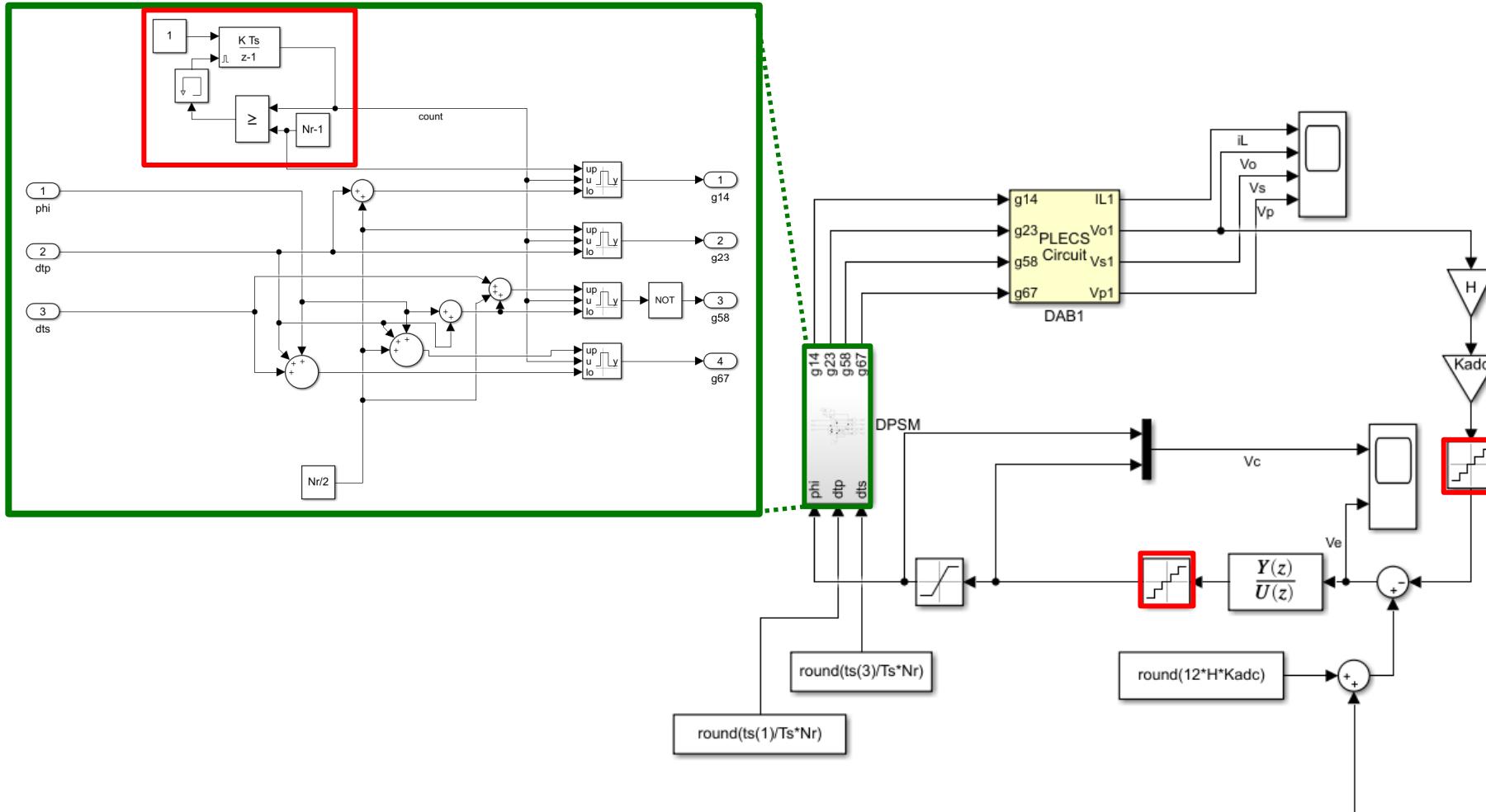

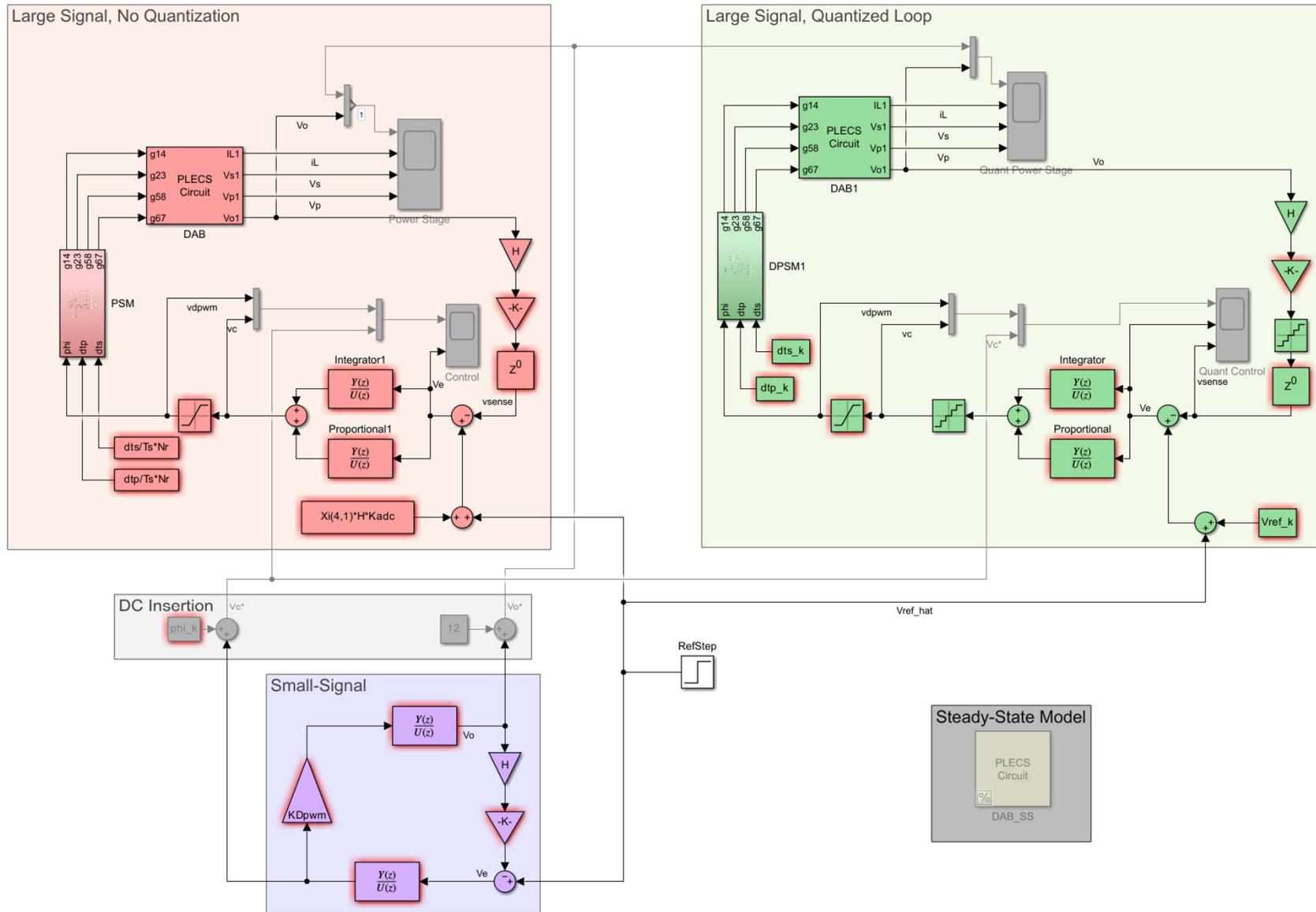


# Simulation with Quantization

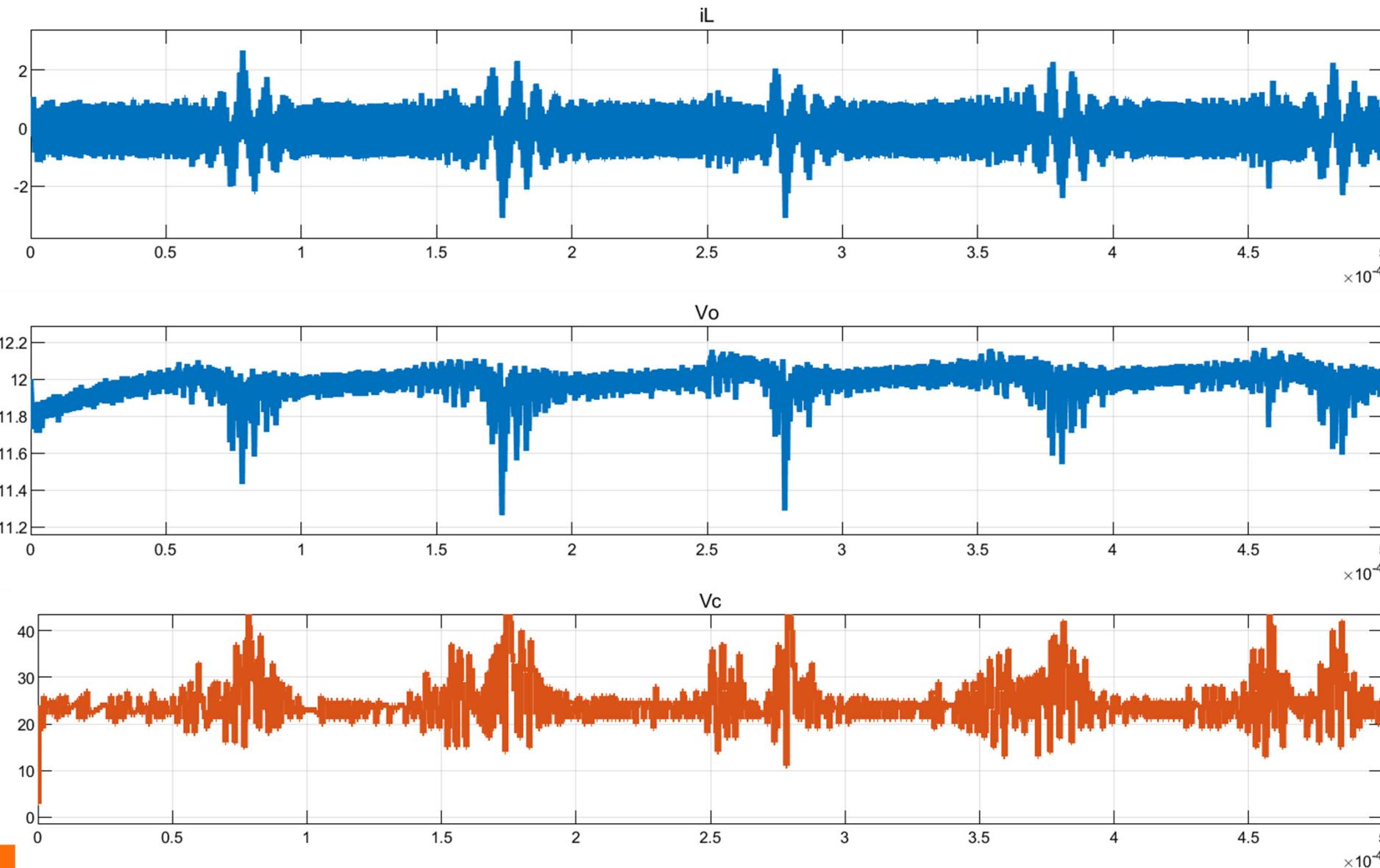


# Quantization Impact

# New Compensator


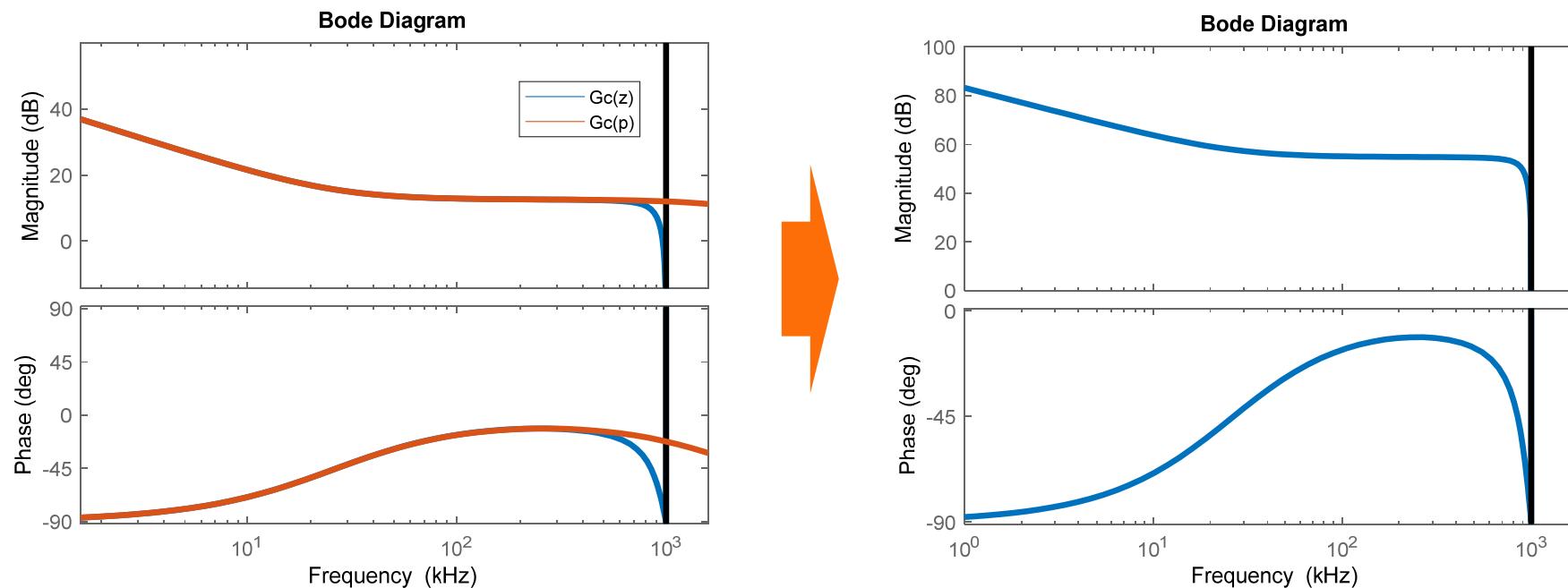


# High Res Modulator

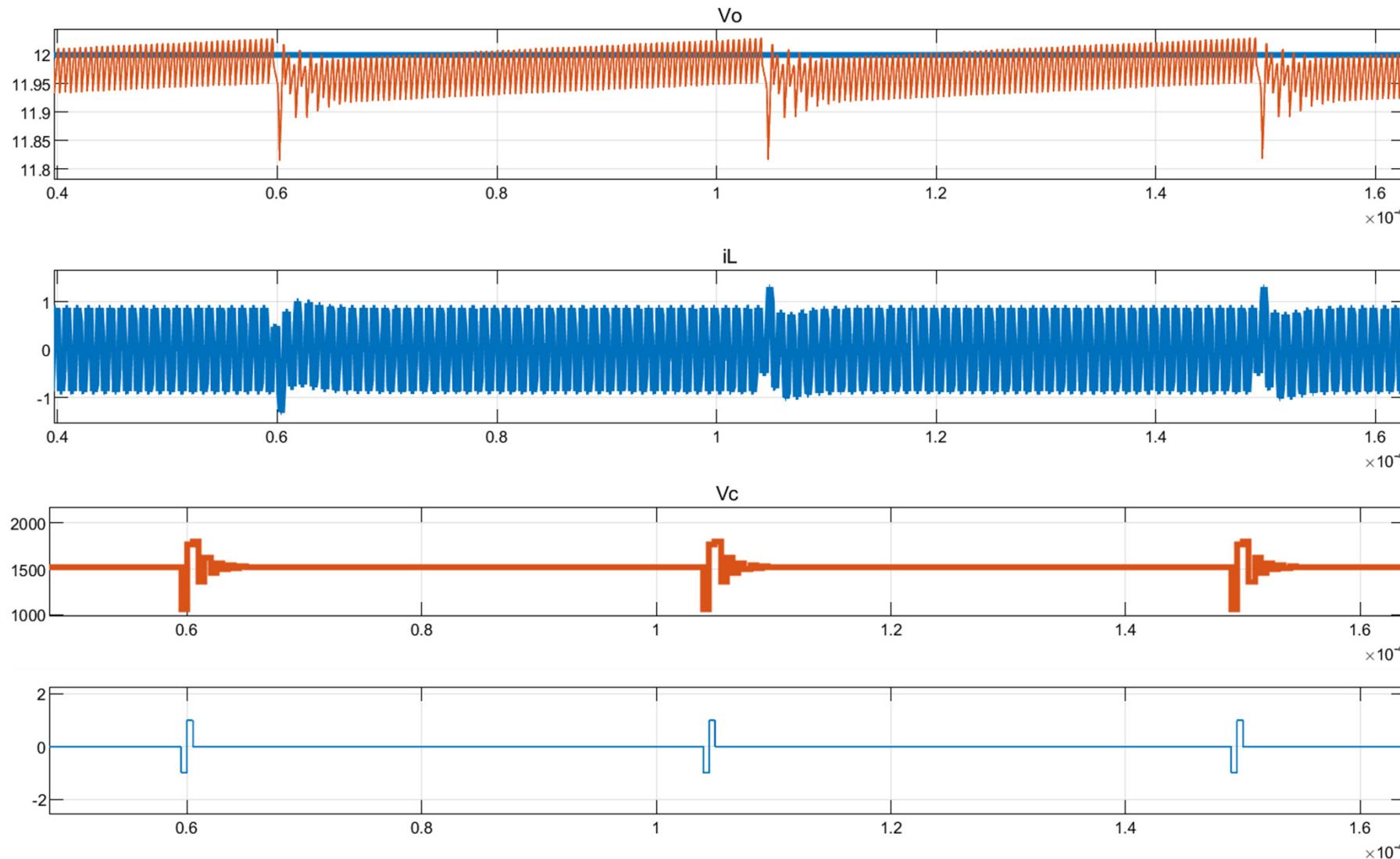


# Integral Gain

# New Compensator

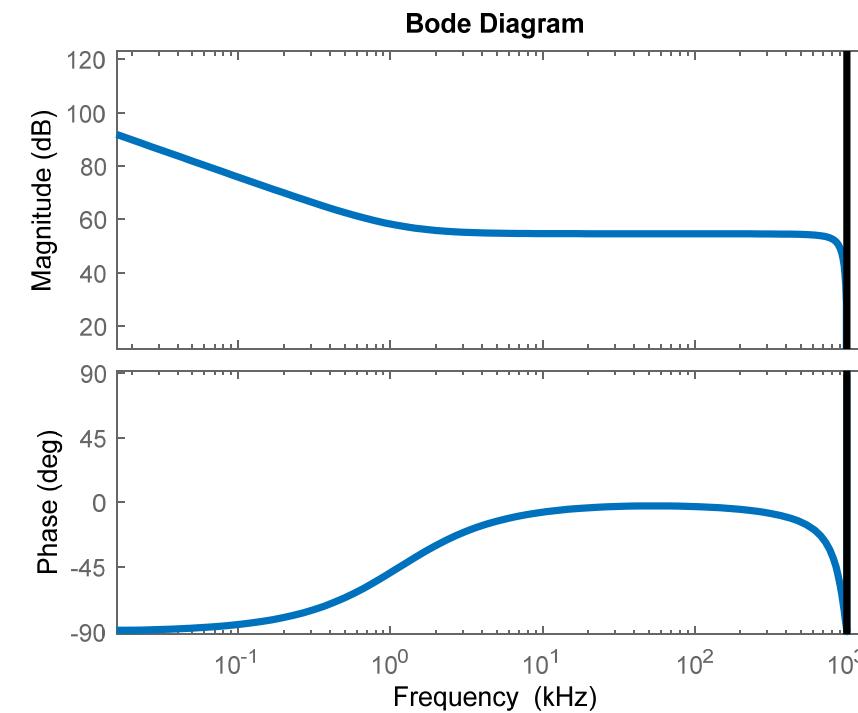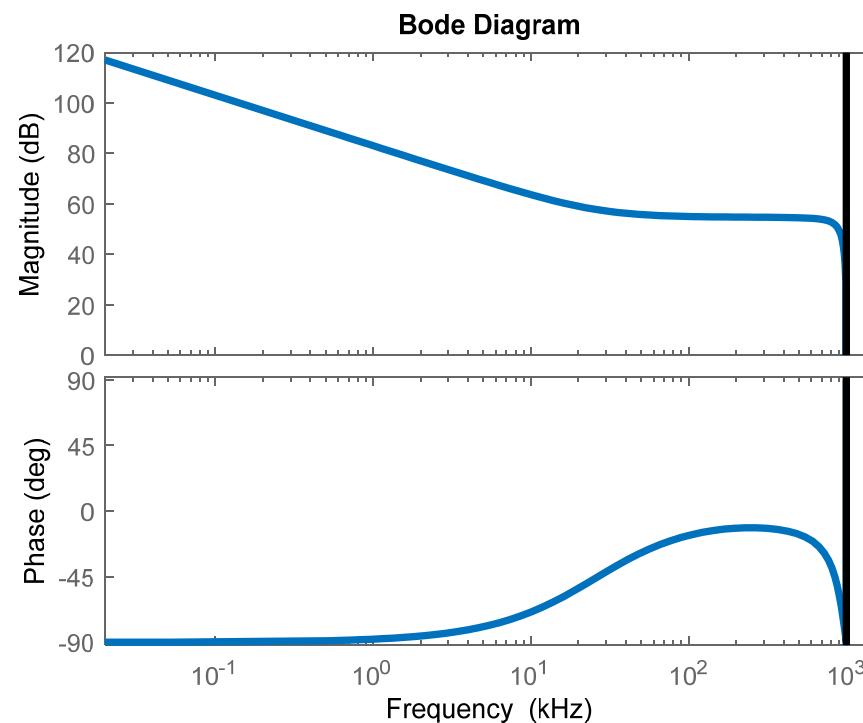

# Low Ki

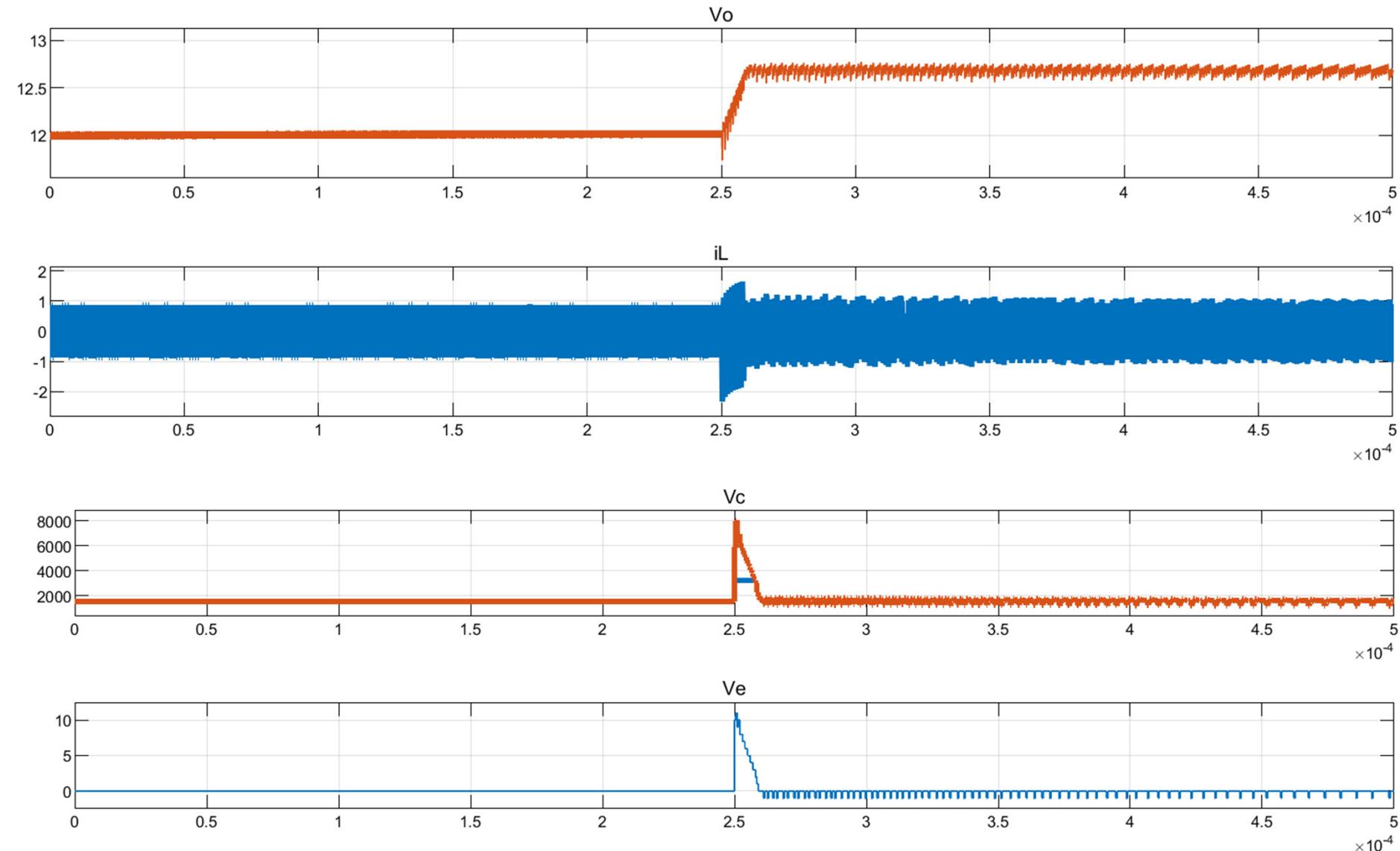

# Low Ki

