

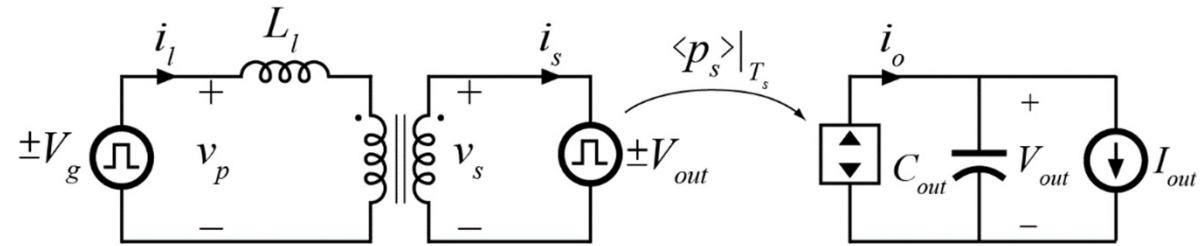


Linear Averaged Modeling of DAB

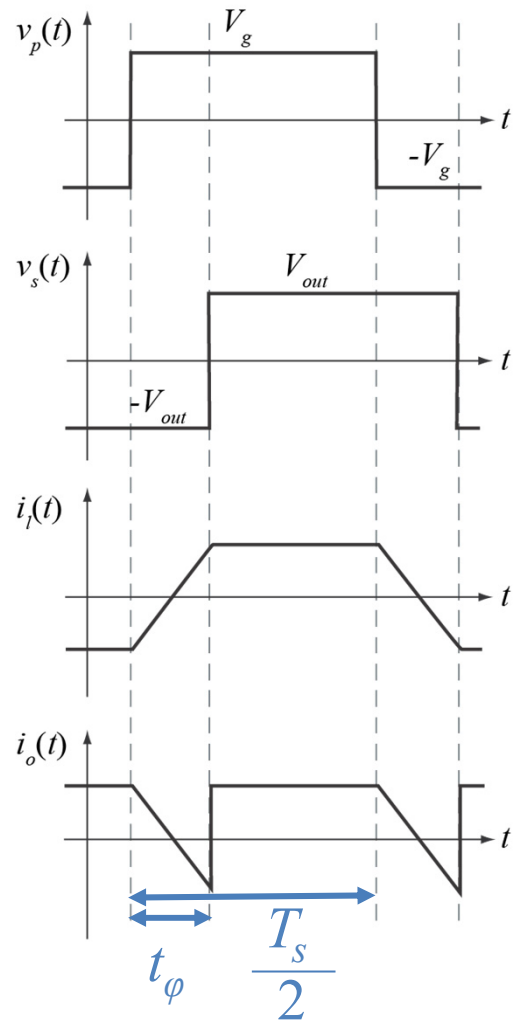

$$\langle i_o \rangle |_{T_s} = \frac{V_g / n_t L_l T_s}{T_s t_\phi - 2t_\phi^2}$$

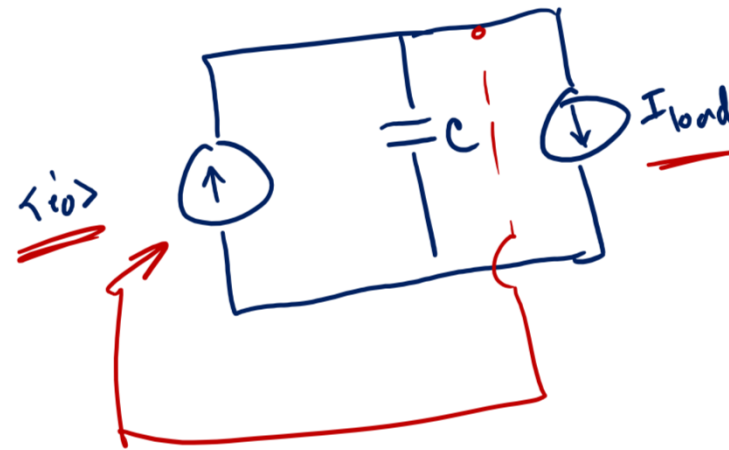

Average Model Transfer Functions

$$\langle i_o \rangle_{T_s} = \frac{V_g}{n_t L_t T_s} (T_s t_\phi - 2t_\phi^2)$$

$$\langle i_o \rangle_{T_s} - I_{load} = C \frac{dV}{dt}$$

$$I_o(s) - I_{load}(s) = sC V(s)$$


$$V(s) = \frac{1}{sC} \left[K_1 I_{load}(s) + k_2 T_\phi(s) + k_3 V_g(s) \right]$$

$$G_{Vg}(s) = \frac{\hat{v}}{\hat{v}_g} = \frac{1}{sC} \frac{\partial i_o}{\partial v_g} \Big|_{DC} = \frac{1}{sC} \left(\frac{1}{n_t L_t T_s} (T_s t_\phi - 2t_\phi^2) \right) \Big|_{DC}$$

$$G_{V\phi}(s) = \frac{\hat{v}}{\hat{t}_\phi} = \frac{1}{sC} \frac{\partial i_o}{\partial t_\phi} = \frac{1}{sC} \left[\frac{V_g}{n_t L_t T_s} (t_s - 4t_\phi) \right] \Big|_{DC}$$

$$G_{Vi}(s) = \frac{\hat{v}}{\hat{i}_{load}} = -\frac{1}{sC}$$

Converter Block Diagram

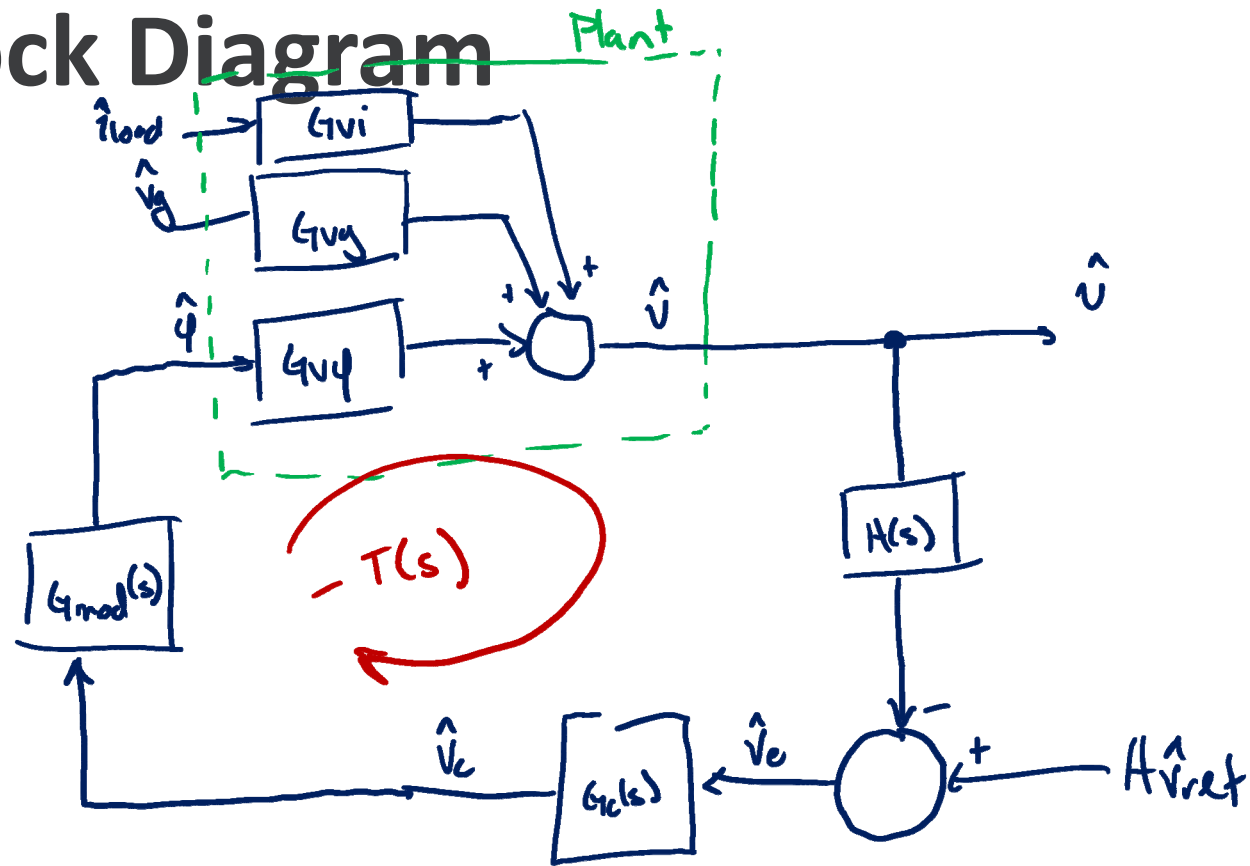


$$\hat{v} = \hat{v}_{ref} \frac{T}{1+T} + \hat{i}_{load} \frac{1}{1+T} + \hat{i}_g \frac{1}{1+T}$$

Compensation Goal : Large $T(s)$ over a wide frequency range
 $f_L \sim f_s/10 \quad \& \quad \phi_m \gg 0^\circ$


Digital Control Block Diagram

MCU/FPGA

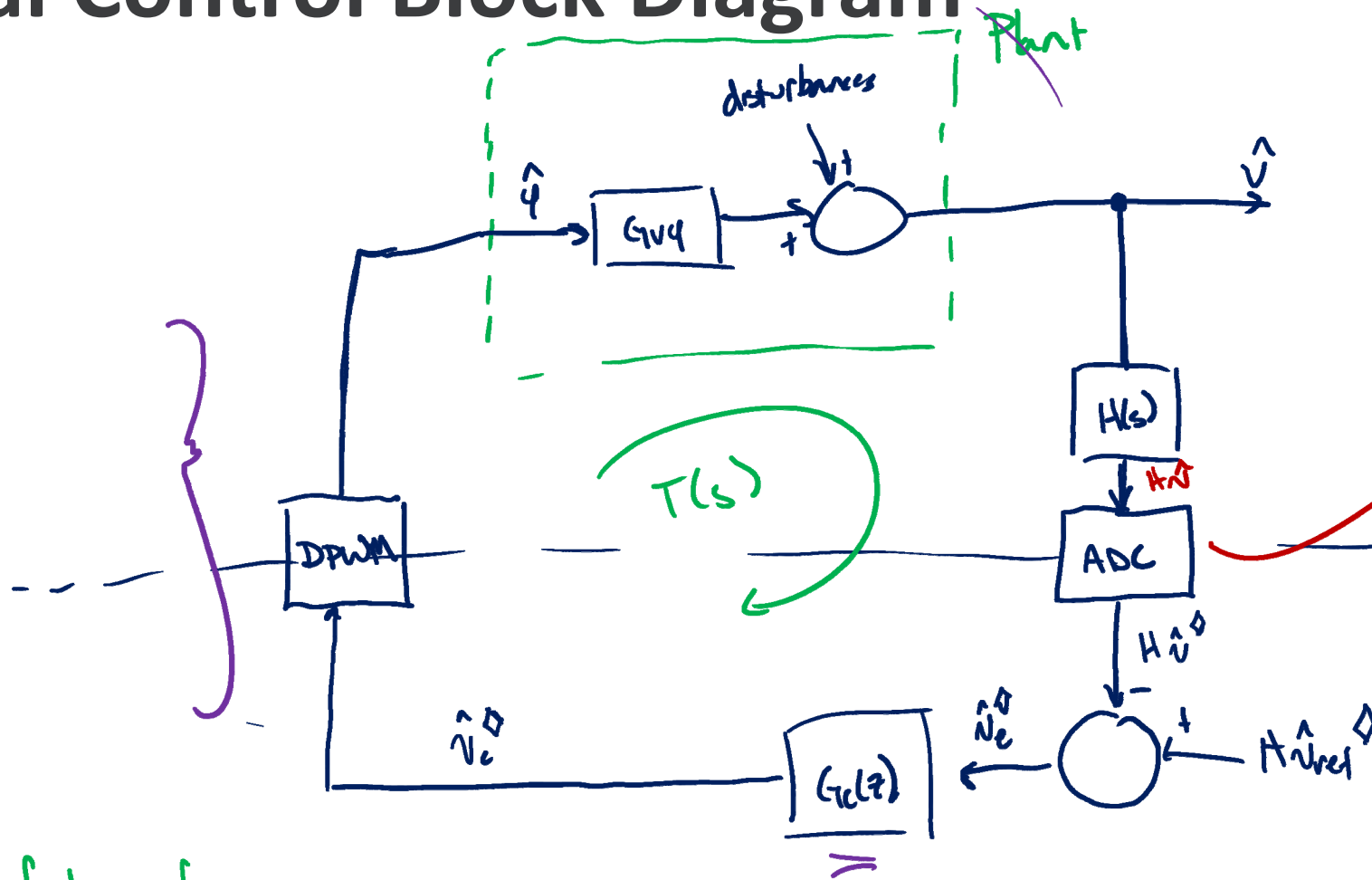

simple model

$$K_{ADC} = \frac{Z^{n_{ADC}}}{V_{PD}}$$

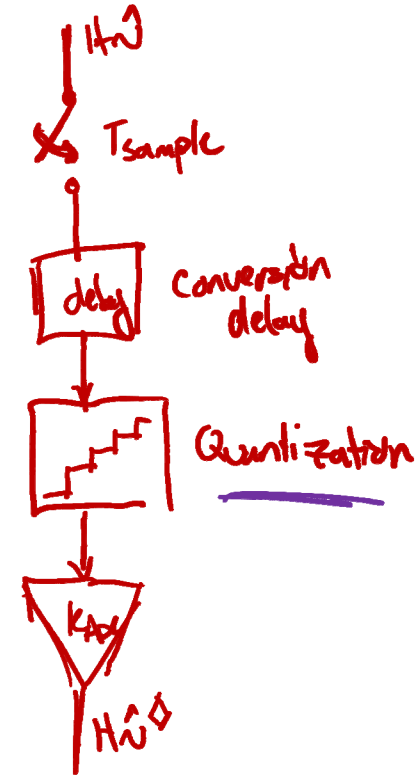


If sampling faster f_c
 If n_{ADC} is sufficiently large (compared to DPWM resolution)
 If all delays are nearly zero relative to T_s
 then digital loop \approx averaged s-domain loop





Model Validation

$$\left\{ \begin{array}{l} R_e = 50\text{m}\Omega \\ C_{os} = 75\text{pF} \end{array} \right.$$

Parameter	Value
V_g	50 V
V_{out}	4 V
I_{load}	3.5 A
C_{out}	20 μF
L_l	9.5 μH
n_t	25:2
f_s	1 MHz
η_{pk}	97%

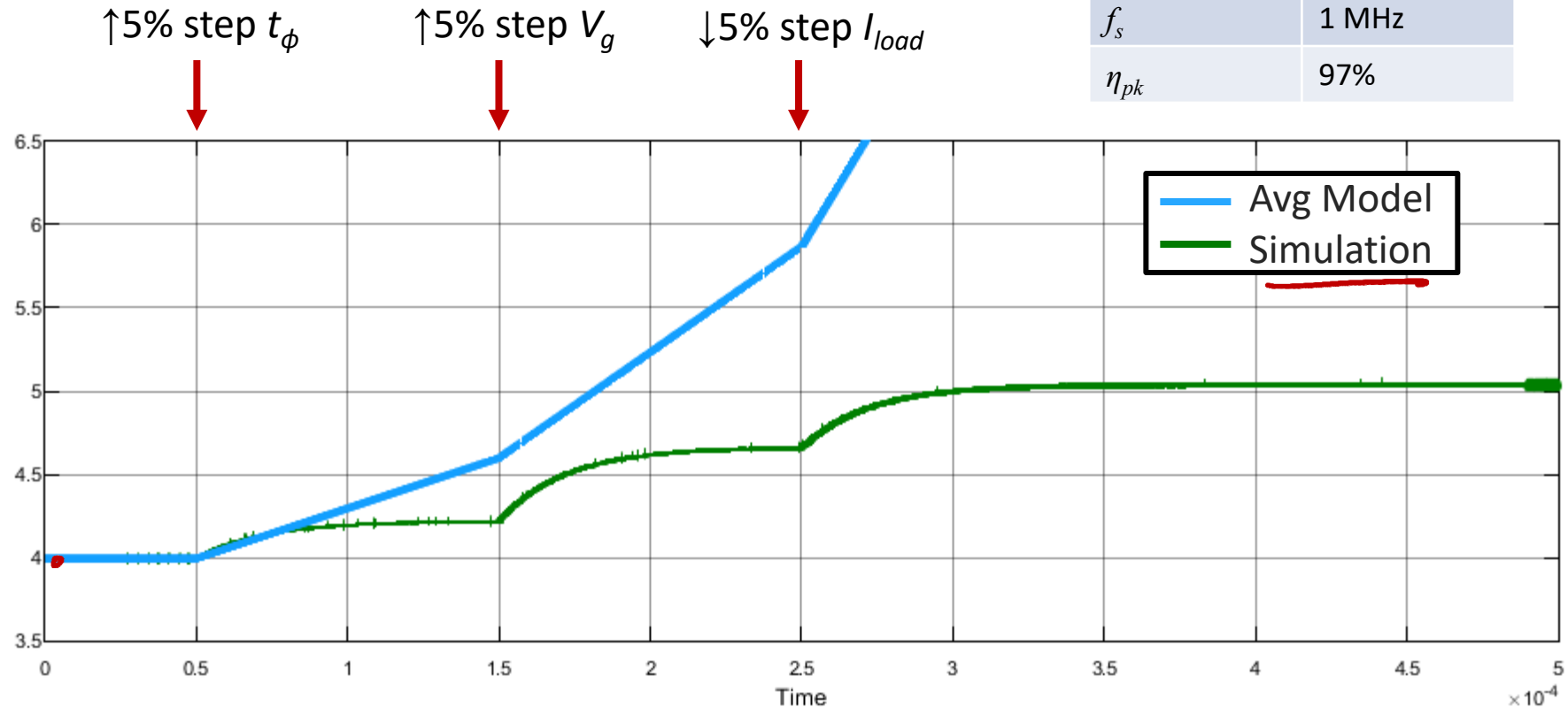

Control Design

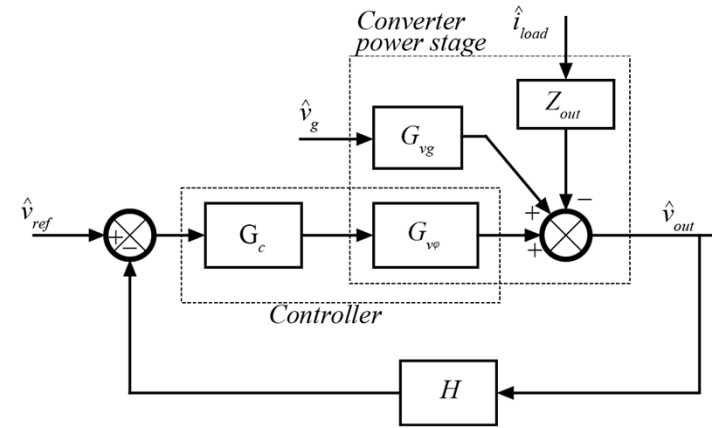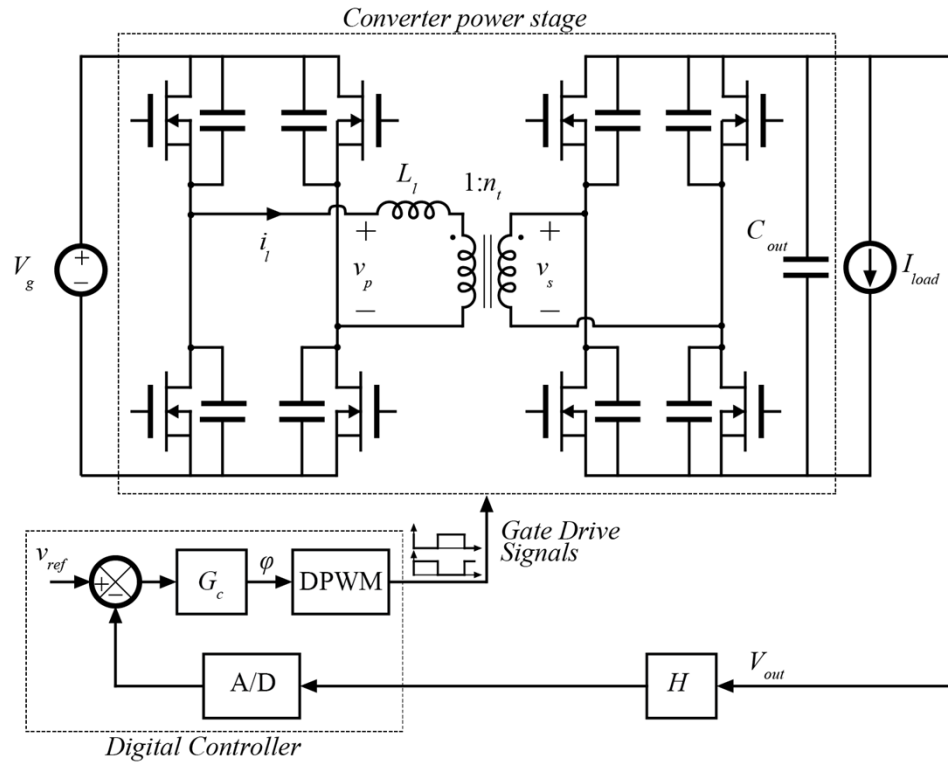

$$G_{vp}(s) = k \frac{1}{s}$$


can be stabilized w/ $G_c(s) = k_p$

$$k_p = 5 \times 10^{-17}$$


$$f_c = 200 \text{ kHz}$$

$$\phi_m = 90^\circ$$


Averaged Model Comparison

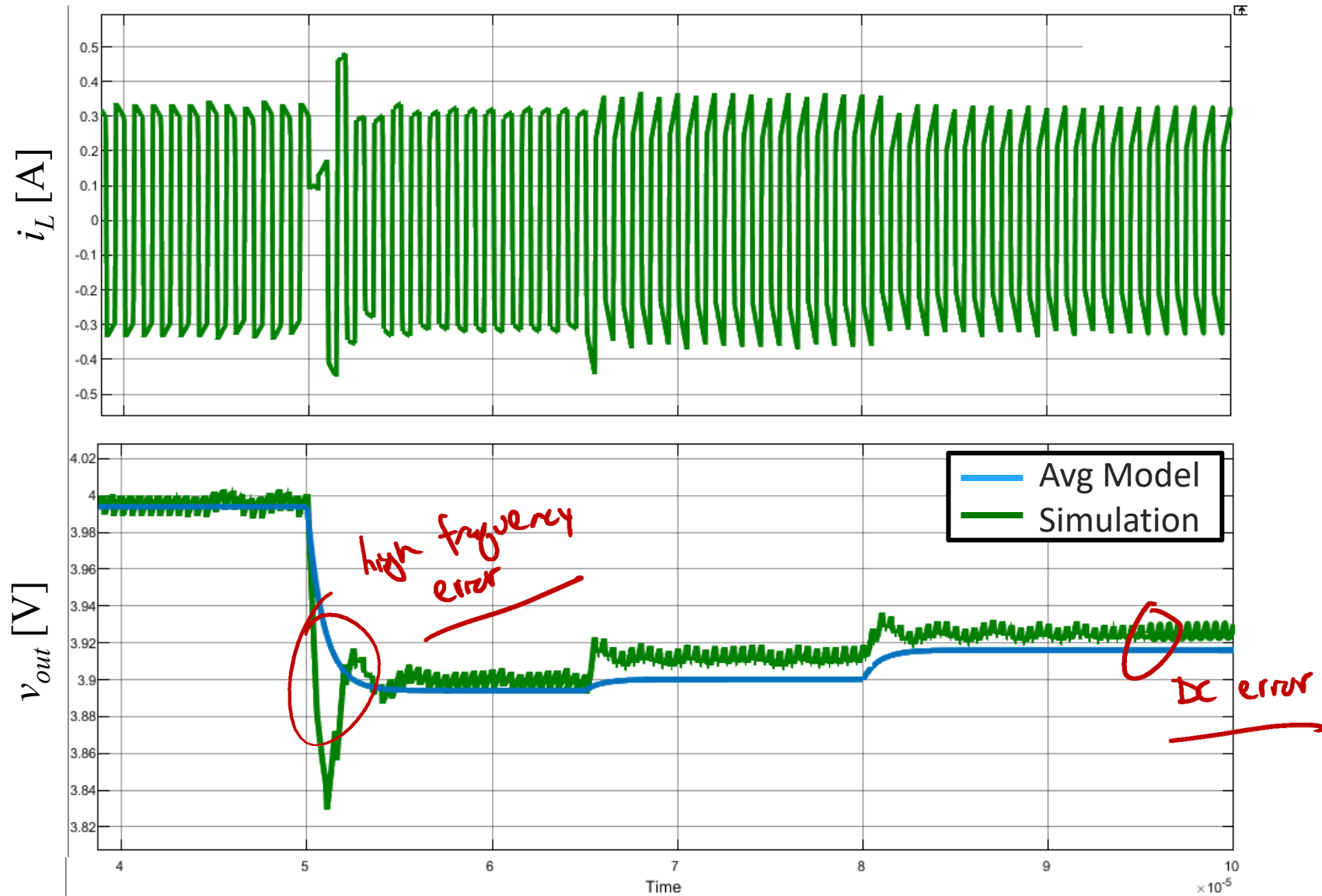

Discrete Time Model Comparison

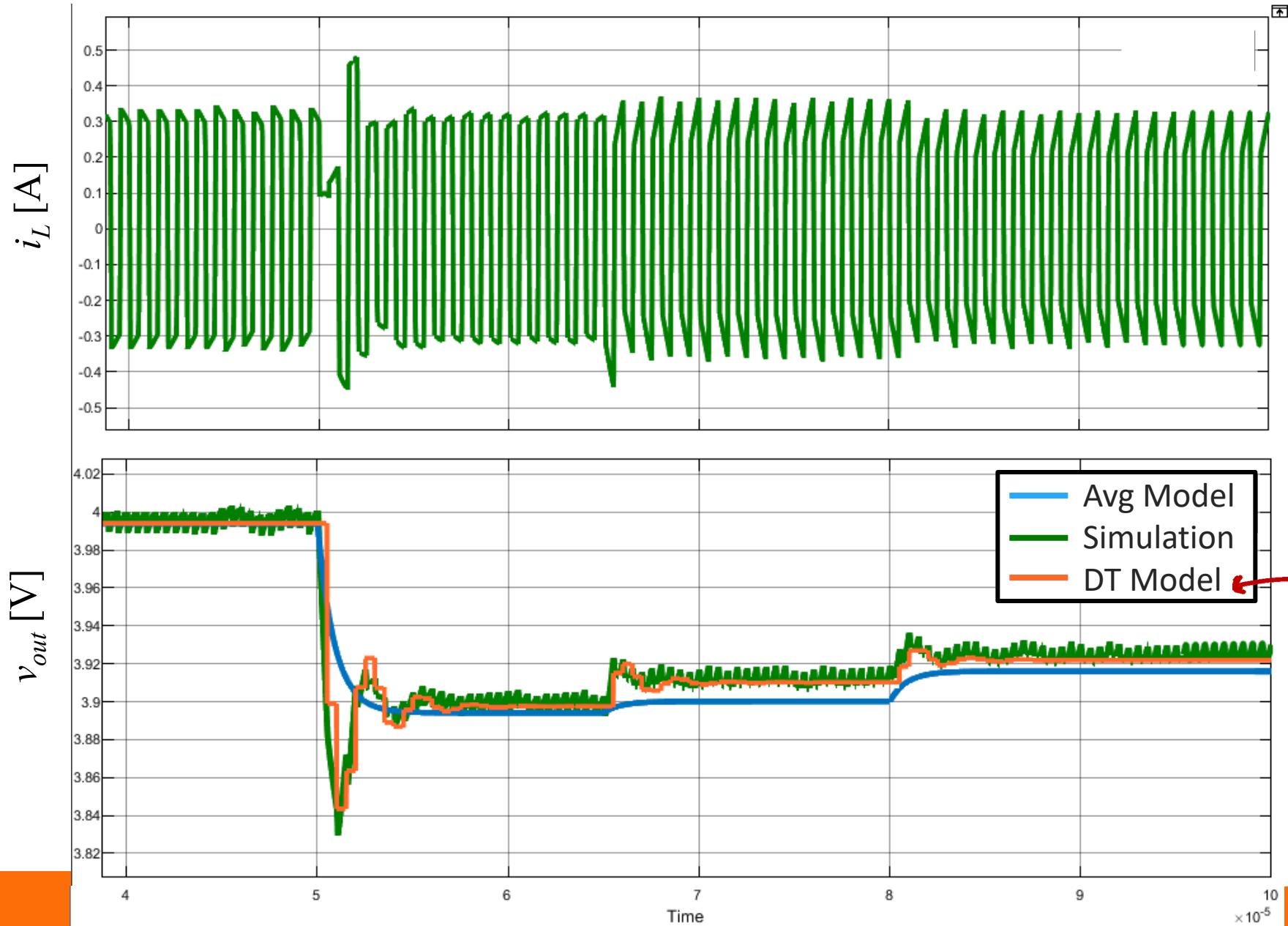



Transfer Function Comparison

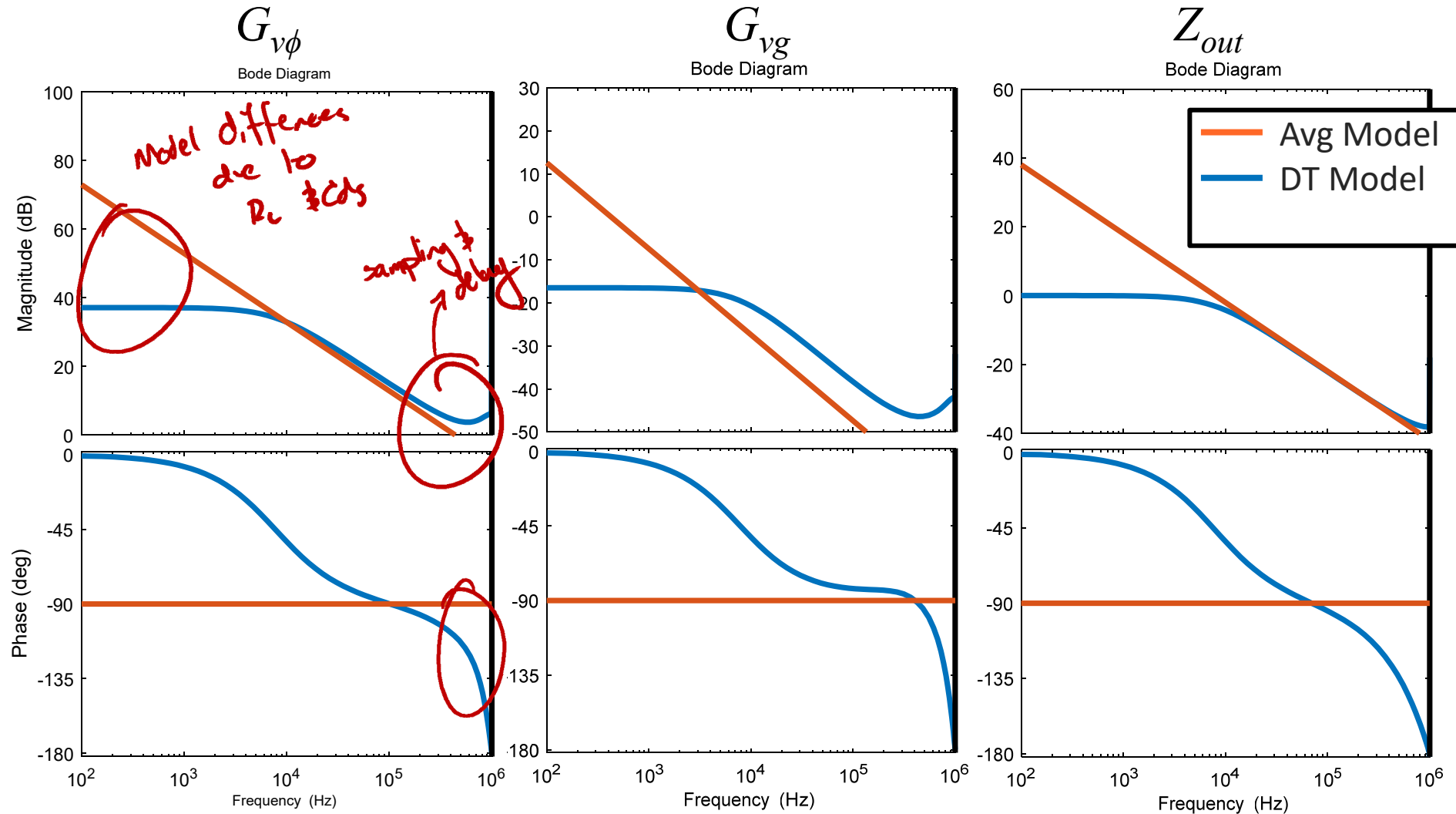



Experimental Measurement of Z_{out}

- Prototype DAB constructed


Parameter	Value
V_g	50 V
V_{out}	4 V
I_{load}	2.5-3.5 A
C_{out}	20 μ F
L_l	9.5 μ H
n_t	25:2
η_{pk}	97%

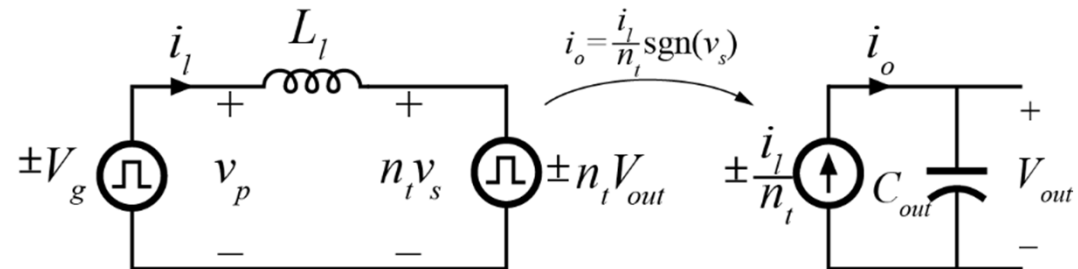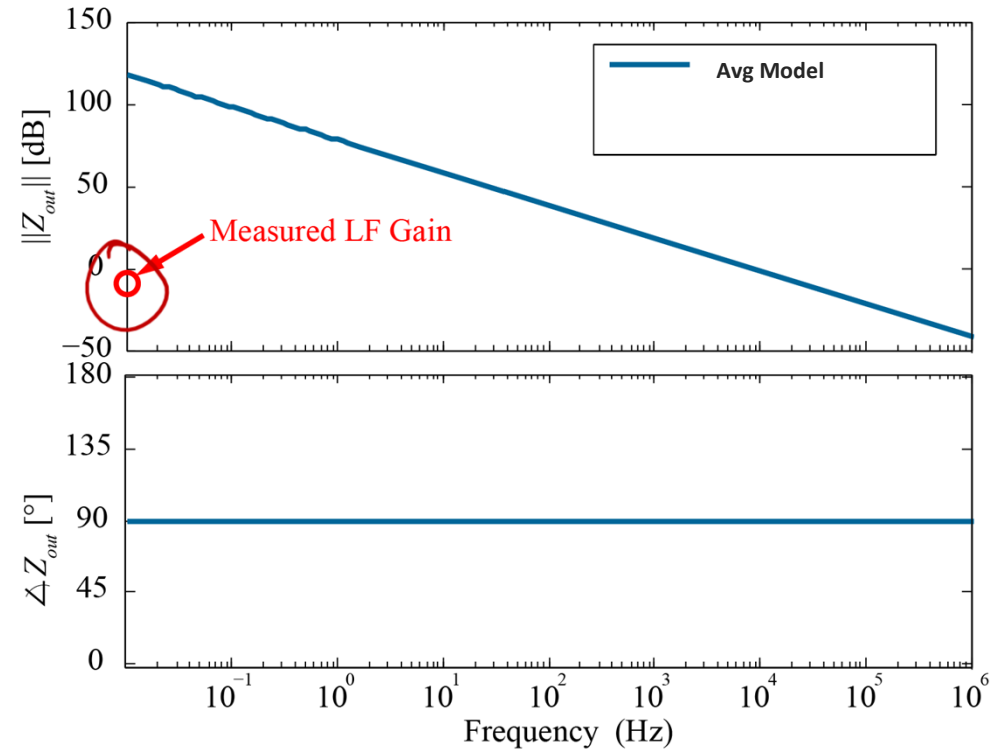


Including Conduction Losses

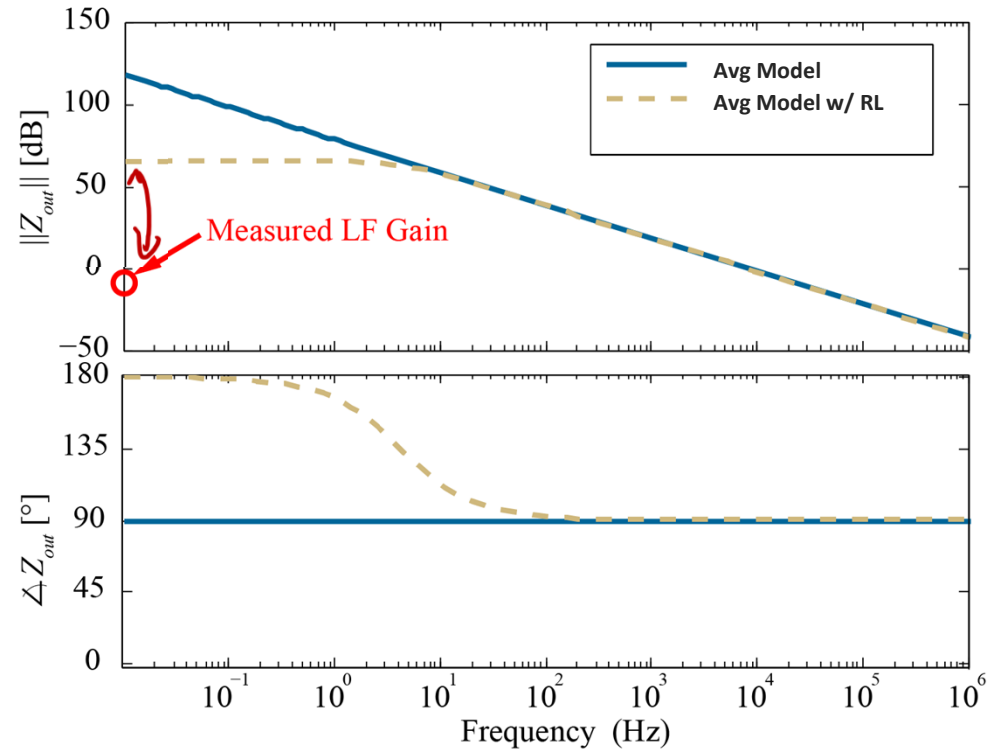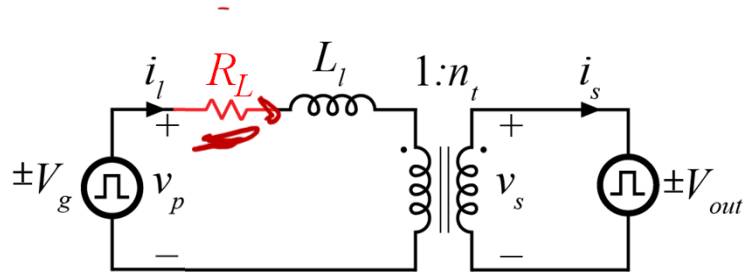



Discrete Time Model: Results

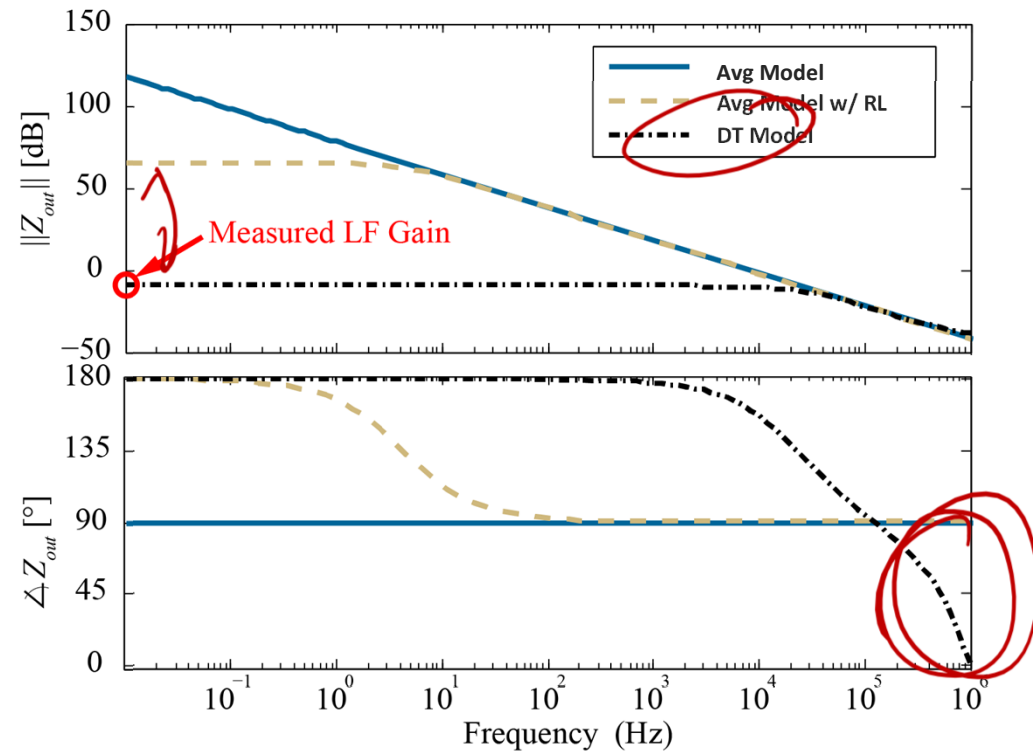

Control-to-Output Transfer Function

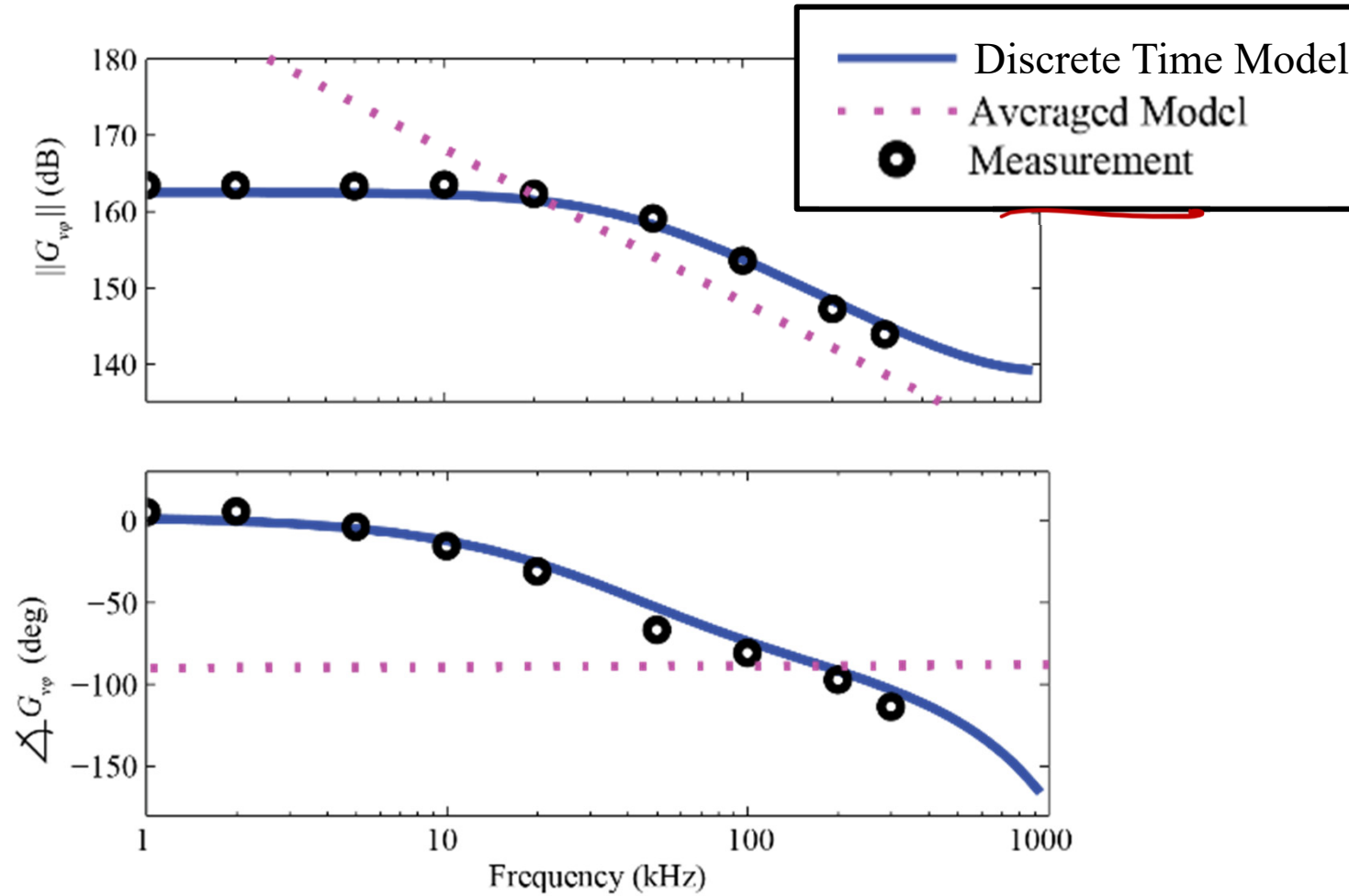

Transient Comparison

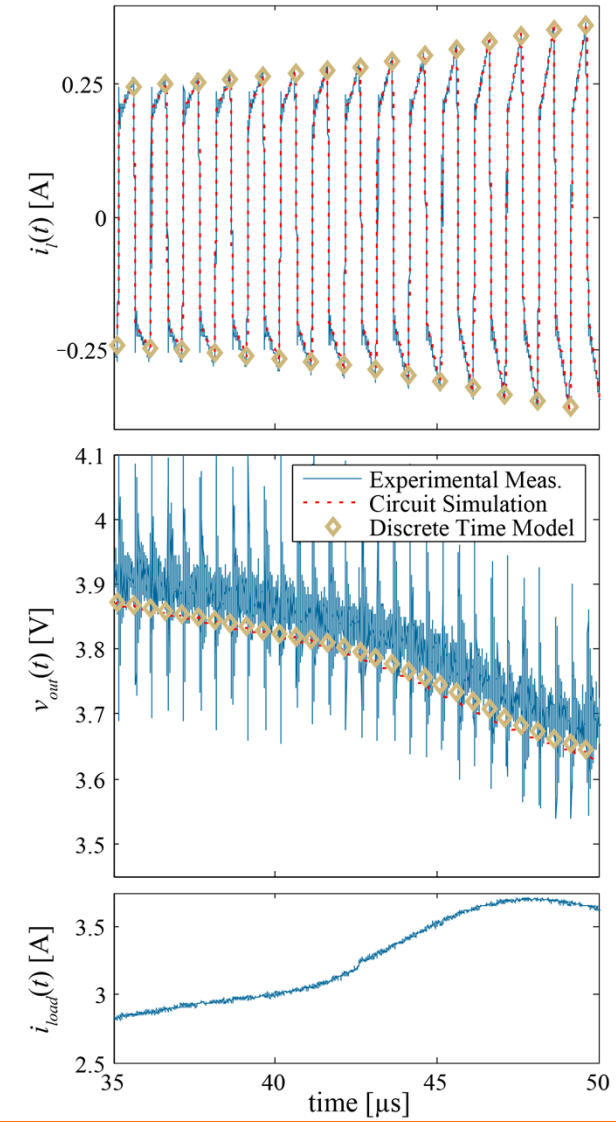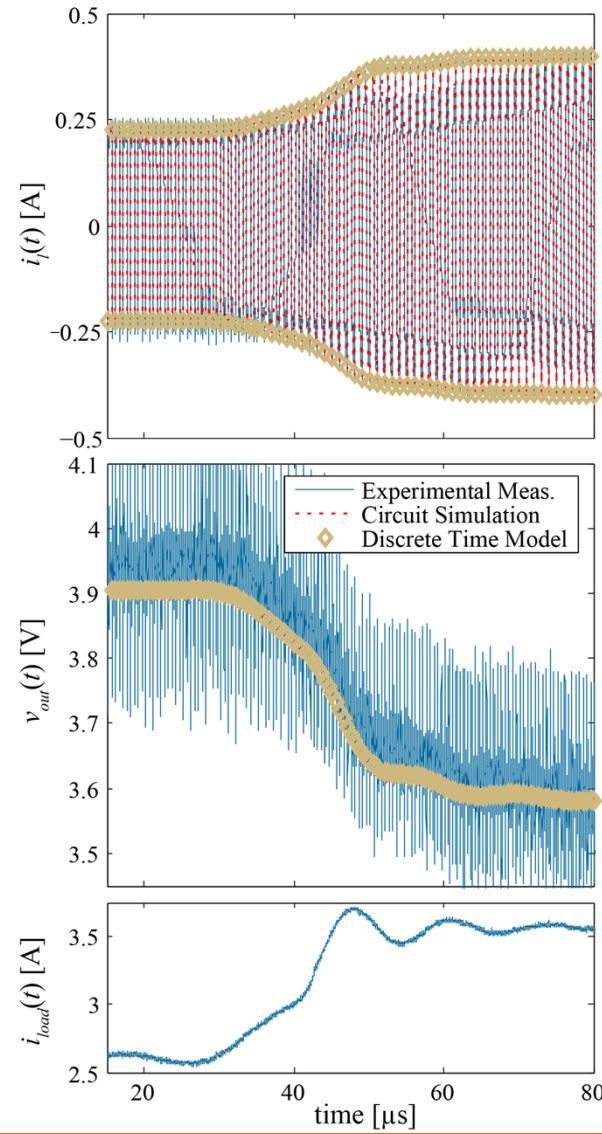

Topics Covered

- Steady-state modeling of switched systems
 - State space representation ✓
 - Discrete time model
 - Steady-state solution
 - Averaging and singularities
- Dynamic models of switched systems
 - Small-signal discrete time modeling
 - Model reduction
 - DPWM and ADC
 - Delays and Quantization
- Digital Control
 - Hardware implementation
 - Compensator Design
 - Advanced techniques
- Additional Topics in design and control of power electronics