

# State Space Representation

For any linear, Time-invariant system, the behaviors are fully characterized by

$$\dot{\underline{x}}(t) = \underline{A} \underline{x}(t) + \underline{B} u(t)$$

notation  $\underline{X} \rightarrow$  matrix  
 $\underline{x} \rightarrow$  vector

$\underline{A}$  &  $\underline{B}$  are matrices which define system (circuit topology)

$\underline{u}(t) \rightarrow$  ( $\underline{v}(t)$  in textbook)  $\rightarrow$  vector of independent inputs


$\underline{x}(t) \rightarrow$  vector of states of the system

$\dot{\underline{x}}(t) \rightarrow$   $\frac{d}{dt}$  of  $\underline{x}(t)$

states: A complete set of information @  $t_0$  that, with  $u(t \geq t_0)$ , fully characterize the system for  $t > t_0$

informally: commonly most or all of the cap voltages & inductor currents

states of a system are not unique

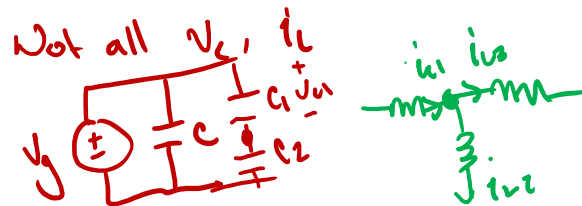

$$\underline{y}(t) = \underline{C}\underline{x}(t) + \underline{D}u(t)$$

$\underline{y}(t)$  → vector of outputs that we select  
 $\underline{C}$  &  $\underline{D}$  associated matrices to find our selected outputs

For a system w/  $n_s$  states,  $m_o$  outputs, &  $p_i$  inputs

$$\underline{A} \in \mathbb{R}^{n_s \times n_s}$$

$$\underline{B} \in \mathbb{R}^{n_s \times p_i}$$

$$\underline{x} \text{ or } \dot{\underline{x}} \in \mathbb{R}^{n_s \times 1}$$



$$\underline{C} \in \mathbb{R}^{m_o \times n_s}$$

$$\underline{D} \in \mathbb{R}^{m_o \times p_i}$$

$$\underline{u} \in \mathbb{R}^{p_i \times 1}$$

$$\underline{y} \in \mathbb{R}^{m_o \times 1}$$

# State Space Formulation Example

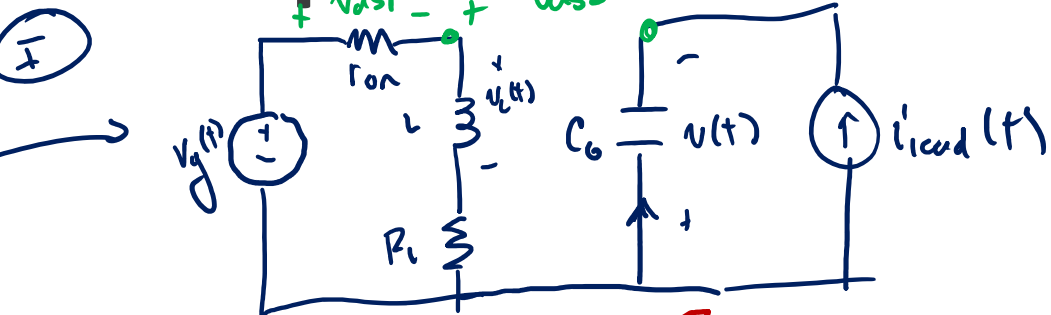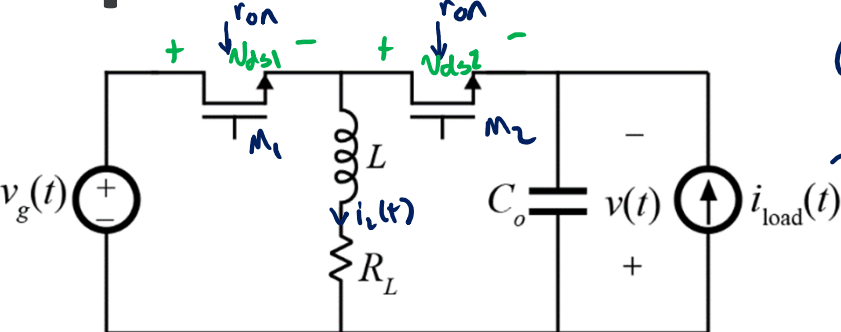

$$\begin{cases} L \frac{di_L(t)}{dt} = v_g(t) - i_L(t)(r_{on} + R_L) \\ C_o \frac{dv_o(t)}{dt} = -i_{load}(t) \end{cases}$$

select  $\underline{x}(t) = \begin{bmatrix} i_L(t) \\ v_o(t) \end{bmatrix}$

$\underline{u}(t) = \begin{bmatrix} v_g(t) \\ i_{load}(t) \end{bmatrix}$

$$\dot{\underline{x}}(t) = \frac{d}{dt} \begin{bmatrix} i_L(t) \\ v_o(t) \end{bmatrix} = \begin{bmatrix} \frac{-r_{on}R_L}{L} & \emptyset \\ \emptyset & \emptyset \end{bmatrix} \begin{bmatrix} i_L(t) \\ v_o(t) \end{bmatrix} + \begin{bmatrix} 1/L & \emptyset \\ \emptyset & -1/C_o \end{bmatrix} \begin{bmatrix} v_g(t) \\ i_{load}(t) \end{bmatrix}$$

$\underline{A}$      $\underline{B}$

$$\underline{K} \underline{\dot{x}}(t) = \underline{A}^* \underline{x}(t) + \underline{B}^* \underline{u}(t)$$

$$\begin{bmatrix} L & 0 \\ 0 & C_o \end{bmatrix} \dot{\underline{x}}(t) = \begin{bmatrix} -(r_{on}+R_L) & \emptyset \\ \emptyset & \emptyset \end{bmatrix} \underline{x}(t) + \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix} \underline{u}(t)$$

$\underline{K}$      $\underline{A}^*$      $\underline{B}^*$

$$\underline{A} = \underline{K}^{-1} \underline{A}^*$$

$$\underline{B} = \underline{K}^{-1} \underline{B}^*$$


let's pick

$$y(t) = \begin{bmatrix} v_{ds1}(t) \\ v_{ds2}(t) \\ v(t) \end{bmatrix}$$

$$\left\{ \begin{array}{l} v_{ds1}(t) = i_L(t) r_{on} \\ v_{ds2}(t) = v_g(t) - i_L(t) r_{on} + v(t) \\ v(t) = v(t) \end{array} \right.$$

$$\begin{bmatrix} v_{ds1}(t) \\ v_{ds2}(t) \\ v(t) \\ \underline{y(t)} \end{bmatrix} = \underbrace{\begin{bmatrix} r_{on} & \phi \\ -r_{on} & \phi \\ \phi & \phi \\ \phi & \phi \end{bmatrix}}_C \begin{bmatrix} i_L(t) \\ v(t) \\ \underline{x(t)} \end{bmatrix} + \underbrace{\begin{bmatrix} \phi & \phi \\ -1 & \phi \\ \phi & \phi \end{bmatrix}}_D \begin{bmatrix} v_g(t) \\ i_{load}(t) \\ \underline{v(t)} \end{bmatrix}$$

# Subinterval II

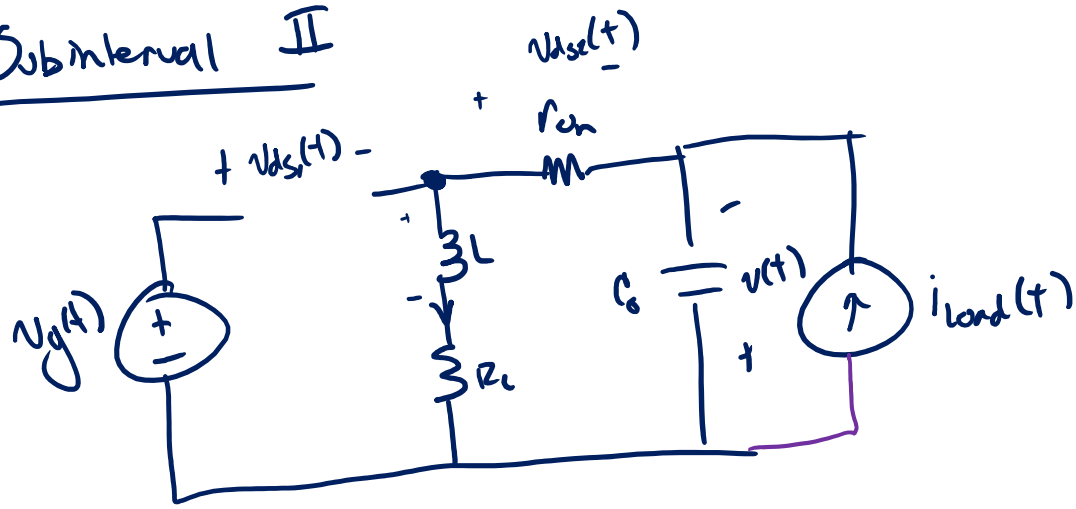

$$\begin{cases} L \frac{di_L(t)}{dt} = -v(t) - i_L(t) (r_{on} + R_L) \\ C \frac{dv(t)}{dt} = i_L(t) - i_{load}(t) \end{cases}$$

$$\begin{cases} v_{ds1}(t) = v_g(t) + v(t) + i_L(t) r_{on} \\ v_{ds2}(t) = -i_L(t) r_{on} \\ v(t) = v(t) \end{cases}$$

$$\dot{\underline{x}}(t) = \begin{bmatrix} -\frac{r_{on} + R_L}{L} & -\frac{1}{L} \\ \frac{1}{C} & \phi \end{bmatrix} \underline{x}(t) + \begin{bmatrix} 0 & 0 \\ \phi & -\frac{1}{C} \end{bmatrix} \underline{u}(t)$$

$$\underline{y}(t) = \begin{bmatrix} r_{on} & -\phi \\ -r_{on} & \phi \\ \phi & 1 \end{bmatrix} \underline{x}(t) + \begin{bmatrix} \phi & \phi \\ \phi & \phi \end{bmatrix} \underline{u}(t)$$


A<sub>2</sub>
B<sub>2</sub>

C<sub>2</sub>
D<sub>2</sub>
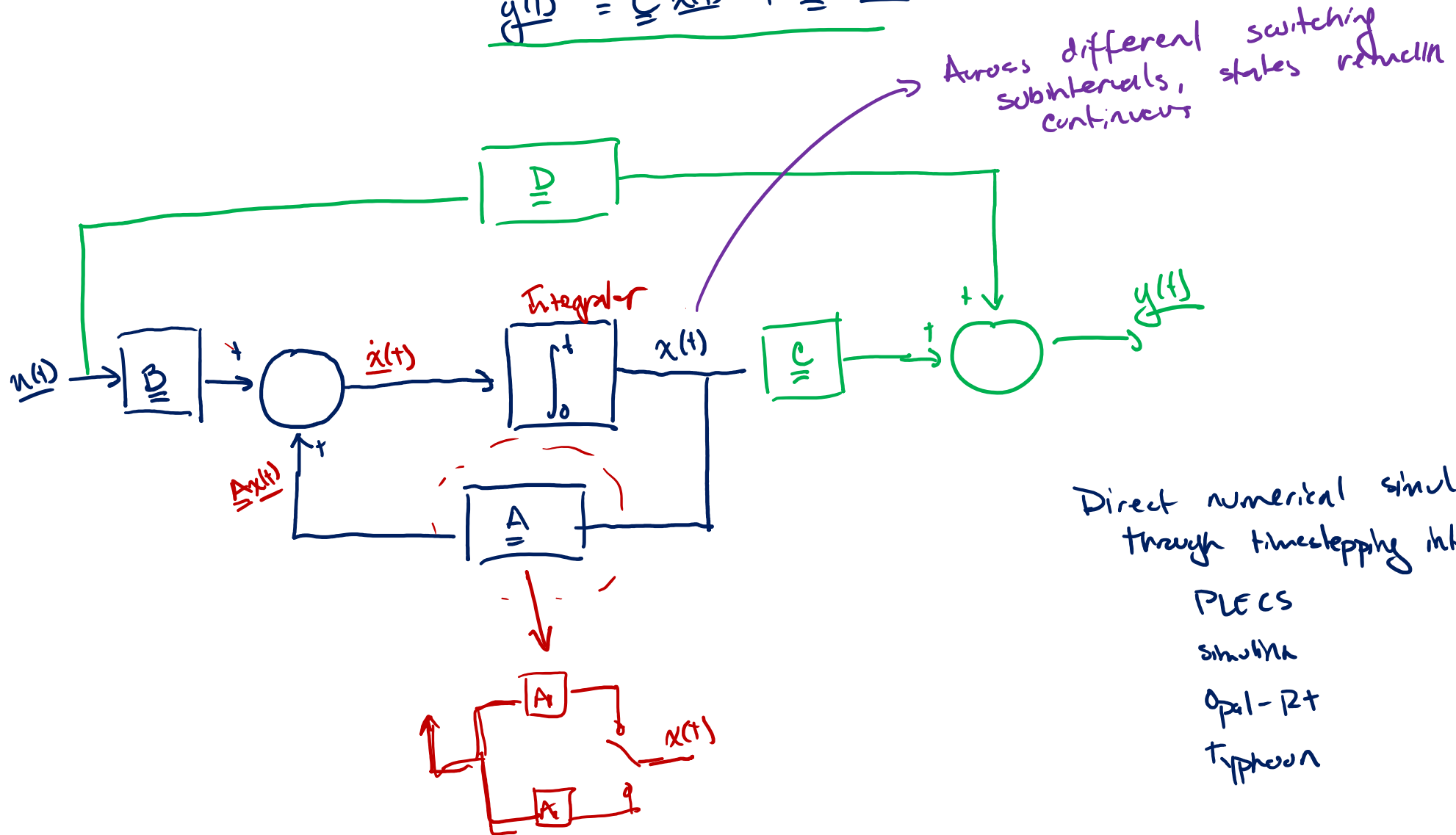
# Block Diagram

$$\dot{x}(t) = \underline{A} x(t) + \underline{B} u(t)$$

$$\underline{y}(t) = \underline{C} x(t) + \underline{D} u(t)$$



Direct numerical simulation  
through time-stepping integration

- PLECS
- simulink
- Opal-RT
- typhoon

# Solution by Laplace Transform

$$\mathcal{L}\{\dot{\underline{x}}(t)\} = \mathcal{L}\{\underline{A}\underline{x}(t) + \underline{B}\underline{u}(t)\}$$

$$s\underline{X}(s) - \underline{x}(0^-) = \underline{A}\underline{X}(s) + \underline{B}\underline{U}(s)$$

$$s\underline{X}(s) - \underline{A}\underline{X}(s) = \underline{x}(0^-) + \underline{B}\underline{U}(s)$$

$$(s\underline{I} - \underline{A})\underline{X}(s) = \underline{x}(0^-) + \underline{B}\underline{U}(s)$$

$$\mathcal{L}^{-1}\{\underline{X}(s)\} = \mathcal{L}^{-1}\left\{ (s\underline{I} - \underline{A})^{-1} \underline{x}(0^-) + (s\underline{I} - \underline{A})^{-1} \underline{B}\underline{U}(s) \right\}$$

$$\underline{x}(t) = \mathcal{L}^{-1}\left\{ (s\underline{I} - \underline{A})^{-1} \right\} \underline{x}(0^-) + \mathcal{L}^{-1}\left\{ (s\underline{I} - \underline{A})^{-1} \underline{B}\underline{U}(s) \right\}$$

$$\underline{x}(t) = \underline{\Phi}(t) \underline{x}(0^-) + \int_0^t \underline{\Phi}(t-\tau) \underline{B} u(\tau) d\tau$$

$$\mathcal{L}^{-1}\{(s\underline{I} - \underline{A})^{-1}\} = \underline{\Phi}(t) \rightarrow \text{resolvent of } \underline{A}$$