

47. For the circuit of Fig. 13.66, $R_1 = 1 \Omega$, $R_2 = 4 \Omega$, and $R_L = 1 \Omega$. Select a and b to achieve a peak voltage of 200 mV magnitude across R_L .


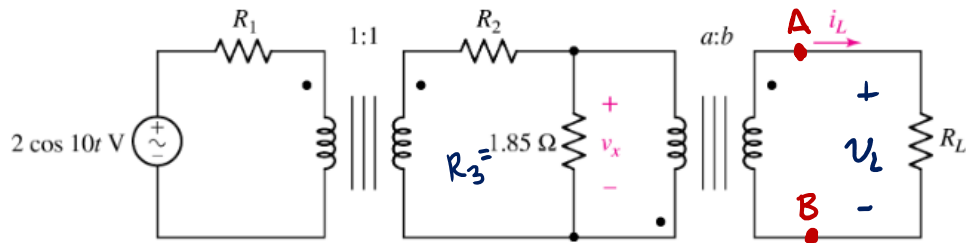


FIGURE 13.66

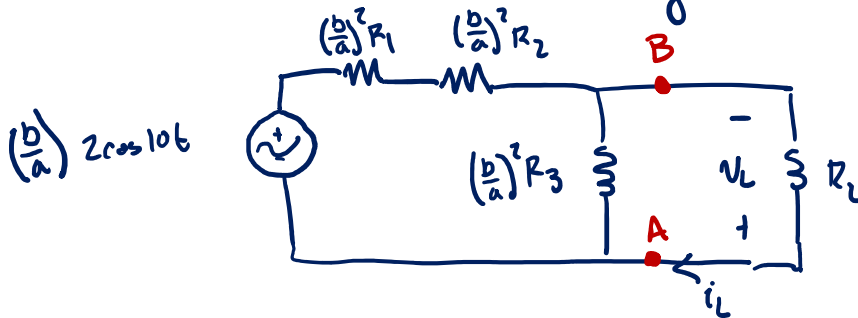First, let's reflect everything to the right. Note that the $a:b$ transformer is inverting



$$V_L = -\left(\frac{b}{a}\right) 2 \cos 10t \frac{R_L \parallel \left(\frac{b}{a}\right)^2 R_3}{R_L \parallel \left(\frac{b}{a}\right)^2 R_3 + \left(\frac{b}{a}\right)^2 R_1 + \left(\frac{b}{a}\right)^2 R_2}$$

by voltage divider with $R_3 \parallel R_L$ in parallel

peak voltage will occur when $\cos 10t = -1$, so we can drop the negative sign & cosine term. Expanding the parallel resistance & dividing through by $\left(\frac{b}{a}\right)^2$:

$$|V_L| = 200 \text{ mV} = \left(\frac{b}{a}\right) 2 \left[\frac{\frac{R_L R_3}{R_L + \left(\frac{b}{a}\right)^2 R_3}}{\frac{R_L R_3}{R_L + \left(\frac{b}{a}\right)^2 R_3} + R_1 + R_2} \right]$$

$$\frac{(R_L + \left(\frac{b}{a}\right)^2 R_3)}{(R_L + \left(\frac{b}{a}\right)^2 R_3)}$$

$$200 \text{ mV} = 2 \frac{b}{a} \frac{R_L R_3}{R_L R_3 + R_L (R_1 + R_2) + \left(\frac{b}{a}\right)^2 R_3 (R_1 + R_2)}$$

collecting terms:

$$0 = (200\text{mV}) (R_1 + R_2) R_3 \left(\frac{b}{a}\right)^2 - 2R_L R_3 \left(\frac{b}{a}\right) + (200\text{mV}) \left[R_L R_3 + (R_1 + R_2) R_L \right]$$

plugging in

$$\phi = 1.85 \left(\frac{b}{a}\right)^2 - 3.7 \left(\frac{b}{a}\right) + 1.37$$

use quadratic formula:

$$\left(\frac{b}{a}\right) = \frac{3.7 \pm \sqrt{3.7^2 - 4(1.85)(1.37)}}{2(1.85)}$$

$$\frac{b}{a} = 0.5 \text{ or } 1.5$$

both are valid solutions. Further, we can choose any combination of b & a that meets this ratio.

MATLAB to find roots:

```
R1 = 1;  
R2 = 4;  
RL = 1;  
R3 = 1.85;
```

```
a = 1/5 * (R1+R2) * R3;  
b = -2 * RL * R3;  
c = 1/5 * (RL * R3) + 1/5 * (R1+R2) * RL;
```


```
roots([a b c])
```

ans =

1.5094

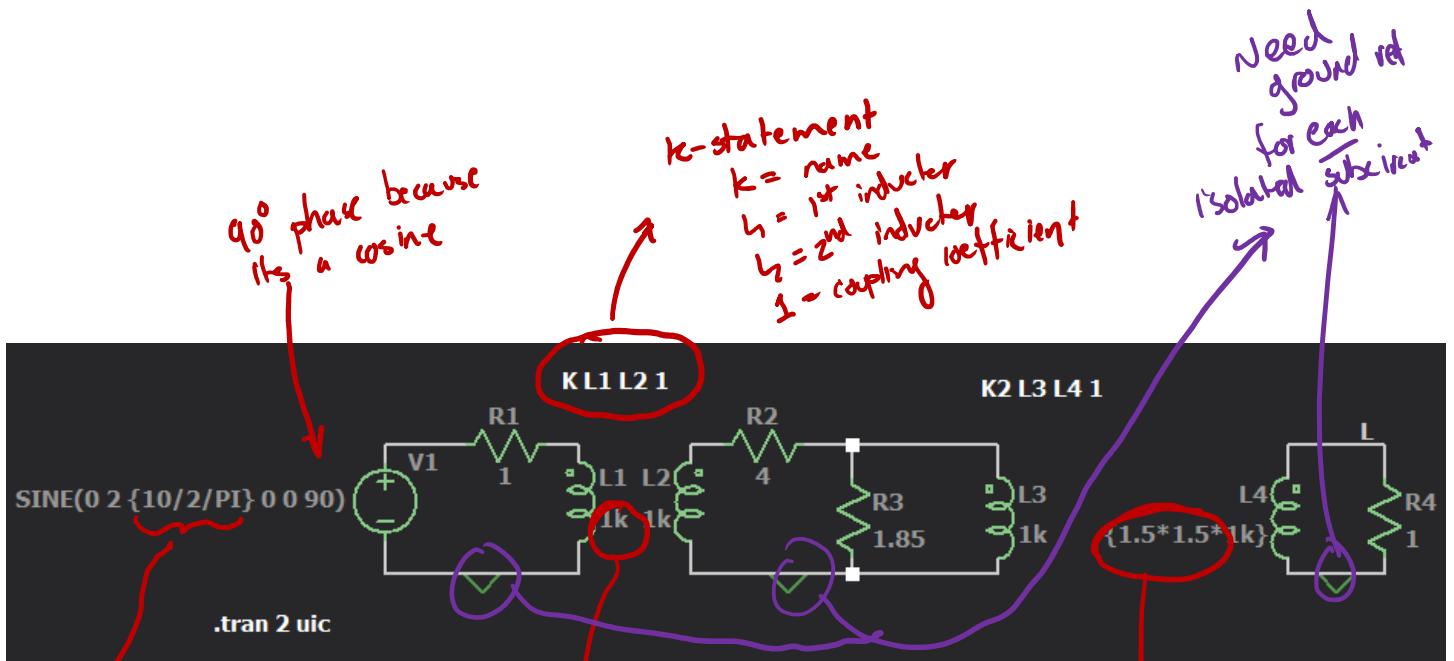0.4906

Though not required, lets check answer using LTspice :



$\omega = 10 \frac{\text{rad}}{\text{sec}}$
 $f = \frac{\omega}{2\pi} \text{ Hz}$

for ideal transformer, inductance should be "large" -> try 1kHenries

Recall from lecture when $k=1$

$$N_1 = N_2 \sqrt{\frac{L_1}{L_2}} = N_2 \sqrt{\frac{N_1^2}{N_2^2}}$$

so

$$\frac{L_1}{L_2} = \frac{N_1^2}{N_2^2} = \left(\frac{b}{a}\right)^2$$

