

54. Determine the input impedance  $Z_{in}(s)$  seen looking into the terminals of the network depicted in Fig. 14.52. Express your answer as a ratio of two s-polynomials.

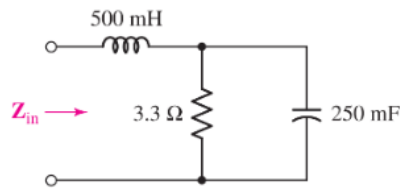


FIGURE 14.52

$$\begin{aligned}
 Z_{in} &= sL + R \parallel \frac{1}{sC} \\
 &= sL + \frac{R}{1 + sRC} \\
 &= \frac{sL + s^2 LCR}{1 + sRC} + \frac{R}{1 + sRC} \\
 &= \frac{s^2 LCR + sL + R}{1 + sRC}
 \end{aligned}$$

Double-check:

at low frequency,  $L \rightarrow$  short,  $C \rightarrow$  open, so  $Z_{in} \rightarrow R$   
as  $s \rightarrow 0$ ,  $\lim_{s \rightarrow 0} \frac{s^2 LCR + sL + R}{1 + sRC} = R \quad \checkmark$

at high frequency,  $C \rightarrow$  short,  $L \rightarrow$  open, so  $Z_{in} \rightarrow sL$   
as  $s \rightarrow \infty$ ,  $\lim_{s \rightarrow \infty} \frac{s^2 LCR + sL + R}{1 + sRC} = \lim_{s \rightarrow \infty} \frac{s^2 LCR}{sRC} = sL \quad \checkmark$

Plugging in

$$Z_{in}(s) = \frac{0.413s^2 + 0.5s + 3.3}{1 + 0.825s}$$