

57. For the circuit given in Fig. 14.55, (a) draw the s-domain equivalent; (b) write the three s-domain mesh equations; (c) determine i_1 , i_2 , and i_3 .


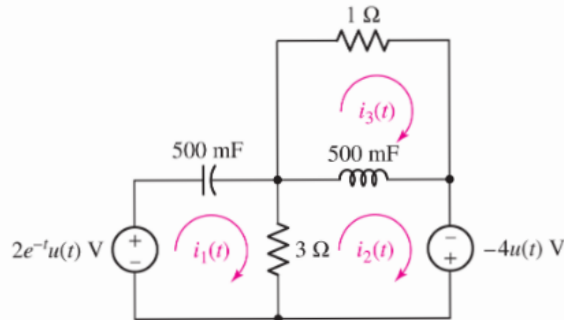


FIGURE 14.55

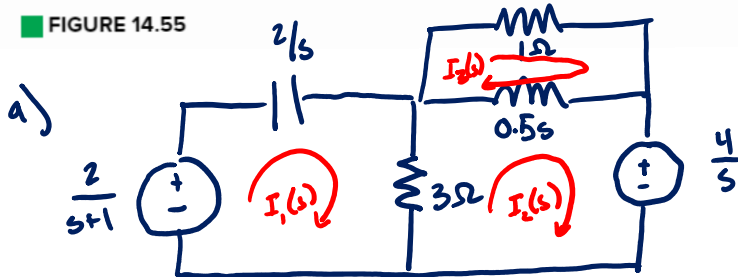

b)

$$\frac{2}{s+1} = I_1 \frac{2}{s} + (I_1 - I_2) 3$$

$$-\frac{4}{s} = (I_2 - I_1) 3 + (I_2 - I_3) 0.5s$$

$$0 = I_3(1) + (I_3 - I_2) 0.5s$$

c)

$$\begin{bmatrix} \frac{2}{s+1} \\ -\frac{4}{s} \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{2}{s} + 3 & -3 & 0 \\ -3 & 3 + 0.5s & -0.5s \\ 0 & -0.5s & 1 + 0.5s \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = \frac{-4s^2 - 24s - 24}{(s+1)(3s^2 + 8s + 12)}$$

$$I_2 = \frac{(s+2)(-6s^2 - 20s - 8)}{s(s+1)(3s^2 + 8s + 12)}$$

$$I_3 = \frac{-6s^2 - 20s - 8}{(s+1)(3s^2 + 8s + 12)}$$

Using residue in Matlab

$$I_1 = \frac{-0.571}{s+1} + \frac{-0.38 + 1.57j}{s + \frac{4}{3} - 1.5j} + \frac{-0.38 - 1.57j}{s + \frac{4}{3} + 1.5j}$$

$$I_2 = \frac{-4/3}{s} + \frac{-0.86}{s+1} + \frac{0.045 + 1.32j}{s + \frac{4}{3} - 1.5j} + \frac{0.045 - 1.32j}{s + \frac{4}{3} + 1.5j}$$

$$I_3 = \frac{0.86}{s+1} + \frac{-1.43 + 0.77j}{s + \frac{4}{3} - 1.5j} + \frac{-1.43 - 0.77j}{s + \frac{4}{3} + 1.5j}$$

so

$$i_1(t) = \left[-0.571e^{-t} + 2(1.62)e^{-\frac{4}{3}t} \cos(1.5t + 103^\circ) \right] u(t)$$

$$i_2(t) = \left[-\frac{4}{3} - 0.86e^{-t} + 2(1.32)e^{-\frac{4}{3}t} \cos(1.5t + 86^\circ) \right] u(t)$$

$$i_3(t) = \left[0.86e^{-t} + 2(1.62)e^{-\frac{4}{3}t} \cos(1.5t + 152^\circ) \right] u(t)$$