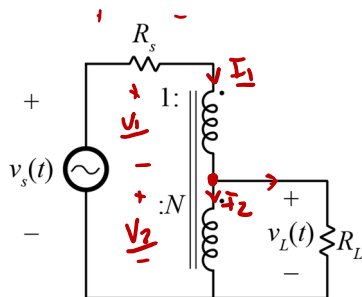


Example Problem

$$\omega = 2\pi 60$$



Find $v_L(t)$ for $v_s(t) = 170\cos(2\pi 60t)$ and for $R_s = 10 \Omega$, $N = 0.1$, and $R_L = 50 \Omega$

$$v_L(t) \rightarrow \underline{V_L} = 170 \angle 0^\circ \quad \text{or} \quad 170 e^{j0} \quad \text{or} \quad 170 + j\phi$$

$$v_s(t) \rightarrow \underline{V_s} = 170 \angle 0^\circ$$

$$R_s \rightarrow R_s \quad R_L \rightarrow R_L$$

$$1 + \frac{1}{N} = \frac{N+1}{N}$$

$$\frac{V_1}{1} = \frac{V_2}{N}, \quad I_1 + N I_2 = 0$$

Loop

$$\underline{V_s} = \underline{V_1} + \underline{V_2} + \underline{I_1} R_s$$

$$\underline{V_s} = \left(\frac{1}{N} + 1\right) \underline{V_L} + \underline{I_1} R_s$$

$$\underline{V_2} = \left(\frac{N+1}{N}\right) \underline{V_L} + \frac{R_s}{R_L} \left(\frac{1}{N+1}\right) \underline{V_L}$$

Node:

$$\underline{I_1} = \underline{I_2} + \frac{\underline{V_L}}{R_L}$$

$$\left(1 + \frac{1}{N}\right) \underline{I_1} = \frac{\underline{V_L}}{R_L}$$

$$\underline{V_L} = \underline{V_s} \frac{1}{\frac{N+1}{N} + \frac{R_s}{R_L} \frac{1}{N+1}}$$

$$= 15.5 \angle 0^\circ$$

compute & inverse transform

$$v_L(t) = 15.5 \cos(2\pi 60t + 0^\circ)$$

Impedance

Phasor equivalent of ohm's law

$$\underline{V} = \underline{I} Z$$

$Z \rightarrow$ "impedance"

$$Z = R + jX$$

"resistance"
 $\text{Re}\{Z\}$

"reactance"
 $\text{Im}\{Z\}$

$$\left\{ \begin{array}{l} Z_R = R \quad \text{for resistor} \\ Z_L = j\omega L \quad \text{for inductor} \\ Z_C = \frac{-j}{\omega C} \quad \text{for capacitor} \end{array} \right.$$

All Z have units of Ohms

$$Y = \text{"Admittance"} = \frac{1}{Z} = G + jB$$

"conductance" \rightarrow G jB \rightarrow "susceptance"


\rightarrow units of siemens (or mhos)

$$\frac{1}{Z} \neq \frac{1}{R} + j \frac{1}{X}$$

$$\frac{1}{Z} = \frac{1}{R + jX} \frac{(R - jX)}{(R - jX)} = \frac{R - jX}{R^2 + X^2} = \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2}$$


Phasor Circuit Analysis

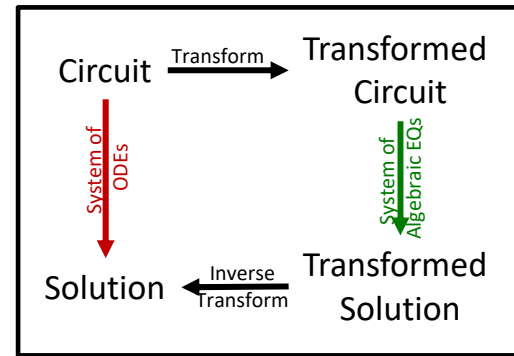Goal: Analyze a LTI circuit to find steady-state solution with only single-frequency sinusoidal source(s)



1. Transform all sources & signals into their phasor equivalents
2. Transform all passives into impedances
3. Solve the circuit
 - Use 201 techniques for DC resistor-only circuits
4. Transform solution back into the time domain

Resonance Example

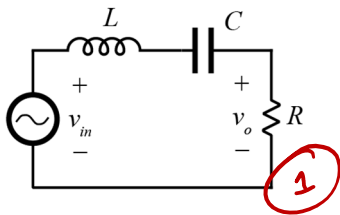


Find $v_o(t)$ for $v_{in}(t) = 10\sin(\omega t)$ and $\omega = 2\pi 100 \text{ kHz}$,
 $R = 10 \Omega$, $L = 10 \mu\text{H}$, and $C = 253 \text{ nF}$

$$10 \cos(\omega t - 90^\circ)$$

$$v_{in}(t) \rightarrow \underline{V_{in}} = 10 \angle -90^\circ = -j10 = 10e^{-j\frac{\pi}{2}}$$

$$v_o(t) \rightarrow \underline{V_o}$$
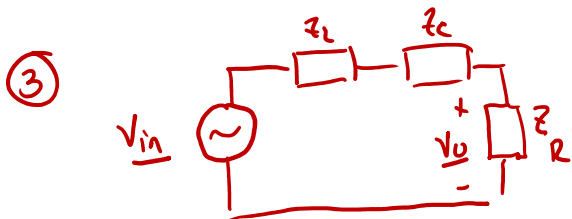
$$\textcircled{2} \quad R \rightarrow z_p = R = 10 \Omega \quad L \rightarrow z_l = j\omega L = j2\pi \quad C \rightarrow z_c = \frac{-j}{\omega C} = -j2\pi$$



$$\underline{V_o} = \underline{V_{in}} \frac{z_R}{z_l + z_c + z_R} = 10 \angle 90^\circ$$

$$\textcircled{4} \quad v_o(t) = |V_o| \cos(\omega t + \angle V_o)$$

$$\underline{V_o(t)} = 10 \cos(\omega t - 90^\circ)$$