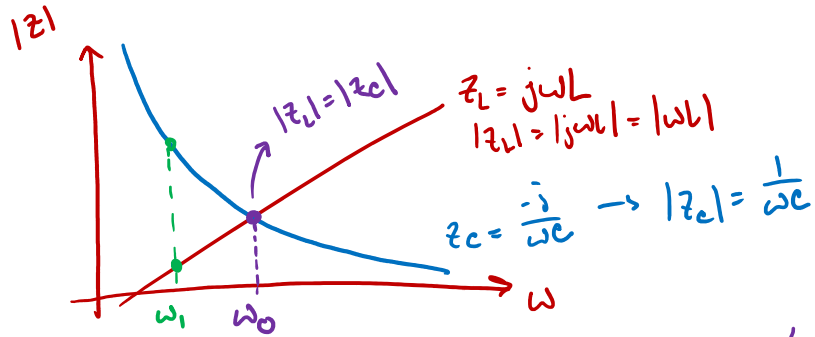



Reactance and Resonance



$\omega = \omega_0 \rightarrow |z_L| = |z_c|$
 $\omega_0 L = \frac{1}{\omega_0 C}$
 $\omega_0 = \frac{1}{\sqrt{LC}}$
 resonant frequency

At low frequency $\omega \rightarrow \phi$

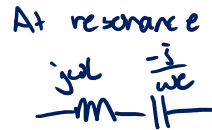
$(\approx DC)$ $z_c \rightarrow \infty$ (open)
 $z_L \rightarrow \phi$ (short)



At resonance \Rightarrow short @ resonance (ω_0)
 $z_{eq} = j\omega L + \frac{-j}{\omega c}$

At high frequency $\omega \rightarrow \infty$

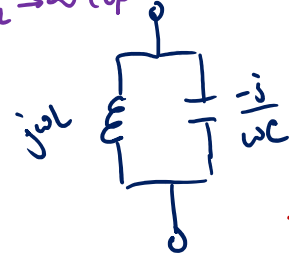$z_c \rightarrow \phi$ (short)
 $z_L \rightarrow \infty$ (open)



\Rightarrow open @ resonance


$z_{eq} = \frac{1}{\frac{1}{j\omega L} + \frac{\omega c}{-j}}$

for only 2 in parallel

$= \frac{j\omega L \cdot (-j/\omega c)}{j\omega L + \frac{-j}{\omega c}}$

Phasor Superposition

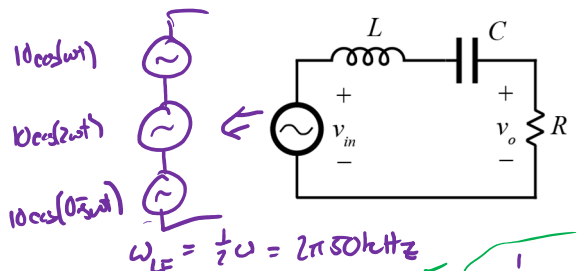3 frequencies \rightarrow apply superposition in time domain



Find $v_o(t)$ for $v_{in}(t) = 10\cos(\omega t) + 10\cos(2\omega t) + 10\cos(0.5\omega t)$
 and $\omega = 2\pi 100 \text{ kHz}$, $R = 10 \Omega$, $L = 10 \mu\text{H}$, and $C = 253 \text{ nF}$


$V_{in} = 10 \angle 0^\circ$
 $Z_L = j\omega_{LF} L = j\pi$
 $Z_C = \frac{-j}{\omega_{LF} C} = -j4\pi$
 $Z_R = R = 10 \Omega$

same

$V_o = V_{in} \frac{Z_R}{Z_L + Z_C + Z_R} = 0.73 \angle 43^\circ$
 $v_{o_{LF}}(t) = 0.73 \cos(0.5\omega t + 43^\circ)$

$\omega = 2\pi 100 \text{ kHz}$

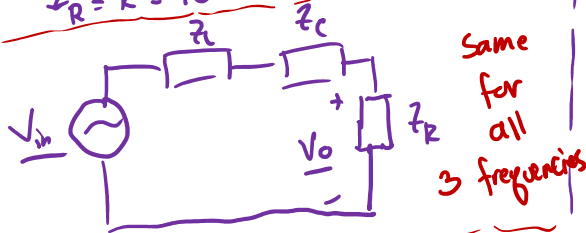$V_{in} = 10 \angle 0^\circ \rightarrow V_o$
 $Z_L = j\omega L = j2\pi$
 $Z_C = \frac{-j}{\omega C} = -j2\pi$
 $Z_R = R = 10$



$V_o = V_{in} \frac{Z_R}{Z_L + Z_C + Z_R} = 10 \angle 0^\circ$
 $v_o(t) = 10 \cos(\omega t)$

$\omega_{HF} = 2\omega = 2\pi 200 \text{ kHz}$

$V_{in} = 10 \angle 0^\circ$
 $Z_L = j\omega_{HF} L = j4\pi$
 $Z_C = \frac{-j}{\omega_{HF} C} = -j\pi$

$V_o = 0.73 \angle -43^\circ$

$v_{o_{HF}}(t) = 0.73 \cos(2\omega t - 43^\circ)$



$v_o(t) = 10 \cos(\omega t) + 0.73 \cos(0.5\omega t + 43^\circ) + 0.73 \cos(2\omega t - 43^\circ)$

Example: WPT Problem


$$v_{tx}(t) = 100 \sin(2\pi \cdot 6.78 \text{ MHz} \cdot t)$$

$$\omega = 2\pi \cdot 6.78 \text{ MHz}$$


$$v_{tx} = 100 \angle -90^\circ$$

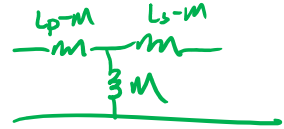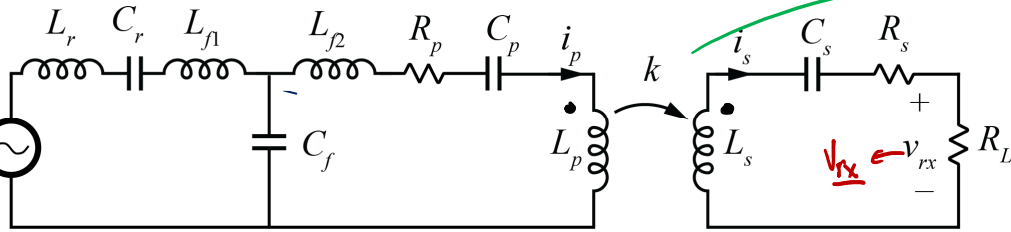


$$m = k \sqrt{L_p L_s}$$

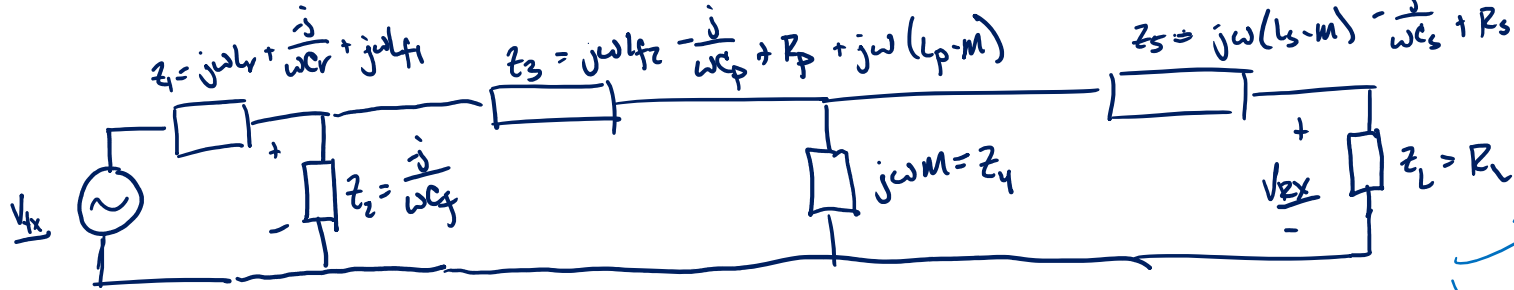

Reminder

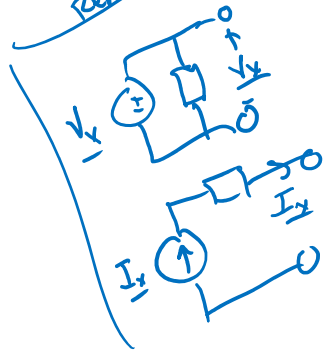

Review

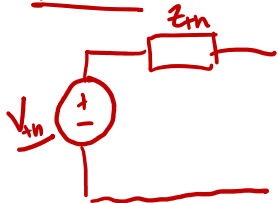


Thevenin equivalent

$$I_N = \frac{v_{th}}{z_{th}}$$



$$z_N = z_{th}$$

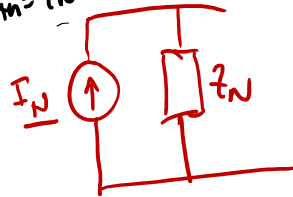

Norton equivalent