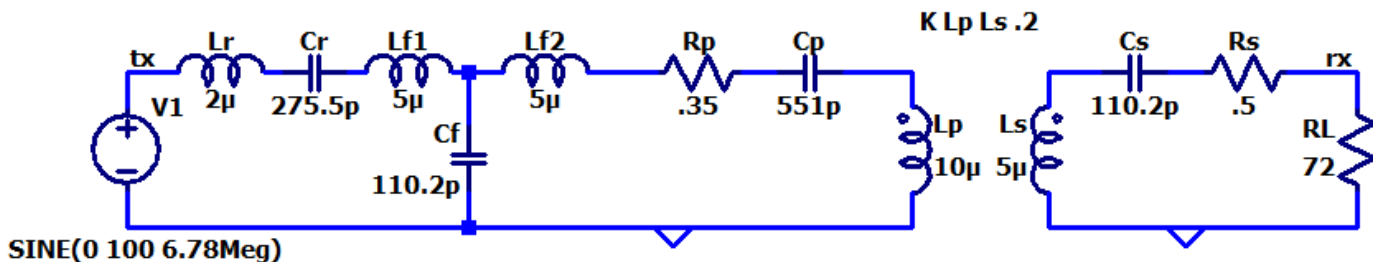


Numerical Example



MATLAB Code:

```
f = 6.78e6;           % Sinusoidal frequency [Hz]
w = 2*pi*f;          % Sinusoidal frequency [rad/sec]
VTX = 100*exp(-1i*pi/2); % Transmitter Voltage Phasor
```

```
Lr = 2e-6;
Cr = 1/w^2/Lr;
```

```
Lf1 = 5e-6;
Lf2 = Lf1;
Cf = 1/w^2/Lf1;
```

```
Rp = .35;
Lp = 10e-6;
Cp = 1/w^2/Lp;
```

```
k = .2;
M = k*sqrt(Lp*Ls);
```

```
Ls = 5e-6;
Cs = 1/w^2/Ls;
Rs = .5;
```

```
RL = 72;
```

```
Z1 = 1j*(w*Lr + w*Lf1 - 1/w/Cr);
Z2 = -1j/w/Cf;
Z3 = Rp + 1j*(w*Lf2 - 1/w/Cp) + 1j*w*(Lp-M);
Z4 = 1j*w*M;
Z5 = Rs + 1j*w*(Ls-M) - 1j/w/Cs;
ZL = RL;
```

```
Za = 1/(1/Z4 + 1/(Z3 + (Z1*Z2/(Z1+Z2))))); % Z4 || (Z3 + Z1||Z2)
Va = VTX/Z1 * (Z1*Z2/(Z1+Z2)) / (Z3 + (Z1*Z2/(Z1+Z2))) * Za;
```




```
VRX = Va*(RL/(RL+Z5+Za))
```

```
mag = abs(VRX)
phase = angle(VRX)/pi*180
```


mag =
28.0892

phase =
-90.0000

Circuit Simulation

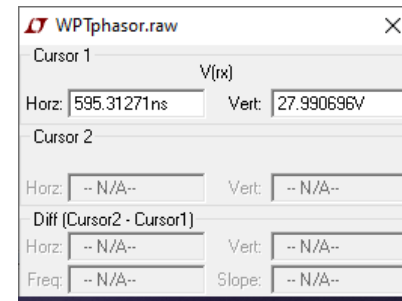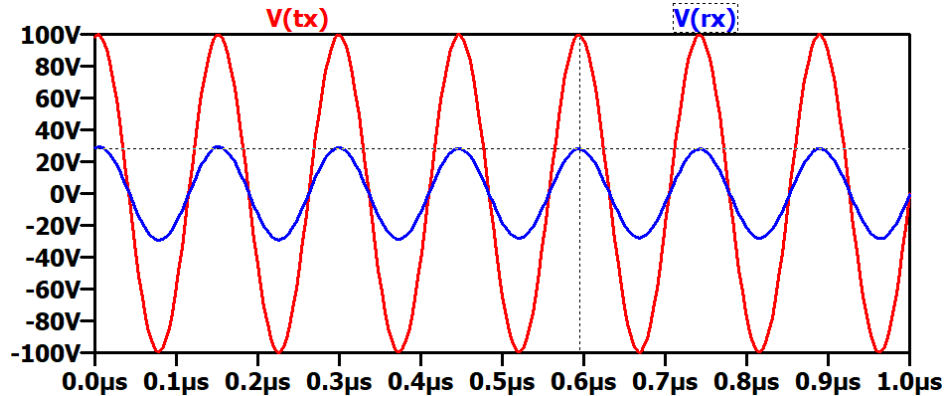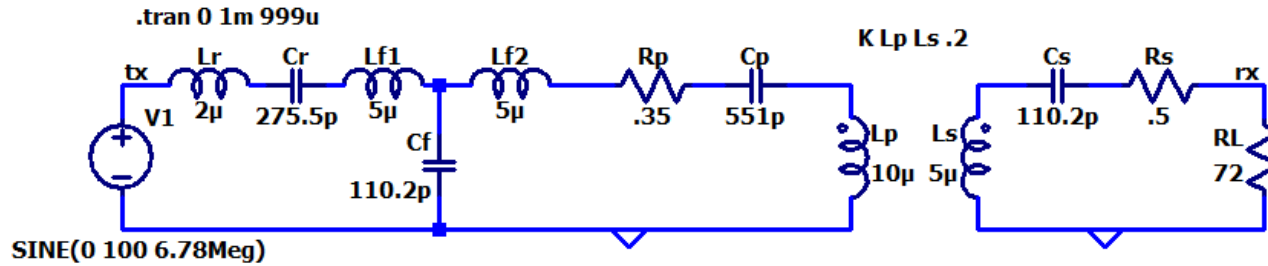

Numerical Example 2


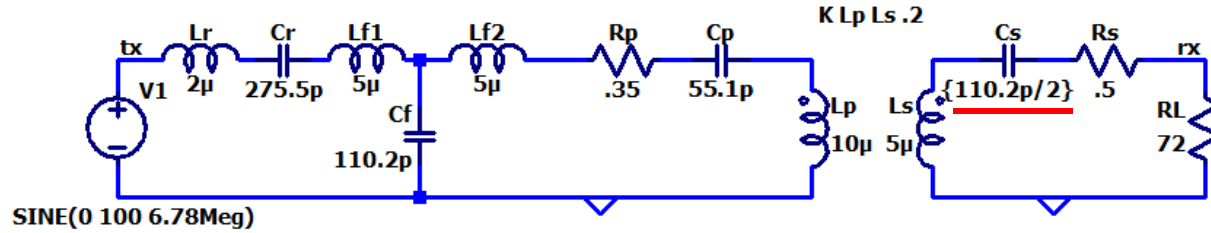


MATLAB Result:

mag =
9.06
phase =
-18.7973




Circuit Simulation 2

.tran 0 1m 999u

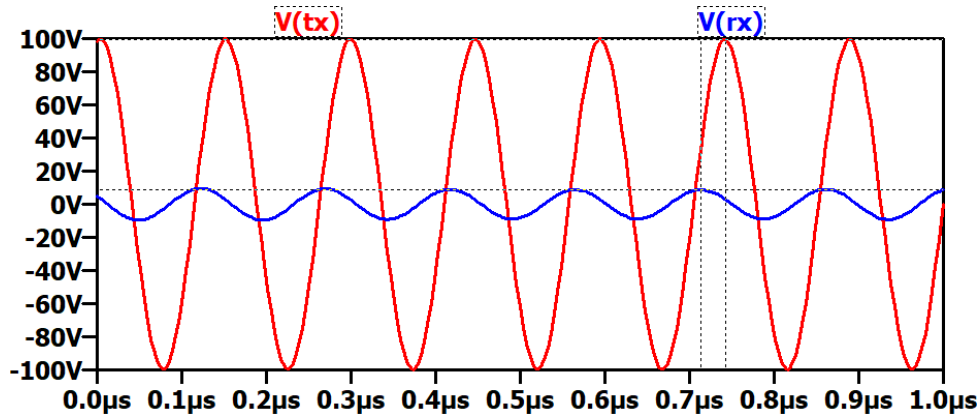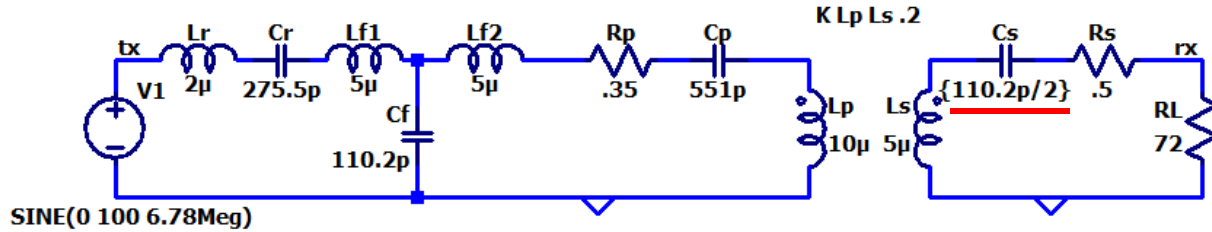

WPTphasor.raw	
Cursor 1	
V(tx)	
Horz: 742.80534ns	Vert: 99.533096V
Cursor 2	
V(rx)	
Horz: 712.84545ns	Vert: 8.8561678V
Diff (Cursor2 - Cursor1)	
Horz: -29.959884ns	Vert: -90.676929V
Freq: 33.377966MHz	Slope: 3.02661e+009

AC Analysis

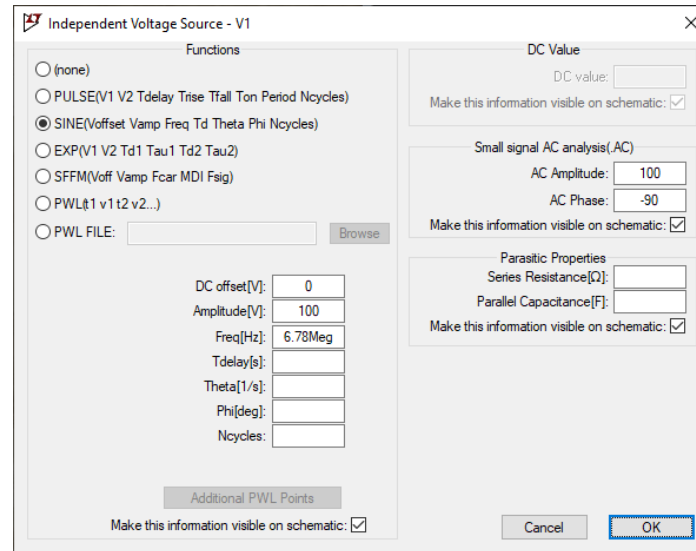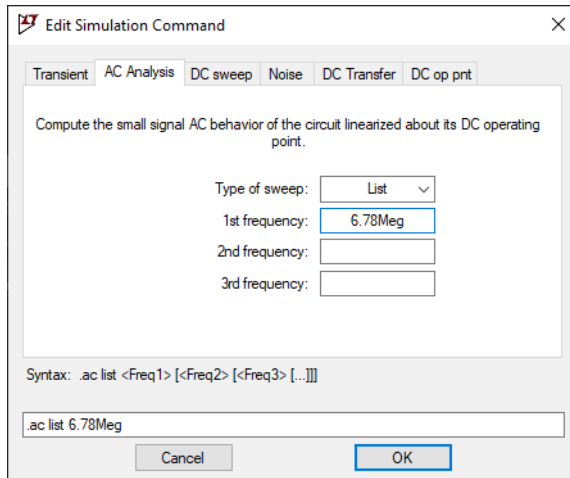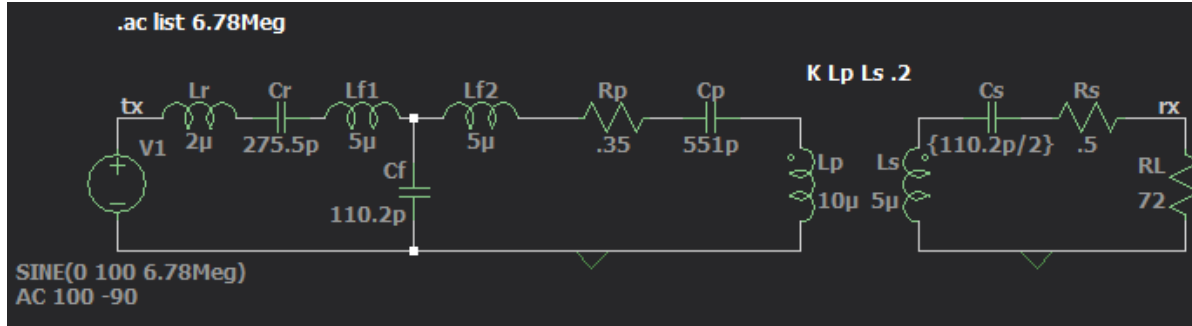




AC Simulation Results (Single Point)

* C:\Users\dcostine\Dropbox\Courses\UTK Courses\ECE 202\In Class Examples\WPTExample-Phasors\WPT... X

--- AC Analysis ---

frequency:	6.78e+006	Hz			
V(tx):	mag:	100	phase:	-90°	voltage
V(n001):	mag:	174.844	phase:	-90.3419°	voltage
V(n002):	mag:	99.9949	phase:	-90.0005°	voltage
V(n003):	mag:	287.109	phase:	-90.5205°	voltage
V(n004):	mag:	187.14	phase:	-90.798°	voltage
V(n006):	mag:	207.132	phase:	-90.6756°	voltage
V(n007):	mag:	54.3051	phase:	-99.138°	voltage
V(n005):	mag:	187.137	phase:	-90.7477°	voltage
V(n008):	mag:	9.11047	phase:	-18.7958°	voltage
V(rx):	mag:	9.04764	phase:	-18.7958°	voltage
I(Cs):	mag:	0.125662	phase:	-18.7958°	device_current
I(Cp):	mag:	0.469369	phase:	179.999°	device_current
I(Cf):	mag:	1.34784	phase:	179.48°	device_current
I(Cr):	mag:	0.878499	phase:	179.202°	device_current
I(Ls):	mag:	0.125662	phase:	-18.7958°	device_current
I(Lp):	mag:	0.469369	phase:	-0.000865793°	device_current
I(LF2):	mag:	0.469369	phase:	179.999°	device_current
I(Lf1):	mag:	0.878499	phase:	-0.798129°	device_current
I(Lr):	mag:	0.878499	phase:	-0.798129°	device_current
I(Rp):	mag:	0.469369	phase:	-0.000865793°	device_current
I(RL):	mag:	0.125662	phase:	161.204°	device_current
I(Rs):	mag:	0.125662	phase:	161.204°	device_current
I(VL):	mag:	0.878499	phase:	179.202°	device_current

Frequency Sweep

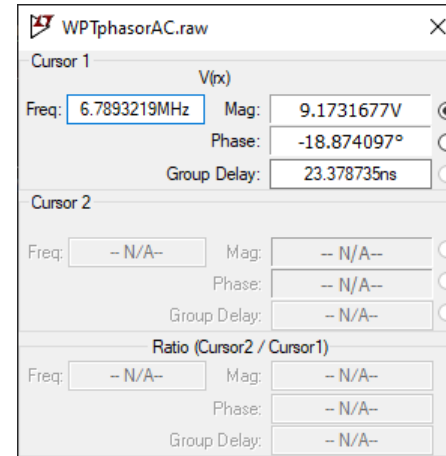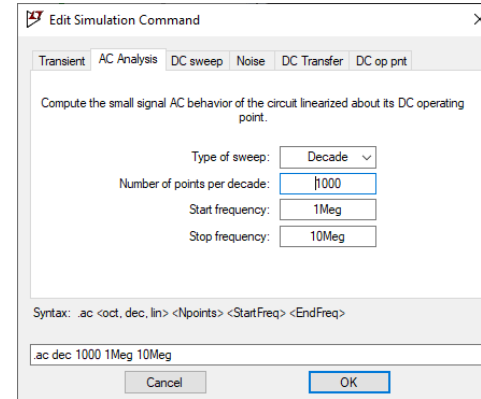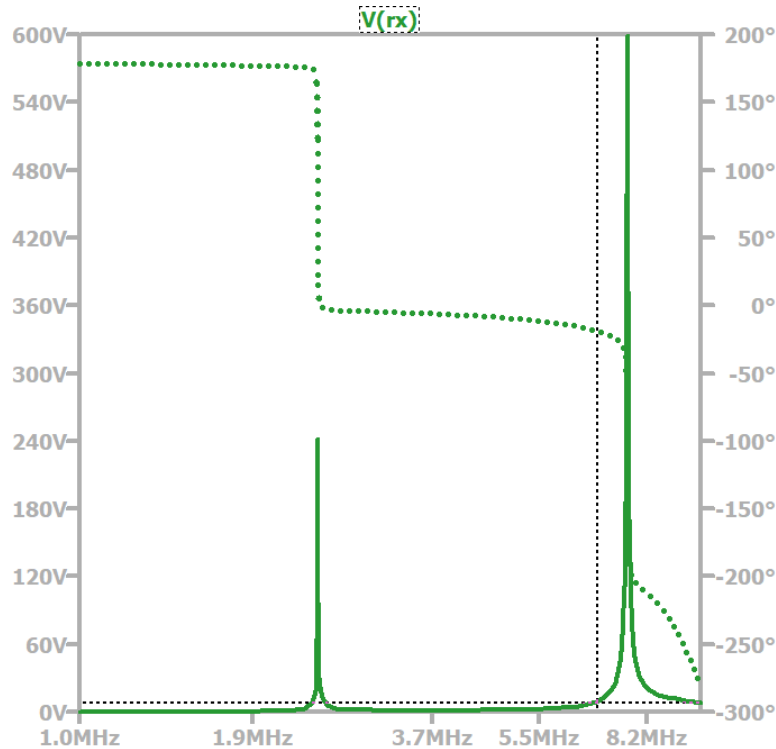

Form of the solution

$$\sum_{i=0}^N b_i \frac{d^i}{dt^i} v_o(t) = \sum_{i=0}^M a_i \frac{d^i}{dt^i} v_i(t)$$