
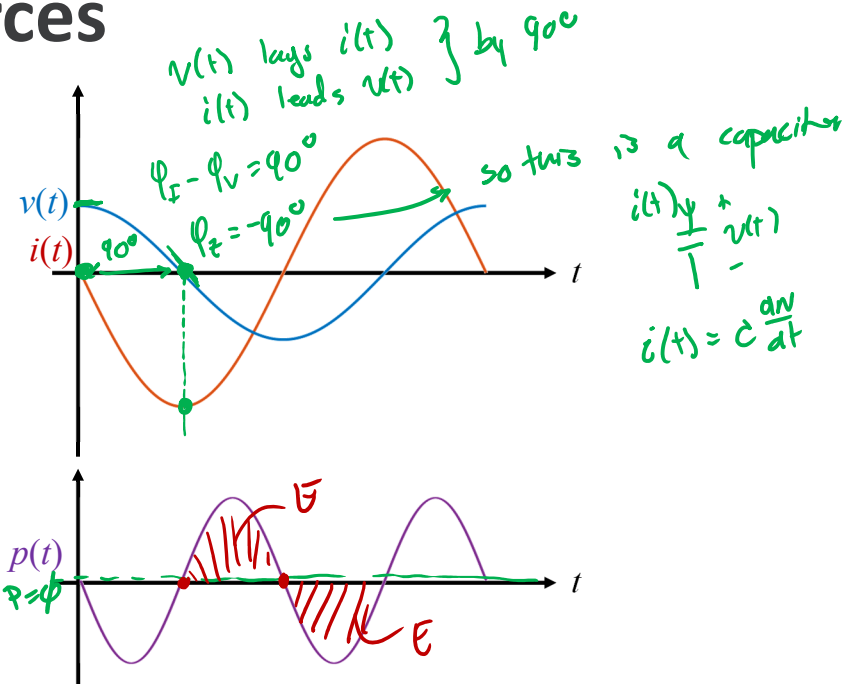
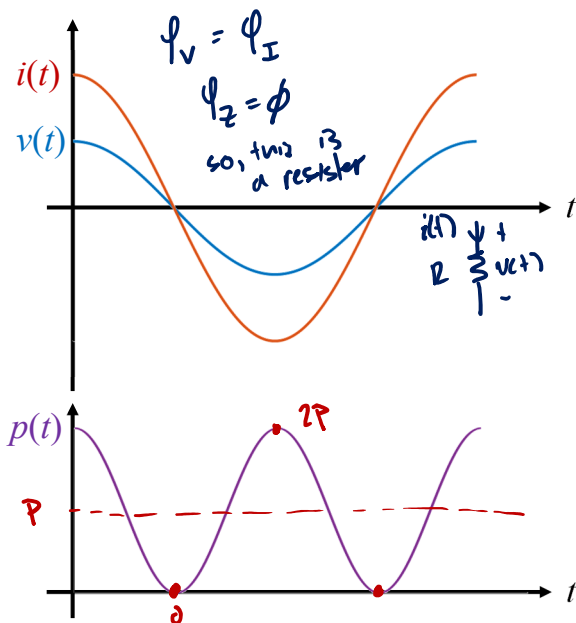


Power with Sinusoidal Sources

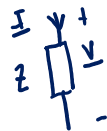

$$P = \frac{V_A I_A}{2} \cos(\phi_v - \phi_i) = \frac{V_A I_A}{2} \cos(\phi_z) = \frac{V_A I_A}{2} \cos(\phi) = \frac{V_A I_A}{2}$$


for a resistor

$$P = \frac{V_A I_A}{2} \cos(-90^\circ) = 0$$

for a capacitor
Capacitors & inductors must have $P=0$ in steady-state

Complex Power
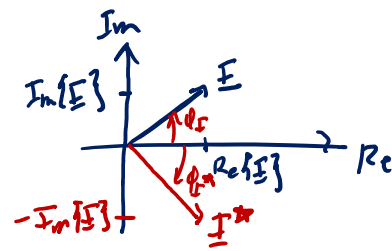
$$\begin{aligned}
 P &= \frac{V_A I_A}{2} \cos(\phi_V - \phi_I) = \left[\frac{1}{2} \operatorname{Re} \{ \underline{V} \underline{I}^* \} \right] \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V_A e^{j\phi_V} \cdot I_A e^{j(-\phi_I)} \right\} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V_A I_A e^{j(\phi_V - \phi_I)} \right\} \\
 &= \frac{1}{2} V_A I_A \cos(\phi_V - \phi_I)
 \end{aligned}$$



What about the imaginary part of $\underline{V} \underline{I}^*$

$$\begin{aligned}
 S &= \frac{1}{2} \underline{V} \underline{I}^* = P + jQ \\
 \uparrow & \qquad \qquad \qquad \uparrow \qquad \qquad \qquad \uparrow \\
 \text{complex power} & \qquad \qquad \text{Average power} & \qquad \qquad \text{Reactive power} \\
 [VA] & \qquad \qquad \qquad \text{"Real power"} & \qquad \qquad [VAR] \\
 \text{Volt-amp} & \qquad \qquad \qquad [W] & \qquad \qquad \text{"volt-amp reactive"} \\
 & \qquad \qquad \qquad \text{watts} & \qquad \qquad
 \end{aligned}$$

Apparent Power & Power Factor

"Apparent Power" = $|S| = \frac{V_A I_A}{2}$
- maximum possible real power for V_A & I_A stresses on circuit

"Power Factor" $PF = \frac{P}{|S|} = \frac{\frac{V_A I_A}{2} \cos(\phi_z)}{\frac{V_A I_A}{2}} = \cos(\phi_z) = \cos(\phi_v - \phi_f)$
either leading or lagging
current with respect to
voltage

$$0 \leq PF \leq 1$$


Power Triangle

$$V_A = \sqrt{2} V_{rms}$$

$$I_A = \sqrt{2} I_{rms}$$


$$\phi_V - \phi_I = \phi_Z$$

$$\underline{V} = \underline{I} Z$$

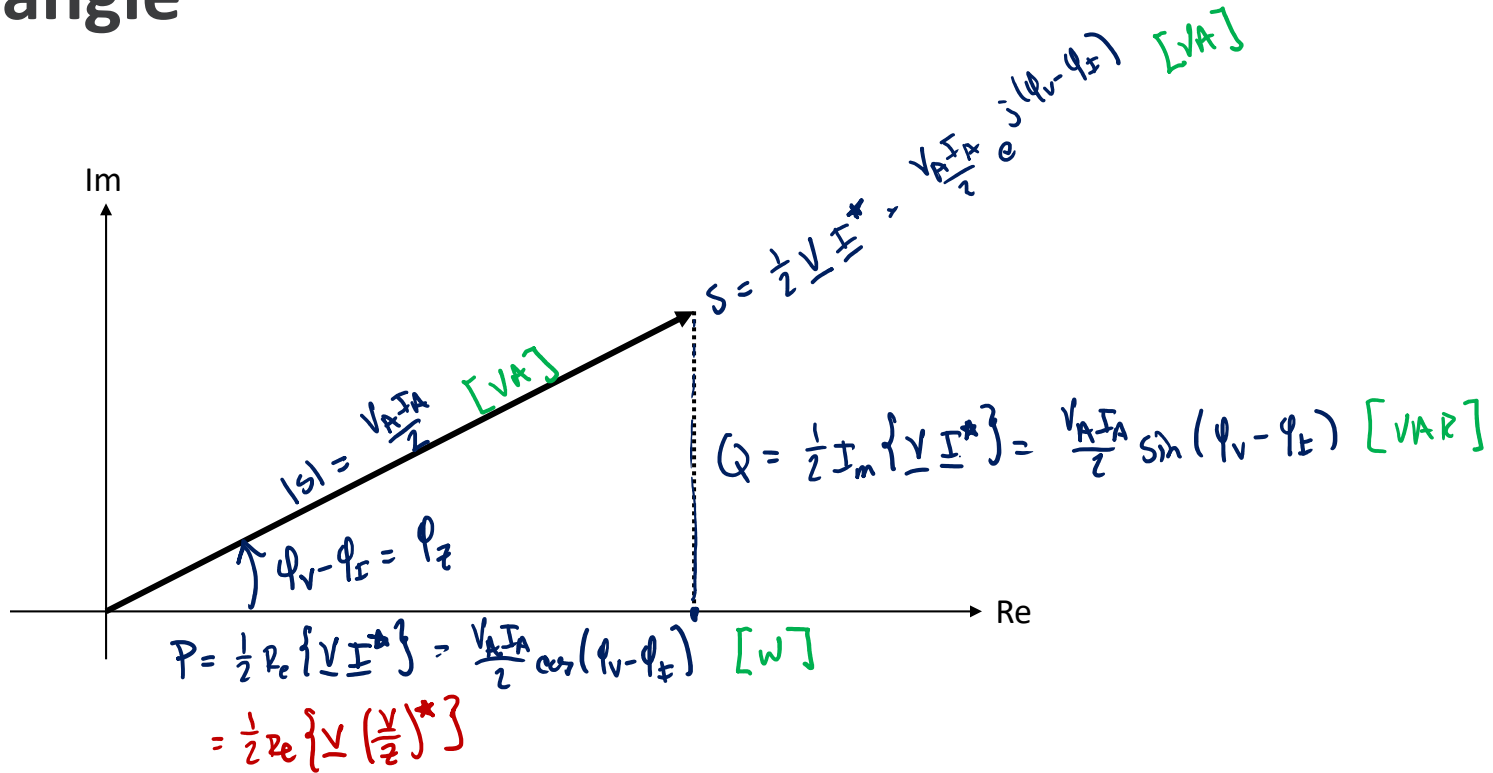

$$\text{PF} = \frac{P}{|S|} = \cos(\phi_V - \phi_I) \quad \text{leading or lagging}$$

Maximum Power Transfer

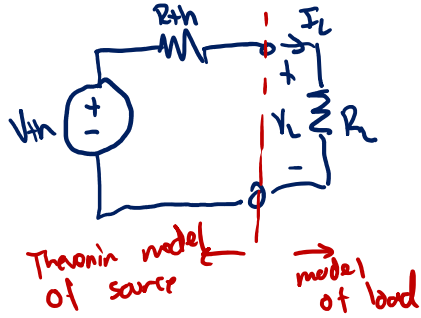

what value of R_L will yield maximum power $P_L = V_L I_L$

Answer: $R_L = R_{th}$

$$P_L = V_L I_L = \left(V_{th} \frac{R_L}{R_L + R_{th}} \right) \left(\frac{V_{th}}{R_L + R_{th}} \right) = V_{th}^2 \frac{R_L}{(R_L + R_{th})^2}$$

to find extrema


$$\frac{\partial P_L}{\partial R_L} = V_{th}^2 \left[\frac{1 \cdot (R_L + R_{th})^2 - R_L (2) (R_L + R_{th})}{(R_L + R_{th})^4} \right] = 0$$

$$0 = \frac{R_L + R_{th} - 2R_L}{(R_L + R_{th})^3} \rightarrow \text{numerator } R_{th} - R_L = 0$$

what value of R_{th} will give maximum power to a fixed R_L ?

$$R_{th} = 0$$

for power

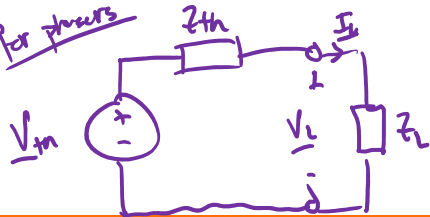

what Z_L will maximize power transfer to the load?

$$Z_L = Z_{th}^*$$