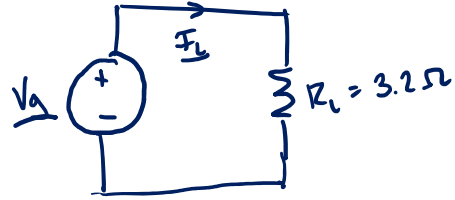


Matching Example

$$\omega = 2\pi 60 \text{ Hz}$$

$$V_g = 170 \angle 0^\circ \text{ V}$$


residential wall outlet is
120Vrms = 170Vpk @ 60Hz



with $R_L = 3.2 \Omega \approx$ equivalent model of plugged-in load

$$\underline{I}_L = \frac{V_g}{R_L} = \frac{170 \angle 0^\circ}{3.2} = \underline{53 \angle 0^\circ \text{ A}}$$
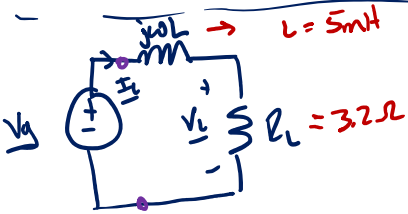
$$S_g = \frac{1}{2} V_g \underline{I}_L = \frac{1}{2} (170 \angle 0^\circ) (53 \angle 0^\circ) = \underline{4.5 \text{ kW} + j0 \text{ VAR}} = 4.5 \angle 0^\circ \text{ kVA}$$



$$Z_L = j(2\pi 60)(5 \times 10^{-3}) = j1.89 \Omega$$

$$\underline{I}_L = \frac{V_g}{j\omega L + R_L} = \frac{170 \angle 0^\circ}{3.2 + j1.89} = \underline{45 \angle -30^\circ \text{ A}}$$

$$\underline{V}_L = R_L \underline{I}_L = (3.2 \Omega) (45 \angle -30^\circ \text{ A}) = 146.5 \angle -30^\circ \text{ V}$$

$$P_L = \frac{1}{2} \text{Re}\{V_L \underline{I}_L^*\} = \frac{1}{2} \frac{|V_L| |I_L|}{2} \cos(\phi_{V_L} - \phi_{I_L}) = \frac{1}{2} (146.5) (45) = \underline{3.3 \text{ kW}}$$

$$S_g = \frac{1}{2} V_g \underline{I}_L^* = \frac{1}{2} (170 \angle 0^\circ) (45 \angle +30^\circ) = 3.8 \angle 30^\circ \text{ kVA} = \underline{3.3 \text{ kW}} + j \underline{1.9 \text{ kVAR}}$$

to R_L to L


$$\text{PF}_g = \frac{P_g}{|S_g|} = \frac{3.3 \text{ kW}}{3.8 \text{ kVA}} = \underline{0.87 \text{ lagging}}$$

↳ current lags voltage

Generally, "lagging" corresponds to inductive loads
"leading" to capacitive

$$\text{PF} = \cos(\phi_V - \phi_I) = \cos(\phi_Z)$$


$$\phi_Z = \angle(j\omega L + R_L)$$

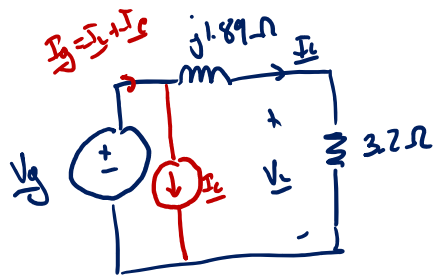

Can we return grid PF to unity

PF = 1, S_g is all real


$$PF = \cos(\phi_v - \phi_i)$$

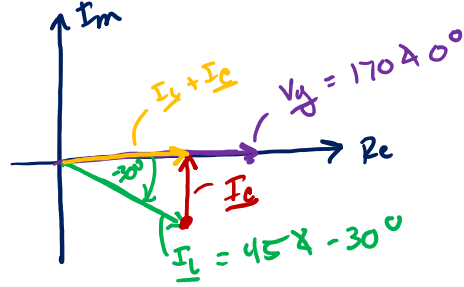

$$\begin{aligned} \underline{I}_c &= j I_m \{ \underline{I}_L^* \} = j 45 \sin(30^\circ) \\ &= j 22.5 \text{ A} = 22.5 \angle +90^\circ \end{aligned}$$

Can this be a passive impedance?
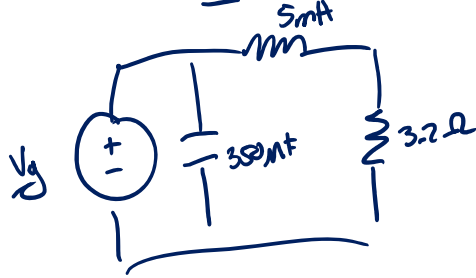
$$z_c = \frac{V_g}{\underline{I}_c} = \frac{170 \angle 0^\circ}{22.5 \angle +90^\circ} = 7.56 \angle -90^\circ = -j 7.56 \Omega = \frac{-j}{\omega C} \rightarrow C = 350 \mu\text{F}$$



$$S_g = \frac{1}{2} (V_g) (\underline{I}_L + \underline{I}_c)^* = 3.3 \text{ kW} + j 0 \text{ VAR}$$