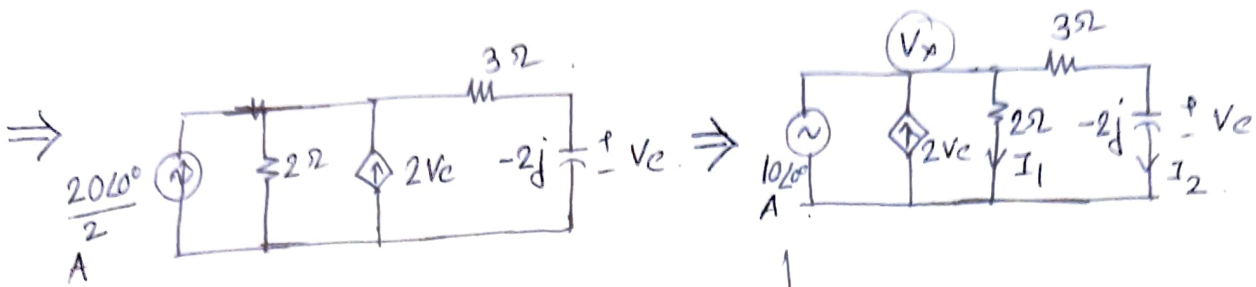


Avg power supplied by the dependent source;



$$I_2 = \frac{(10\angle 0^\circ + 2V_c) * 2}{(2 + 3 - 2j)}$$

$$V_c = -2j I_2 = -2j \frac{2(10\angle 0^\circ + 2V_c)}{5 - 2j}$$

$$5V_c - 2V_c j = -40j - 8j V_c$$

$$V_c(5 - 2j + 8j) = -40j$$

$$V_c = \frac{-40j}{5 + 6j} = -3.93 - 3.28j = 5.12 \angle -140.15^\circ \text{ V}$$

Volt across of source $2V_c$

$$V_x = V_c + 3I_2$$


$$= V_c + 3 \frac{2(10 + 2V_c)}{5 - 2j}$$

$$= \frac{60}{5 - 2j} + V_c + \frac{12V_c}{5 - 2j} = \frac{60}{5 - 2j} + V_c \left(\frac{17 - 2j}{5 - 2j} \right) = 9.23 \angle -83.79^\circ \text{ V}$$

$$S = V_x (2V_c)^* = 9.23 \angle -83.79^\circ (2 * 5.12 \angle -140.15^\circ)^* \\ = 94.5 \angle 56.36^\circ$$

$$\text{Avg Power } P = \frac{1}{2} \text{Re}(S) = \frac{1}{2} * 94.5 \cos 56.36^\circ \\ = 26.175 \text{ watt}$$

Method - 2

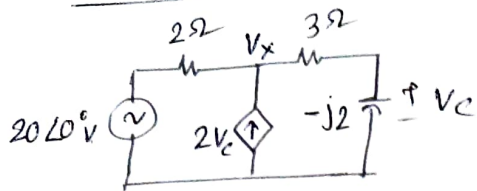

$$\text{KCL: } -\frac{20\angle 0^\circ - V_x}{2} + 2V_c = \frac{V_x}{3-2j} \rightarrow \textcircled{1}$$

$$V_c = \frac{V_x}{3-2j} (-2j) \rightarrow \textcircled{2}$$

Substitute (2) in (1).

$$\frac{20\angle 0^\circ - V_x}{2} + 2 \frac{V_x}{3-2j} (-2j) = \frac{V_x}{3-2j}$$

$$10\angle 0^\circ - \frac{V_x}{2} - \frac{4j V_x}{3-2j} = \frac{V_x}{3-2j}$$

$$V_x \left(\frac{-1}{3-2j} + \frac{4j}{3-2j} + \frac{1}{2} \right) = 10$$

$$V_x = 9.23 \angle -83.9^\circ \text{ V}$$

$$\text{From } \textcircled{2}, \quad V_c = \frac{-2j}{3-2j} V_x = 5.119 \angle -140.2^\circ \text{ A V}$$


Power supplied ?

$$S = \bar{V}_x (2\bar{V}_c)^*$$

$$= 9.23 \angle -83.9^\circ (2 \times 5.119 \angle -140.2^\circ)^*$$

$$= 94.5 \angle 56.36^\circ$$
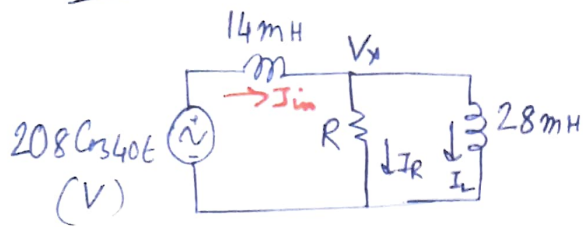
$$\text{Avg power} = \frac{1}{2} \text{Re}(S) = \frac{1}{2} \times 94.5 \cos 56.36^\circ = 26.175 \text{ watt}$$



a) What is the value of R for which voltage across 14mH and R will have same RMS value?


b) Find the RMS voltage across R .

Solⁿ

~~RMS~~ volt across $R =$ ~~RMS~~ volt across 28mH .

$$|I_{in}| \times 40 \times (14\text{m}) = |I_L| \times 40 \times 28\text{m}$$

$$|I_{in}| = 2|I_L|$$

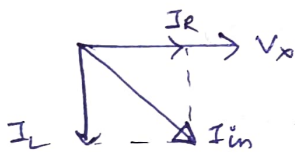

$$\Rightarrow |I_{in}| = \sqrt{I_R^2 + I_L^2}$$

$$(2I_L)^2 = \sqrt{I_R^2 + I_L^2}$$

$$|I_R| = \sqrt{3}|I_L|$$

$$|I_R| = \frac{V_x}{R} \quad \& \quad |I_L| = \left| \frac{V_x}{j40 \times 28\text{m}} \right| = \frac{V_x}{40 \times 28\text{m}}$$

$$\frac{V_x}{R} = \sqrt{3} \frac{V_x}{40 \times 28\text{m}}$$

$$R = \frac{40 \times 28\text{m}}{\sqrt{3}} = 0.6466\Omega$$

~~$$V_{RMS} = \frac{208}{\sqrt{2}} \frac{1}{\sqrt{2}} (208) \quad V_x = 208 \angle 0^\circ$$~~

Verify

$$R = 0.6466\Omega$$

$$I_{in} = \frac{208 \angle 0^\circ}{j14\text{m} \times 40 + \frac{Rj28\text{m} \times 40}{R + j28 \times 40}} = 214.45 \angle -60^\circ \text{ A}$$

volt across 14mH

$$= \bar{V}_L = j I_{in} (14\text{m} \times 40) = 120 \angle 30^\circ \text{ V}$$

$$\bar{V}_x = 208 \angle 0^\circ - 120 \angle 30^\circ = 120 \angle -30^\circ \text{ V} \Rightarrow \text{RMS} = \frac{V_L}{\sqrt{2}} = 84.85 \text{ V}$$

Method - II

$$Z = R \parallel (j\omega 28m) = R \parallel j1.12j = \frac{j1.12R}{R + j1.12}$$

$$V_R = \frac{Z}{j\omega 14m + Z} V_S = \frac{Z}{j0.56 + Z} 200\angle 0^\circ$$

$$= \frac{j1.12}{-0.6272 + j1.68R} (200\angle 0^\circ) \text{ V} \rightarrow \textcircled{1}$$

$$V_L : \text{VOLT across } 14mH = \frac{j0.56}{j0.56 + Z} (200\angle 0^\circ) \text{ V}$$

$$= \frac{-0.6272 + j0.56R}{-0.6272 + j1.68R} 200\angle 0^\circ \text{ V} \rightarrow \textcircled{2}$$

$$V_{R, \text{RMS}} = V_{L, \text{RMS}}$$

$$|V_R| = |V_L| \quad (\text{from } \textcircled{1} \text{ \& } \textcircled{2})$$

$$\Rightarrow \frac{.1.12R}{\sqrt{0.6272^2 + (1.68R)^2}} = \frac{\sqrt{0.6272^2 + (0.56R)^2}}{\sqrt{0.6272^2 + (1.68R)^2}}$$


$$1.12R = \sqrt{0.6272^2 + (1.68R)^2}$$

$$R = \frac{0.6272}{\sqrt{0.9408}} = 0.6466 \Omega$$

Put R in (1) or (2)

$$V_{R, \text{RMS}} = V_{L, \text{RMS}} = \frac{120}{\sqrt{2}} = 84.92 \text{ V}$$

(49)

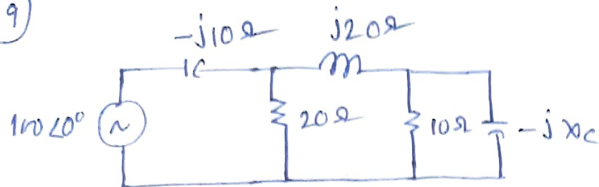

Find X_c that improves Pf to 0.95.

Solution
Method 1

Without X_c , find the Pf.

$$Z_{eq} = -j10 + 20 \parallel (10 + j20)$$

$$= 11.435 \angle -19.65^\circ \Omega$$

$$\cos(19.65^\circ) = 0.94 \text{ leading}$$

$$\rightarrow \text{as } \angle Z_{eq} = -19.65^\circ$$

indicates predominantly capacitive loading

With X_c Pf improves to 0.95 leading.

$$Z_1 = 10 \parallel -jX_c = \frac{-j10X_c}{10 - jX_c}$$

$$Z_2 = j20 - \frac{j10X_c}{10 - jX_c} = \frac{20X_c + j(200 - 10X_c)}{10 - jX_c}$$

$$Z_3 = 20 \parallel Z_2 = \frac{2(20X_c + j(200 - 10X_c))}{(20 + 2X_c) + j(20 - 3X_c)}$$

$$Z_{eq}^{new} = Z_3 - 10j = -10j + \frac{2(20X_c + j(200 - 10X_c))}{(20 + 2X_c) + j(20 - 3X_c)}$$

Simplify through a number of steps!

$$= \frac{8000 - 800X_c + 140X_c^2}{(20 + 2X_c)^2 + (20 - 3X_c)^2} + j \frac{-50X_c^2}{(20 + 2X_c)^2 + (20 - 3X_c)^2}$$




$\angle Z_{eq}^{new}$

$$= \tan^{-1} \frac{-50X_c^2}{8000 - 800X_c + 140X_c^2} = \cos^{-1}(0.95)$$

$$X_c = 8.82 \Omega$$

For 50 Hz supply, $C = 360.89 \mu\text{F}$

Method 2

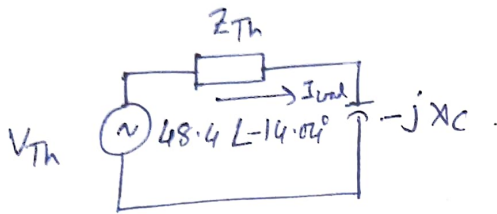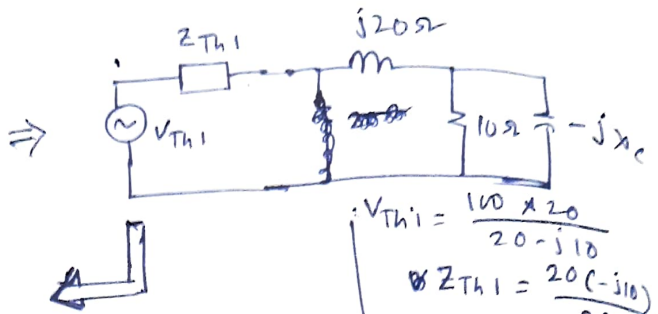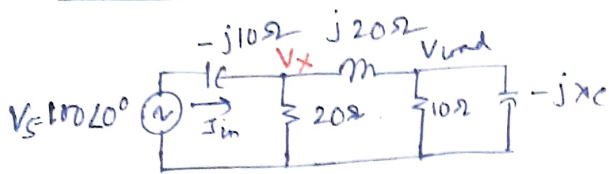

$$Z_{Th} = \frac{10(4 + j12)}{4 + j12} = 5.88 + j3.53 \Omega$$

$$V_{Th1} = \frac{100 \times 20}{20 - j10}$$

$$Z_{Th1} = \frac{20(-j10)}{20 - j10}$$

$$V_{Th2} = \frac{V_{Th1} \cdot 10}{10 + j20}$$

$$Z_{Th} = \frac{10 \parallel (Z_{Th1} + j20)}{10 + Z_{Th1} + j20}$$

$$\bar{I}_{Load} = \frac{V_{Th}}{Z_{Th} - jX_c} = \frac{48.4 \angle -14.04^\circ}{5.88 + j(3.53 - X_c)} \text{ A}$$

Need to find I/P Pf i.e. the angle between V_s and I_{in} across is of interest.

* Note that, what we have found above is \bar{I}_{Load} , not \bar{I}_{in} .

From \bar{I}_{Load} , $\bar{V}_{Load} = -jX_c \bar{I}_{Load}$


$$\bar{V}_x = \bar{V}_{Load} + \left(\frac{\bar{V}_{Load}}{10} + \bar{I}_{Load} \right) j20$$

↪ Ct in j20Ω

$$\bar{I}_{in} = \frac{\bar{V}_s - \bar{V}_x}{-j10}$$

$$\angle I_{in} = \cos^{-1} 0.95 = 18.19^\circ$$

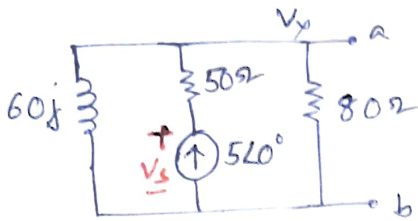~~Equation~~ From this X_c can be found. However, this method is not less computationally intensive than the previous method.



$$a) \quad \frac{\bar{V}_x}{80} + \frac{\bar{V}_x}{j60} = 5$$

$$\bar{V}_x = 144 + 192j$$

$$\bar{V}_s - 50 * 5\angle 0^\circ = \bar{V}_x$$

$$\bar{V}_s = 250 + \frac{80(j60)}{80 + j60} = 394 + 192j$$

$$b) \quad i) \quad S_{80} = VI^* = \left[\frac{5(80 * j60)}{80 + j60} \right] \left[\frac{1}{80} \frac{5(80 + j60)}{80 + j60} \right]^*$$

$$= (144 + 192j) \frac{(144 - 192j)}{80} = 720 + j0 \text{ VA}$$

$$ii) \quad S_{j60} = (144 + 192j) \left(\frac{144 + 192j}{j60} \right)^*$$


$$= 0 + 960j \text{ VA}$$

$$iii) \quad S_{50} = \frac{1}{2} (V_s - V) * 5 = \frac{1}{2} (394 + 192j - 144 - 192j) * 5$$

$$= (1250 + 0j) \text{ VA}$$

$$c) \quad S_{\text{source}} = V_s * 5 = 1970 + 960j$$
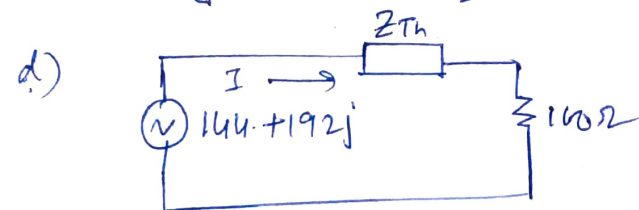
$$\text{Avg. Power} = \frac{1}{2} * 1970 = 985 \text{ watt}$$



$$Z_{th} = 80 + j60$$

$$= 48 \angle 53.13^\circ \Omega$$

$$V_{th} = 5(80 + j60)$$

$$= 144 + 192j \text{ V}$$

$$I = \frac{144 + 192j}{48 \angle 53.13^\circ + 160} = 1.7856 \angle 36.53^\circ \text{ A}$$

$$\text{Avg Power} = \frac{1}{2} I^2 R \approx 160 \text{ watt}$$