

Announcements

- Experiment 2 Posted
- Guest lecture feedback (Dr. Mukhopadhyay)
 - Worked problems posted to website
- Midterm Wednesday March 6th

HW4 and Quiz 2 Notes

- $v(t)$ is always a time domain expression
 - $v(t) = V_A \cos(\omega t + \varphi)$
 - $V = \underline{V} = A + j X = V_A e^{j\varphi} = V_A \angle \varphi$
- SI prefixes

PREFIX	ABBREVIATION	MEANING
pico-	p	0.000000000001 or 10^{-12}
nano-	n	0.000000001 or 10^{-9}
micro-	μ	0.000001 or 10^{-6}
milli-	m	0.001 or 10^{-3}
kilo	k	1,000 or 10^3
Mega-	M	1,000,000 or 10^6
Giga-	G	1,000,000,000 or 10^9
Tera-	T	1,000,000,000,000 or 10^{12}

Midterm

- Midterm Wednesday March 6th
 - Covers coupled inductors and transformers, phasor circuit analysis and complex power
 - 3 problems, ~3x quiz length, Full class period for the exam
 - Lectures 1-16, HW 1-5, Quiz 1-2, Chapters 10,11, & 13
 - Recommended:
 - Review all lecture slides and in-class examples
 - Review solutions to HW problems where you missed points
 - Rework Quizzes
 - Create crib sheet
 - Practice complex numbers on your calculator
 - Read through Experiment 1 and 2 review/introductions

Midterm Problems:

1. Phasor circuit analysis with transformer and multiple sources
 - Solve for output signal
2. Phasor circuit analysis with mutual inductances
 - Understand coupling coefficient and dot notation
 - Solve for output signal
3. Phasor power
 - Solve for and implement matched load impedance (Max Power)
 - Solve S and PF

Chapter 13

MUTUAL INDUCTANCE

Inductance: Review

We know inductor has circuit behavior $V_1 = L_1 \frac{di_1}{dt}$



for an inductor

$$\Phi = \Phi_r$$

$$J_1 = \alpha \frac{d\Phi}{dt}$$

= L for single-turn

For an N -turn inductor

$$\Phi = Nai_1$$



$$V_1 = N \frac{d\Phi}{dt}$$

$$N_1 = N^2 \alpha \frac{di_1}{dt}$$


Amperes law
total flux
 $\oint B \cdot d\ell = \mu_0 I_{enc}$

$$\oint B \cdot d\ell = \mu_0 I_{enc}$$

parameter depends on geometry & physical constants

Faraday's law
 $V_1 = \frac{d\Phi_r}{dt}$

Mutual Inductance

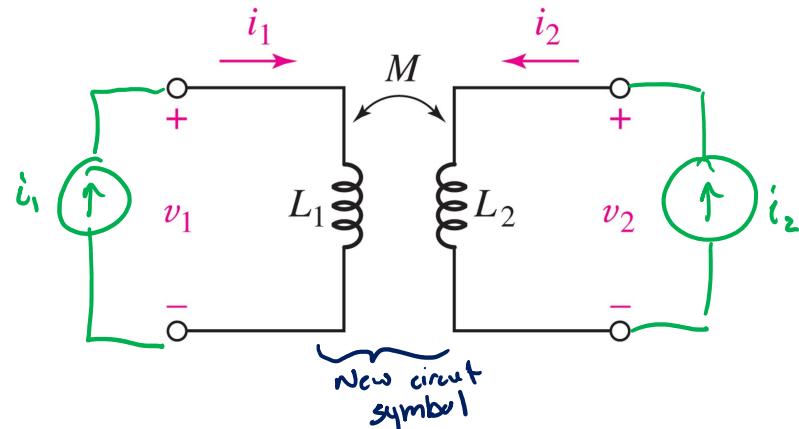

By superposition

$$\left\{ \begin{array}{l} V_1 = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} \\ V_2 = \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{array} \right.$$

Apply superposition

with $i_2 = \phi$

$$\left\{ \begin{array}{l} V_1 = L_1 \frac{di_1}{dt} \\ V_2 = M \frac{di_1}{dt} \end{array} \right.$$


with $i_1 = \phi$

$$\left\{ \begin{array}{l} V_1 = M \frac{di_2}{dt} \\ V_2 = L_2 \frac{di_2}{dt} \end{array} \right.$$


Symbols and Dot Convention

* Make sure to use passive sign convention

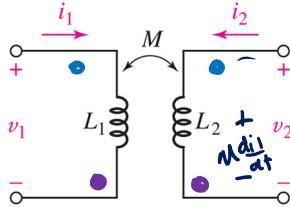
$$\left\{ \begin{array}{l} V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ V_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{array} \right.$$



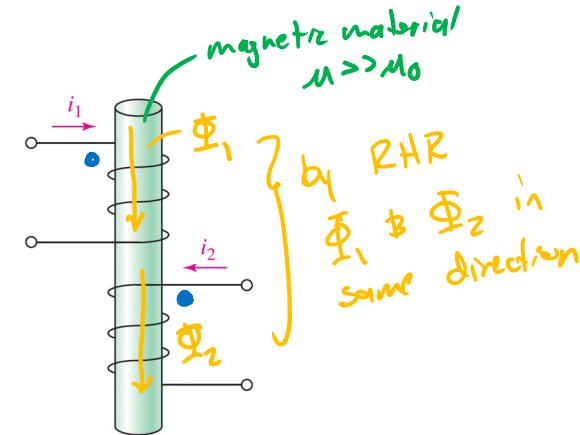
Physical: If both i_1 & i_2 enter the dotted terminals of L_1 & L_2 , they produce additive flux



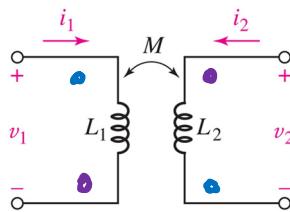
$$\left\{ \begin{array}{l} V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ V_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{array} \right.$$



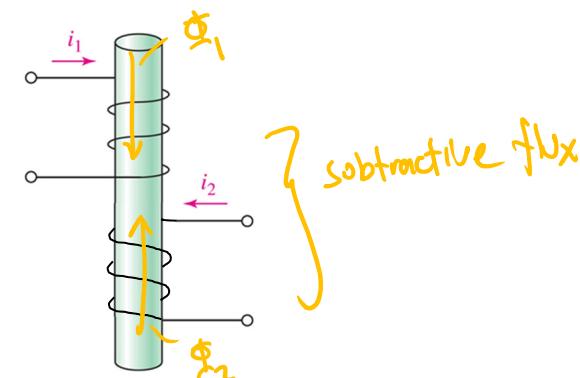
Circuit: current flowing into the dotted terminal will produce a positive voltage relative to the dotted terminal of the other winding (in open circuit)




Dot Notation Example

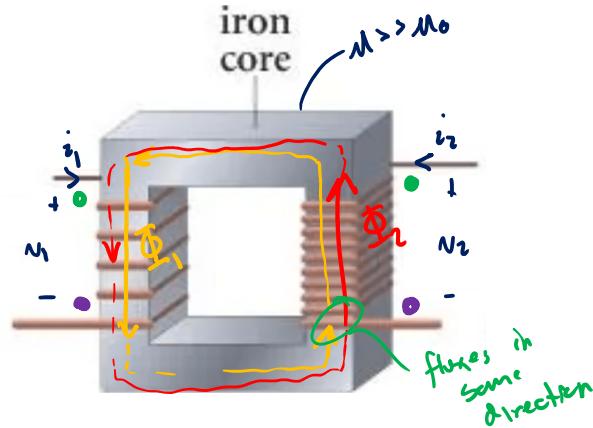

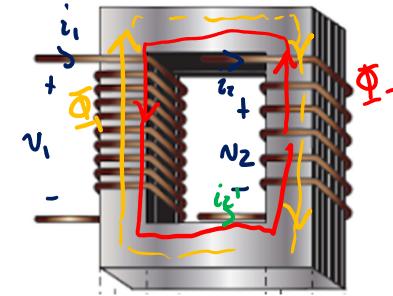Find which terminals should be dotted
on each winding (2 possibilities)




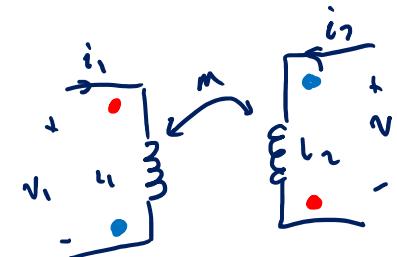Sketch circuit symbol with some
reference polarities



Energy Storage

@ $t=\phi$, $i_1=\phi$, $i_1=I_0$

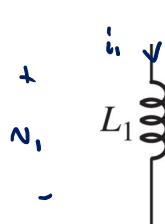


Review

$$E_L = \int_0^{t_0} v_1 \cdot i_1 dt = \int_0^{t_0} L_1 \left[i_1 \cdot \frac{di_1}{dt} \right] dt$$

$$= \frac{1}{2} L_1 \int_0^{t_0} \frac{d}{dt} i_1(t)^2 dt = \frac{1}{2} L_1 \left[i_1(t=t_0)^2 - i_1(t=0)^2 \right]$$

$E_L = \frac{1}{2} L_1 I_0^2$
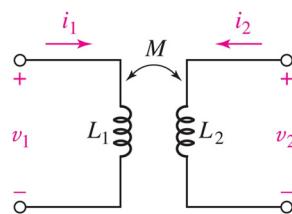
$$i_1 \frac{di_1}{dt} = \frac{1}{2} \left[\frac{d}{dt} i_1(t)^2 \right] = \frac{1}{2} \left[2i_1(t) \frac{di_1}{dt} \right]$$



At $t=\phi$ $i_1=\phi \neq i_2=\phi$, at $t=t_0$ $i_1=I_1$ $i_2=I_2$

$$E = \int_0^{t_0} (v_1 i_1 + v_2 i_2) dt$$

$$= \int_0^{t_0} \left(L_1 i_1 \frac{di_1}{dt} + M i_1 \frac{di_2}{dt} + L_2 i_2 \frac{di_2}{dt} + M i_2 \frac{di_1}{dt} \right) dt$$

$$= \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm \int_0^{t_0} \left(M i_1 \frac{di_2}{dt} + M i_2 \frac{di_1}{dt} \right) dt$$

$$\Rightarrow E = M \frac{d}{dt} (i_1 \cdot i_2)$$

$E = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2$

starting from zero currents & ramping up to $I_1 = I_1$ & $I_2 = I_2$, must be true that

$$E = \frac{1}{2}L_1 I_1^2 + \frac{1}{2}L_2 I_2 + M I_1 I_2 \geq 0$$

$$M \leq \frac{\frac{1}{2}L_1 I_1^2 + \frac{1}{2}L_2 I_2}{I_1 I_2} = \frac{1}{2}L_1 \frac{I_1}{I_2} + \frac{1}{2}L_2 \frac{I_2}{I_1}$$

find minimum of $\frac{1}{2}L_1 x + \frac{1}{2}L_2 \frac{1}{x}$, $x = \frac{I_1}{I_2}$

$$\frac{\partial M}{\partial x} = \frac{1}{2}L_1 - \frac{1}{2}L_2 \frac{1}{x^2} = 0 \quad x = \sqrt{\frac{L_2}{L_1}}$$

$$\frac{\partial^2 M}{\partial x^2} = L_2 \frac{1}{x^3} \quad \checkmark$$

so,

$$M \leq \frac{1}{2}L_1 \sqrt{\frac{L_2}{L_1}} + \frac{1}{2}L_2 \sqrt{\frac{L_1}{L_2}} = \frac{1}{2}\sqrt{L_1 L_2} + \frac{1}{2}\sqrt{L_1 L_2}$$

$$M \leq \sqrt{L_1 L_2}$$

Coupling Coefficient



define coupling coefficient $k = \frac{M}{\sqrt{L_1 L_2}}$

$$0 \leq k \leq 1$$


$k=0 \rightarrow$ two separate inductors

$k=1 \rightarrow$ perfect coupling between them
all of Φ_1 flows through L_2 & vice versa
known as a "transformer"

Equivalent Circuits

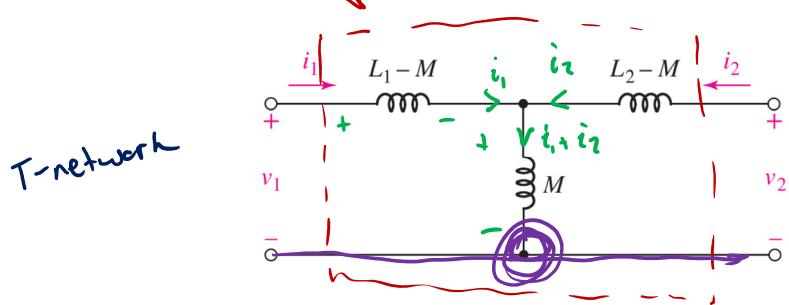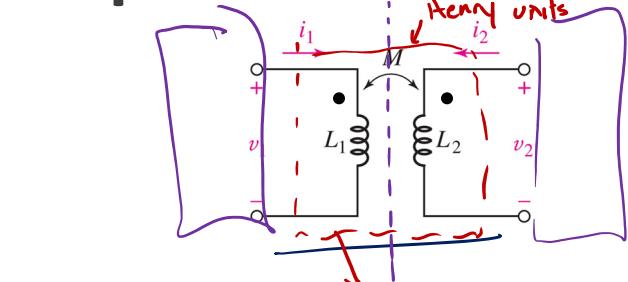


unitless
 t between
0 and 1

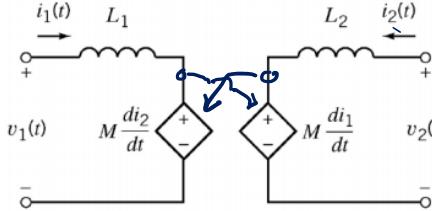

$$\begin{cases} N_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ N_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

T₁-network

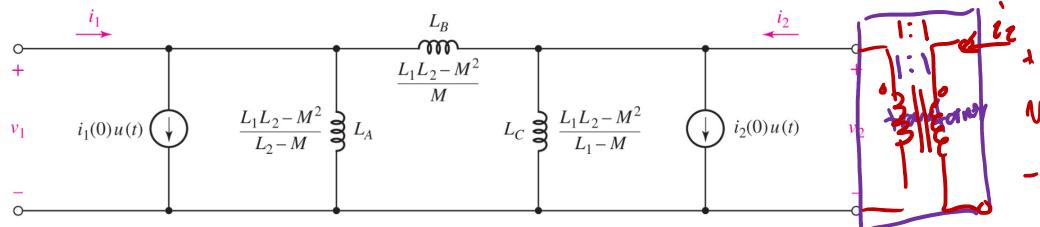


Transformers

Special case of coupled inductors

$$\begin{cases} N_1 = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} \\ N_2 = \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

with $k=1$ \longleftrightarrow perfect coupling $\longleftrightarrow M = \sqrt{L_1 L_2}$
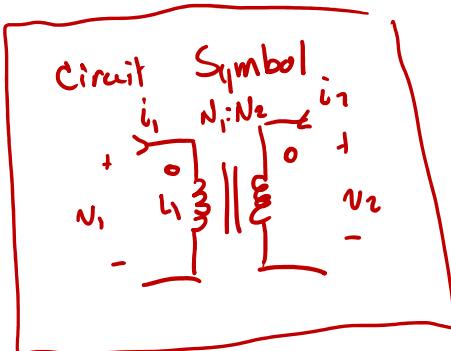
$$\xrightarrow{M = \sqrt{L_1 L_2}} \begin{cases} V_1 = L_1 \frac{di_1}{dt} \pm \sqrt{L_1 L_2} \frac{di_2}{dt} \\ V_2 = \pm \sqrt{L_2} L_2 \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$



$N_1 : N_2$ is the same as $1 : N$, $N = \frac{N_2}{N_1}$

$$N_1 = \sqrt{\frac{L_1}{L_2}} V_2$$

$$V_1 = -\sqrt{\frac{N_1^2}{N_2^2}} V_2$$

$$N_1 = \frac{N_1}{N_2} N_2$$

if $k=1$, it must be true that $\alpha_1 = \alpha_2$

$\frac{N_1}{N_2}$ is the "turns ratio"


Ideal Transformer

"Ideal" transformer has very large L_1 & L_2

Recall: Inductors (~~transformers~~) cannot have DC voltage applied to their windings

- $N_1 = L_1 \frac{di_1}{dt} \rightarrow i_1 = \frac{1}{L_1} \int_0^t V_1 dt \rightarrow$ DC voltage causes current to go to ∞
- Materials \rightarrow core materials needed for $K \approx 1$ & will saturate & stop working at some finite current
- $V = N \frac{d\phi}{dt} \rightarrow$ Faraday's Law, need time-varying waveforms

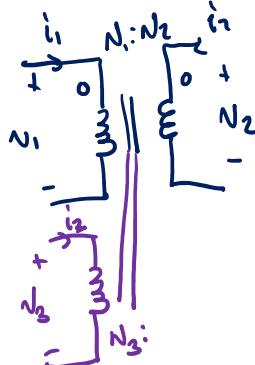when L_1 & L_2 are large enough \rightarrow No energy storage



$$V_1 = \frac{N_1}{N_2} V_2$$

No energy storage, so

$$V_1 i_1 + V_2 i_2 = \emptyset$$

$$\left(\frac{N_1}{N_2} V_2 \right) i_1 + V_2 i_2 = \emptyset$$

$$N_1 i_1 + N_2 i_2 = \emptyset$$

$$i_1 = -\frac{N_2}{N_1} i_2$$

for more than two turns

$$\frac{N_1}{N_1} = \frac{V_2}{N_2} = \frac{V_3}{N_3} = \dots$$

$$N_1 i_1 + N_2 i_2 + N_3 i_3 + \dots = \emptyset$$




Transformer Reflection

$$\frac{v_1}{i_1} = \frac{N_2}{N}$$


$$1i_1 + N_1 i_2 = \phi$$

$$N_1 = \frac{N_2}{N}$$


$$i_1 = -N_1 i_2$$

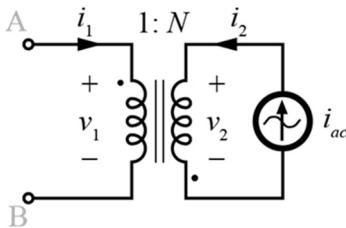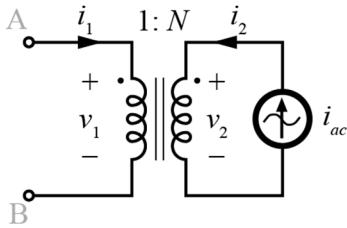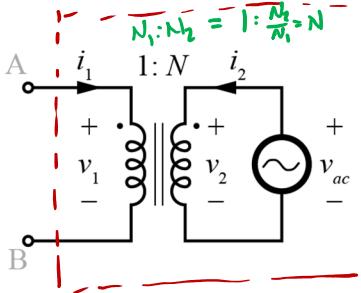


equivalent circuit
at primary

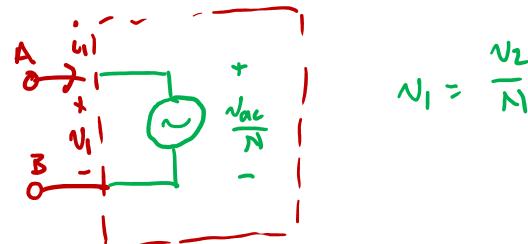



$$N_1 = \frac{N_2}{N}$$

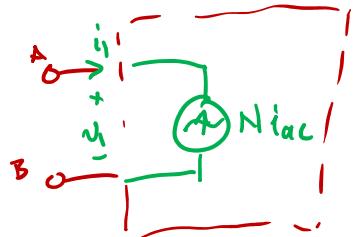

$$i_1 = -N_1 i_2$$

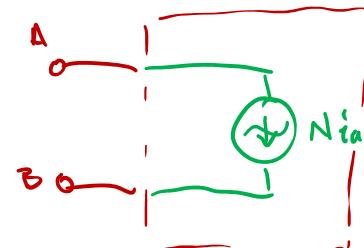

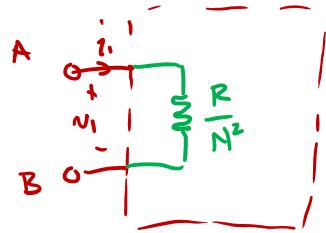
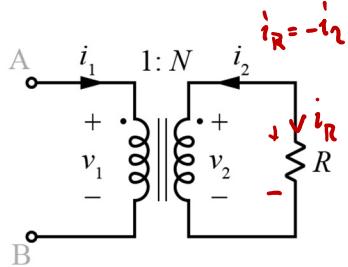
$$\left. \begin{aligned} v_1 &= \frac{N_2}{N} v_2 \\ i_1 &= -N i_2 \end{aligned} \right\}$$



$$v_2 = (-i_2) R$$

$$N v_1 = \left(\frac{1}{N}\right) i_1 R$$
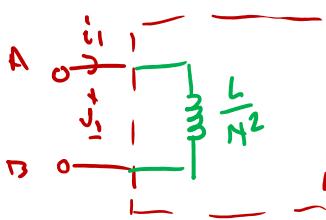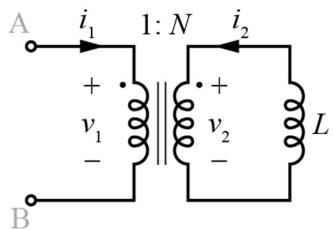
$$v_1 = \left(\frac{1}{N^2} R\right) i_1$$



$$v_2 = L \frac{d(-i_2)}{dt}$$



$$N v_1 = L \frac{d}{dt} \left(\frac{1}{N} i_1 \right)$$

$$v_1 = \frac{1}{N^2} L \frac{d i_1}{dt}$$

$$-i_2 = C \frac{d N_2}{dt}$$

$$\frac{1}{N} i_1 = C \frac{d}{dt} N v_1$$

$$i_1 = N^2 C \frac{d N_2}{dt}$$

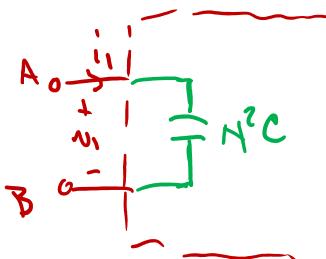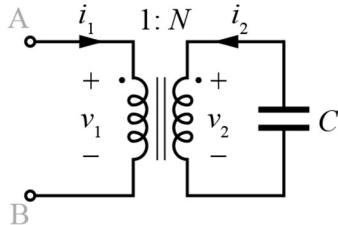

Chapter 10


PHASOR MODELING

Sinusoids as Complex Numbers

$$\begin{aligned} v(t) &= A \cos(\omega t + \phi) \\ &= \operatorname{Re} \left\{ A e^{j(\omega t + \phi)} \right\} \\ &= \operatorname{Re} \left\{ A e^{j\omega t} e^{j\phi} \right\} \end{aligned}$$

cosine *magnitude* *sinusoid* *phase*
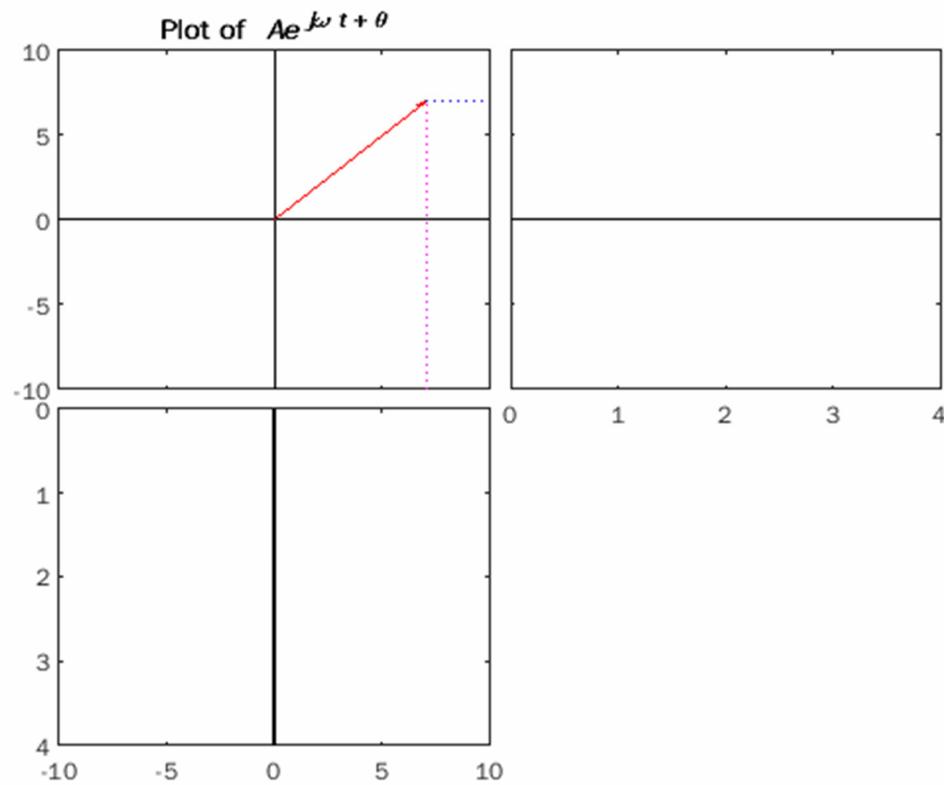
$$\begin{aligned} \frac{d}{dt} v(t) &= -A \omega \sin(\omega t + \phi) = A \omega \cos(\omega t + \phi + 90^\circ) \\ &= \operatorname{Re} \left\{ A \omega e^{j\omega t} e^{j\phi} e^{j\frac{\pi}{2}} \right\} \\ &= \operatorname{Re} \left\{ A (\underline{j\omega}) e^{j\omega t} e^{j\phi} \right\} \end{aligned}$$



Phasor Transformation

"Phasor" is a complex number that represents a sinusoid
→ useful in analyzing single-frequency sinusoidal circuits in steady-state

$$A \cos(\omega t + \phi)$$

{
A amplitude
 ϕ phase
 ω frequency
cos sinusoidal
t time

→ for single-frequency circuits

function → by convention, always use
cos

→ steady-state, single-frequency

$$A \cos(\omega t + \phi) = \text{Re} \{ A e^{j\omega t} e^{j\phi} \}$$

phasor transform

$$\xrightarrow{} Ae^{j\phi}$$

Phasor Notation

$$v(t) = A \cos(\omega t + \phi) = \operatorname{Re} \{ A e^{j\omega t} e^{j\phi} \}$$

$$\underline{v} = Ae^{j\phi} \xleftrightarrow{\text{transform}} A \angle \phi \text{ (short hand)}$$

Bold in book
underline in lecture


$$\begin{aligned} i(t) &= B \sin(\omega t + \theta) \\ &= B \cos(\omega t + \theta - 90^\circ) \\ &\quad \downarrow \text{transform} \\ \underline{i} &= Be^{j(\theta - \frac{\pi}{2})} \xleftrightarrow{} B \angle (\theta - \frac{\pi}{2}) \end{aligned}$$

Comments:

- Phasor transform works for all voltage / current sources & signals
- Everything must be at same frequency ω
- Using complex numbers in transformation
 - No "t" in any phasor expression
 - No complex # in time domain


Phasor Circuit Elements

Time Domain

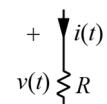

$$v(t) = i(t)R$$

Phasor Domain

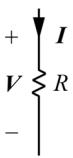

$$v(t) = A \cos(\omega t + \phi)$$


$$i(t) = \frac{A}{R} \cos(\omega t + \phi)$$

$$v(t) = i(t)R$$


$$\underline{V} = A e^{j\phi}$$

$$\underline{I} = \frac{A}{R} e^{j\phi}$$

$$\underline{V} = \underline{I} R$$

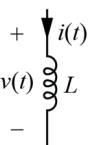

$$v(t) = L \frac{di}{dt}$$

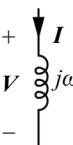

$$i(t) = A \cos(\omega t + \phi)$$


$$v(t) = A L \omega \cos(\omega t + \phi + 90^\circ)$$

$$\underline{I} = A e^{j\phi}$$


$$\underline{V} = A \omega L e^{j(\phi + \frac{\pi}{2})}$$

$$\underline{V} = A j \omega L e^{j\phi}$$
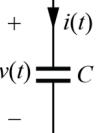
$$\underline{V} = (j \omega L) \underline{I}$$



$$i(t) = C \frac{dv}{dt}$$

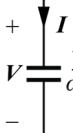

$$v(t) = A \cos(\omega t + \phi)$$

$$i(t) = A C \omega \cos(\omega t + \phi + 90^\circ)$$


$$\underline{V} = A e^{j\phi}$$

$$\underline{I} = A C \omega e^{j\phi} e^{j\frac{\pi}{2}}$$

$$\underline{I} = A j \omega C e^{j\phi}$$

$$\underline{V} = \frac{1}{j \omega C} \underline{I} = \frac{-j}{\omega C} \underline{I}$$


Time Domain

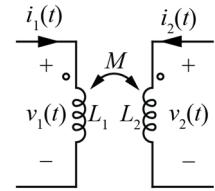

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

Phasor Domain

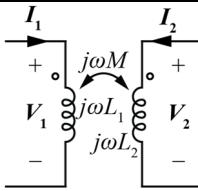


$$\underline{V}_1 = j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2$$
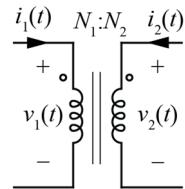
$$\underline{V}_2 = j\omega M \underline{I}_1 + j\omega L_2 \underline{I}_2$$



$$\frac{v_1(t)}{N_1} = \frac{v_2(t)}{N_2}$$

$$N_1 i_1(t) + N_2 i_2(t) = 0$$

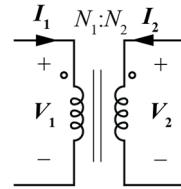

$$\frac{\underline{V}_1}{N_1} = \frac{\underline{V}_2}{N_2}$$

$$N_1 \underline{I}_1 + N_2 \underline{I}_2 = \phi$$



Impedance

Phasor equivalent of ohm's law

$$\underline{V} = \underline{I} Z$$

$$Z \rightarrow \text{"impedance"}, \quad Z = R + jX$$

↑ "resistance" $\text{Re}\{Z\}$ ↑ "reactance" $\text{Im}\{Z\}$

$$Y = \text{"Admittance"} = \frac{1}{Z} = G + jB$$

↑ "conductance" ↑ "susceptance"

→ units of siemens (or mhos)

$$\frac{1}{Z} \neq \frac{1}{R} + j \frac{1}{X}$$


$$\frac{1}{Z} = \frac{1}{R+jX} \cdot \frac{(R-jX)}{(R-jX)} = \frac{R-jX}{R^2+X^2} = \frac{R}{R^2+X^2} - j \frac{X}{R^2+X^2}$$

$$\left\{ \begin{array}{l} Z_R = R \quad \text{for resistor} \\ Z_L = j\omega L \quad \text{for inductor} \\ Z_C = \frac{-j}{\omega C} \quad \text{for capacitor} \end{array} \right.$$

All Z have units of Ohms


Phasor Circuit Analysis

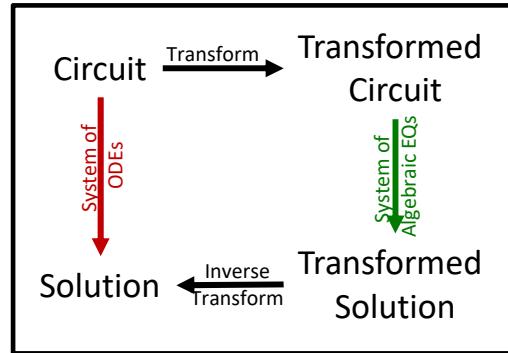Goal: Analyze a LTI circuit to find steady-state solution with only single-frequency sinusoidal source(s)



1. Transform all sources & signals into their phasor equivalents
2. Transform all passives into impedances
3. Solve the circuit
 - Use 201 techniques for DC resistor-only circuits
4. Transform solution back into the time domain

Reactance and Resonance

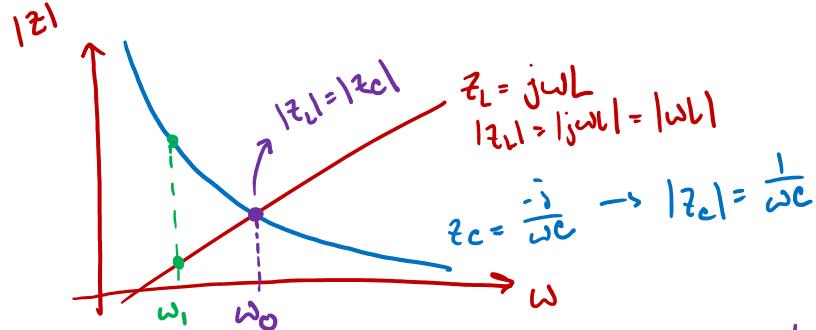

At low frequency $\omega \rightarrow 0$

At resonance


$$j\omega L - \frac{-j}{\omega C} = 0$$

$$\Rightarrow \text{short } @ \text{resonance } (\omega_0)$$

$$Z_{eq} = j\omega L + \frac{-j}{\omega C}$$

($\approx DC$) $Z_C \rightarrow 0$ (open)
 $Z_L \rightarrow \infty$ (short)

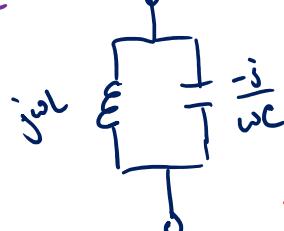$Z_C \rightarrow \infty$ (short)
 $Z_L \rightarrow 0$ (open)



\Rightarrow open @ resonance

$$@ \omega_0 \rightarrow |Z_L| = |Z_C|$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

resonant frequency

$$\text{for only } Z \text{ in parallel}$$

$$Z_{eq} = \frac{1}{\frac{1}{j\omega L} + \frac{1}{\frac{-j}{\omega C}}} = \frac{j\omega L \cdot \left(\frac{-j}{\omega C}\right)}{j\omega L + \frac{-j}{\omega C}}$$

Phasor Superposition

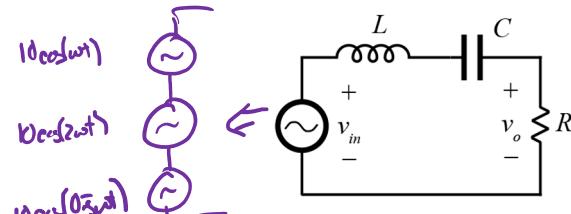

$$\omega_{LF} = \frac{1}{2}\omega = 2\pi 50 \text{ kHz}$$

$$V_{in} = 10 \angle 0^\circ$$

$$z_L = j\omega L = j\pi$$

$$z_R = R = 10 \Omega$$

$$z_C = \frac{j}{\omega_{LF} C} = -j4\pi$$

same

$$V_o = V_{in} \frac{z_L}{z_L + z_C + z_R} = 0.73 \angle 43^\circ$$

$$N_{oLF}(t) = 0.73 \cos(0.5\omega t + 43^\circ)$$

3 frequencies → apply superposition in time domain

Find $v_o(t)$ for $v_{in}(t) = 10\cos(\omega t) + 10\cos(2\omega t) + 10\cos(0.5\omega t)$
and $\omega = 2\pi 100 \text{ kHz}$, $R = 10 \Omega$, $L = 10 \mu\text{H}$, and $C = 253 \text{ nF}$

$$\omega = 2\pi 100 \text{ kHz}$$

$$V_{in} = 10 \angle 0^\circ$$

$$z_L = j\omega L = j2\pi$$

$$z_R = R = 10$$


$$z_C = \frac{j}{\omega C} = -j2\pi$$

$$\omega_{HF} = 2\omega = 2\pi 200 \text{ kHz}$$

$$V_{in} = 10 \angle 0^\circ$$

$$z_L = j\omega_{HF} L = j4\pi$$
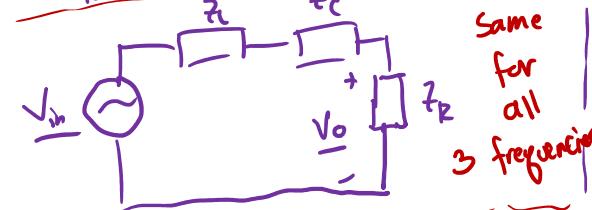
$$z_C = \frac{-j}{\omega_{HF} C} = -j\pi$$



$$V_o = V_{in} \frac{z_L}{z_L + z_C + z_R} = \{10 \angle 0^\circ\}$$

$$v_o(t) = 10\cos(\omega t)$$

$$V_o = 0.73 \angle -43^\circ$$


$$N_{oHF}(t) = 0.73 \cos(2\omega t - 43^\circ)$$

$$N_o(t) = 10\cos(\omega t) + 0.73 \cos(0.5\omega t + 43^\circ) + 0.73 \cos(2\omega t - 43^\circ)$$

Chapter 11

POWER IN SINUSOIDAL STEADY STATE


Average Power

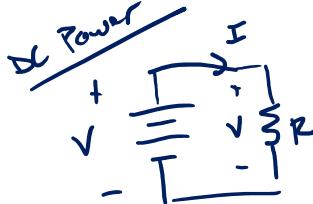

$$P_R = V \cdot I \rightarrow \text{Generally true for any 2-terminal element}$$

for a resistor $V = IR$

$$P_R = I^2 R = \frac{V^2}{R}$$

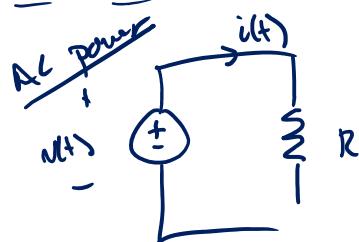

$$P_R(t) = v(t) \cdot i(t) \rightarrow \text{Generally true of all 2-terminal elements}$$

for a resistor $P_R(t) = i(t)^2 R = \frac{v(t)^2}{R}$

In any case, power calculation is not LTI

Average Power

capital "P" denotes average


$$\rightarrow P = \frac{1}{T} \int_{t_1}^{t_1+T} p(t) dt$$

Average power over all time

$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$$

Average power defined over some time interval

$$t \in [t_1, t_1 + T]$$

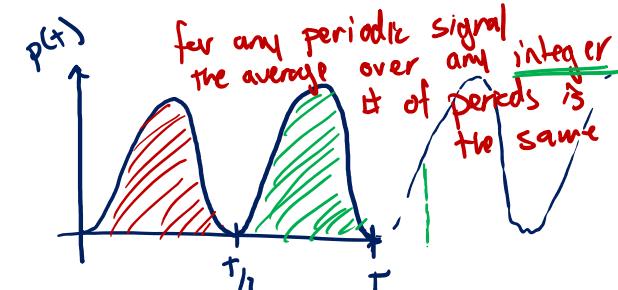

Power in a Resistor

Average power in a resistor with periodic (e.g. sinusoidal) sources

$$\begin{aligned} P_R &= \frac{1}{T} \int_0^T P_R(t) dt = \frac{1}{T} \int_0^T i(t)^2 R dt \\ &= R \underbrace{\frac{1}{T} \int_0^T i(t)^2 dt}_{\text{rms}}^2 \\ P_R &= R \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}^2 \end{aligned}$$

$$P_R = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$$

rms is 'root mean squared'

$$\text{Define rms } X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

Note: Book calls this "effective" instead of rms

$$I_{\text{eff}} = I_{\text{rms}} \quad V_{\text{eff}} = V_{\text{rms}}$$

RMS of a sinusoid

$$i(t) = I_A \cos(\omega t + \phi)$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T (I_A \cos(\omega t + \phi))^2 dt}$$

$$I_{rms}^2 = \frac{1}{T} \int_0^T I_A^2 \cos^2(\omega t + \phi) dt$$

$$I_{rms}^2 = \frac{1}{T} I_A^2 \frac{1}{2} \int_0^T 1 + \cos(2\omega t + 2\phi) dt$$

$$I_{rms}^2 = \frac{1}{T} I_A^2 \frac{1}{2} \left[t + \sin(2\omega t + 2\phi) \frac{1}{2\omega} \right] \Big|_0^T \quad \text{where } T = \frac{2\pi}{\omega}$$

$$I_{rms}^2 = \frac{1}{T} I_A^2 \frac{1}{2} \left[\left(\frac{2\pi}{\omega} - 0 \right) + \frac{1}{2\omega} (\sin(4\pi + 2\phi) - \sin(2\phi)) \right]$$

~~$$I_{rms}^2 = \frac{\omega}{2\pi} I_A^2 \frac{1}{2} \frac{2\pi}{\omega}$$~~

~~$$I_{rms}^2 = \frac{I_A^2}{2}$$~~



$$\boxed{I_{rms} = \frac{I_A}{\sqrt{2}}}$$


$$\omega = 2\pi f \quad T = \frac{1}{f} = \frac{2\pi}{\omega}$$

trig identity

$$\cos^2(\theta) = \frac{1}{2}(1 + \cos 2\theta)$$

for any sinusoidal signal

Power with Sinusoidal Sources

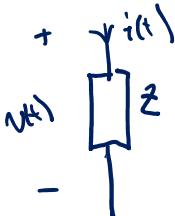

In steady-state with single-frequency sinusoidal sources @ ω

$$\begin{aligned} v(t) &\rightarrow \underline{V} = V_A e^{j\phi_V} \\ i(t) &= \underline{I} = I_A e^{j\phi_I} \end{aligned} \quad \left. \begin{array}{l} \text{with } \underline{V} = \underline{I}Z \\ \text{and } \underline{Z} = \frac{\underline{V}}{\underline{I}} = \frac{V_A e^{j\phi_V}}{I_A e^{j\phi_I}} = \frac{V_A}{I_A} e^{j(\phi_V - \phi_I)} \end{array} \right\}$$

Power: since power is not LTI, we don't know how to calculate power w/ phasors
Not $\underline{V} \cdot \underline{I}$ → go back to time domain to calculate




$$\begin{aligned} p(t) &= i(t) \cdot v(t) = I_A \cos(\omega t + \phi_I) \cdot V_A \cos(\omega t + \phi_V) \\ &= I_A V_A \left(\underbrace{\cos(2\omega t + \phi_I + \phi_V)}_{\text{sinusoid } @ 2\omega} + \underbrace{\cos(\phi_I - \phi_V)}_{\text{constant (not time-varying)}} \right) \end{aligned}$$

Trig Identity: $2 \cos \theta \cos \phi = \cos(\theta + \phi) + \cos(\theta - \phi)$

Average Power


$$P_Z = \boxed{\frac{I_A V_A}{2} \cos(\phi_I - \phi_V)} = \frac{I_A V_A}{2} \cos(\phi_Z) = V_{\text{rms}} I_{\text{rms}} \cos(\phi_Z)$$

Power with Sinusoidal Sources

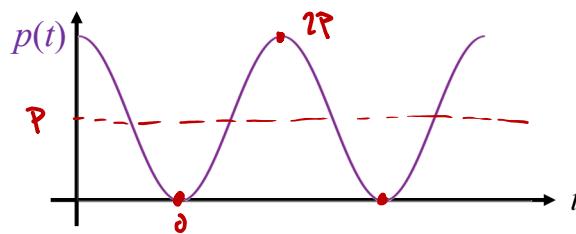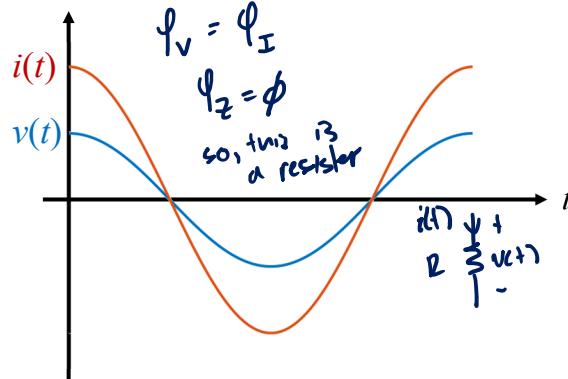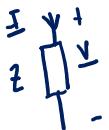

$$P = \frac{V_A I_A}{2} \cos(\varphi_V - \varphi_I) = \frac{V_A I_A}{2} \cos(\varphi_Z) = \frac{V_A I_A}{2} \cos(\phi) = \frac{V_A I_A}{Z}$$

for a resistor

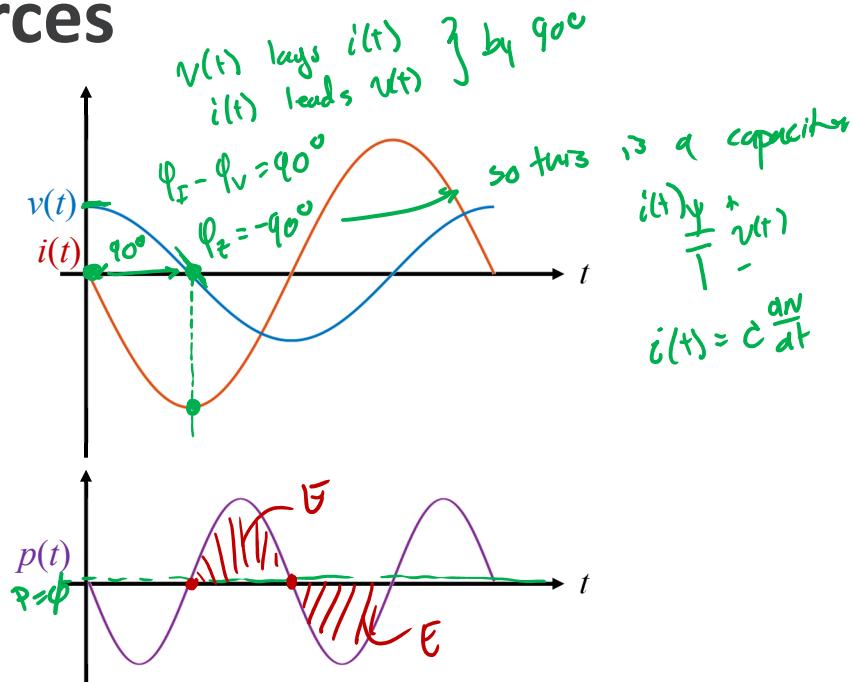

for a capacitor

$$P = \frac{V_A I_A}{2} \cos(-90^\circ) = 0$$


Capacitors & inductors must have $P=0$ in steady-state

Complex Power

$$\begin{aligned}
 P &= \frac{V_A I_A}{2} \cos(\phi_V - \phi_I) = \left| \frac{1}{2} R_c \right\{ V I^* \} \boxed{\checkmark} \\
 &= \frac{1}{2} R_c \left\{ V_A e^{j\phi_V} \cdot I_A e^{j(1-\phi_I)} \right\} \\
 &= \frac{1}{2} R_c \left\{ V_A I_A e^{j(\phi_V - \phi_I)} \right\} \\
 &= \frac{1}{2} V_A I_A \cos(\phi_V - \phi_I) \quad \boxed{\checkmark}
 \end{aligned}$$

What about the imaginary part of $V I^*$
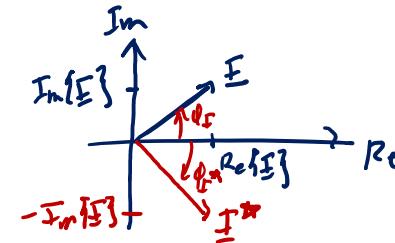
$$S = \frac{1}{2} V I^* = \begin{matrix} P \\ \uparrow \\ \text{complex power} \\ [VA] \\ \text{volt-amps} \end{matrix} + \begin{matrix} jQ \\ \uparrow \\ \text{"Real power"} \\ ["Real power"] \\ [W] \\ \text{watts} \end{matrix} \quad \begin{matrix} \text{Reactive power} \\ [VAR] \end{matrix} \quad \begin{matrix} "volt-amp reactive" \\ ["volt-amp reactive"] \end{matrix}$$




Power Triangle

$$V_A = \sqrt{2} V_{rms}$$

$$I_A = \sqrt{2} I_{rms}$$


$$\varphi_V - \varphi_I = \varphi_Z$$

$$Y = \underline{I}^2$$

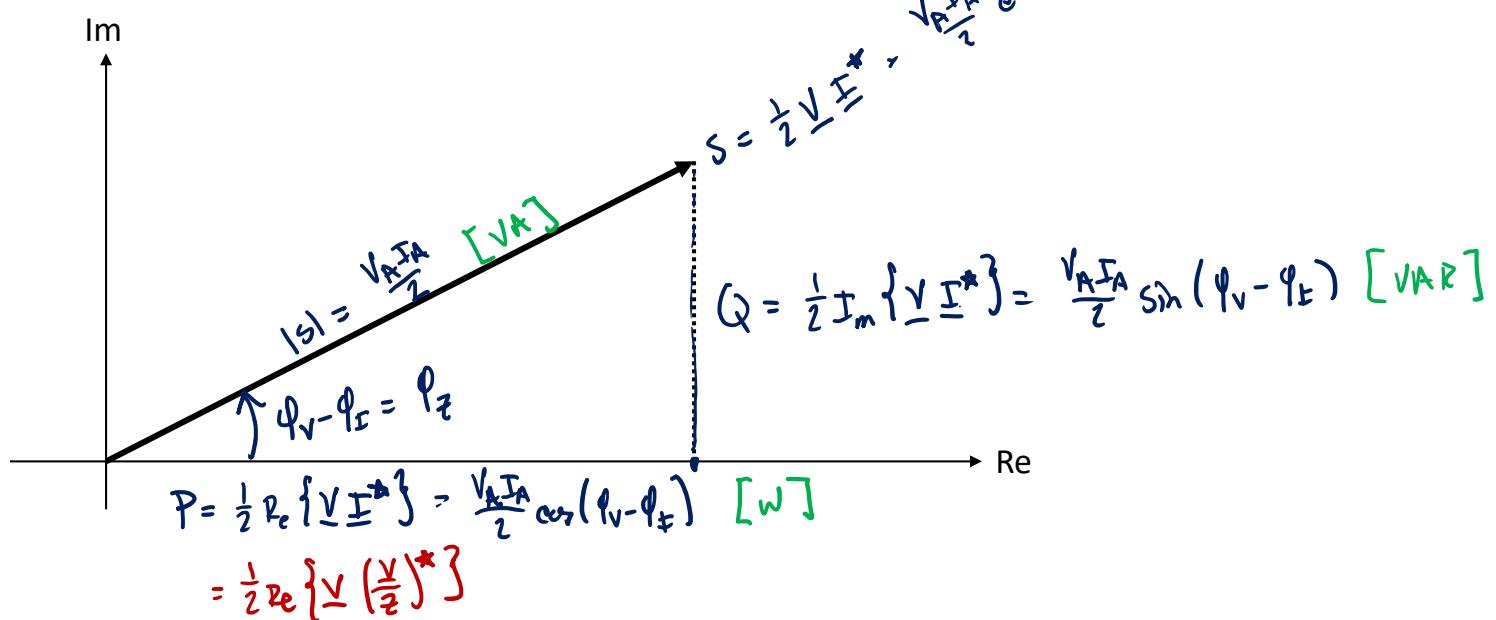

$$PF = \frac{P}{|S|} = \cos(\varphi_V - \varphi_I) \quad \text{leading or lagging}$$

Maximum Power Transfer

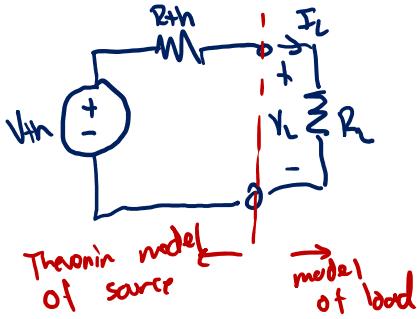

What value of R_L will yield maximum power

$$P_L = V_L I_L$$

Answer: $R_L = R_{th}$

$$P_L = V_L I_L = \left(V_{th} \frac{R_L}{R_L + R_{th}} \right) \left(\frac{V_{th}}{R_L + R_{th}} \right) = V_{th}^2 \frac{R_L}{(R_L + R_{th})^2}$$


to find extrema

$$\frac{\partial P_L}{\partial R_L} = V_{th}^2 \left[\frac{1 \cdot (R_L + R_{th})^2 - R_L (2) (R_L + R_{th})}{(R_L + R_{th})^4} \right] = \phi$$

$$0 = \frac{R_L + R_{th} - 2R_L}{(R_L + R_{th})^3} \rightarrow \text{numerator } R_{th} - R_L = \phi$$

What value of R_{th} will give maximum power to a fixed R_L ?


$$R_{th} = \phi$$

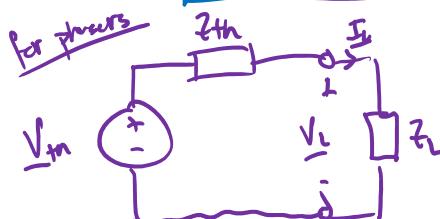

what Z_L will maximize power transfer to the load?

$$Z_L = Z_{th}^*$$


Impedance Matching

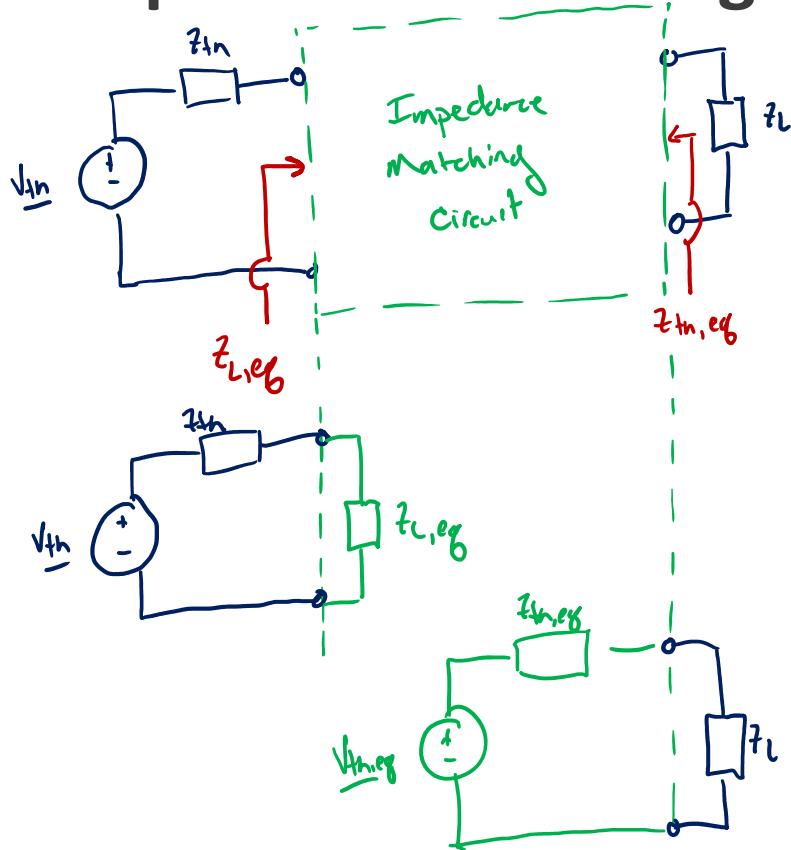

Impedance matching goals

- Maximize power transfer $\rightarrow Z_L = Z_{th,eq} \star$
- Minimize distortion $\rightarrow Z_L = Z_{th,eq}$
- Maximize efficiency $\rightarrow \text{Re}\{Z_{th,eq}\} \ll \text{Re}\{R_L\}$
- Maximize Quality Factor $\rightarrow \text{Im}\{Z_{th,eq}\} = \phi$


Example Matching Circuits

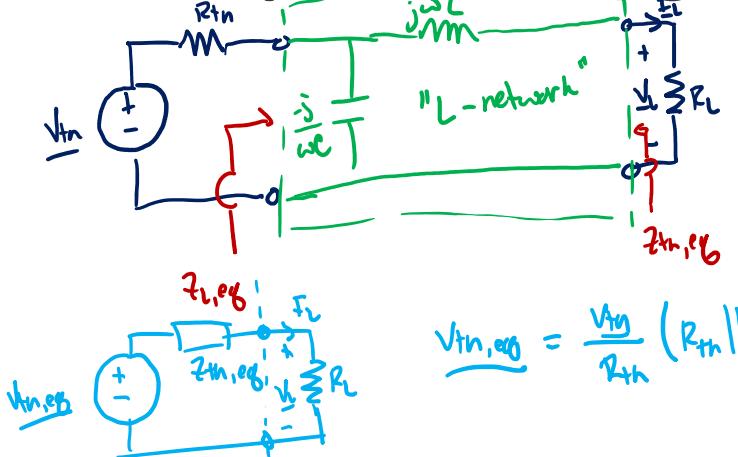

$$V_{th,eq} = \frac{V_{th}}{R_{th}} (R_{th} \parallel -jX_C)$$

$$X_C = \sqrt{\frac{R_L R_{th}^2}{R_{th}^2 - R_L}}$$
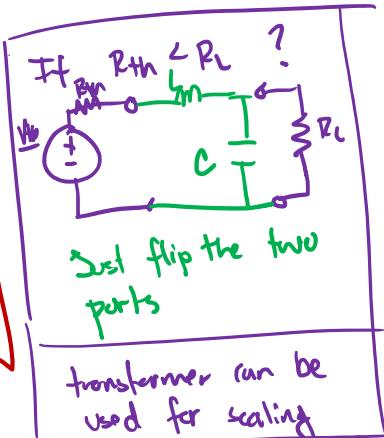
$$X_L = \frac{X_C R_{th}}{R_{th}^2 + X_C^2}$$



$R_m > R_L$, but want maximum possible power to R_L

Using "L-network" set

$$Z_L = jwL = jX_L, \quad X_L = wL$$

$$Z_C = \frac{j}{wC} = -jX_C, \quad X_C = \frac{1}{wC}$$

$$Z_{th,eq} = (R_{th} \parallel -jX_C) + jX_L$$

$$= \frac{-jX_C R_{th}}{R_{th} - jX_C} \frac{(R_{th} + jX_C)}{(R_{th} + jX_C)} + jX_L$$

$$= \frac{-jX_C R_{th}^2 + X_C^2 R_{th}}{R_{th}^2 + X_C^2} + jX_L$$


$$= \frac{X_C^2 R_{th}}{R_{th}^2 + X_C^2} + j \left[X_L - \frac{X_C^2 R_{th}}{R_{th}^2 + X_C^2} \right]$$

$$\text{Im}\{Z_{th,eq}\} = 0$$

$$\text{Im}\{Z_{th,eq}\} = \emptyset$$

$X_C \rightarrow \infty \quad \text{Re}\{Z_{th,eq}\} \rightarrow R_{th}$ } thus circuit reaches R_{th}
 $X_C \rightarrow \emptyset \quad \text{Re}\{Z_{th,eq}\} \rightarrow \emptyset$

Matching Example

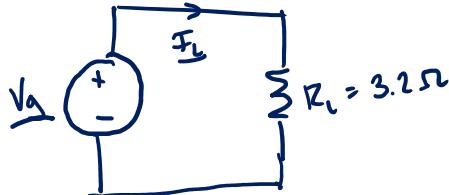

$$\omega = 2\pi 60 \text{ Hz}$$

$$V_g = 170 \angle 0^\circ \text{ V}$$

with $R_L = 3.2 \Omega \approx$ equivalent model of plugged-in load

residential wall outlet 13
120 V_{rms} = 170 V_{ph} @ 60 Hz


$$V_g = 170 \angle 0^\circ \text{ V}$$

$$I_L = \frac{V_g}{R_L} = \frac{170 \angle 0^\circ}{3.2} = 53 \angle 0^\circ \text{ A}$$

$$S_g = \frac{1}{2} V_g I_L = \frac{1}{2} (170 \angle 0^\circ) (53 \angle 0^\circ) = 4.5 \text{ kW} + j0 \text{ VAR}$$

$$j\omega L \rightarrow L = 5 \text{ mH}$$
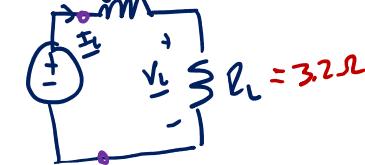
$$Z_L = j(2\pi\omega)(S_g - 3) = j1.89 \Omega$$



$$I_L = \frac{V_g}{j\omega L R_L} = \frac{170 \angle 0^\circ}{3.2 + j1.89} = 45 \angle -30^\circ \text{ A}$$

$$V_L = R_L I_L = (3.2 \Omega) (45 \angle -30^\circ \text{ A}) = 146.5 \angle -30^\circ \text{ V}$$

$$P_L = \frac{1}{2} R_L \{V_L I_L^*\} = \frac{M |I_L|}{2} \cos(\varphi_{V_L} - \varphi_{I_L}) = \frac{1}{2} (146.5) (45) = 3.3 \text{ kW}$$

$$S_g = \frac{1}{2} V_g I_L^* = \frac{1}{2} (170 \angle 0^\circ) (45 \angle -30^\circ) = 3.8 \angle 30^\circ \text{ kVA}$$


$$PF_g = \frac{P_g}{|S_g|} = \frac{3.3 \text{ kW}}{3.8 \text{ kVA}} = 0.87 \text{ lagging}$$

$$PF = \cos(\varphi_V - \varphi_I) = \cos(\varphi_2)$$

$$\varphi_2 = \angle (j\omega L + R_L)$$


↳ current v/s voltage

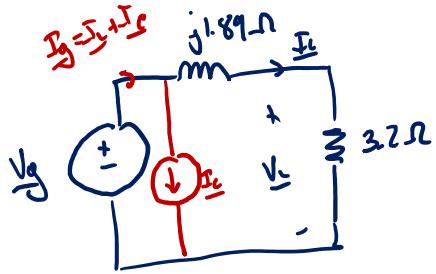Generally, "lagging" corresponds to inductive loads,
"leading" to capacitive




$$\underline{I_t} = j \underline{I_m} \{ \underline{I_t^*} \} = j 45 \sin(30^\circ) \\ = j 22.5 A = 22.5 \angle +90^\circ$$

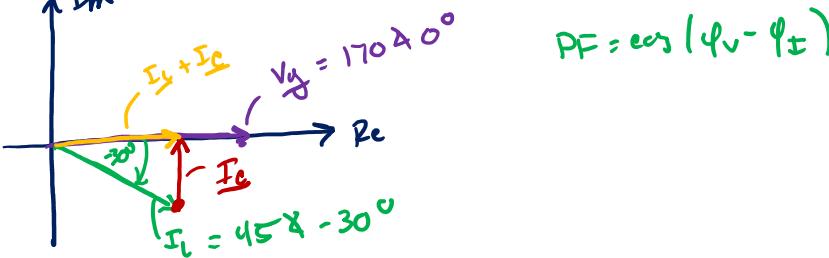Can we return grid PF to unity
PF = 1, Sg is all real



Can this be a passive impedance?


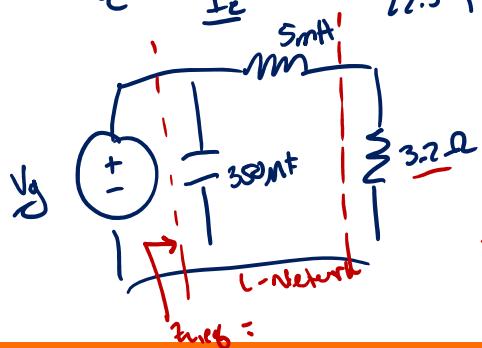
$$Z_C = \frac{V_g}{I_C} = \frac{170 \angle 0^\circ}{22.5 \angle +90^\circ} = 7.56 \angle -90^\circ = -j 7.56 \Omega = \frac{-j}{\omega C} \rightarrow C = 350 \mu F$$



$$S_g = i(V_g) (\underline{I_t} + \underline{I_C})^* = \underline{3.3 \text{ kW}} + j 0 \text{ VAR}$$

$$\underline{I_t} = 45 \cos(30^\circ) = 39 A$$
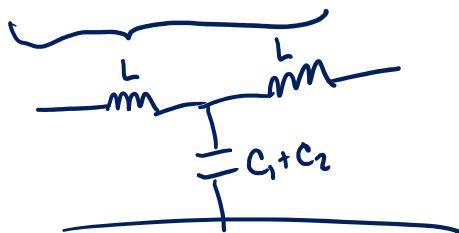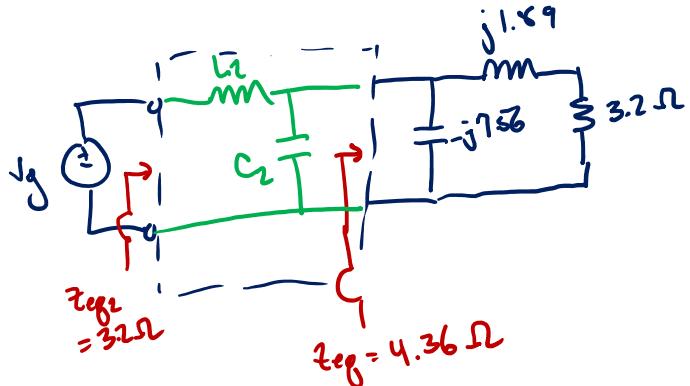
$$Z_{L, eq} = \frac{V_g}{I_t} = 4.36 \Omega > 3.2 \Omega$$



from L-Network Analysis:

$$3.2\Omega = \frac{X_{C2}^2 (4.3)}{(4.3)^2 + (X_{C2})^2}$$

$$\phi = \underline{X_{D2}} - \frac{X_{C2} (4.3)}{(4.3)^2 + (X_{C2})^2}$$

Cap: $X_{C2} = 7.4\Omega \rightarrow C_2 = 360\mu F$

Ind: $X_{L2} = 1.58\Omega \rightarrow L_2 = 5mH$

Simulation Example

