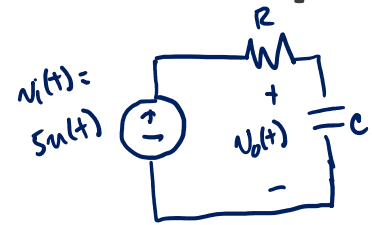


# Example Laplace Circuit Analysis



$v_o(t) @ t \leq 0$  is zero



$v_o(t) = (5 - 5e^{-\frac{t}{RC}})u(t)$





$$V_o(s) = V_i(s) \frac{Z_C}{Z_C + Z_R} = \frac{5}{s} \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{5}{s} \frac{\frac{1}{RC}}{\frac{1}{RC} + s}$$

$$v_o(t) = \mathcal{L}^{-1}\{V_o(s)\} = \mathcal{L}^{-1}\left\{\frac{A}{s} + \frac{B}{\frac{1}{RC} + s}\right\} = \mathcal{L}^{-1}\left\{\frac{5}{s} + \frac{-5}{\frac{1}{RC} + s}\right\}$$

PFE (more review coming)
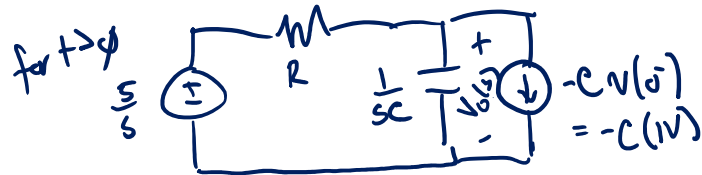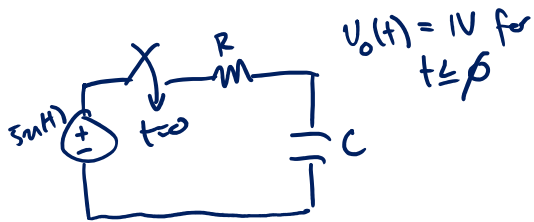
$$v(t) = \mathcal{L}^{-1}\left\{\frac{5}{s}\right\} + \mathcal{L}^{-1}\left\{\frac{-5}{\frac{1}{RC} + s}\right\} = \boxed{5u(t) - 5e^{-\frac{t}{RC}}u(t)}$$



$$V_o(s) = V_I(s) \frac{Z_C}{Z_C + Z_R} + C(1V) \left[ R \parallel \frac{1}{sC} \right]$$

# Inverse Transforms

# Transfer Functions

$$H(s) = \frac{\sum_{i=0}^M a_i s^i}{\sum_{i=0}^N b_i s^i} = \frac{(s - z_1)(s - z_2) \cdots (s - z_M)}{(s - p_1)(s - p_2) \cdots (s - p_N)}$$

# Partial Fraction Expansion / Decomposition $M < N$

$$\frac{\sum_{i=0}^M a_i s^i}{\sum_{i=0}^N b_i s^i} = \frac{(s - z_1)(s - z_2) \cdots (s - z_M)}{(s - p_1)(s - p_2) \cdots (s - p_M)} = \frac{k_1}{(s - p_1)} + \frac{k_2}{(s - p_2)} + \cdots + \frac{k_N}{(s - p_N)}$$

$$\frac{(s - z_1)(s - z_2) \cdots (s - z_M)}{(s - p_1)(s - p_2) \cdots (s - p_M)} = \frac{k_1}{(s - p_1)} + \frac{k_2}{(s - p_2)} + \cdots + \frac{k_N}{(s - p_N)}$$

# PFE: Repeated Roots



