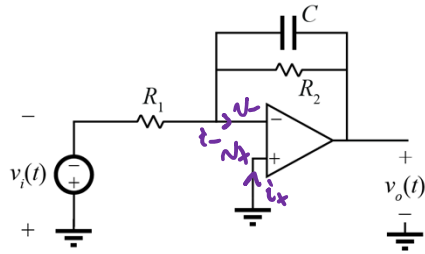


Example Problem



Ideal op-amp assumptions:

if there is negative feedback

(1) virtual short: $v_+ = v_- \rightarrow v_+(s) = v_-(s)$

(2) $i_+ = i_- = 0 \rightarrow I_+(s) = I_-(s) = 0$

Example Problem

