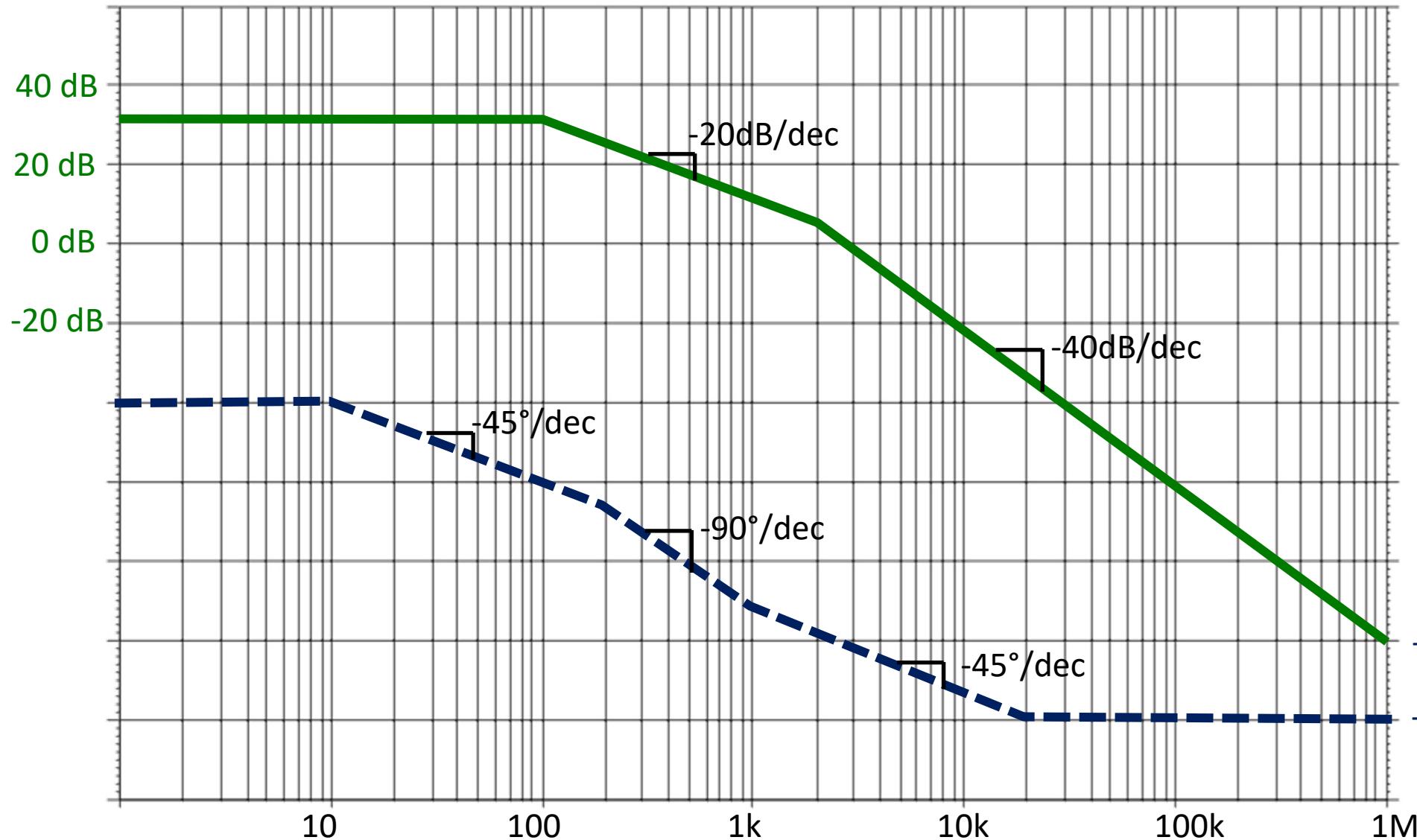


Example 1




$$H(s) = \frac{H_0}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

$$H_0 = 40$$

$$f_1 = 100\text{Hz}$$

$$f_2 = 2\text{kH}z$$

Example 2

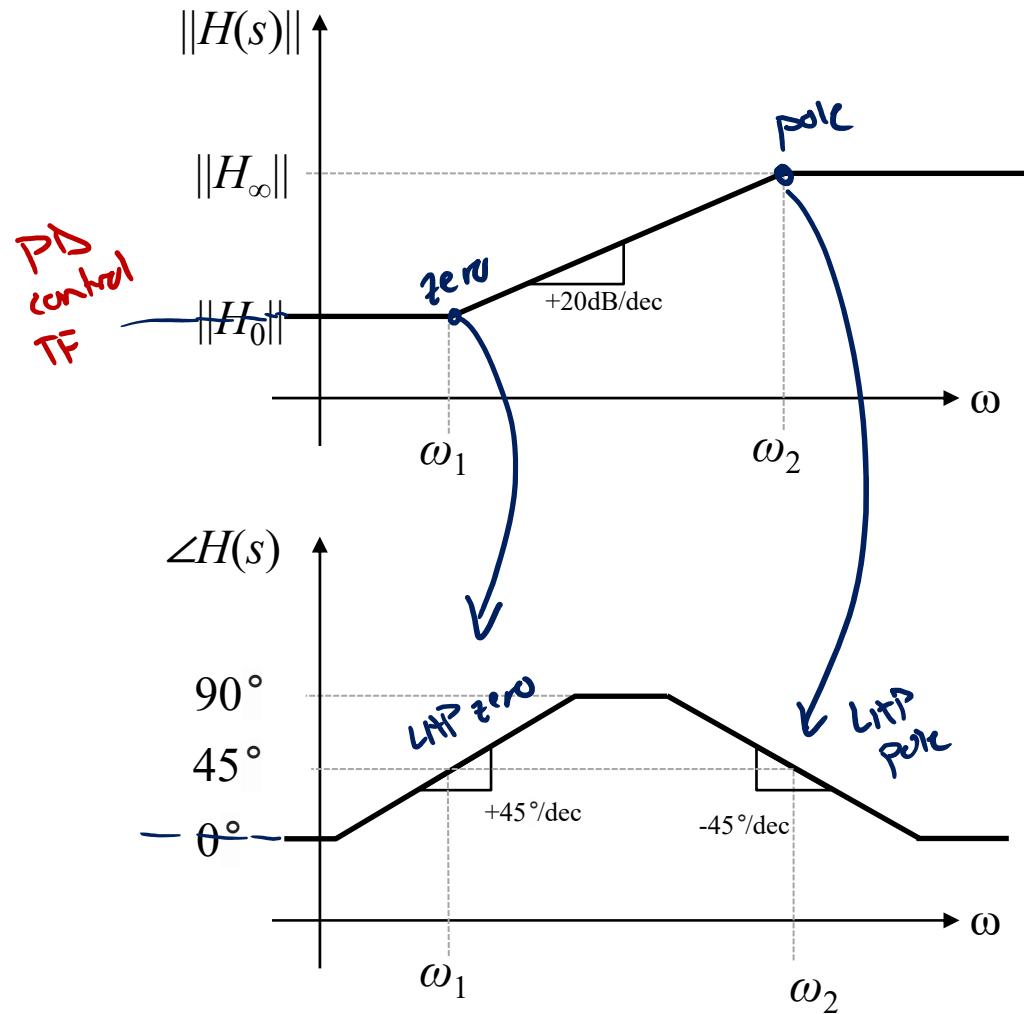

$$H(s) = H_0 \frac{(1 + \frac{s}{\omega_1})}{(1 + \frac{s}{\omega_2})}$$


what is H_∞ ?

High frequency gain as $s \rightarrow j\omega$, $\omega \rightarrow \infty$

$$\|H_\infty\| = \left| \lim_{\omega \rightarrow \infty} \frac{1 + \frac{j\omega}{\omega_1}}{1 + \frac{j\omega}{\omega_2}} \right|$$

$$\boxed{H_\infty = H_0 \frac{\omega_2}{\omega_1}}$$

Example 3

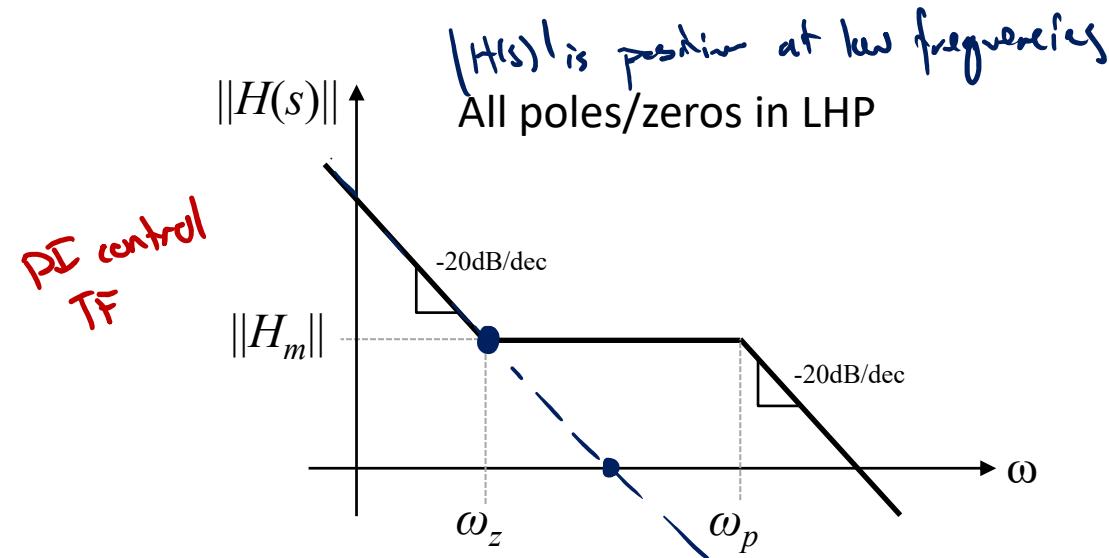


$$H(s) = H_m \omega_z \cdot \frac{1}{s} \cdot \frac{\left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_p}\right)}$$

$\text{at } \omega_z \quad \left| \frac{A}{s} \right| = |H_m|$

$$\left| \frac{A}{j\omega_z} \right| = |H_m| \rightarrow A = H_m \omega_z$$

Complex Poles

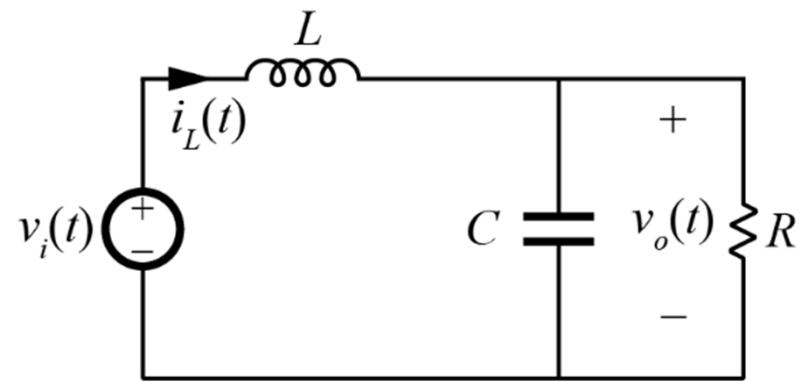

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sL + R + \frac{1}{sC}}}{\frac{1}{sL + R + \frac{1}{sC}}} = \frac{\frac{1}{1 + R_s C}}{sL + \frac{R}{1 + R_s C}}$$

$$H(s) = \frac{1}{s^2 LC + s \frac{R}{L} + 1}$$

Standard form for 2nd order polynomial

$$\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q\omega_0} + 1$$

find $\omega_0 \neq Q$ by matching coefficients

$$\frac{1}{\omega_0^2} = LC \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{1}{Q\omega_0} = \frac{L}{R} \rightarrow Q = \frac{R}{\sqrt{LC}} = \frac{R}{R_0}$$

Also define $R_0 = \sqrt{LC}$, "characteristic impedance"

Standard Form for Complex Poles

$$H(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q\omega_0} + 1}$$

$$H(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + 2\zeta \frac{s}{\omega_0} + 1}$$

- ω_0 , Q , and ζ are real for real circuits
 - Found by coefficient matching to solved transfer function
- ω_0 is the angular/resonant frequency
 - Q is the “quality factor”
 - Roots are complex when $Q > \frac{1}{2}$
 - If $Q < \frac{1}{2}$, the polynomial can be factored into two real poles
 - ζ is the “damping factor”
 - Roots are complex when $\zeta > 1$
 - If $\zeta > 1$, the polynomial can be factored into two real poles

$$\zeta = \frac{1}{2Q}, \quad Q = \frac{1}{2\zeta}$$


Magnitude Asymptotes

When $Q > \frac{1}{2}$

$$H(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q\omega_0} + 1}$$


$$\|H(j\omega)\| = \sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}$$

$$\|H(j\omega)\|_{dB} \approx \begin{cases} 0 dB & , \omega \ll \omega_0 \\ 20 \log(Q) & , \omega = \omega_0 \\ 40 \log(\omega_0) - 40 \log(\omega) & , \omega \gg \omega_0 \end{cases}$$
$$|H(j\omega)| = \frac{1}{(\omega/\omega_0)^2}$$

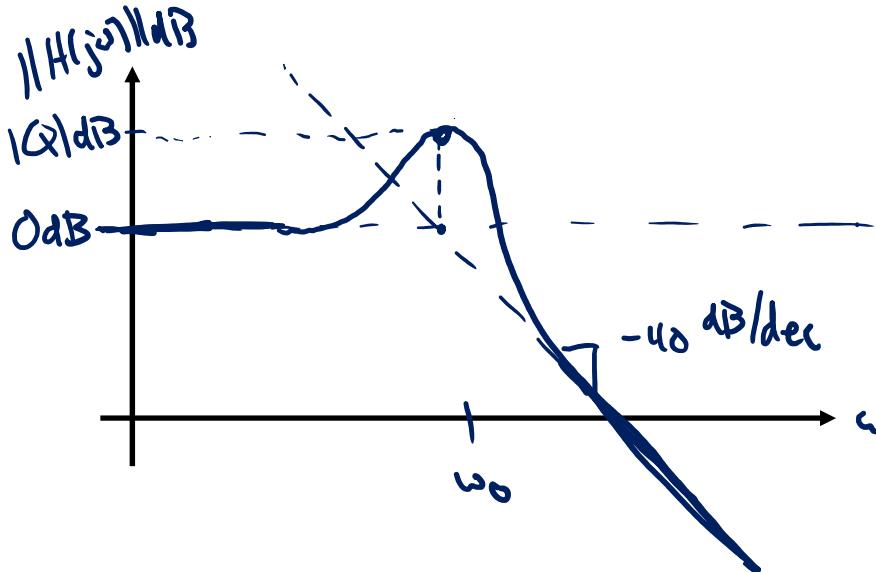


Asymptotes for Complex Poles, $Q>0.5$


Magnitude

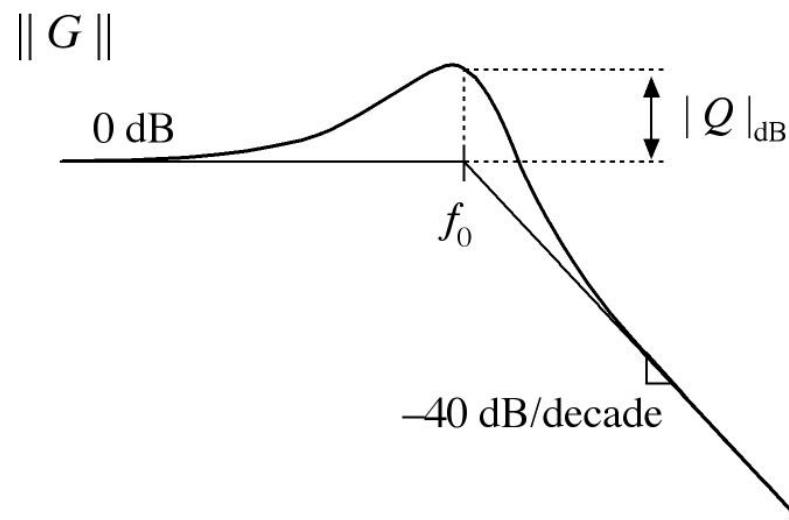

Phase

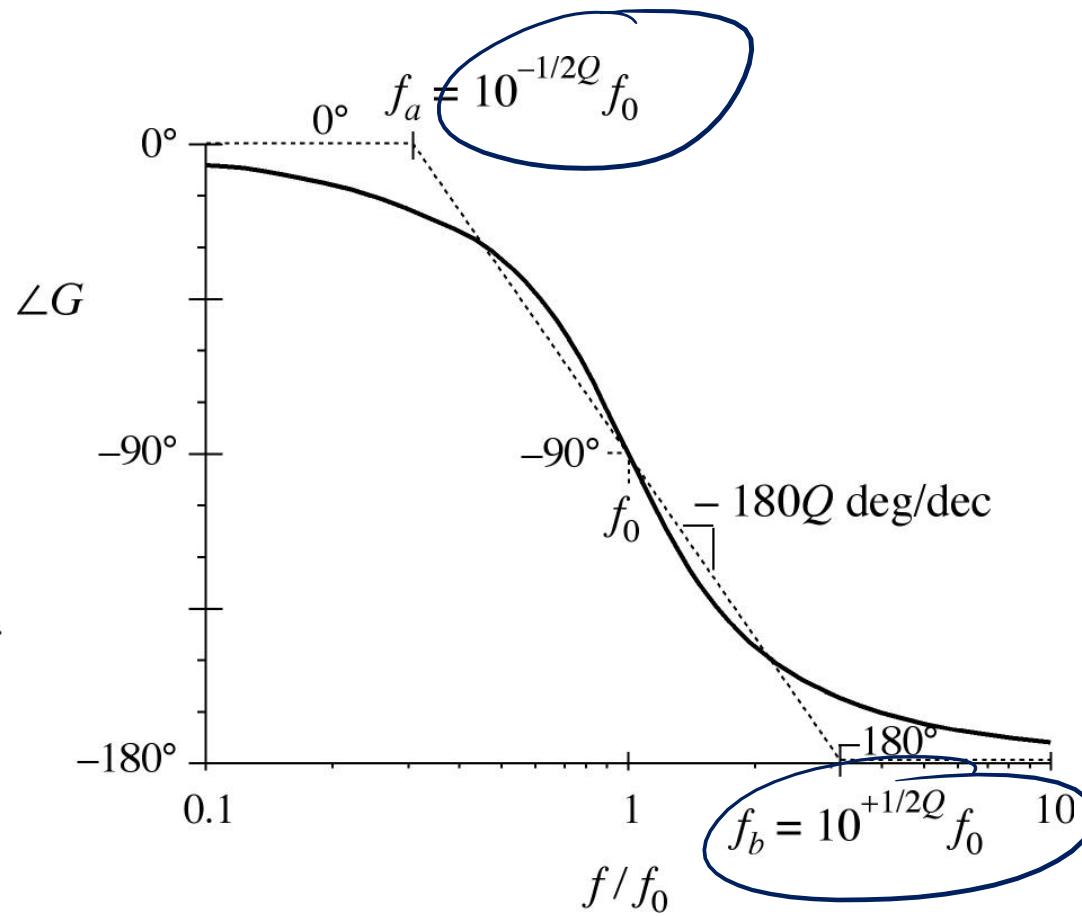


Curves for Varying Q

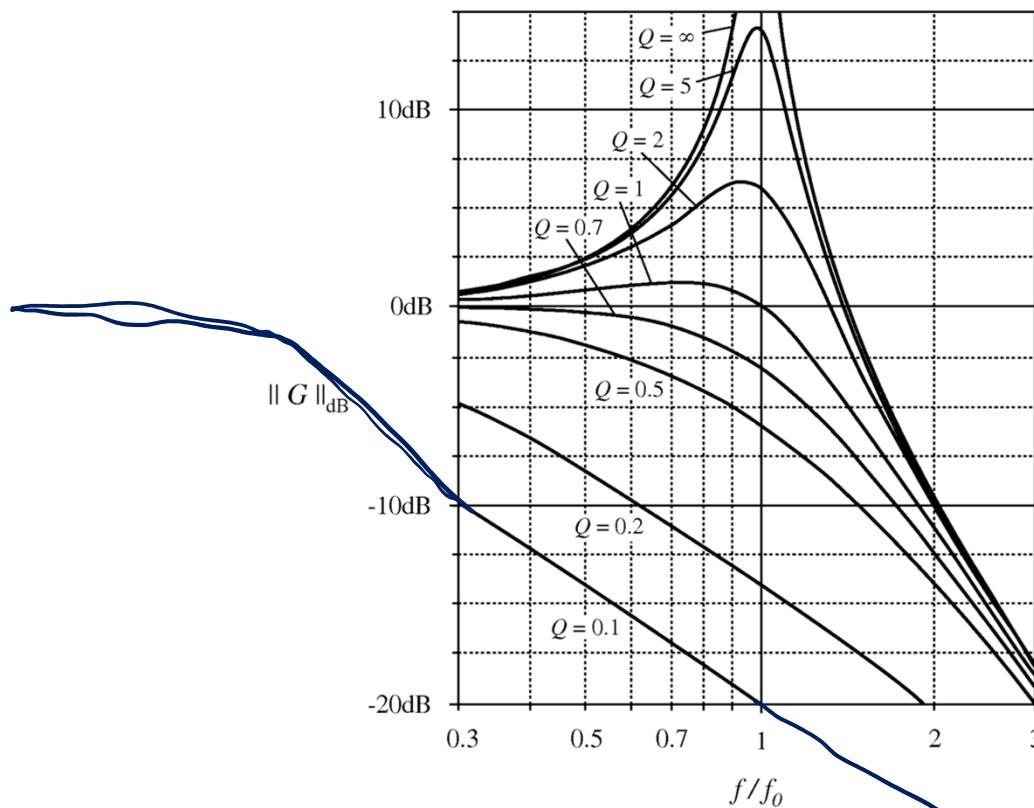

Fundamentals of Power Electronics

44

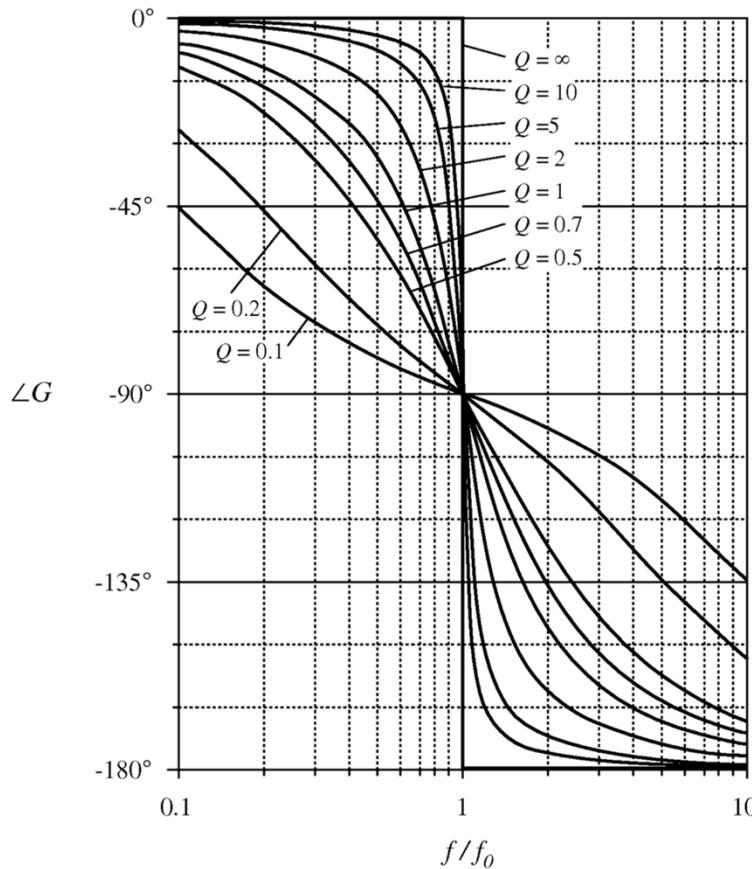


Chapter 8: Converter Transfer Functions

Example

A	w_{z1}	w_{z2}	ω_0	Q	ω_p
1000	100	10k	1k	10	100k

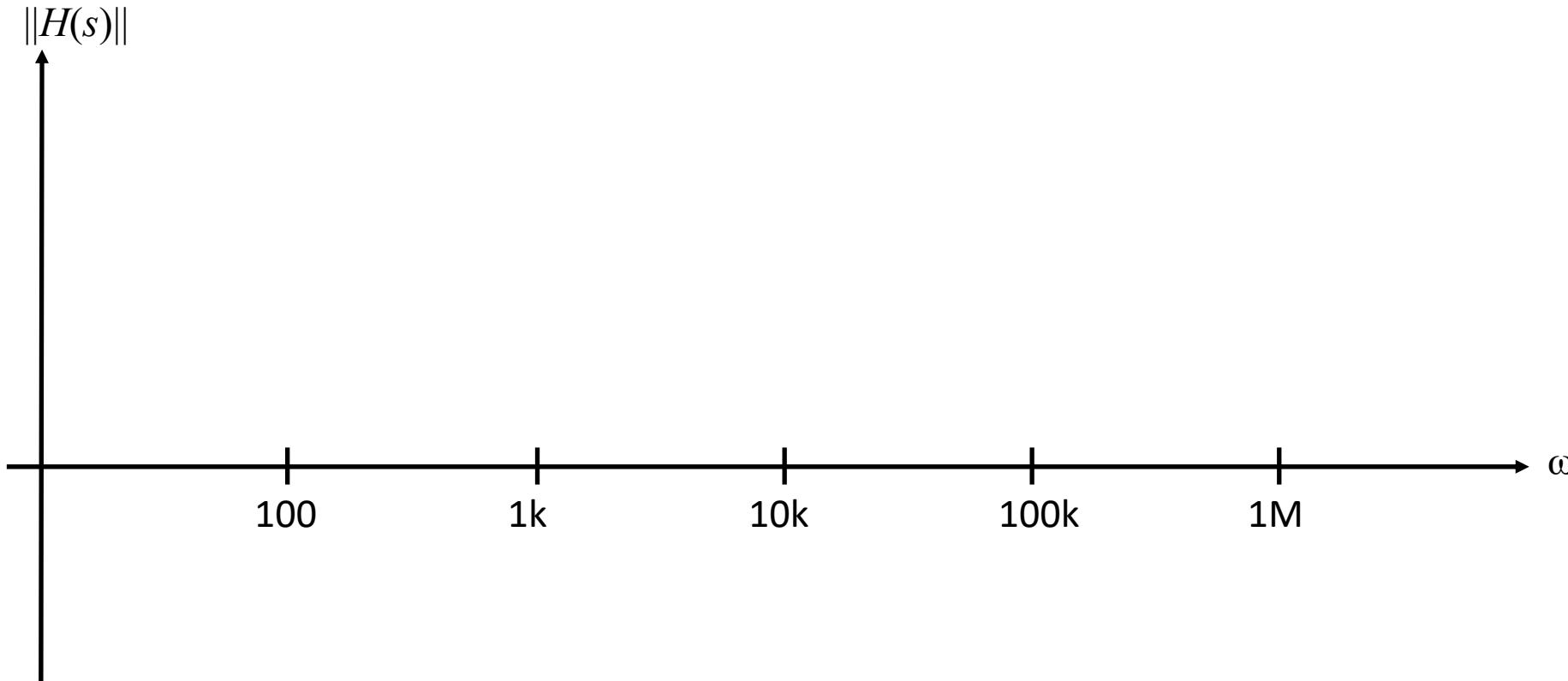
$$H(s) = \frac{A}{s} \frac{\left(1 + \frac{s}{w_{z1}}\right)\left(1 + \frac{s}{w_{z2}}\right)}{\left(\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q\omega_0} + 1\right)\left(1 + \frac{s}{\omega_p}\right)}$$



Example

A	w_{z1}	w_{z2}	ω_0	Q	ω_p
1000	100	10k	1k	10	100k
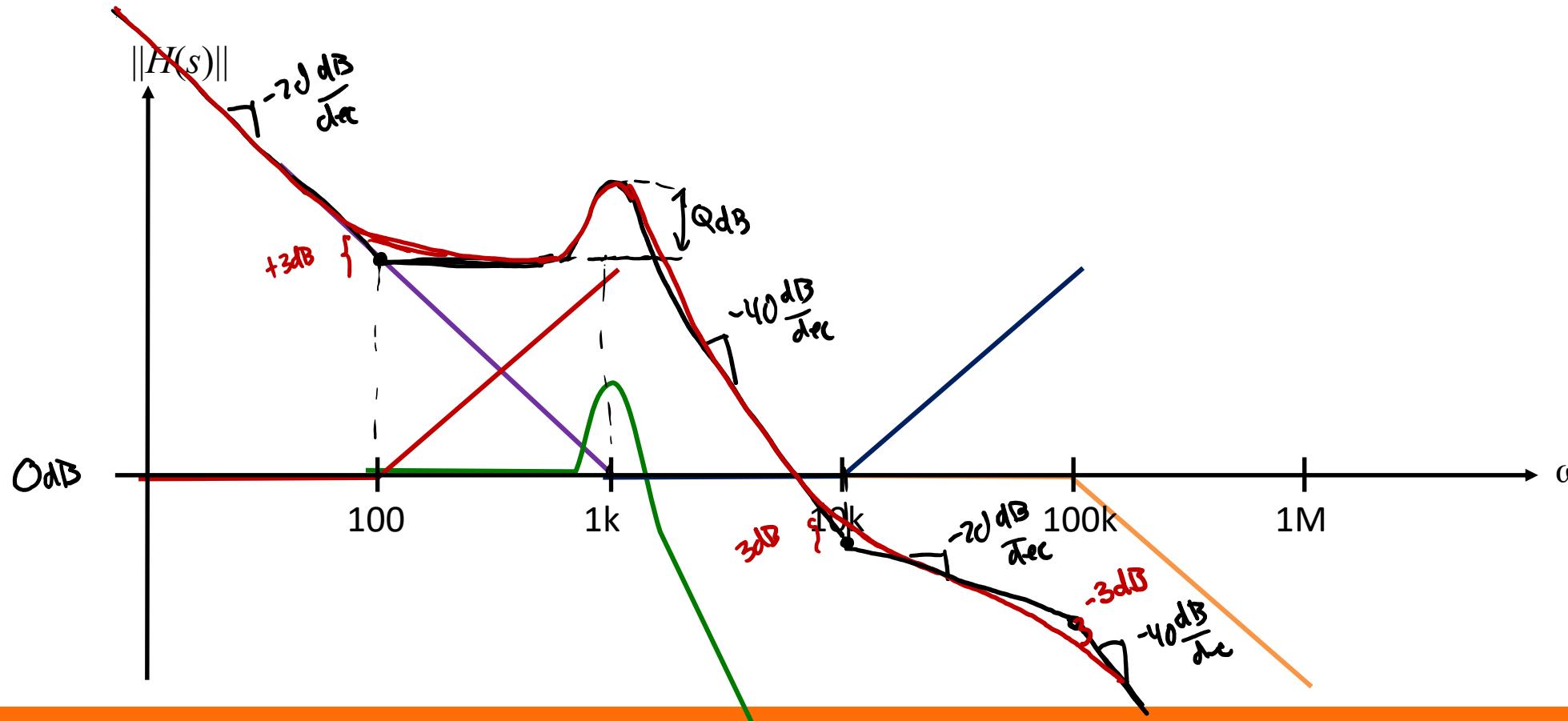
$$H(s) = \frac{A}{s} \frac{\left(1 + \frac{s}{w_{z1}}\right)\left(1 + \frac{s}{w_{z2}}\right)}{\left(\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q\omega_0} + 1\right)\left(1 + \frac{s}{\omega_p}\right)}$$



MATLAB

```
A = 1000;  
wz1 = 100;  
wz2 = 10e3;  
w0 = 1e3;  
Q = 10;  
wp = 100e3;  
  
s = tf('s');  
  
H = A*(1+s/wz1)*(1+s/wz2)/...  
      (s*(1+s/wp)*((s/w0)^2+s/Q/w0+1));  
  
bode(H)
```

