

Announcements

- Return Analog Discovery Studio
- Office Hours
 - No (Dr. Costinett) Wednesday office hours due to EECS faculty meeting
 - Available via e-mail; Thursday *office hours as normal*
- TNvoice Open
 - Please fill out – Closes midnight May 8
 - +5 pts EC on final for 100% response rate

Final Exam

- Thursday May 9th, 3:30-6:00pm
- Roughly 2x midterm in length, w/ 3x time
- Covers all course material
 - Chapters 10-11, 13-15 & 17(partial)
 - All homeworks, quizzes, exams, and experiments 1-3
 - All lectures

Final Exam Problems (Tentative)

- Power and impedance matching with sinusoidal input
- Bode plot (plot $\rightarrow H(s)$ and/or $H(s) \rightarrow$ plot)
- Identify bounded/stable systems
- Solve Laplace with complex and repeated poles and zeroes
- Evaluate Fourier Series and frequency response
- Solve and compare different descriptions of circuit (e.g. $H(s)$, $h(t)$, Phasor circuit, etc.)

- Additional Notes:
 - Circuits will contain
 - coupled inductors and/or transformers
 - op-amps







Exam Tables

TABLE 14.1 Laplace Transform Pairs



$f(t) = \mathcal{L}^{-1}\{F(s)\}$	$F(s) = \mathcal{L}\{f(t)\}$	$f(t) = \mathcal{L}^{-1}\{F(s)\}$	$F(s) = \mathcal{L}\{f(t)\}$
$\delta(t)$	1	$\frac{1}{\beta - \alpha}(e^{-\alpha t} - e^{-\beta t})u(t)$	$\frac{1}{(s + \alpha)(s + \beta)}$
$u(t)$	$\frac{1}{s}$	$\sin \omega t u(t)$	$\frac{\omega}{s^2 + \omega^2}$
$tu(t)$	$\frac{1}{s^2}$	$\cos \omega t u(t)$	$\frac{s}{s^2 + \omega^2}$
$\frac{t^{n-1}}{(n-1)!}u(t), n = 1, 2, \dots$	$\frac{1}{s^n}$	$\sin(\omega t + \theta)u(t)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
$e^{-\alpha t}u(t)$	$\frac{1}{s + \alpha}$	$\cos(\omega t + \theta)u(t)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$
$te^{-\alpha t}u(t)$	$\frac{1}{(s + \alpha)^2}$	$e^{-\alpha t} \sin \omega t u(t)$	$\frac{\omega}{(s + \alpha)^2 + \omega^2}$
$\frac{t^{n-1}}{(n-1)!}e^{-\alpha t}u(t), n = 1, 2, \dots$	$\frac{1}{(s + \alpha)^n}$	$e^{-\alpha t} \cos \omega t u(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega^2}$


$$2|k|e^{\sigma t} \cos(\omega t - \angle k) u(t) \quad \frac{k}{s - (\sigma + j\omega)} + \frac{k^*}{s - (\sigma - j\omega)}$$

Operation	$f(t)$	$F(s)$
Addition	$f_1(t) \pm f_2(t)$	$F_1(s) \pm F_2(s)$
Scalar multiplication	$kf(t)$	$kF(s)$
Time differentiation	$\frac{df}{dt}$	$sF(s) - f(0^-)$
	$\frac{d^2f}{dt^2}$	$s^2F(s) - sf(0^-) - f'(0^-)$
	$\frac{d^3f}{dt^3}$	$s^3F(s) - s^2f(0^-) - sf'(0^-) - f''(0^-)$
Time integration	$\int_0^t f(t) dt$	$\frac{1}{s}F(s)$
	$\int_{-\infty}^t f(t) dt$	$\frac{1}{s}F(s) + \frac{1}{s} \int_{-\infty}^0 f(t) dt$
Convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$
Time shift	$f(t - a)u(t - a), a \geq 0$	$e^{-as}F(s)$
Frequency shift	$f(t)e^{-at}$	$F(s + a)$
Frequency differentiation	$tf(t)$	$-\frac{dF(s)}{ds}$
Frequency integration	$\frac{f(t)}{t}$	$\int_s^\infty F(s) ds$
Scaling	$f(at), a \geq 0$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
Initial value	$f(0^+)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$, all poles of $sF(s)$ in LHP
Time periodicity	$f(t) = f(t + nT), n = 1, 2, \dots$	$\frac{1}{1 - e^{-Ts}}F_1(s)$, where $F_1(s) = \int_0^T f(t)e^{-st} dt$

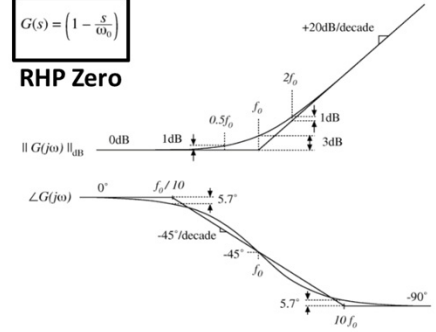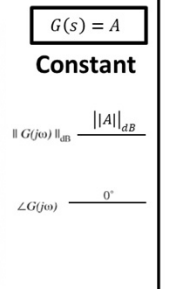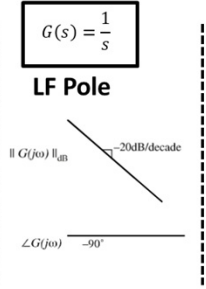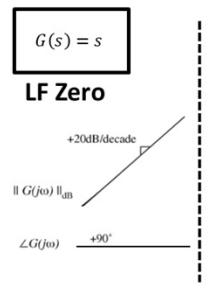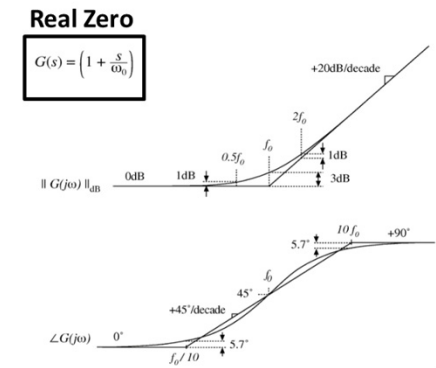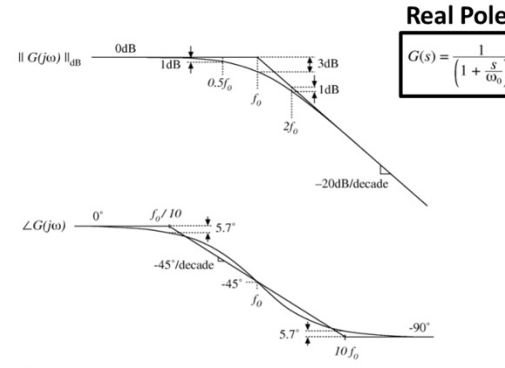

Complex Poles

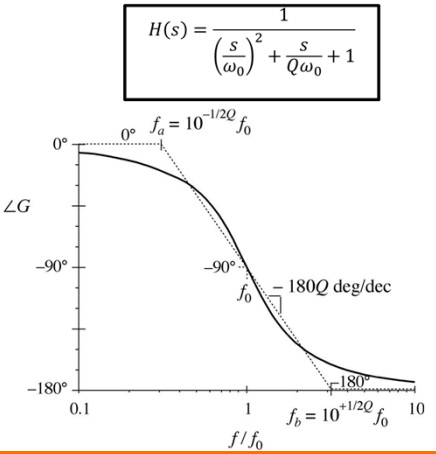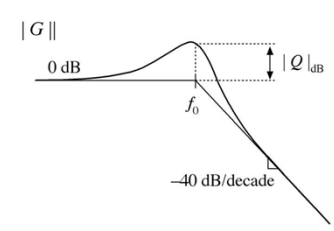

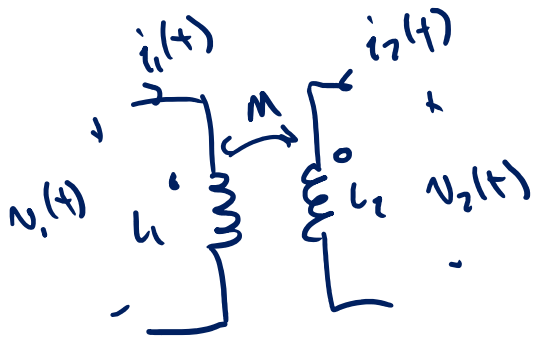

$$\begin{cases} v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{cases}$$


Time

$$\begin{cases} \underline{v}_1 = L_1(j\omega) \underline{I}_1 + M(j\omega) \underline{I}_2 \\ \underline{v}_2 = L_2(j\omega) \underline{I}_2 + M(j\omega) \underline{I}_1 \end{cases}$$

Phasor

Laplace:
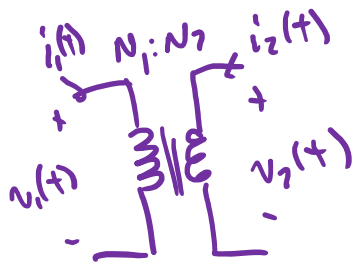
$$\begin{cases} v_1 = L_1(sI_1 - i_1(0^-)) + M(sI_2 - i_2(0^-)) \\ v_2 = L_2(sI_2 - i_2(0^-)) + M(sI_1 - i_1(0^-)) \end{cases}$$



$$\frac{v_1(t)}{N_1} = \frac{v_2(t)}{N_2}$$

$$N_1 i_1(t) + N_2 i_2(t) = \phi$$

Time

Phasor

$$\frac{v_1}{N_1} = \frac{v_2}{N_2} \quad \& \quad N_1 \underline{I}_1 + N_2 \underline{I}_2 = \phi$$

Laplace

$$\frac{v_1(s)}{N_1} = \frac{v_2(s)}{N_2} \quad \& \quad N_1 I_1(s) + N_2 I_2(s) = \phi$$


$$F(s) = \frac{7s^2 + 3s + 1}{s^2 + 2s + 5}$$

$m = N$, order of numerator = order of denominator

$$\begin{array}{r} s^2 + 2s + 5 \overline{) 7s^2 + 3s + 1} \\ \underline{-7s^2 - 14s - 35} \\ 0 - 11s - 34 \end{array}$$

$$F(s) = 7 + \frac{-11s - 34}{s^2 + 2s + 5}$$

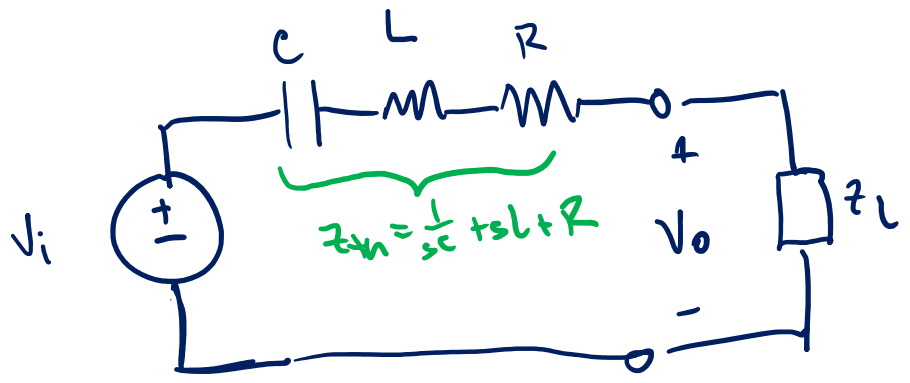Find z_L that maximizes P_{out} (Real power to z_L)



For max power transfer

$$z_L = z_{th}^*$$


$$z_{th} = R + j(\omega L - \frac{1}{\omega C})$$

$$z_L = z_{th}^* = R - j(\omega L - \frac{1}{\omega C})$$

$$Y_L = \frac{1}{z_L} = \frac{R + j(\omega L - \frac{1}{\omega C})}{R^2 + (\omega L - \frac{1}{\omega C})^2} = G + jB$$


if $\omega L > \omega C$
 $z_L = R - jX$

$X > \phi$
 $\frac{-j}{\omega C} = -jX$

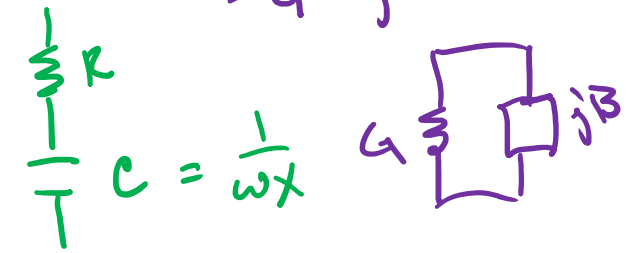

if $\omega L < \omega C$
 $z_L = R + jX$

$X > \phi$
 $j\omega L = jX$

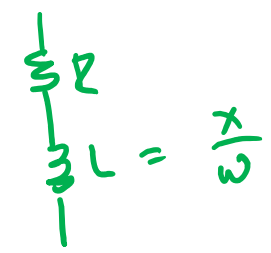


COURSE REVIEW

Course Content


- Magnetically Coupled Circuits (Ch 13)
- Sinusoidal Steady-State Analysis (Ch 10)
- AC Circuit Power Analysis (Ch 11)
- Circuit An Analysis in the s-Domain (Ch 14)
- Frequency Response (Ch 15)
- Fourier Circuit Analysis (Ch 17)
- Polyphase Circuits (Ch 12)
- Two-Port Networks (Ch 16)

Transform Domains

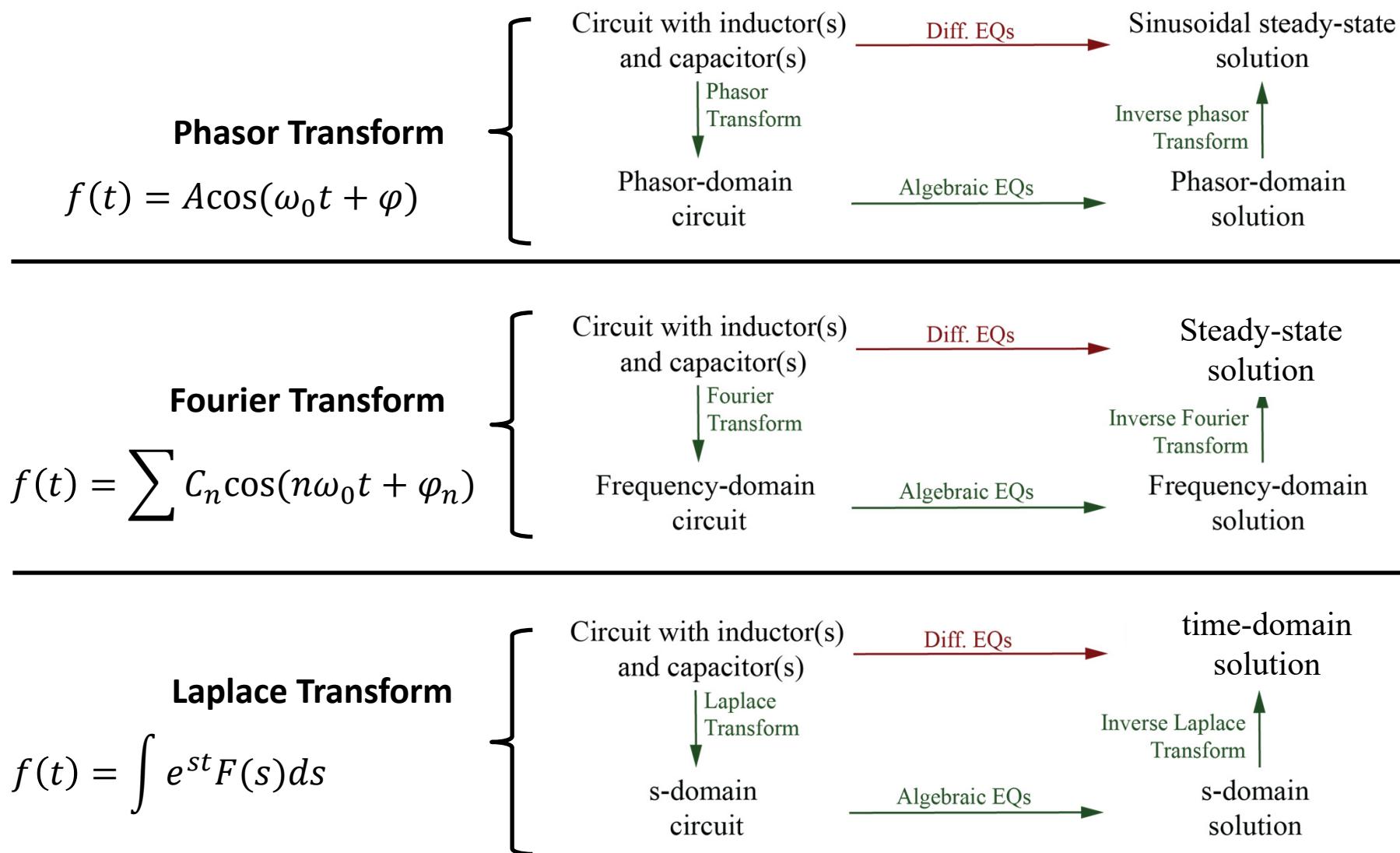

Ch 13 – Magnetically Coupled Circuits

Coupled Inductors

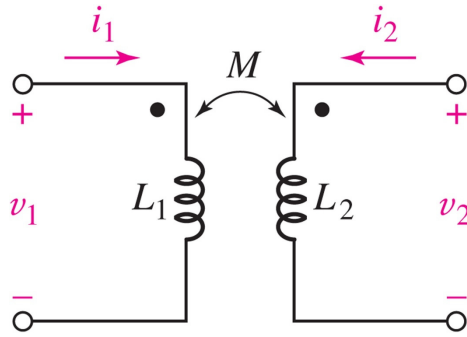

Defining Equations

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

Dot convention

- Current into the dot on one terminal produces a positive open circuit voltage w.r.t. the dot on the other


Coupling Coefficient

$$k = \frac{M}{\sqrt{L_p L_s}}$$

Recall

- Equivalent circuits

Ideal Transformer

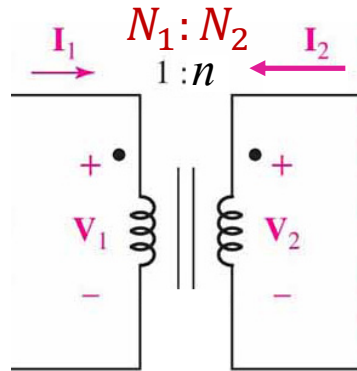

Defining Equations

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} = \dots$$

$$0 = N_1 I_1 + N_2 I_2 + \dots$$

Coupled inductors with:


- no energy storage ($L \rightarrow \infty$)
- Perfect coupling ($k=1$)

Recall


- Z/V/I reflection

Ch 10 – Sinusoidal Steady State


Time Domain

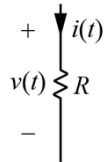


$$v(t) = i(t)R$$

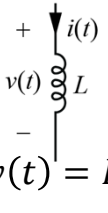

$$v(t) = L \frac{di}{dt}$$

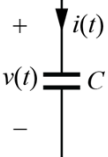


$$i(t) = C \frac{dv}{dt}$$

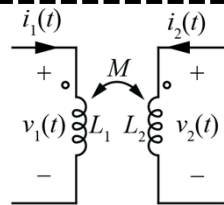


$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$


Phasor Domain

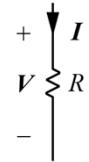


$$V = IR$$

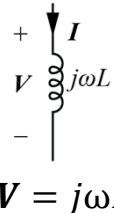

$$V = j\omega LI$$

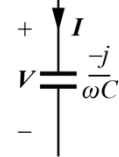

$$V = \frac{-j}{\omega C} I$$

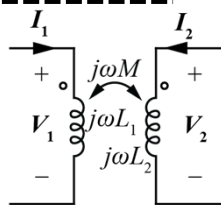

$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

Phasor Notation

$$A \cos(\omega t + \varphi) \Leftrightarrow A \angle \varphi$$

$$= \text{Re}\{A e^{j(\omega t + \varphi)}\}$$

$$= \text{Re}\{A \cos(\omega t + \varphi) + j A \sin(\omega t + \varphi)\}$$

Impedance and Admittance

$$Z = R + jX$$

Impedance

Resistance

Reactance

$$Y = \frac{1}{Z} = G + jB$$

Admittance

Conductance

Susceptance

Circuit Analysis

- Real circuits always have all real signals in the time domain
- All 201 analysis techniques apply
- Gives only forced/steady-state/particular response, for single sinusoidal source
- Phasor superposition

Ch 11 – AC Power Analysis

Average (DC) Power: $P = \int_{-\infty}^{\infty} p(t)dt$ For periodic signals: $P = \int_{t_0}^{t_0+T} p(t)dt$

Average power in a resistor: $P_R = \left[\underbrace{\int i(t)^2 dt}_{I_{rms} = I_{eff}} \right]^2 R$ For sinusoids: $I_{rms} = \frac{I_A}{\sqrt{2}}$


Sinusoidal Power

$$p(t) = [V_A \cos(\omega t + \varphi_V)][I_A \cos(\omega t + \varphi_I)]$$

$$= \underbrace{\frac{V_A I_A}{2} \cos(2\omega t + \varphi_V + \varphi_I)}_{\text{Double-frequency}} + \underbrace{\frac{V_A I_A}{2} \cos(\varphi_V - \varphi_I)}_{\text{DC = average}} \qquad \frac{V_A I_A}{2} = V_{rms} I_{rms}$$

Complex Power

$$S = \frac{VI^*}{2} = V_{rms} I_{rms}$$

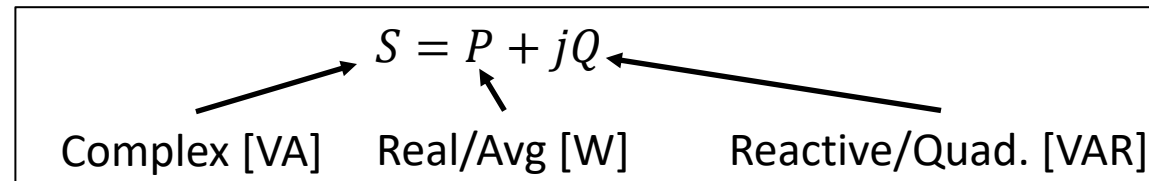

Apparent Power: $|S| = \frac{V_A I_A}{2} = V_{rms} I_{rms}$ Power Factor: $PF = \frac{P}{|S|}$ (leading/lagging)

Impedance match for max power transfer: $Z_L = Z_{th}^*$

Ch 14 – Laplace Transform

Unilateral Laplace Transform: $F(s) = \mathcal{L}\{f(t)\} = \int_{0^-}^{\infty} e^{-st} f(t) dt$

Inverse Laplace Transform: $f(t) = \mathcal{L}^{-1}\{F(s)\} = \frac{1}{2\pi j}$



, σ_0 in ROC
(to the right of all
poles in complex
plane)

Complex frequency = Laplace variable = $s = \sigma + j\omega$

Laplace transform is a **linear transformation**. Other properties and transforms in tables

Inverse Transforms: *Long Division* → *Factor* → *PFE* → *Tables*

PFE Special cases:

Repeated: $\frac{N(s)}{(s+5)^2} = \frac{k_1}{s+5} + \frac{k_2}{(s+5)^2}$ (Differentiation or coefficient matching)

Complex: $\frac{N(s)}{s^2+4} = \frac{k_1s+k_2}{s^2+4} = \frac{k_1}{s-j2} + \frac{k_1^*}{s+j2}$

Other properties from tables including delay and time periodicity

Ch 14 – Laplace Circuit Analysis



Poles and Zeros:

$$F(s) = \frac{N(s)}{D(s)}$$


Zeros: roots of $N(s)$

Poles: roots of $D(s)$

Circuit Transformation:

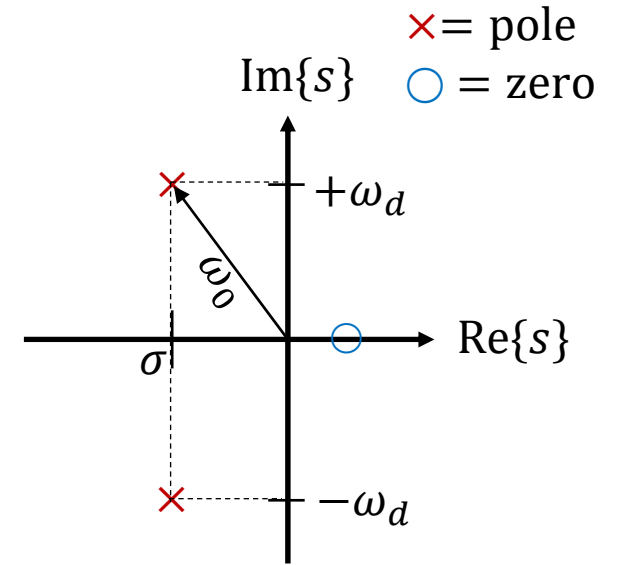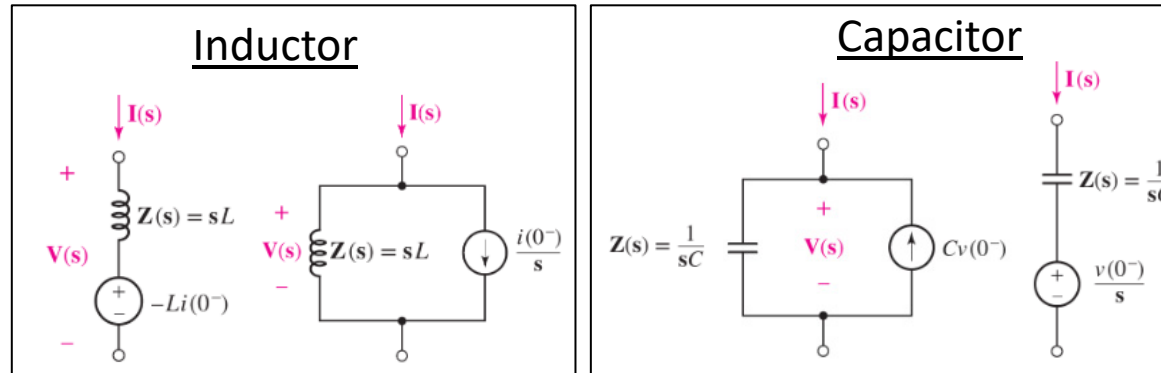

Convolution:

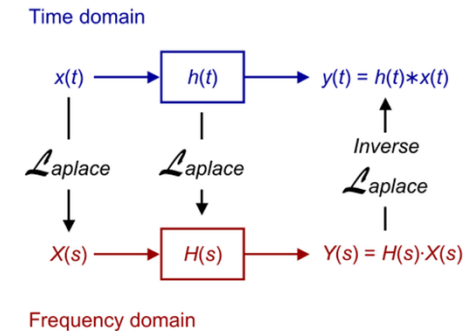

$$v_o(t) = v_i(t) * h(t) = \int_{-\infty}^{\infty} v_i(t - \tau)h(\tau)d\tau$$

Transfer Functions:


$$H(s) = \frac{V_o(s)}{V_i(s)}$$

Poles of $H(s)$ define “form” of terms in natural response of the circuit

Poles of $V_i(s)$ define “form” of terms in forced response of the circuit

$$V_o(s) = V_i(s)H(s) = \left(\frac{\sum_{i=0}^{M_I} c_i s^i}{\sum_{i=0}^{N_I} d_i s^i} \right) \left(\frac{\sum_{i=0}^{M_H} a_i s^i}{\sum_{i=0}^{N_H} b_i s^i} \right) = \frac{(s - z_1)(s - z_2) \cdots (s - z_{M_H+M_I})}{(s - p_1)(s - p_2) \cdots (s - p_{N_H+N_I})} = \frac{k_1}{(s - p_1)} + \frac{k_2}{(s - p_2)} + \cdots + \frac{k_x}{(s - p_x)}$$

Ch 15 – Frequency Response

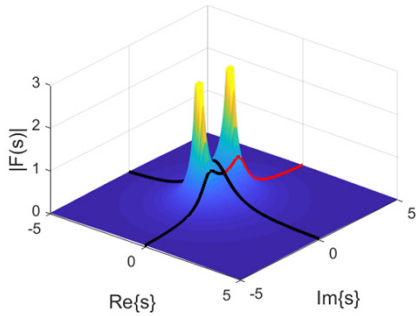




Frequency Response: $H(s \rightarrow j\omega)$

- Circuit response to sinusoidal inputs
- Valid if all poles in LHP

Bode plot: mag-phase plots on log-log axes

- $\|H(j\omega)\|_{dB} = 20 \log(|H(j\omega)|)$
- $\neq H(j\omega)$

Templates and Approximations:

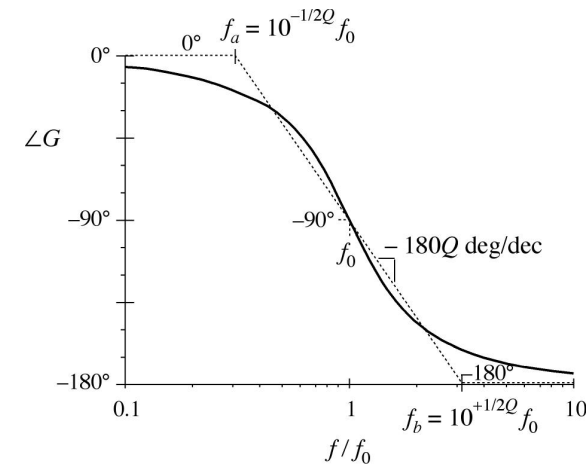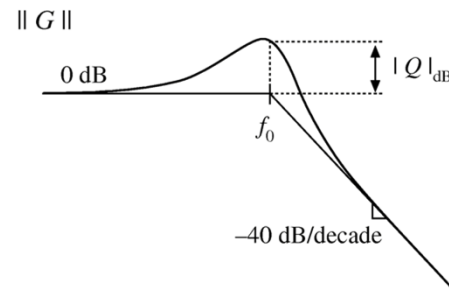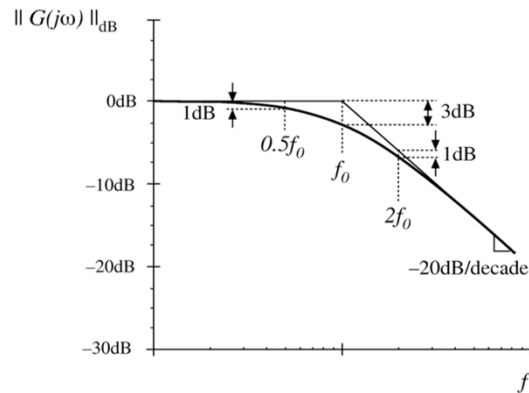

Filter Design

- Graphical analysis, Chebyshev and Butterworth, Sallen-Key Amplifier
- Resonant circuits

Ch 17 – Fourier Series and Transform



https://en.wikipedia.org/wiki/Fourier_transform

Fourier Series:

For periodic $f(t)$ with period $T_0 = \frac{2\pi}{\omega_0}$

$$f(t) = a_0 + \sum_{k=1}^{\infty} a_k \cos(k\omega_0 t) + b_k \sin(k\omega_0 t)$$

$$a_k = \frac{2}{T_0} \int_{t_0}^{t_0+T_0} f(t) \cos(k\omega_0 t) dt$$

$$b_k = \frac{2}{T_0} \int_{t_0}^{t_0+T_0} f(t) \sin(k\omega_0 t) dt$$

Fourier Transform:

For periodic or non-periodic $f(t)$

$$F(\omega) = \mathcal{F}\{f(t)\} = \int_{-\infty}^{\infty} e^{-j\omega t} f(t) dt$$


$$f(t) = \mathcal{F}^{-1}\{F(\omega)\} = \frac{1}{2\pi} \int_{-\infty}^{\infty} e^{j\omega t} F(\omega) d\omega$$

- Frequency content of a signal
- Gives mag/phase of sinusoids that add up to original signal
- Symmetry can speed up calculations

FUTURE TOPICS

Nonlinear Circuits

- ECE 335 & 336 – Electronic Devices

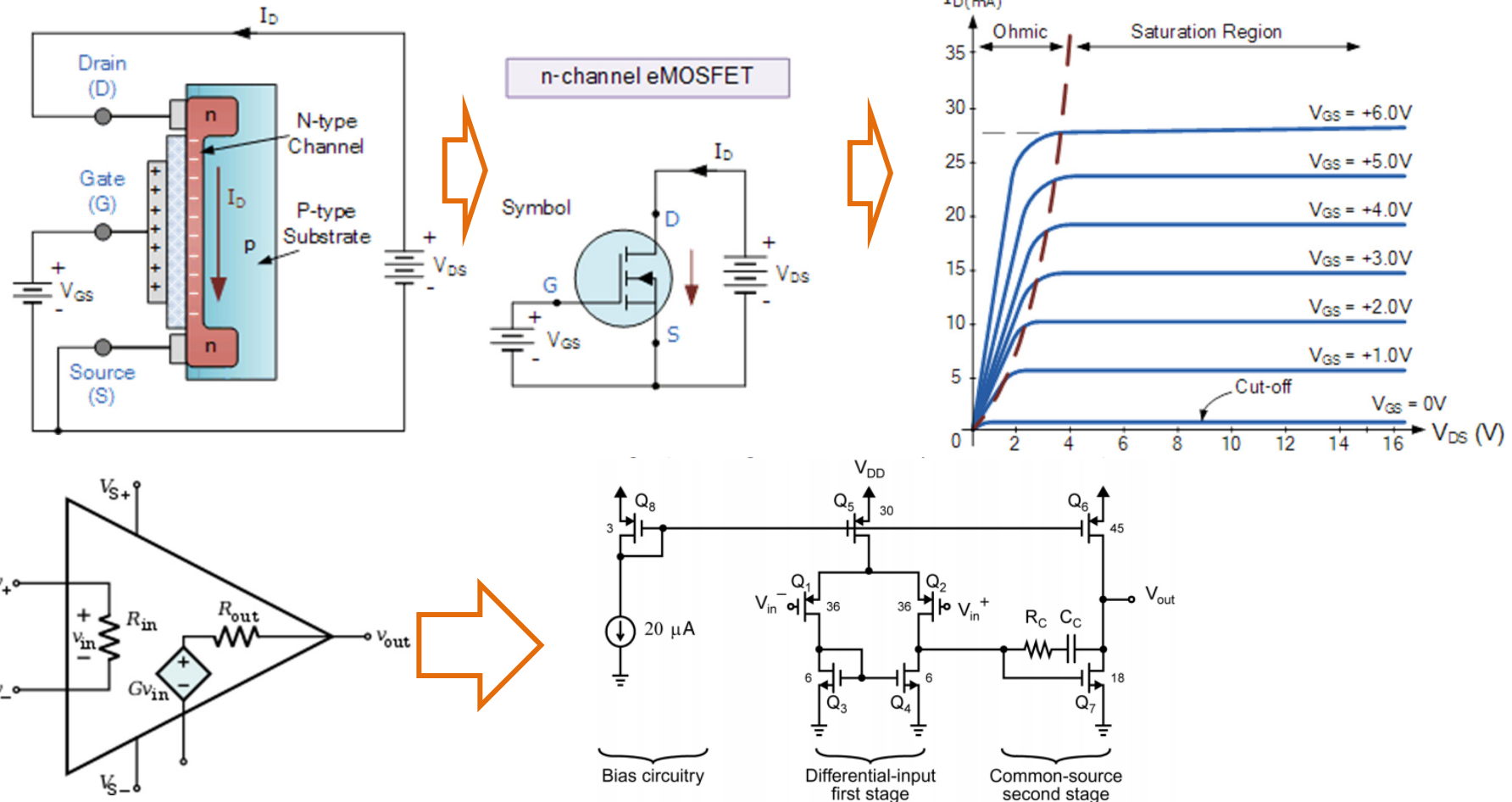

Digital / Discrete Time Signals



- ECE 315 – Signals and Systems

Cont. time $\sum_n A_n \frac{d^n}{dt^n} v_o(t) = \sum_m B_m \frac{d^m}{dt^m} v_i(t) \xrightarrow{\mathcal{L}} \sum_n A_n s^n V_o(s) = \sum_m B_m s^m V_i(s)$

Discrete time $\sum_n A_n y[k - n] = \sum_m B_m u[k - m] \xrightarrow{\mathcal{Z}} \sum_n A_n z^{-n} Y(z) = \sum_m B_m z^{-m} U(z)$




Sampling and aliasing:

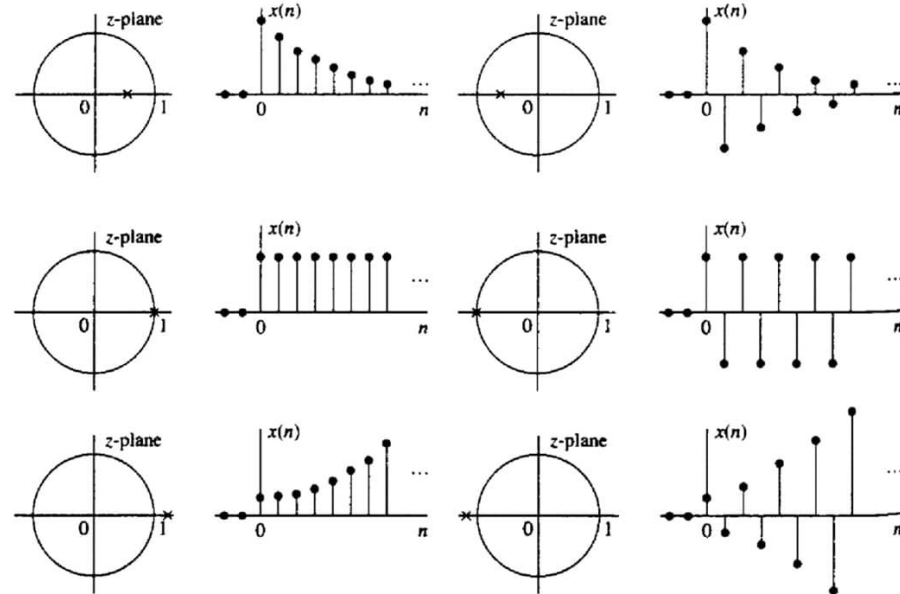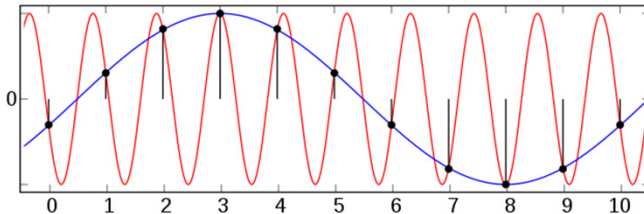


Closed-Loop Control

- ECE 316 – Signals and Systems


Classic Control

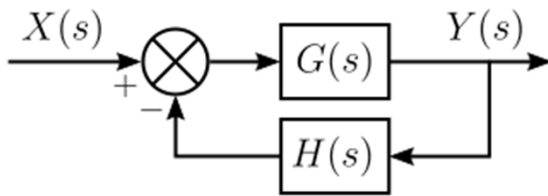

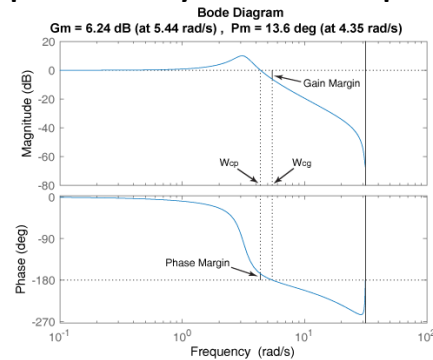
Margin Test: Examine closed-loop stability on bode plot



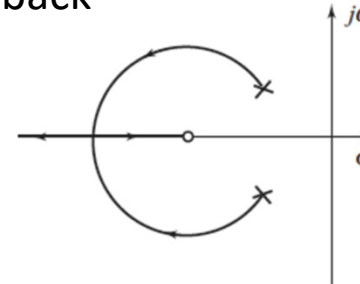Root Locus: How poles and zeros move as you change feedback



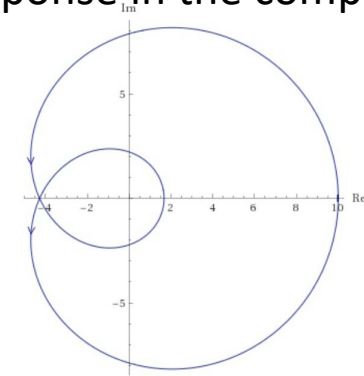Nyquist Plots: Frequency response in the complex plane




Modern Control

$$\dot{\mathbf{x}}(t) = \mathbf{A}(t)\mathbf{x}(t) + \mathbf{B}(t)\mathbf{u}(t)$$
$$\mathbf{y}(t) = \mathbf{C}(t)\mathbf{x}(t) + \mathbf{D}(t)\mathbf{u}(t)$$

$$H(s) = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{D}$$


Power Systems

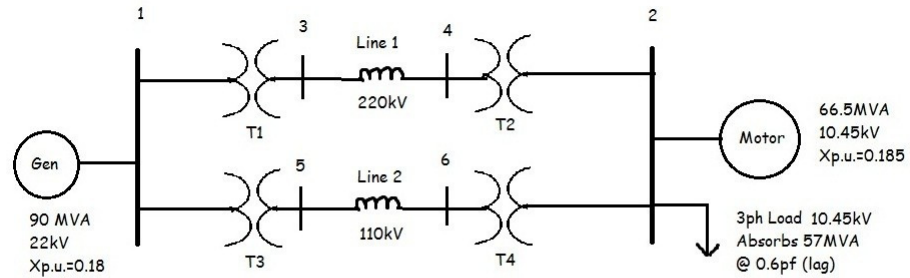- ECE 325 -- Electric Energy System Components



T1: 50MVA 22/220kV $X_{p.u.}=0.10$
 T2: 40MVA 220/11kV $X_{p.u.}=0.06$
 T3: 40MVA 22/110kV $X_{p.u.}=0.064$
 T4: 40MVA 110/11kV $X_{p.u.}=0.08$
 Line 1: 48.4Ohms (total)
 Line 2: 65.43Ohms (total)

PEguru.com

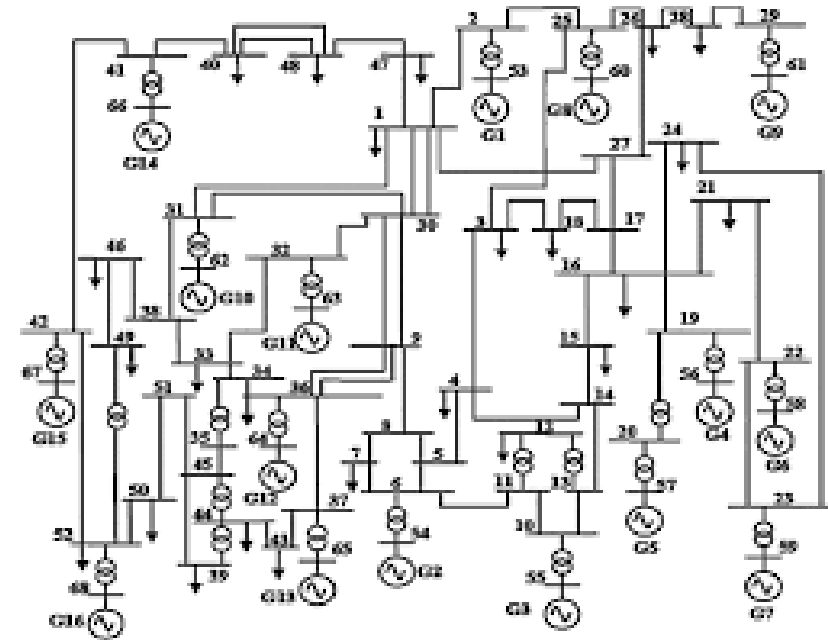

FINAL REMARKS

Thank you for all your hard work

Good luck with all your finals



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE