
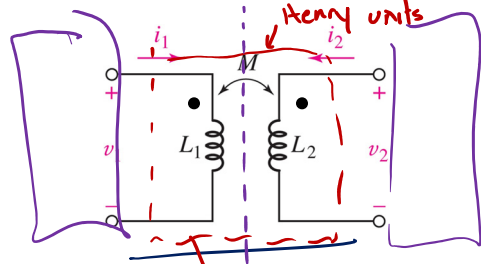



# Equivalent Circuits

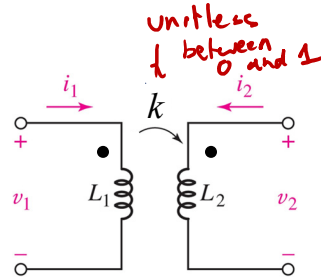

Henry units




unitless  
k between 0 and 1

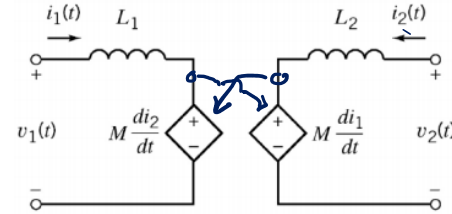

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} \\ v_2 = \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$


T-network

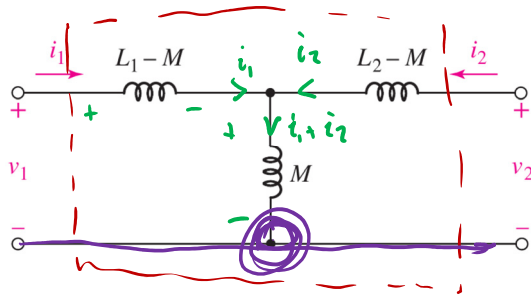

$$\begin{cases} v_1 = (L_1 - M) \frac{di_1}{dt} + M \frac{d(i_1 + i_2)}{dt} \\ v_2 = M \frac{d(i_1 + i_2)}{dt} + (L_2 - M) \frac{di_2}{dt} \end{cases}$$

for positive polarity

π-network

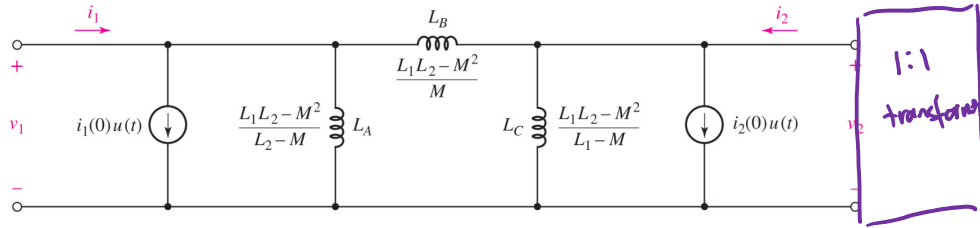

# Transformers

Special case of coupled inductors

$$\begin{cases} V_1 = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt} \\ V_2 = \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

with  $k=1 \iff$  perfect coupling  $\iff M = \sqrt{L_1 L_2}$

$$M = \sqrt{L_1 L_2}$$



$$\begin{cases} V_1 = L_1 \frac{di_1}{dt} \pm \sqrt{L_1 L_2} \frac{di_2}{dt} \\ V_2 = \pm \sqrt{L_1 L_2} \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

$$V_1 = \sqrt{\frac{L_1}{L_2}} V_2$$




$$V_1 = \sqrt{\frac{\cancel{\alpha_1} N_1^2}{\cancel{\alpha_2} N_2^2}} V_2$$

if  $k=1$ , it must be true that  $\alpha_1 = \alpha_2$

$$V_1 = \frac{N_1}{N_2} V_2$$

$\frac{N_1}{N_2}$  is the "turns ratio"

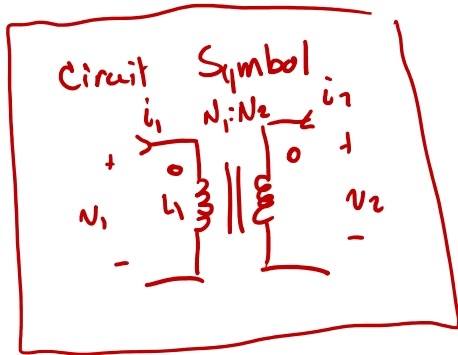

$N_1:N_2$  is the same as

$$1:N$$

$$N = \frac{N_2}{N_1}$$


# Ideal Transformer

"Ideal" transformer has very large  $L_1 \& L_2$

Recall: Inductors ( $\neq$  transformers) cannot have DC voltage applied to their windings

- $V_1 = L_1 \frac{di_1}{dt} \rightarrow i_1 = \frac{1}{L_1} \int_0^t V_1 dt \rightarrow$  DC voltage causes current to go to  $\infty$
- Materials  $\rightarrow$  core materials needed for  $K \approx 1$   $\&$  will saturate  $\&$  stop working at some finite current
- $V = N \frac{d\Phi}{dt} \rightarrow$  Faraday's Law, need time-varying waveforms

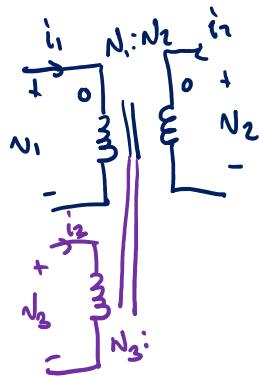When  $L_1 \& L_2$  are large enough  $\rightarrow$  no energy storage



$$V_1 = \frac{N_1}{N_2} V_2$$

No energy storage, so  $V_1 i_1 + V_2 i_2 = \phi$

$$\left(\frac{N_1}{N_2} V_2\right) i_1 + V_2 i_2 = \phi$$

$$N_1 i_1 + N_2 i_2 = \phi$$

$$i_1 = -\frac{N_2}{N_1} i_2$$

for more than two turns  $\rightarrow$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} = \frac{V_3}{N_3} = \dots$$

$$N_1 i_1 + N_2 i_2 + N_3 i_3 + \dots = \phi$$

# Applications of Coupled Inductors

