
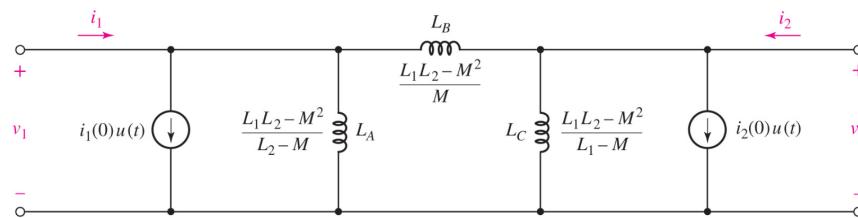
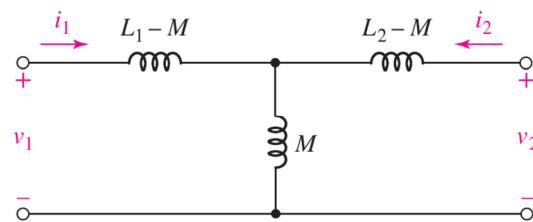
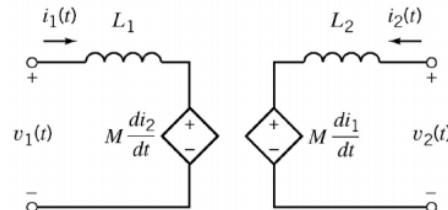
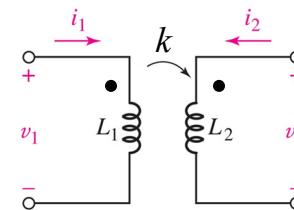





Equivalent Circuits

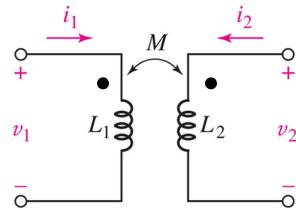


Transformers

Ideal Transformer


Applications of Coupled Inductors

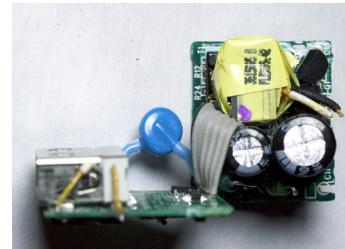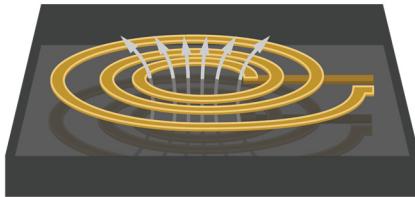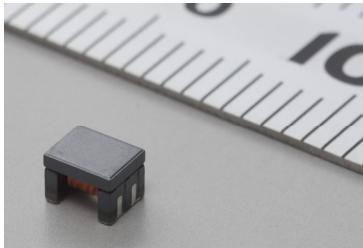


Example Transformer

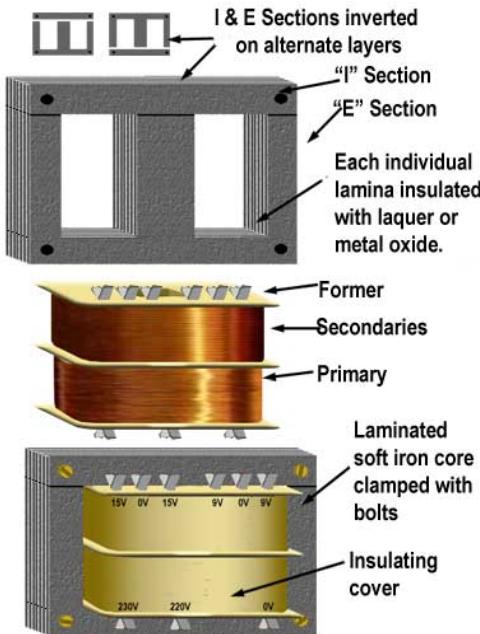

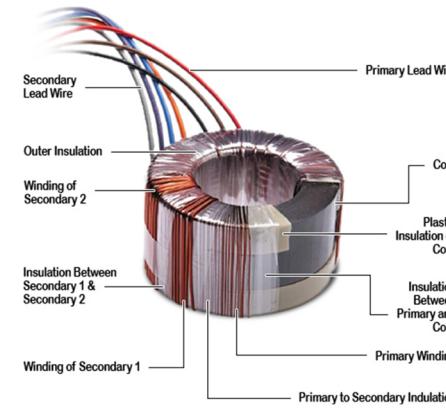http://www.learnabout-electronics.org/ac_theory/transformers03.php








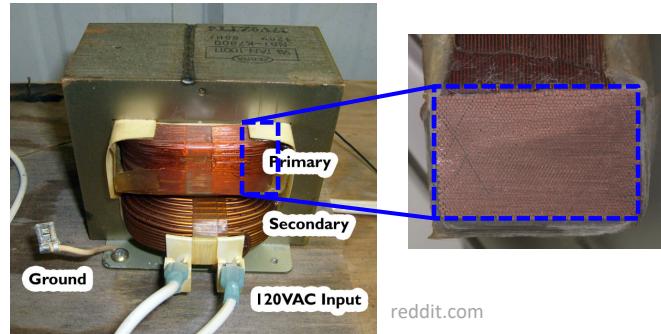
<https://www.altrancorp.com/products/toroidal-power-transformers/>



[reddit.com](https://www.reddit.com)

Transformer Reflection

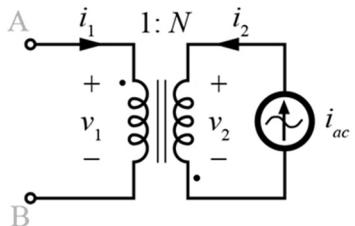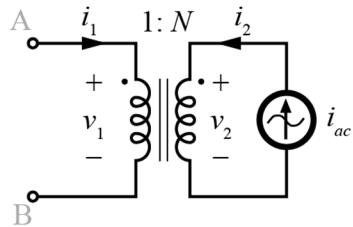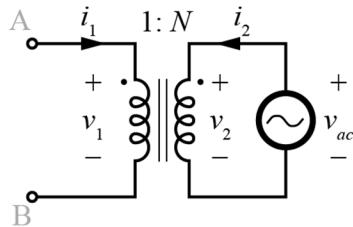

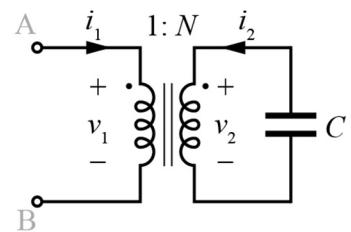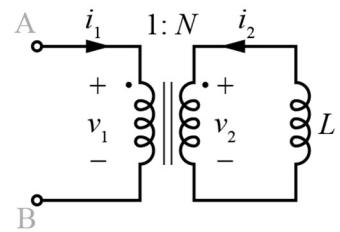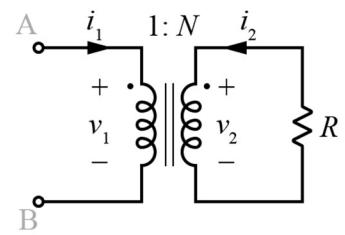

Example Circuit Simplification

