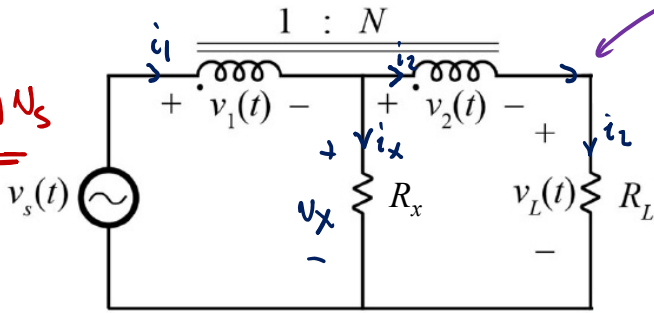


Ideal Transformer Example

Autotransformer (Variac)

$V_L = f(N, R_L, R_x) V_s$



solve for $v_L(t)$

Transformer equations

$$v_1 = \frac{v_2}{N}$$

$$i_1 = -N i_2$$

other elements

$$v_x = i_x R_x$$

$$v_L = i_L R_L$$

KVL :

$$v_x = v_2 + v_L$$


$$v_s = v_1 + v_2 + v_L$$

KCL :


$$i_1 = i_2 + i_x$$

Spice Mutual Inductance and XFs

Coupled Inductors

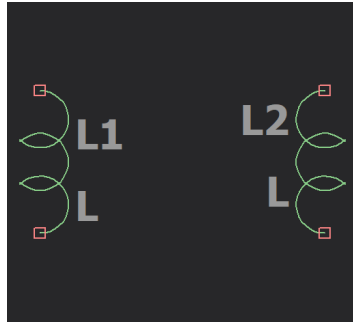


Ideal Transformer

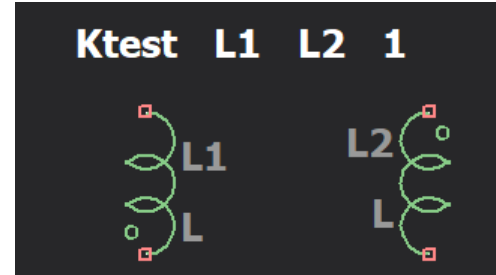


CHAPTER 10: SINUSOIDAL STEADY-STATE

Motivation

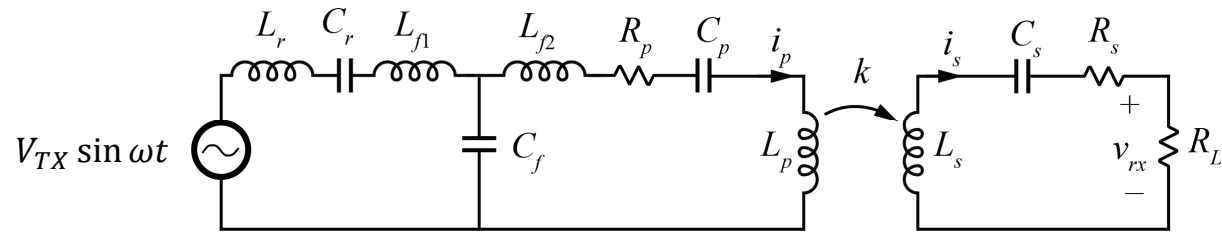

Motivation

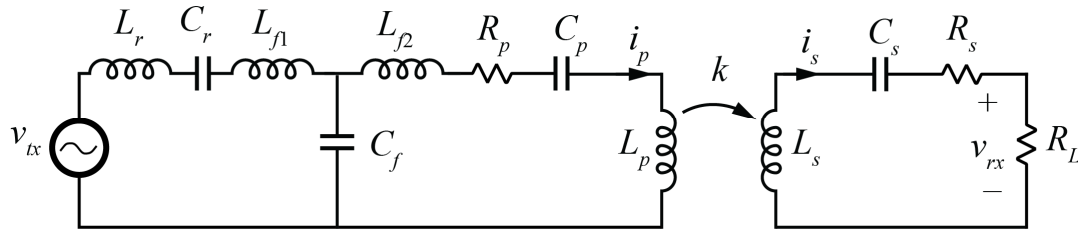

Numerical


Analytical

Time Domain

Frequency Domain

$$\left\{ \begin{array}{l} \frac{dA}{dt} = \beta_A \cdot \frac{D^n}{K_{DA}^n + D^n} \cdot \left(1 - \frac{C^n}{K_{CA}^n + C^n} \right) - \alpha_A \cdot A \\ \frac{dX}{dt} = \beta_X \cdot \frac{A^n}{K_{AX}^n + A^n} - \alpha_X \cdot X \\ \frac{dC}{dt} = \beta_C \cdot \frac{K_{AXC}^n}{K_{AXC}^n + (A+X)^n} - \alpha_C \cdot C \\ \frac{dB}{dt} = \beta_B \cdot \frac{C^n}{K_{CB}^n + C^n} \cdot \left(1 - \frac{D^n}{K_{DB}^n + D^n} \right) - \alpha_B \cdot B \\ \frac{dY}{dt} = \beta_Y \cdot \frac{B^n}{K_{BY}^n + B^n} - \alpha_Y \cdot Y \\ \frac{dD}{dt} = \beta_D \cdot \frac{(B+Y)^n}{K_{BYD}^n + (B+Y)^n} - \alpha_D \cdot D \end{array} \right.$$

Motivation

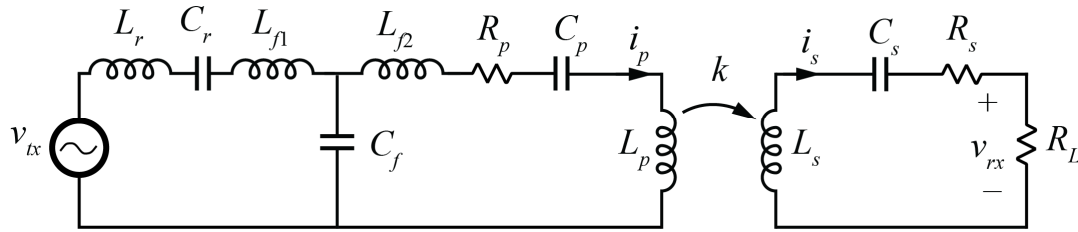


Numerical

Analytical


Time Domain

Frequency Domain

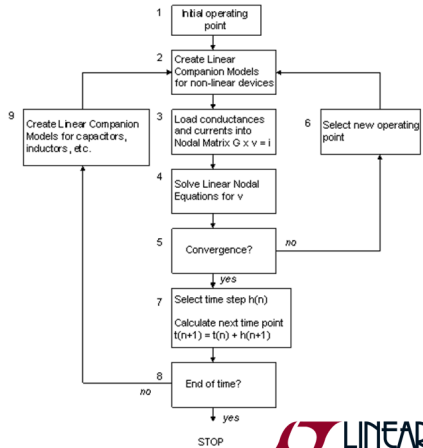

$$\left\{ \begin{array}{l} \frac{dA}{dt} = \beta_A \cdot \frac{D^n}{K_{DA}^n + D^n} \cdot \left(1 - \frac{C^n}{K_{CA}^n + C^n} \right) - \alpha_A \cdot A \\ \frac{dX}{dt} = \beta_X \cdot \frac{A^n}{K_{AX}^n + A^n} - \alpha_X \cdot X \\ \frac{dC}{dt} = \beta_C \cdot \frac{(A+X)^n}{K_{AC}^n + (A+X)^n} - \alpha_C \cdot C \\ \frac{dB}{dt} = \beta_B \cdot \frac{C^n}{K_{CB}^n + C^n} \cdot \left(1 - \frac{D^n}{K_{DB}^n + D^n} \right) - \alpha_B \cdot B \\ \frac{dY}{dt} = \beta_Y \cdot \frac{B^n}{K_{BY}^n + B^n} - \alpha_Y \cdot Y \\ \frac{dD}{dt} = \beta_D \cdot \frac{(B+Y)^n}{K_{DY}^n + (B+Y)^n} - \alpha_D \cdot D \end{array} \right.$$

Motivation

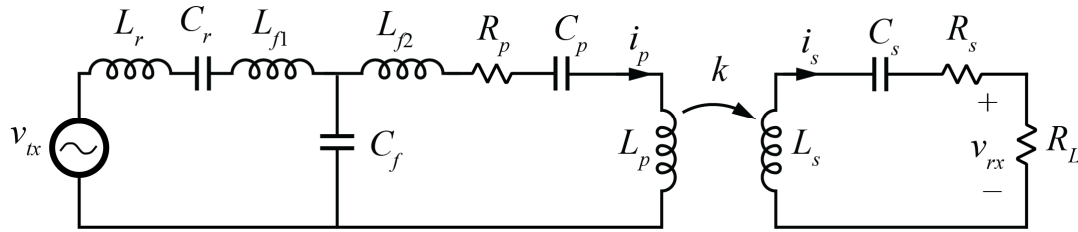


Numerical


Analytical

Time Domain

Frequency Domain

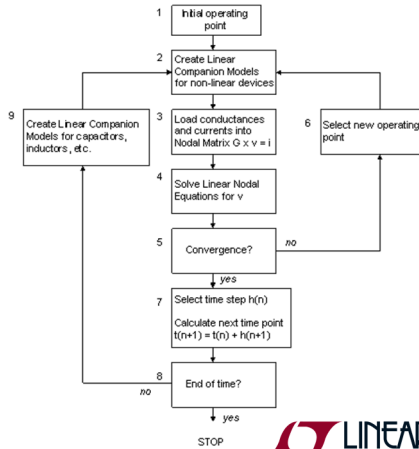

$$\left\{ \begin{array}{l} \frac{dA}{dt} = \beta_A \cdot \frac{D^n}{K_{DA}^n + D^n} \cdot \left(1 - \frac{C^n}{K_{CA}^n + C^n} \right) - \alpha_A \cdot A \\ \frac{dX}{dt} = \beta_X \cdot \frac{A^n}{K_{AX}^n + A^n} - \alpha_X \cdot X \\ \frac{dC}{dt} = \beta_C \cdot \frac{K_{AXC}^n}{K_{AXC}^n + (A+X)^n} - \alpha_C \cdot C \\ \frac{dB}{dt} = \beta_B \cdot \frac{C^n}{K_{CB}^n + C^n} \cdot \left(1 - \frac{D^n}{K_{DB}^n + D^n} \right) - \alpha_B \cdot B \\ \frac{dY}{dt} = \beta_Y \cdot \frac{B^n}{K_{BY}^n + B^n} - \alpha_Y \cdot Y \\ \frac{dD}{dt} = \beta_D \cdot \frac{K_{BYD}^n}{K_{BYD}^n + (B+Y)^n} - \alpha_D \cdot D \end{array} \right.$$

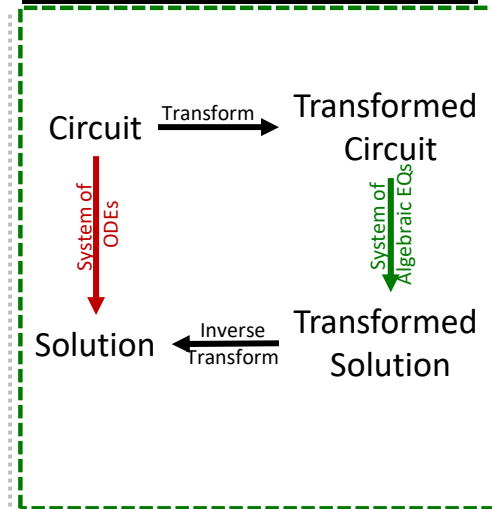

Form of the Solution

N^{th} order circuit with sinusoidal input described by

$$b_N \frac{d^N}{dt^N} v_o(t) + \dots + b_1 \frac{d}{dt} v_o(t) + b_0 v_o(t) = a_M \frac{d^M}{dt^M} v_i(t) + \dots + a_1 \frac{d}{dt} v_i(t) + a_0 v_i(t)$$

$$\sum_{i=0}^N b_i \frac{d^i}{dt^i} v_o(t) = \sum_{i=0}^M a_i \frac{d^i}{dt^i} v_i(t)$$

solution for $v_o(t)$ will be of the form

$$v_o(t) = v_{o,h}(t) + v_{o,p}(t)$$

Transient Response

$v_{o,h}(t)$ is the *homogeneous solution* to the differential equation, the *natural response* of the system, or the *transient response* of the system. For any non-ideal (damped) circuit, $v_{o,h}(t)$ will tend to zero over time

$v_{o,h}(t)$ is the solution to the equation

$$\sum_{i=0}^N b_i \frac{d^i}{dt^i} v_{o,h}(t) = 0$$

which will be of the form

$$v_{o,h}(t) = \sum_{i=0}^N A_i e^{s_i t}$$

$s_i \rightarrow$ roots of characteristic polynomial

$A_i \rightarrow$ determined by initial conditions

Note: some of the time constants (s_i) of a circuit are independent of the input

Steady-State Response

$v_{o,p}(t)$ is the *particular solution* to the differential equation, the *forced response* of the system, or the *steady-state response* of the system. In general, it does not tend to zero, if non-zero inputs are present.

$v_{o,p}(t)$ is the non-zeroing solution to the equation

$$\sum_{i=0}^N b_i \frac{d^i}{dt^i} v_o(t) = \sum_{i=0}^M a_i \frac{d^i}{dt^i} v_i(t)$$

LTI Systems

For a function $f(\cdot)$

Linearity

$$\text{if: } v_{o,1}(t) = f(v_{i,1}(t)) \quad v_{o,2}(t) = f(v_{i,2}(t))$$

$$\text{then: } av_{o,1}(t) + bv_{o,2}(t) = f(av_{i,1}(t) + bv_{i,2}(t))$$

Time Invariance

$$\text{if: } v_o(t) = f(v_i(t))$$

$$\text{then: } v_o(t - T) = f(v_i(t - T))$$

$$\text{LTI: } v_x(t) + v_y(t), \quad \alpha v_x(t), \quad \frac{dv_x(t)}{dt}, \quad \int_0^t v_x(t)dt \quad (\text{neglecting ICs})$$

$$\text{Not LTI: } v_x(t) \cdot v_y(t), \quad v_x(t)^2, \quad |v_x(t)|$$

Causality

- Causal systems cannot predict the future
- $v_o(t_0)$ does not depend on values of $v_i(t)$, $t > t_0$

$$v_{o,1}(t) = f(v_{i,1}(t)) \quad v_{o,2}(t) = f(v_{i,2}(t))$$

$$\text{if: } v_{i,1}(t) = v_{i,2}(t) \quad \forall \quad t < t_0$$

$$\text{then: } v_{o,1}(t) = v_{o,2}(t) \quad \forall \quad t < t_0$$

Preview of Frequency Domain