 


## Estimating Delays

- ▶ Would be nice to have a “back of the envelope” method for sizing gates for speed
- ▶ Logical Effort
  - ▶ Book by Sutherland, Sproull, Harris
  - ▶ Chapter 1 is on our web page
  - ▶ See also section 4.4.3 in your text



## Gate Delay Model

- ▶ First, normalize a model of delay to dimensionless units to isolate fabrication effects
  - ▶  $d_{abs} = d \tau$
  - ▶  $\tau$  is the delay of a minimum inverter driving another minimum inverter in some process
  - ▶ In a 0.6u process, this is approx 50ps
  - ▶ Now we can think about delay in terms of  $d$  and scale it to whatever process we're building the circuit in

## Gate Delay

- ▶ Delay of a gate  $d$  has two components
  - ▶ A fixed part called *parasitic delay*  $p$
  - ▶ A part proportional to the load on the output called the *effort delay* or *stage effort*  $f$
  - ▶ **Total delay** is measured in units of  $\tau$ , and is sum of these delays
  - ▶  $d = f + p$


## Effort Delay

- ▶ The **effort delay** (due to load) can be further broken down into two terms
  - ▶  $f = g * h$
  - ▶  $g$  = **logical effort** which captures properties of the gate's structure
  - ▶  $h$  = **electrical effort** which captures properties of load and transistor sizes
    - ▶  $h = C_{out}/C_{in}$
    - ▶  $C_{out}$  is capacitance that loads the output
    - ▶  $C_{in}$  is capacitance presented at the input
  - ▶ So,  $d = gh + p$
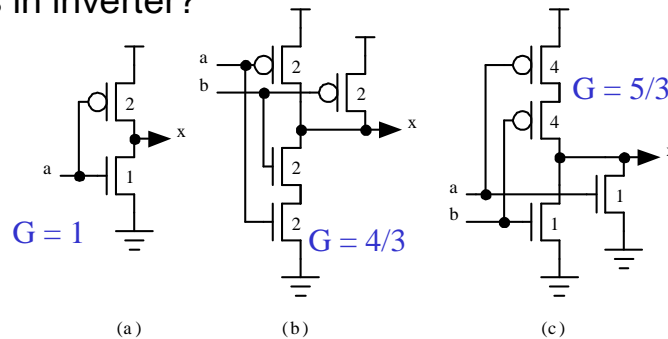
## Logical Effort

▶ Logical effort normalizes the output drive capability of a gate to match a unit inverter

▶ How much more input capacitance does a gate need to present to offer the same drive as in inverter?



## Logical Effort of Other Gates

▶ Logical effort of common gates assuming that P/N size ratio is 2

Number of inputs

Gate Type	1	2	3	4	5	$n$
<i>Inverter</i>	1					
<i>NAND</i>		4/3	5/3	6/3	7/3	$(n+2)/3$
<i>NOR</i>		5/3	7/3	9/3	11/3	$(2n+1)/3$
<i>MUX</i>		2	2	2	2	2
<i>XOR</i>		4	12	32		


## Electrical Effort

- ▶ Value of **logical effort g** is independent of transistor size
  - ▶ It's related to the ratios and the topology
- ▶ **Electrical effort h** captures the drive capability of the transistors via sizing
  - ▶ Electrical effort  $h = C_{out}/C_{in}$
  - ▶ Note that as transistor sizes for a gate increase, **h** decreases because  $C_{in}$  goes up

## Parasitic Delay


- ▶ Parasitic delay **p** is caused by the internal capacitance of the gate
  - ▶ It's constant and independent of transistor size
  - ▶ As you increase the transistor size, you also increase the cap of the gate/source/drain areas which keeps it constant
  - ▶ For our purposes, normalize  $p_{inv}$  to 1
    - ▶ N-input NAND =  $n * p_{inv}$
    - ▶ N-input NOR =  $n * p_{inv}$
    - ▶ N-way mux =  $2n * p_{inv}$
    - ▶ XOR =  $4 * p_{inv}$

## Plots of Gate Delay

 


## Delay Estimation

### Delay Estimation

 

$$A\_delay = g \cdot h + p = 1 \cdot (C_{inB}/C_{inA}) + 1$$
 
$$= 1 \cdot (4 \cdot C_{inA}/C_{inA}) + 1 = 4 + 1 = 5 \text{ time units}$$



$$A\_delay = g \cdot h + p = (4/3) \cdot (C_{inB}/C_{inA}) + 2 \cdot 1$$

$$C_{in\_B} = 4 \cdot 3 = 12, \quad C_{in\_A} = 4$$

$$A\_delay = (4/3) \cdot (12/4) + 2 = 4 + 2 = 6 \text{ units}$$


Nand2 worse because of higher parasitic delay than inverter.

Note that  $g \cdot h$  term was same for both because NAND2 sized to provide same current drive.

## Multi Stage Delay
 
### MultiStage Delay

- Recall rule of thumb that said to balance the delay at each stage along a critical path
- Concepts of logical effort and electrical effort can be generalized to multistage paths



$$\text{Path logical effort} = g_1 * g_2 * g_3 * g_4$$


$$\text{In general, Path logic effort } G = \prod g(i)$$

$$\text{Path electrical effort } H = \text{Cout} / \text{Cin}_{\text{first\_gate}}$$

Must remember that electrical effort only is concerned with effect of logic network on input drivers and output load.

## Off-Path Load

### Off Path Load

 

Off path load will divert electrical effort from the main path, must account for this. Define a *branching effort*  $b$  as:

$$b = (\text{Con}_{\text{path}} + \text{Coff}_{\text{path}}) / \text{Con}_{\text{path}}$$

The branching effort will modify the electrical effort needed at that stage. The branch effort  $B$  of the path is:

$$B = \prod b(i)$$

## Path Effort F

Path effort F is:

$$F = \text{path logic effort} * \text{path branch effort} * \text{path electrical effort} \\ = G * B * H$$

Path branch effort and path electrical effort is related to the electrical effort of each stage:

$$B * H = C_{out}/C_{in} * \prod b(i) = \prod h(i)$$

*Our goal is choose the transistor sizes that effect each stage effort  $h(i)$  in order to minimize the path delay!!!!!!!*

## Minimizing Path Delay

The absolute delay will have the parasitic delays of each stage summed together.

However, can *focus on just Path effort F* for minimization purposes since parasitic delays are constant.

For an N-stage network, *the path delay is least when each stage in the path bears the same stage effort.*

$$f(\min) = g(i) * h(i) = F^{1/N}$$

Minimum achievable path delay

$$D(\min) = N * F^{1/N} + P$$

Note that if  $N=1$ , then  $d = f + p$ , the original single gate equation.

## Choosing Transistor Sizes

Remember that the stage effort  $h(i)$  is related to transistor sizes.

$$f(\min) = g(i) * h(i) = F^{1/N}$$

So


$$h(i) \min = F^{1/N} / g(i)$$

To size transistors, start at end of path, and compute:

$$C_{in}(i) = g_i * C_{out}(i) / f(\min)$$

Once  $C_{in}(i)$  is know, can distribute this among transistors of that stage.

## Example

 

Size the transistors of the nand2 gates for the three stages shown.

$$\text{Path logic effort} = G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$$

$$\text{Branching effort } B = 1.0 \text{ (no off-path load)}$$

$$\text{Electrical effort } H = C_{out}/C_{in} = C/C = 1.0$$

$$\begin{aligned} \text{Min delay achievable} &= 3 * (G * B * H)^{1/3} + 3 (2 * p_{inv}) \\ &= 3 * (2.37 * 1 * 1)^{1/3} + 3 (2 * 1.0) = 10.0 \end{aligned}$$



## Example, continued

The effort of each stage will be:

$$f_{\min} = (G \cdot B \cdot H)^{1/3} = (2.37 \cdot 1.0 \cdot 1.0)^{1/3} = 1.33 = 4/3$$

Cin of last gate should equal:


$$\begin{aligned} C_{\text{in last gate (min)}} &= g_i \cdot C_{\text{out (i)}} / f(\min) \\ &= 4/3 \cdot C / (4/3) = C \end{aligned}$$

Cin of middle gate should equal:

$$\begin{aligned} C_{\text{in middle gate}} &= g_i \cdot C_{\text{in last gate}} / f(\min) \\ &= 4/3 \cdot C / (4/3) = C \end{aligned}$$

All gates have same input capacitance, distribute it among transistors.

## Transistor Sizes for Example

 

Where gate capacitance of  
 $2 \cdot W \cdot L$  Mosfet =  $C/2$

Choose W accordingly.

## Another Example, Larger Load

Let Load = 8C, what changes?

Size the transistors of the nand2 gates for the three stages shown.

Path logic effort =  $G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$

Branching effort  $B = 1.0$  (no off-path load)

Electrical effort  $H = C_{out}/C_{in} = 8C/C = 8.0$

Min delay achievable =  $3 * (G*B*H)^{1/3} + 3 * (2 * \text{pinv})$   
 $= 3 * (2.37 * 1 * 8)^{1/3} + 3 * (2 * 1.0) = 14.0$

## 8C Load Example Cont.

The effort of each stage will be:

$$f_{\min} = (G*B*H)^{1/3} = (2.37 * 1.0 * 8)^{1/3} = 2.67 = 8/3$$

Cin of last gate should equal:

$$C_{in \text{ last gate (min)}} = g_i * C_{out (i)} / f(\min)$$

$$= 4/3 * 8C / (8/3) = 4C$$

Cin of middle gate should equal:


$$C_{in \text{ middle gate}} = g_i * C_{in \text{ last gate}} / f(\min)$$

$$= 4/3 * 4C / (8/3) = 2C$$

Note that each stage gets progressively larger, as is typical with a multi-stage path driving a large load.

## Example 1.6 from Chap 1

Size path from  
A to B

 

Path logic effort  $G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$

Branch effort, 1<sup>st</sup> stage  $= (y+y)/y = 2$ .

Branch effort, 2<sup>nd</sup> stage  $= (z+z+z)/z = 3$

Path Branch effort  $B = 2 * 3 = 6$ .

Path electrical effort  $H = C_{out}/C_{in} = 4.5C/C = 4.5$

Path stage effort  $= F = G*B*H = 2.37*6*4.5 = 64$ .

Min delay  $= N(F)^{1/N} + P = 3*(64)^{1/3} + 3(2pinv) = 18.0$  units

## Example 1.6 Continued

Stage effort of each stage should be:

$$f(\min) = (F)^{1/N} = (GBH)^{1/N} = (64)^{1/3} = 4$$

Determine  $C_{in}$  of last stage:

$$C_{in}(z) = g * C_{out} / f(\min) = 4/3 * 4.5C / 4 = 1.5 C$$

Determine  $C_{in}$  of middle stage:


$$C_{in}(y) = g * (3*C_{in}(z)) / f(\min) = 4/3 * (3*1.5C) / 4 = 1.5C$$

Is first stage correct?

$$C_{in}(A) = g * (2*C_{in}(y)) / f(\min) = 4/3 * (2*1.5C) / 4 = C$$

Yes, self-consistent.

## Example 1.7 from Chap 1

 

Path logic effort  $G = g_0 * g_1 * g_2 * g_3 = 1 * 5/3 * 4/3 * 1 = 20/9$

Path Branch effort  $B = 1$

Path electrical effort  $H = C_{out}/C_{in} = 20/10 = 2$

Path stage effort  $F = G * B * H = (20/9) * 1 * 2 = 40/9$

For Min delay, each stage has effort  $(F)^{1/N} = (40/9)^{1/4} = 1.45$

$z = g * C_{out}/f(\text{min}) = 1 * 20 / 1.45 = 14$




$y = g * C_{in}(z) / f(\text{min}) = 4/3 * 14 / 1.45 = 13$

$x = g * C_{in}(y) / f(\text{min}) = 5/3 * 13 / 1.45 = 15$


## Misc. Comments

- ▶ Note that you never size the first gate
  - ▶ This gate is assumed to be fixed
  - ▶ If you were allowed to size it, the algorithm would try to make it as large as possible
- ▶ This is an estimation algorithm
  - ▶ Authors claim that sizing a gate by 1.5x too big or small still results in a path delay within 5% of minimum
- ▶ In general, the best stage effort is between 3 and 4 (not  $e$  as often stated)
  - ▶ The  $e$  value doesn't use parasitics...

## Evaluating Different Options

   

## Option #1

 

Path logic effort  $G = g_0 * g_1 * g_2 = 1 * 6/3 * 1 = 2$

Path Branch effort  $B = 1$

Path electrical effort  $H = C_{out}/C_{in} = 8C/C = 8$


Path stage effort =  $F = G * B * H = 2 * 1 * 8 = 16$

Min delay: =  $N * (F)^{1/N} + P$

=  $3 * (16)^{1/3} + (p_{inv} + 4 * p_{inv} + p_{inv})$

=  $3 * (2.5) + 6 = 13.5$

## Option #2

 

Path logic effort  $G = g_0 * g_1 * g_2 = 1 * 4/3 * 5/3 = 20/9$

Path Branch effort  $B = 1$

Path electrical effort  $H = C_{out}/C_{in} = 8C/C = 8$

Path stage effort  $= F = G * B * H = 20/9 * 1 * 8 = 160/9$

$$\begin{aligned} \text{Min delay: } &= N * (F)^{1/N} + P \\ &= 3 * (160/9)^{1/3} + (p_{inv} + 2 * p_{inv} + 2 * p_{inv}) \\ &= 3 * 2.6 + 5 = 12.8 \end{aligned}$$

Option #2 appears to be better than Option #1, by a slight margin.

## Choosing the Best # of Stages

▶ You can solve the delay equations to determine the number of stages  $N$  that will achieve the minimum delay

▶ Approximate by  $\text{Log}_4 F$

Path Effort $F$	Best $N$	Min Delay $D$	Stage effort $f$
0-5.83	1	1.0-6.8	0-5.8
5.83-22.3	2	6.8-11.4	2.4-4.7
22.3-82.2	3	11.4-16.0	2.8-4.4
82.2-300	4	16.0-20.7	3.0-4.2
300-1090	5	20.7-25.3	3.1-4.1
1090-3920	6	25.3-29.8	3.2-4.0

## Summary

- ▶ Compute path effort  $F = GBH$
- ▶ Use table, or estimate  $N = \log_4 F$  to decide on number of stages
- ▶ Estimate minimum possible delay  
 $D = NF^{1/N} + \sum p_i$
- ▶ Add or remove stages in your logic to get close to  $N$
- ▶ Compute effort at each stage  $f = F^{1/N}$
- ▶ Starting at output, work backwards to compute transistor sizes  $C_{in} = (g_i/f)C_{out}$