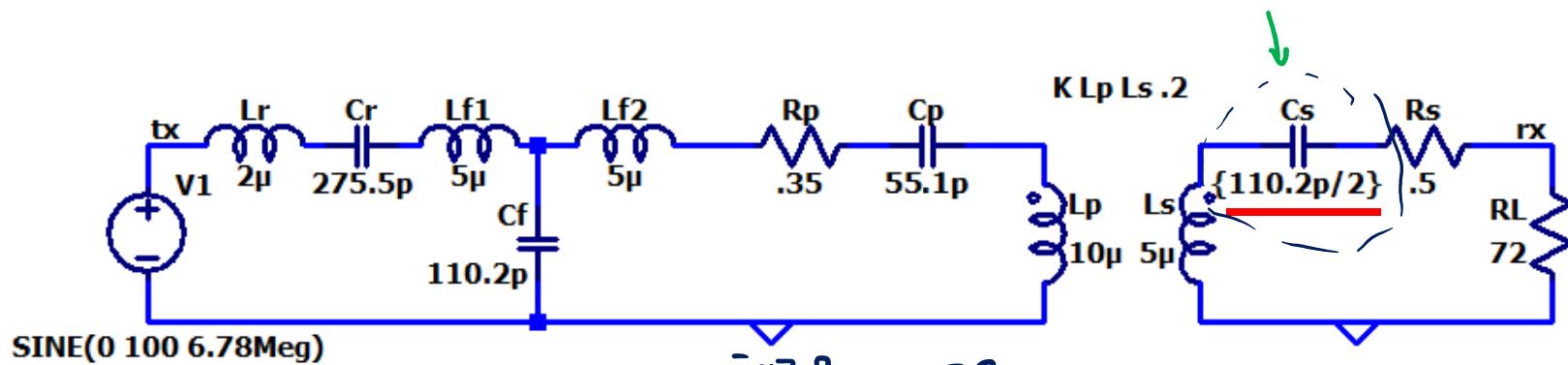


$$\underline{V_{RL}} = \frac{\underline{V_{IN}}}{j213} (j60) \frac{72}{72 + 0.5}$$

$$\underline{V_{RL}} = 28 \angle -90^\circ$$


Numerical Example 2

$$z_{cs} \cdot \frac{j}{jC_s} = \frac{-j^{426}}{(-j^{2\sqrt{3}})R + -j^{2B\omega})}$$



MATLAB Result:

mag =
9.06
phase =
-18.7973

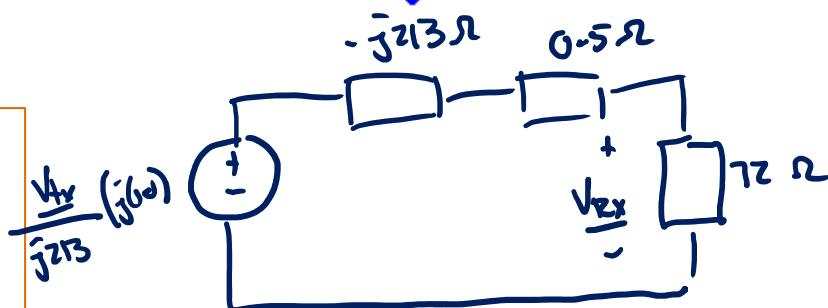


$$\underline{V}_{rx} = \underline{\underline{Z}} \frac{60}{2\sqrt{3}} \frac{72}{72 + 0.5 - j^{2\sqrt{3}}}$$

$\downarrow 100^{\circ} 4 - 90^{\circ}$

$$\underline{V}_{rx} = 9 \angle -18^{\circ}$$

Circuit Simulation 2


.tran 0 1m 999u

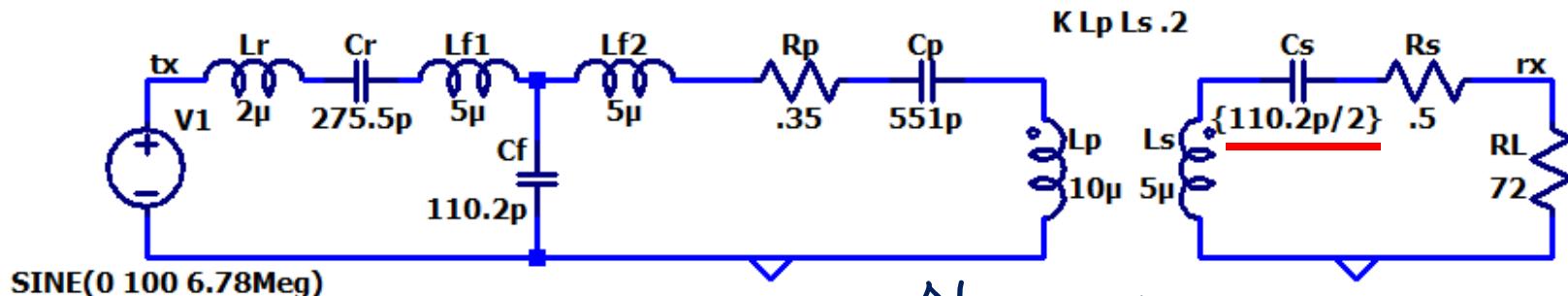

SINE(0 100 6.78Meg)


$$\phi_{tx} - \phi_{rx} = \frac{\Delta t}{T} \cdot 360^\circ$$

$$T = \frac{1}{6.78\text{MHz}}$$

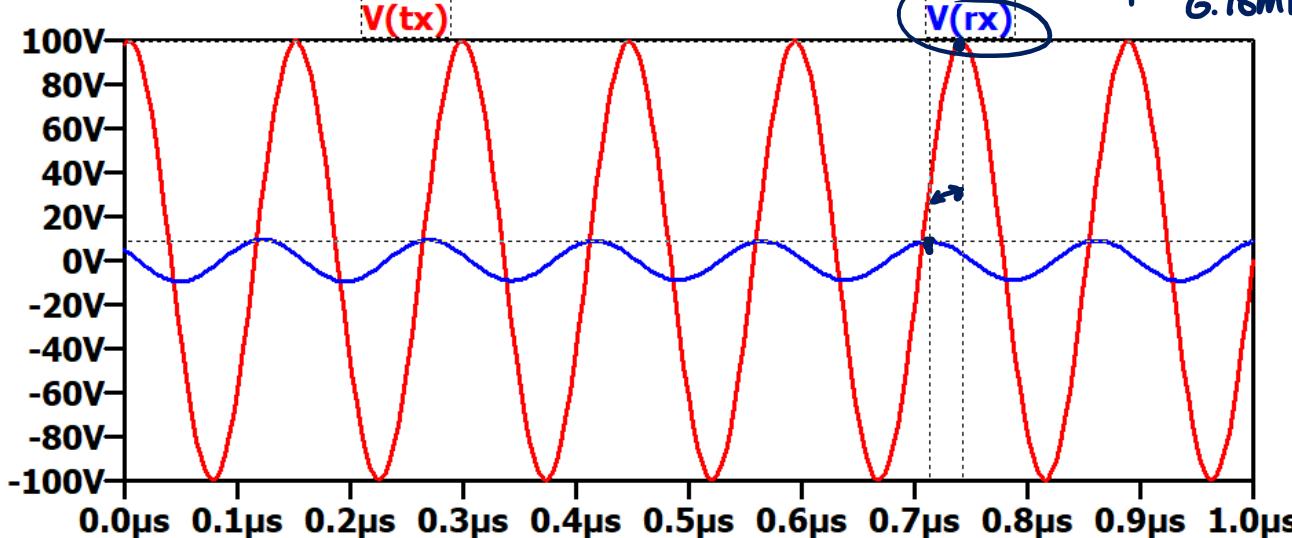

WPTphaser.raw	
Cursor 1	$V(tx)$
Horz:	742.80534ns
Vert:	99.533096V
Cursor 2	$V(rx)$
Horz:	712.84545ns
Vert:	8.8561678V
Diff (Cursor2 - Cursor1)	
Horz:	-29.959884ns
Vert:	-90.676929V
Freq:	33.377966MHz
Slope:	3.02661e+009

AC Analysis

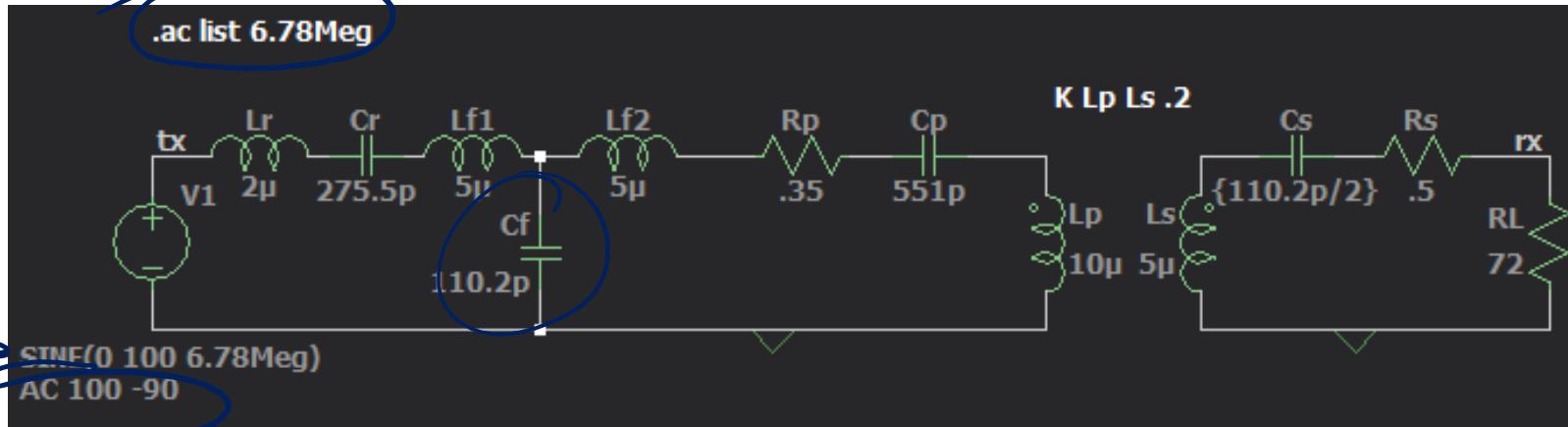

Edit Simulation Command

AC Analysis (highlighted)

Compute the small signal AC behavior of the circuit linearized about its DC operating point.

Type of sweep: List (highlighted)

1st frequency: 6.78Meg (highlighted)

2nd frequency: _____

3rd frequency: _____

Syntax: **.ac list <Freq1> [<Freq2> [<Freq3> [...]]]**

.ac list 6.78Meg

Cancel **OK**

Independent Voltage Source - V1

Functions

- (none)
- PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Voff Vamp Ecar MDI Tsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE: _____ **Browse**

DC Value

 Make this information visible on schematic:

Small signal AC analysis(.AC)

AC Amplitude: **100**
 AC Phase: **-90**
 Make this information visible on schematic:

Parasitic Properties

Series Resistance[Ω]: _____
 Parallel Capacitance[F]: _____
 Make this information visible on schematic:




Additional PWL Points
 Make this information visible on schematic:

Cancel **OK**

AC Simulation Results (Single Point)

--- AC Analysis ---			
frequency:	<u>6.78e+006</u>	Hz	
V(tx):	mag: 100	phase: -90°	voltage
V(n001):	mag: 174.844	phase: -90.3419°	voltage
V(n002):	mag: 99.9949	phase: -90.0005°	voltage
V(n003):	mag: 287.109	phase: -90.5205°	voltage
V(n004):	mag: 187.14	phase: -90.798°	voltage
V(n006):	mag: 207.132	phase: -90.6756°	voltage
V(n007):	mag: 54.3051	phase: -99.138°	voltage
V(n005):	mag: 187.137	phase: -90.7477°	voltage
V(n008):	mag: 9.11047	phase: -18.7958°	voltage
V(rx):	mag: 9.04764	phase: -18.7958°	voltage
I(Cs):	mag: 0.125662	phase: -18.7958°	device_current
I(Cp):	mag: 0.469369	phase: 179.999°	device_current
I(Cf):	mag: 1.34784	phase: 179.48°	device_current
I(Cr):	mag: 0.878499	phase: 179.202°	device_current
I(Ls):	mag: 0.125662	phase: -18.7958°	device_current
I(Lp):	mag: 0.469369	phase: -0.000865793°	device_current
I(Lf2):	mag: 0.469369	phase: 179.999°	device_current
I(Lf1):	mag: 0.878499	phase: -0.798129°	device_current
I(Lr):	mag: 0.878499	phase: -0.798129°	device_current
I(Rp):	mag: 0.469369	phase: -0.000865793°	device_current
I(Rl):	mag: 0.125662	phase: 161.204°	device_current
I(Rs):	mag: 0.125662	phase: 161.204°	device_current
I(V1):	mag: 0.878499	phase: 179.202°	device_current

Frequency Sweep

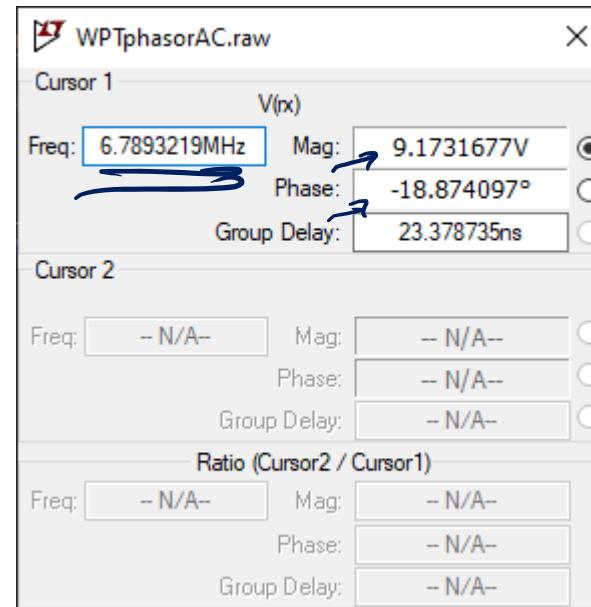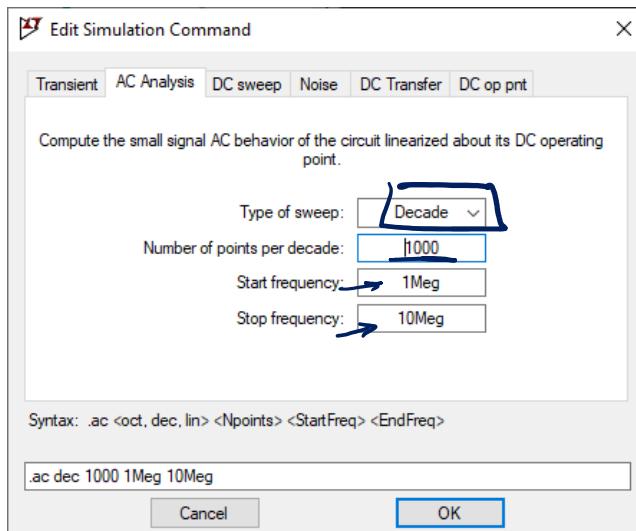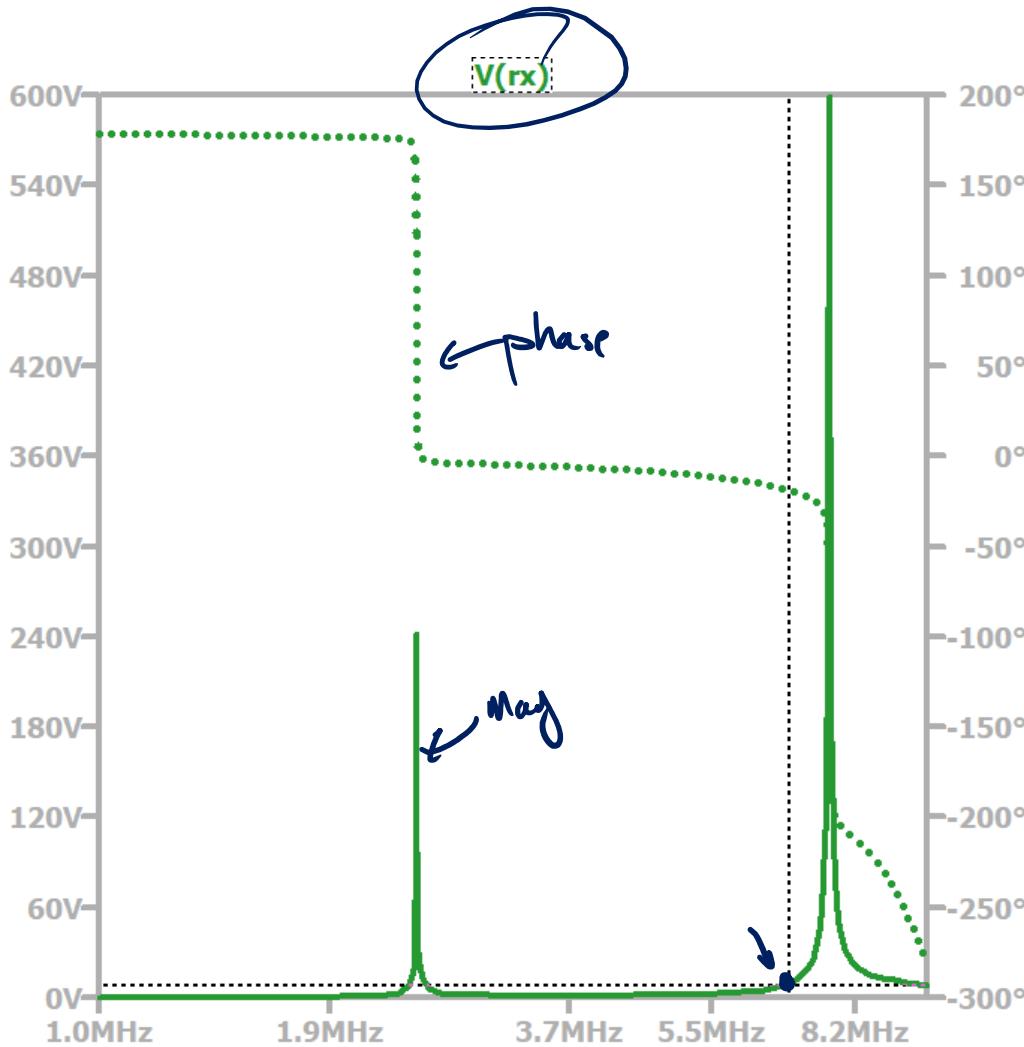

Form of the solution

$$\sum_{i=0}^N b_i \frac{d^i}{dt^i} v_o(t) = \sum_{i=0}^M a_i \frac{d^i}{dt^i} v_i(t)$$

phasor transform

$$\sum_{i=0}^N b_i (j\omega)^i \underline{v}_o = \sum_{i=0}^M a_i (j\omega)^i \underline{v}_i$$

$$\underline{v}_o = \underline{v}_i$$


$$\frac{\sum_{i=0}^M a_i (j\omega)^i}{\sum_{i=0}^N b_i (j\omega)^i}$$

$$H(j\omega)$$

Chapter 11

AC CIRCUIT POWER ANALYSIS


Average Power

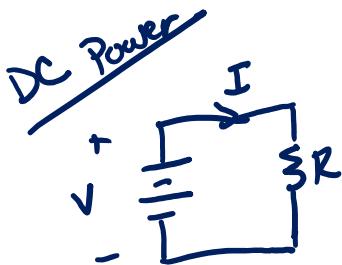

$$P = V \cdot I \rightarrow \text{Generally true for any 2-terminal element}$$

for resistors $V = IR$
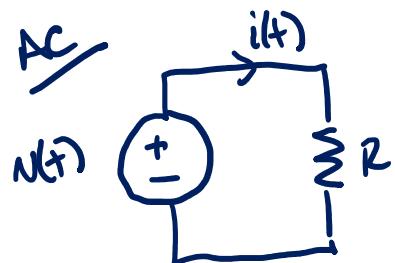
$$P_R = \frac{V^2}{R} = \underline{\underline{I^2 R}}$$



$$p(t) = \underline{\underline{v(t) \cdot i(t)}} \rightarrow \text{Generally true for any 2-terminal element}$$

for resistors $P_R(t) = \frac{v(t)^2}{R} = \underline{\underline{i(t)^2 R}}$

power calculation is not LTI

Average Power


capital P
for average

Average power over some interval $[t_1, t_1 + T]$

$$P = \frac{1}{T} \int_{t_1}^{t_1+T} p(t) dt$$

Average power over all time
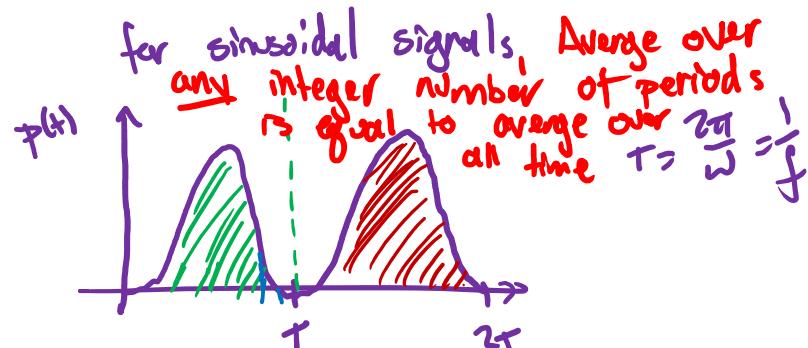
$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$$



Power in a Resistor

Average power in a resistor with some periodic (e.g. sinusoidal) current

$$P_R = \frac{1}{T} \int_0^T P_R(t) dt = \frac{1}{T} \int_0^T i_R(t)^2 R dt$$

$$= R \underbrace{\frac{1}{T} \int_0^T i_R(t)^2 dt}_{\text{rms}}$$

$$P_R = R \left(\sqrt{\frac{1}{T} \int_0^T i_R(t)^2 dt} \right)^2 \rightarrow P_R = \underline{(I_{\text{rms}})^2 R}$$

rms = "root mean square"

Define rms \rightarrow

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

$$X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T X(t)^2 dt}$$

Note: book calls this "effective" instead of rms

$$I_{\text{eff}}, V_{\text{eff}}, \Leftarrow \sqrt{V_{\text{rms}}} I_{\text{rms}}$$