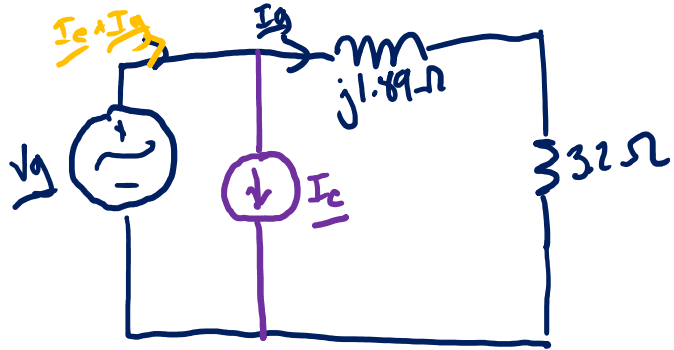



Announcements

Quiz Wednesday

- Circuit with many L/R/C and sinusoidal input
 - Sketch Phasor circuit
 - Solve circuit for output
 - Sketch a Thevenin equivalent
- Series/parallel resonances may or may not occur



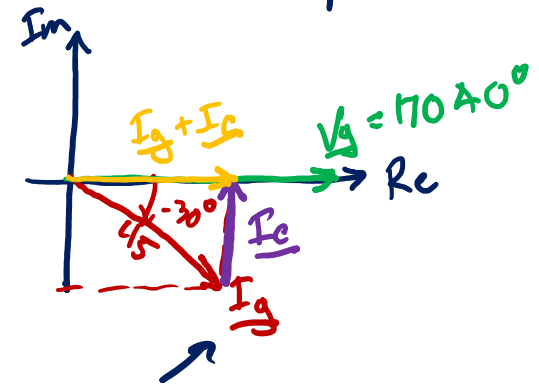Can we return the grid PF to unity?
 Look at $\underline{I_g}$
 from previous slide
 $\underline{I_g} = 45 \angle -30^\circ$




How do we generate $\underline{I_c}$?

$$\underline{I_c} = 45 \sin(30^\circ) \angle +90^\circ$$

$$= 22.5 \angle 90^\circ \text{ A} = j22.5 \text{ A}$$

$$z_c = \frac{V_g}{\underline{I_c}} = \frac{170 \angle 0^\circ}{22.5 \angle 90^\circ} = 7.56 \angle -90^\circ = -j7.56 = \frac{-j}{\omega C}$$

$$\hookrightarrow C = 350 \mu\text{F}$$


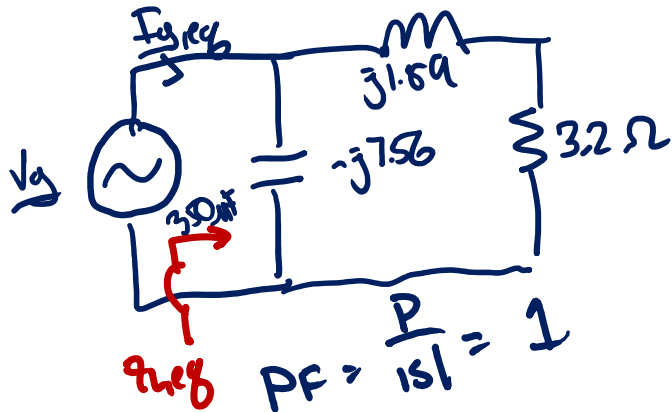


$$S_g = \frac{1}{2} V_g \underline{I_{g,reg}}^* = \underline{3.3 \text{ kW} + j0 \text{ VAR}}$$

$$z_{reg} = -j7.56 \parallel (j1.89 + 3.2) = 4.3 \angle \phi$$

$$\underline{I_{g,reg}} = \frac{V_g}{z_{reg}} = \frac{170 \angle 0^\circ}{4.3 \angle \phi} = 4.3 \angle 0^\circ$$

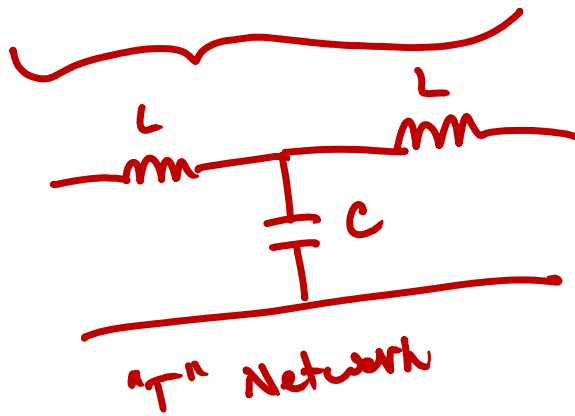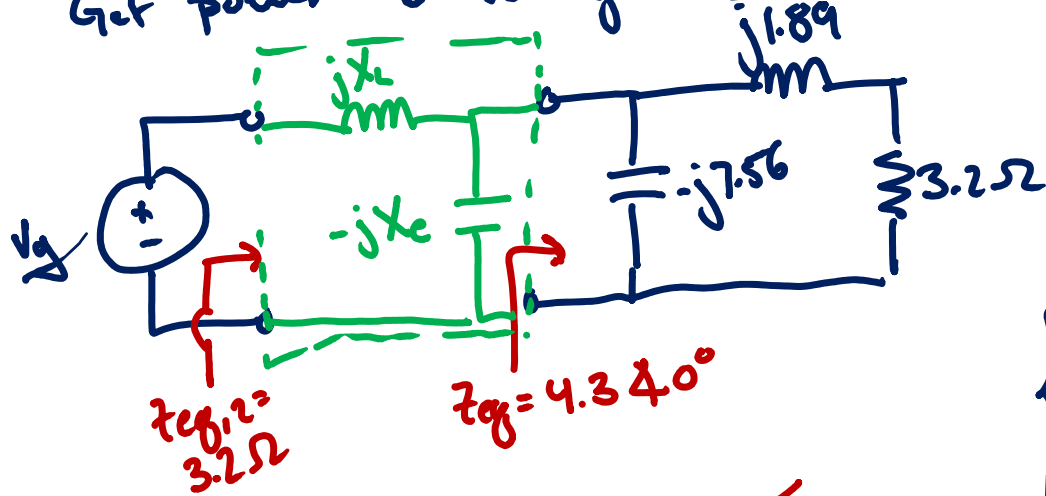Get power & voltage to load back to 4.5kW / 170Vpk



from previous slide:

$$3.2 \Omega = \frac{x_c^2 (4.3)}{4.3^2 + x_c^2}$$

$$0 = x_c - \frac{x_c (4.3)^2}{4.3^2 + x_c^2}$$



$$x_c = 7.4 \Omega = \frac{1}{\omega C}$$

$$x_L = 1.88 \Omega = \omega L$$

$$C = 360 \mu\text{F} \quad @ \quad \omega = 2\pi 60$$

$$L = 5 \text{mH}$$

Simulation Example

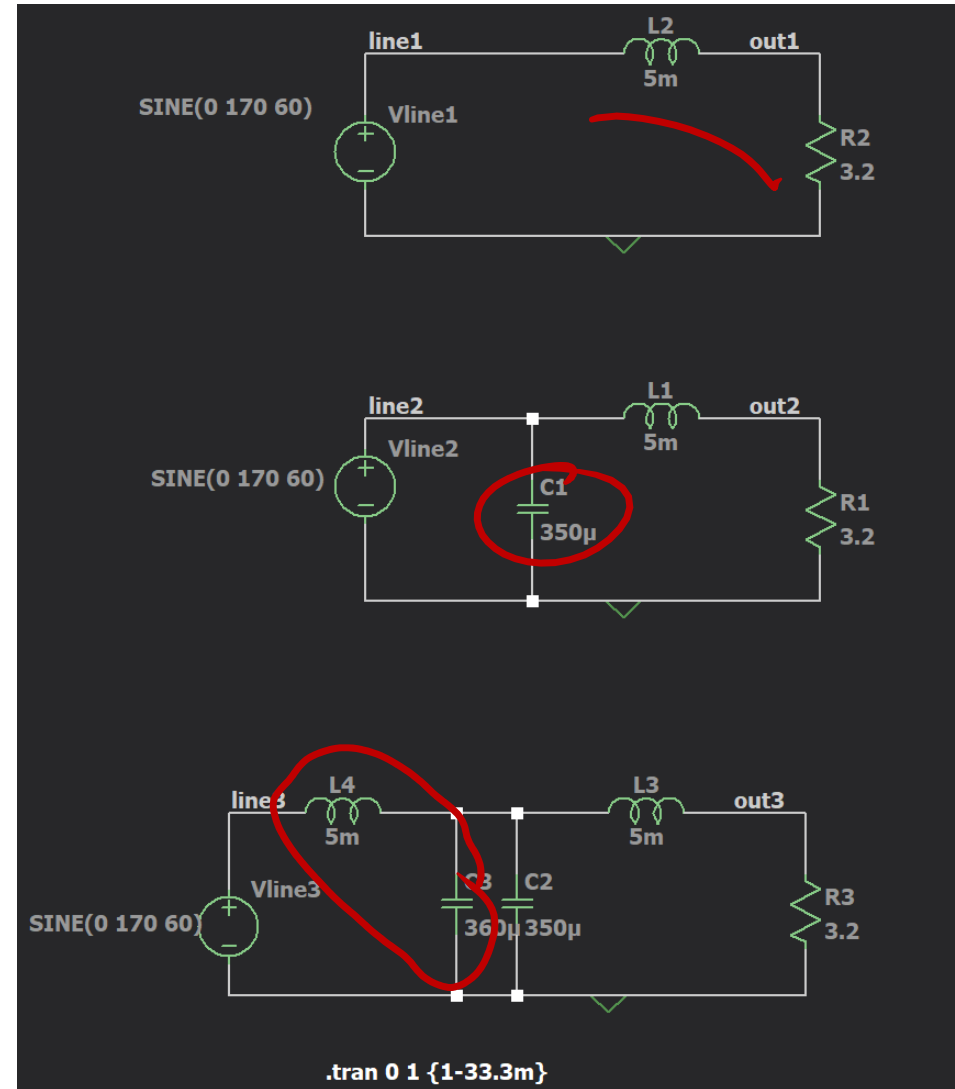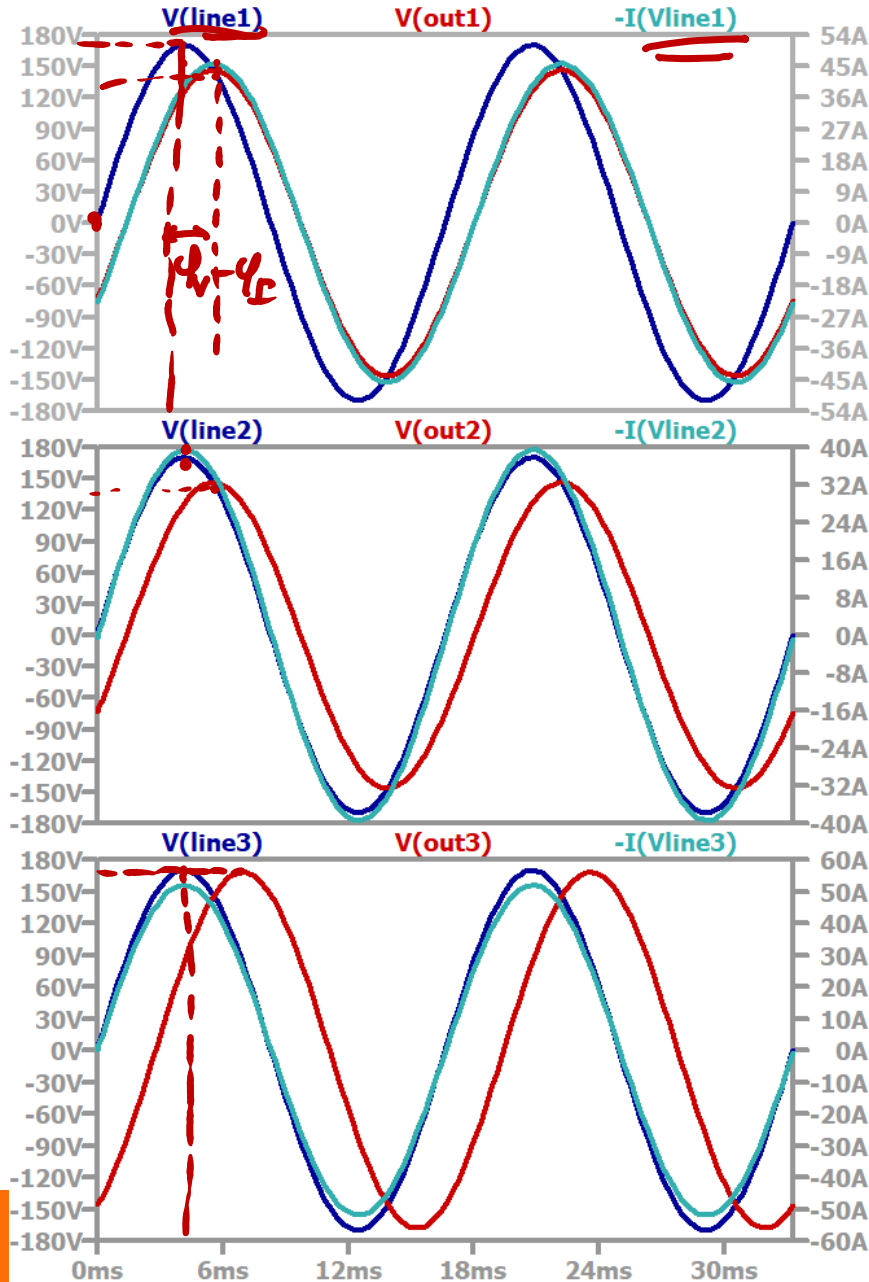


Power Triangle

$$\left. \begin{aligned} \underline{V} &= V_A e^{j\phi_V} \\ \underline{I} &= I_A e^{j\phi_I} \end{aligned} \right\} S = \frac{1}{2} \underline{V} \underline{I}^* = \frac{1}{2} V_A I_A e^{j(\phi_V - \phi_I)}$$

$$\underline{V} = \underline{I} Z$$

$$X_{rms} = \frac{XA}{\sqrt{2}}$$
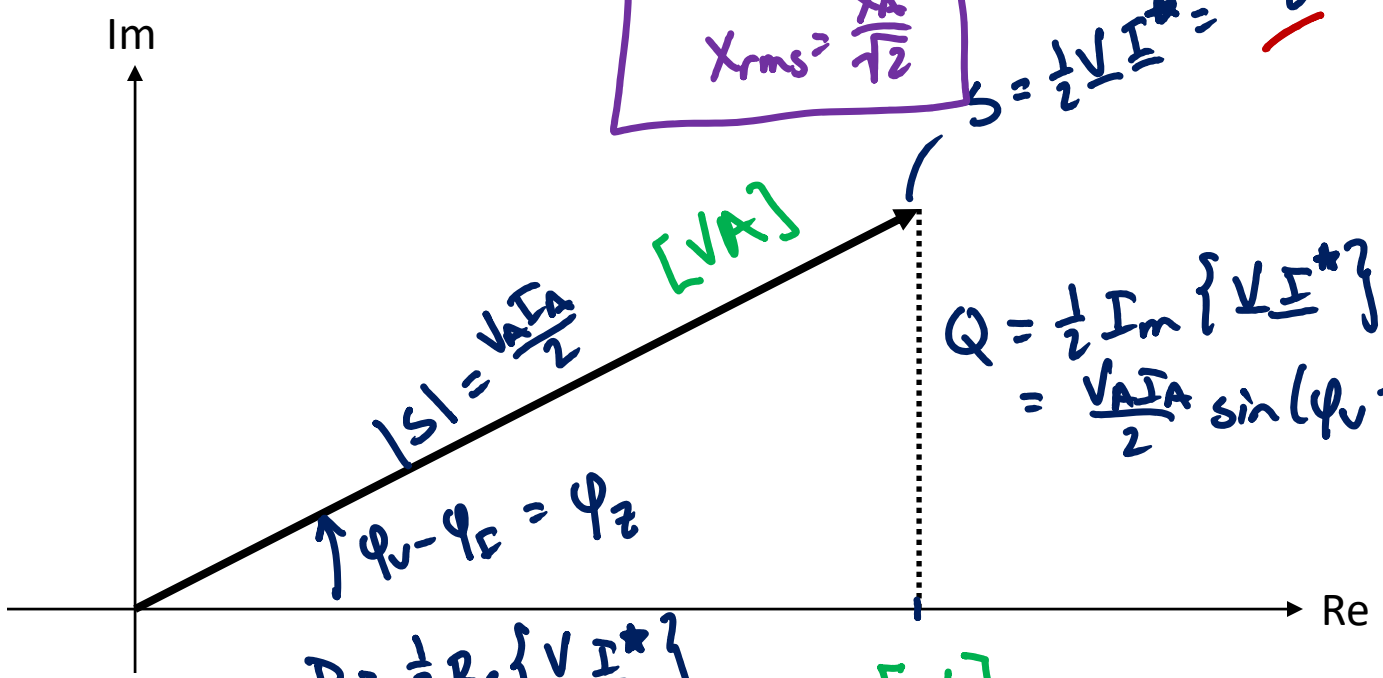
$$S = \frac{1}{2} \underline{V} \underline{I}^* = \frac{V_A I_A}{2} e^{j(\phi_V - \phi_I)}$$



$$Q = \frac{1}{2} \text{Im} \{ \underline{V} \underline{I}^* \} \quad [\text{VAR}]$$

$$= \frac{V_A I_A}{2} \sin(\phi_V - \phi_I)$$

$$P = \frac{1}{2} \text{Re} \{ \underline{V} \underline{I}^* \} \quad [\text{W}]$$


$$= \frac{V_A I_A}{2} \cos(\phi_V - \phi_I)$$

$$\text{PF} = \frac{P}{|S|} = \cos(\phi_V - \phi_I)$$

(leading or lagging)
 (current w.r.t. voltage)
 ↘ capacitive
 ↘ inductive

Power Spectrum

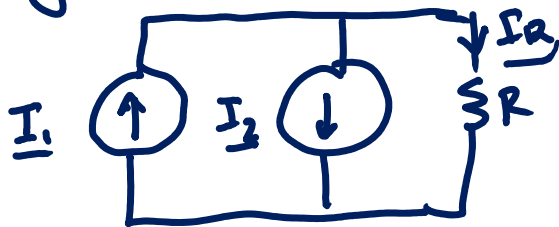Recall that power is a non-LTI calculation so superposition is not guaranteed to work



$I_1 = I_2$ by inspection $I_R = 0$ & $P_R = \emptyset$

If I incorrectly apply superposition to power calculations

$P_1 = I_{1,rms}^2 R$ $P_2 = I_{2,rms}^2 R$
 $P_{tot} = (I_{1,rms}^2 + I_{2,rms}^2) R > \emptyset$

Superposition still works for calculating I_R

Interestingly, it does work if $i_1(t)$ & $i_2(t)$ are at different frequencies

$$P_R(t) = i_1(t)^2 R + i_2(t)^2 R = [I_{A1}^2 \cos^2(\omega_1 t) + I_{A2}^2 \cos^2(\omega_2 t)] R$$

$$P_R(t) = [i_1(t) - \underbrace{i_2(t)}_{\substack{\text{by} \\ \text{superposition}}}]^2 R$$

$$P = \frac{R}{T} \int_0^T I_{A1}^2 \cos^2(\omega_1 t) + I_{A2}^2 \cos^2(\omega_2 t) - 2 I_{A1} I_{A2} \cos(\omega_1 t) \cos(\omega_2 t) dt$$

$$P = P_1 + P_2$$

~~$I_{A1} I_{A2} (\cos(\omega_1 + \omega_2) + \cos(\omega_1 - \omega_2))$~~ \emptyset

END OF MATERIAL FOR MIDTERM EXAM 1

Chapters 10, 11, 13

Homeworks 1-5

Quiz 1 & 2

Experiment 1 

Lectures 1-16 (& 19)