


# Experiment 1

- Due Friday, March 25<sup>th</sup>, prior to start of class
  - Start on prelab now
  - Procedure “Background” is review of content (less transformers)
- Prelab
  - Must be completed, individually, prior to labwork
  - Submitted to canvas
  - Design problem – informal
- Labwork
  - Begin *after* completing prelab
  - Completed in groups of 2-3
  - Should take ~2-3 hours
    - If you’ve completed and understood the prelab
    - No mistakes wiring
  - Either
    - Bring ECE 201/202 parts kit and USB drive to save oscilloscope waveforms
    - Check-out and use Analog Discovery Studio (with some modifications)
- Lab Reports
  - Completed as a group
  - General guidelines document posted to website





# Experiment 1 Goal

Table II: Starting Values for System Design



$f$	$L$	$k$ (@ 9mm)	$R_L$	$V_{th}, R_{th}$
300 kHz	25 $\mu\text{H}$	0.32	25 $\Omega$	10 V, 50 $\Omega$

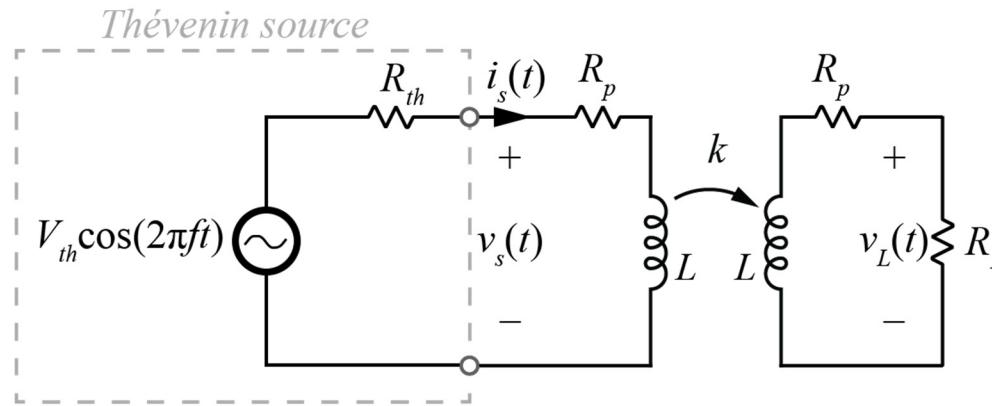


# WPT Setup

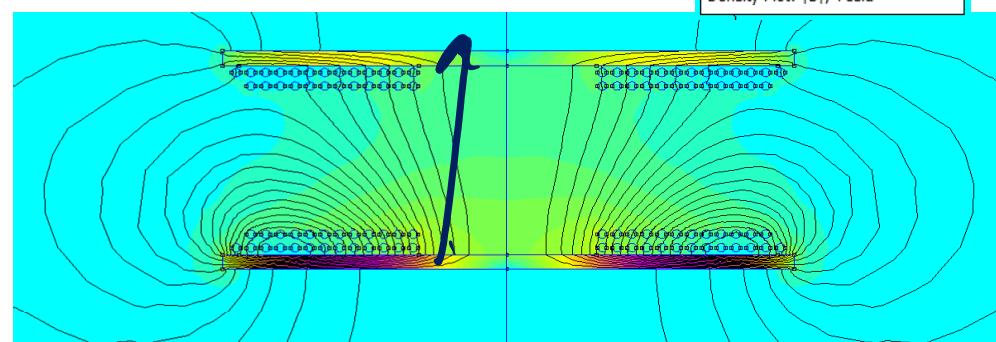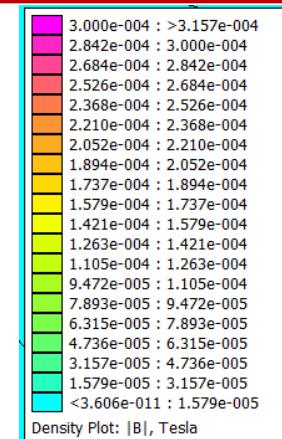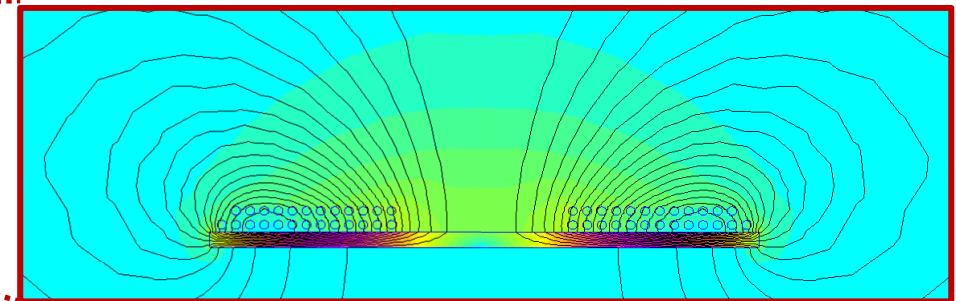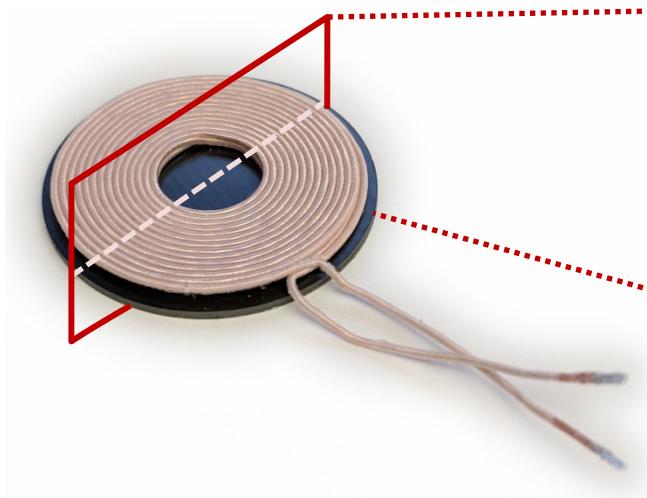

# Initial Setup

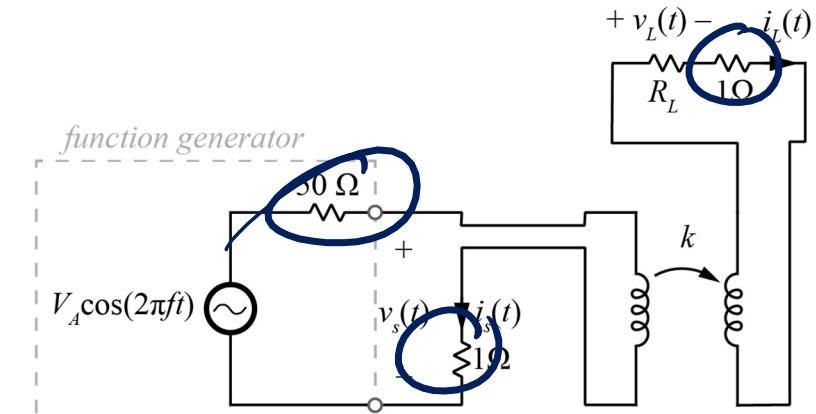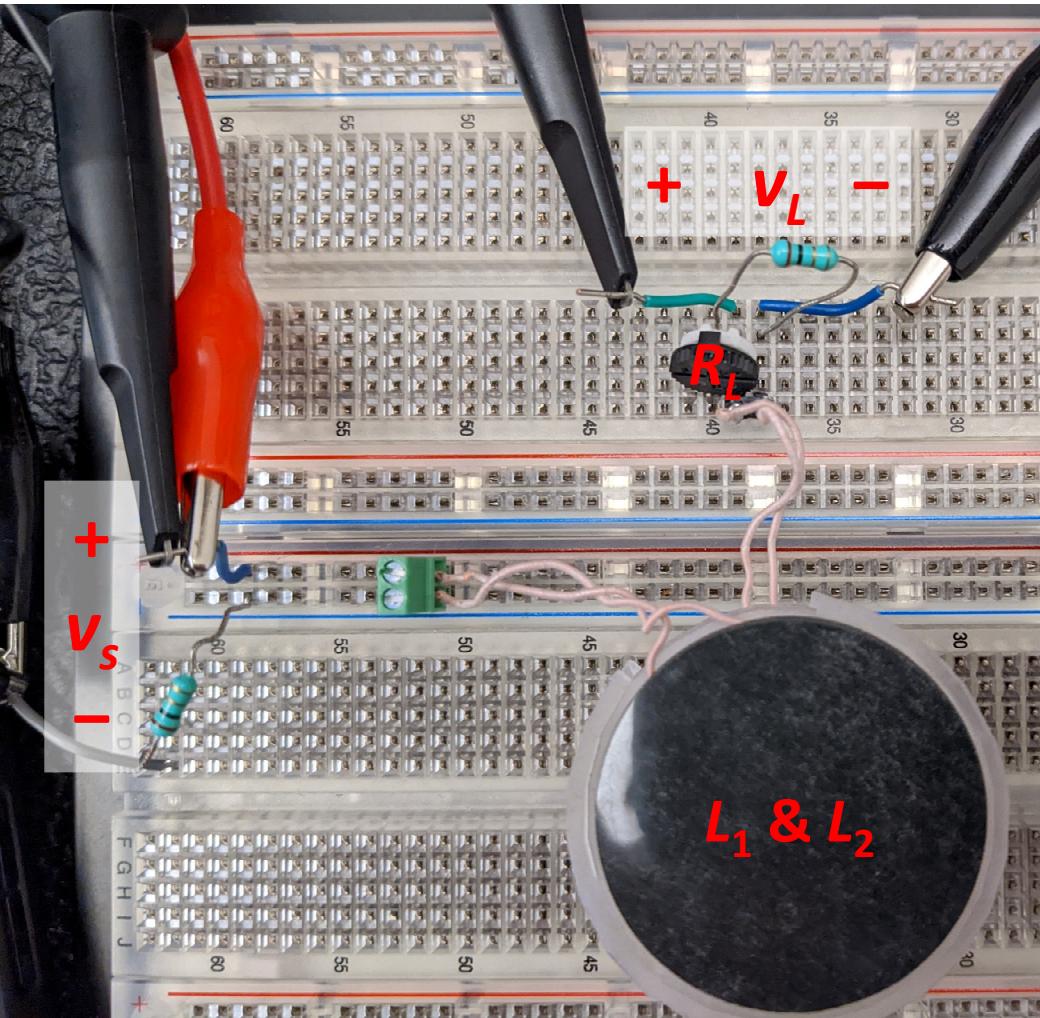

# Initial Calculations

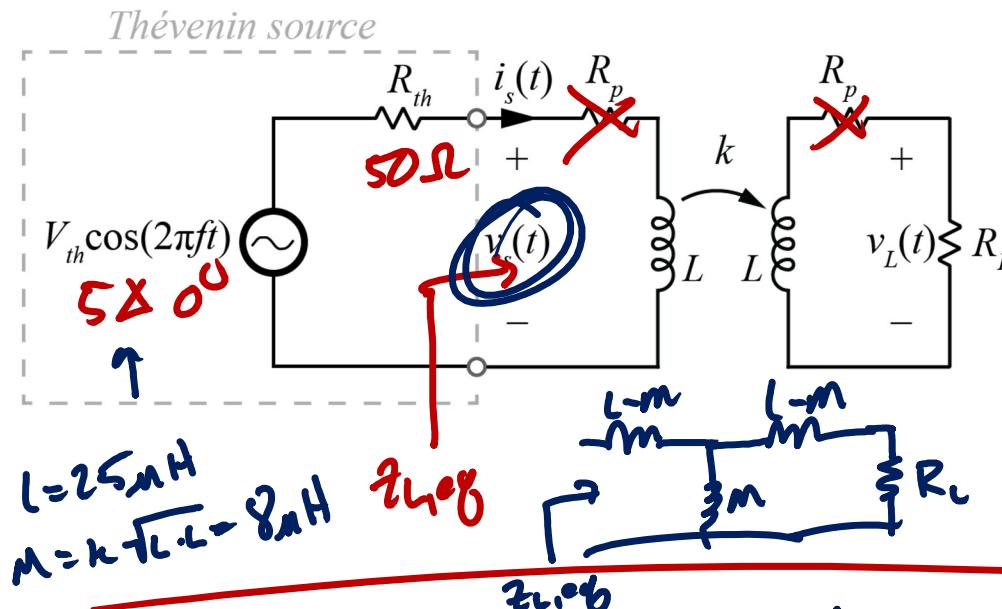

for max power  
 $z_{L,eq} = 50\Omega$

maximum possible power

$$P_{max} = \left(\frac{V_{th}}{\sqrt{2}}\right)^2 \cdot \frac{1}{2} = \frac{1}{2} \cdot \frac{(V_{th})^2}{2 \cdot 50\Omega} = 62.5mW$$

$$z_{L,eq} = \frac{j\omega(L-m)}{2 + j4\sqrt{3}\Omega}$$

$$R_L = 25\Omega$$

$$\omega = 2\pi 300\text{kHz}$$

$$V_s = (58.0^\circ) \frac{z_{L,eq}}{z_{L,eq} + 50} = 3.2 \times 47^\circ V$$

$$S_s = \frac{1}{2} V_s I_s^* = \frac{1}{2} V_s \left(\frac{V_s}{z_{L,eq}}\right)^* = \underline{5.4mW} + \underline{j118mVR}$$

