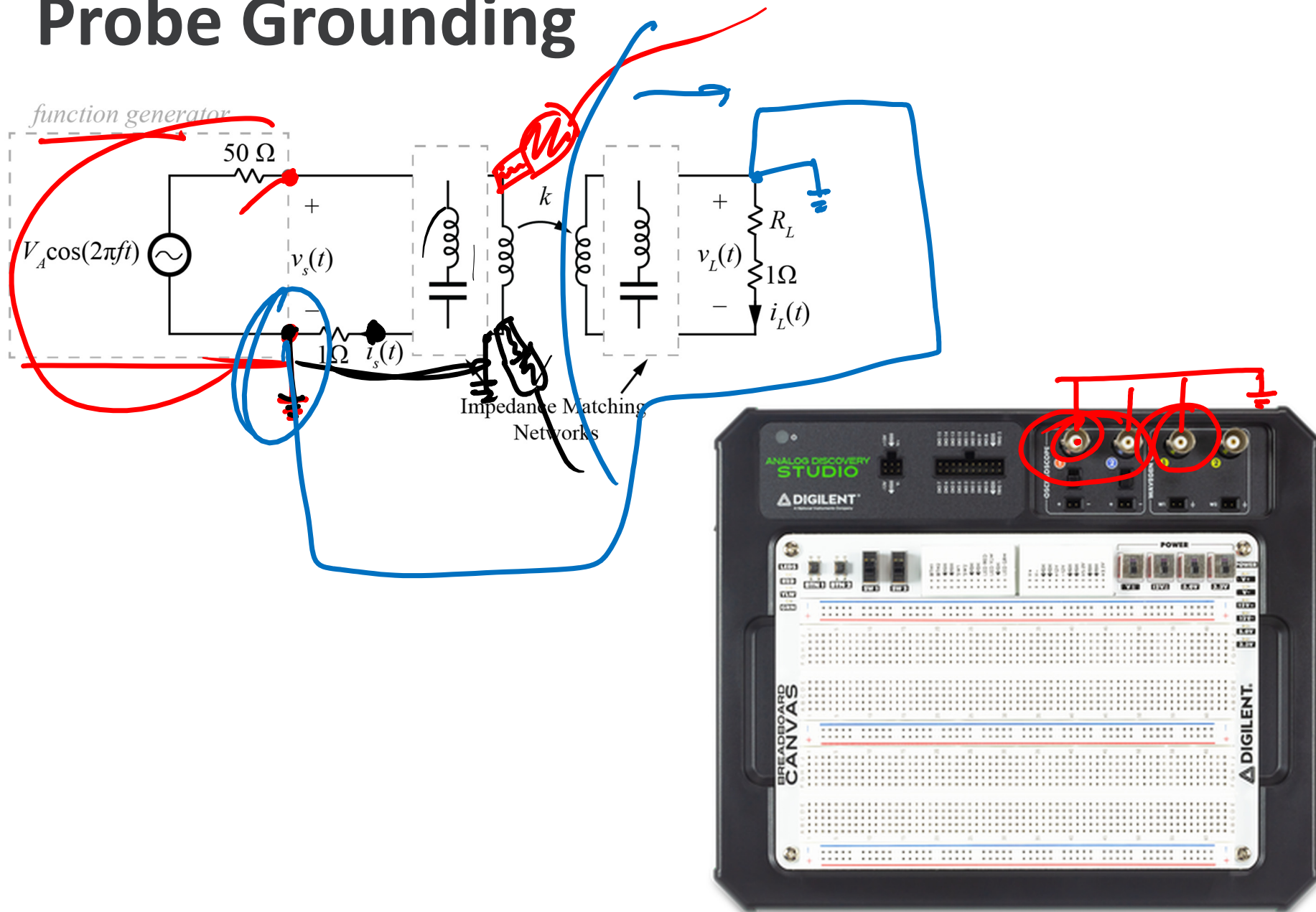


# Probe Grounding




# LTSpice Parameter Sweeps

- Tutorial on website
  - linked from Experiment 1 on Assignments page
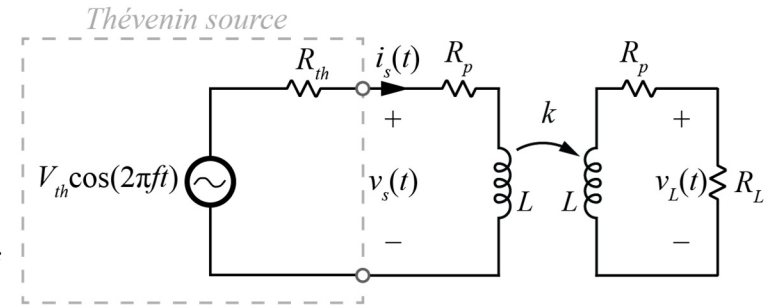
# Elementwise Matrix Calculations in MATLAB

```


→ R = 1:1:50; 50 pts
→ w = 2*pi*linspace(100e3,500e3,100); 100 pts
[w,R] = meshgrid(w,R);
→ Zeq = 1j*w*(L-M)+1./(1./(1j*w*M) + 1./(1j*w*(L-M) + R));
contourf(R,w/2/pi/1000,angle(Zeq)*180/pi);
cb = colorbar;
    
```



```

ylabel('Frequency [kHz]');
xlabel('Load Resistance [\Omega]');

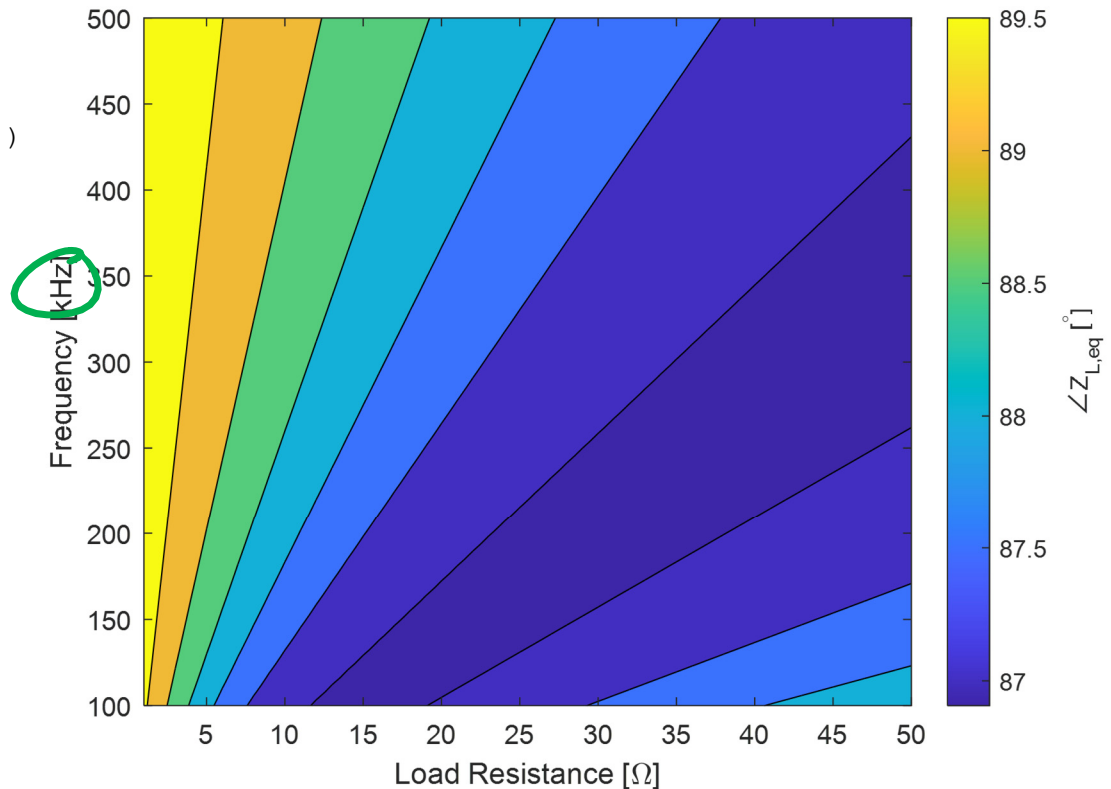ylabel(cb, '\angle Z_{L,eq} [^\circ]')
    
```



# Limitations of Phasor Analysis

- ① single frequency
- ② sinusoids only
- ③ only steady-state waveforms
- ④ LTI systems only

Developed by looking at particular solution of circuit ODE under sinusoidal inputs

Next: develop methods to expand on ①-③

- Approaches:
- ① use superposition (in time domain) to produce multiple single-frequency circuits  
→ Frequency Response Ch 15
  - ② Find a way to decompose any signal into a sum of sinusoids  
→ Fourier Series & Transform Ch 17
  - ③ Need to include exponentials in signals  
→ Laplace Transform Ch 14

# Frequency Response

$$\underline{V_o} = \underline{V_I} \frac{z_c}{z_r + z_c} = \underline{V_I} \frac{-j/\omega c}{R - j/\omega c}$$

$$\underline{V_o} = \underline{V_I} \frac{1}{j\omega RC + 1}$$


Frequency Response

$$\frac{\underline{V_o}}{\underline{V_I}} = \frac{1}{j\omega RC + 1} = \underline{H(j\omega)}$$

$$H(j\omega) = |H(j\omega)| \angle H(j\omega)$$

$$\underline{V_o} = \underline{V_I} \cdot H(j\omega) = |\underline{V_I}| \cdot |H(j\omega)| \angle [\angle \underline{V_I} + \angle H(j\omega)]$$
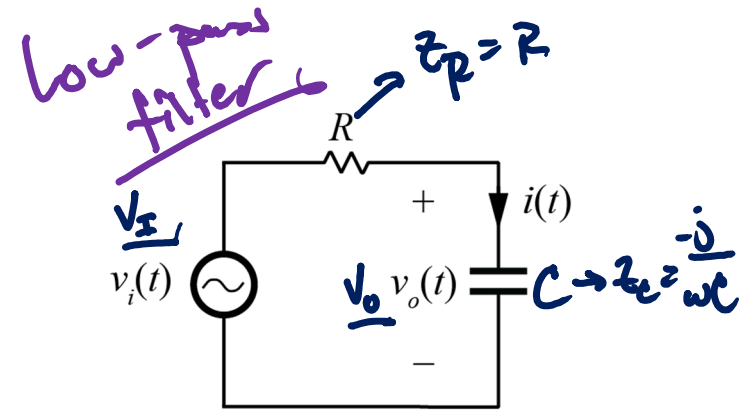
$$H(j\omega) = \frac{1}{j\omega RC + 1} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle \tan^{-1}(-\omega RC)$$



= Frequency Response  $\rightarrow$  some complex number that varies with  $\omega$  and describes the  $t$ - $\omega$  relationship of the circuit or system.

