

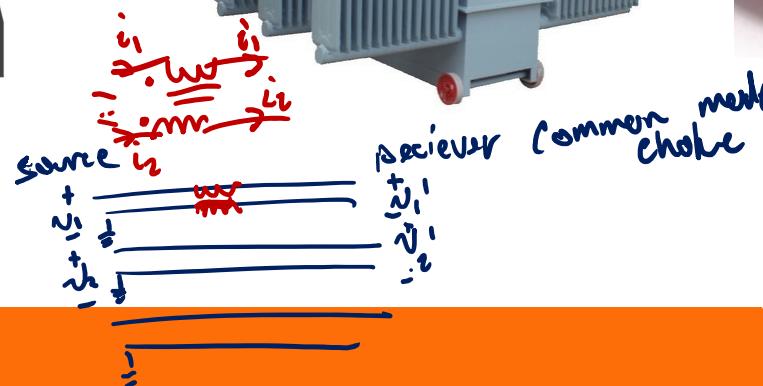
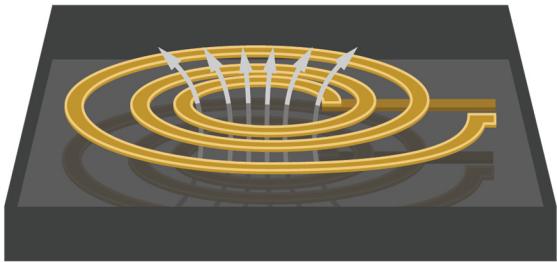
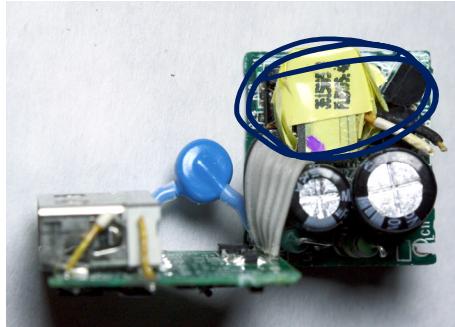
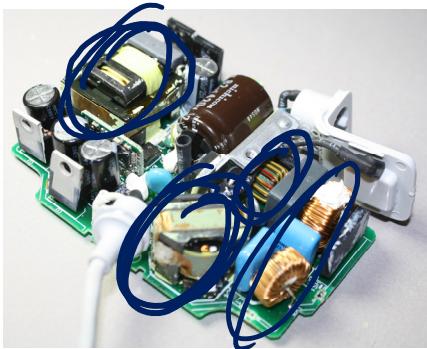



Applications of Coupled Inductors

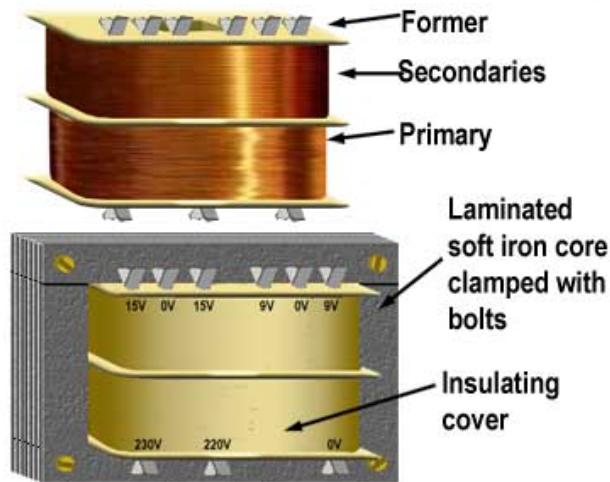


Example Transformer

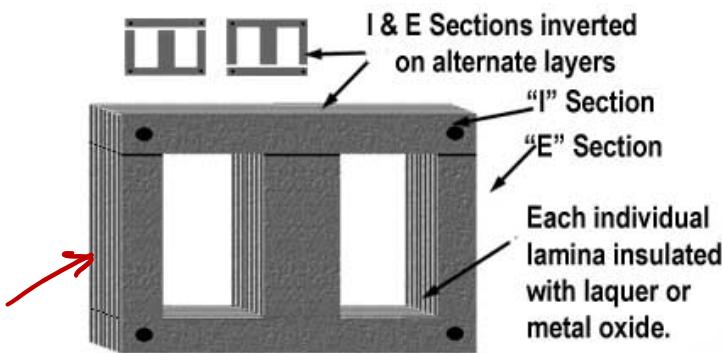

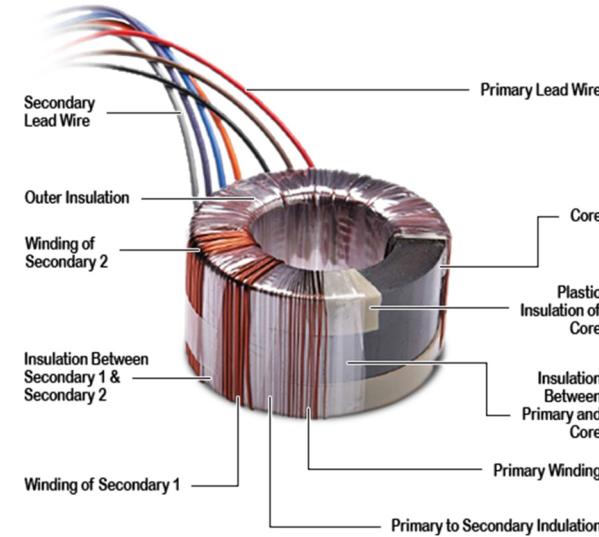http://www.learnabout-electronics.org/ac_theory/transformers03.php








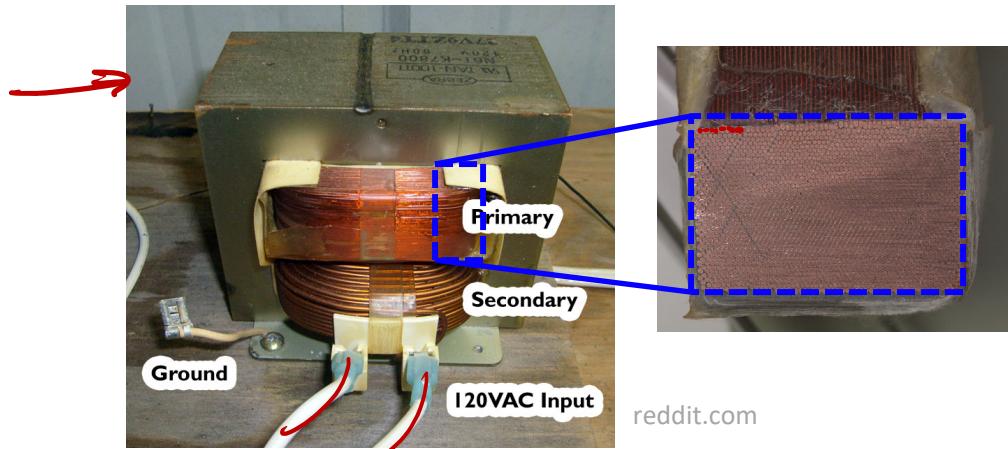
<https://www.altrancorp.com/products/toroidal-power-transformers/>



[reddit.com](https://www.reddit.com)

Transformer Reflection

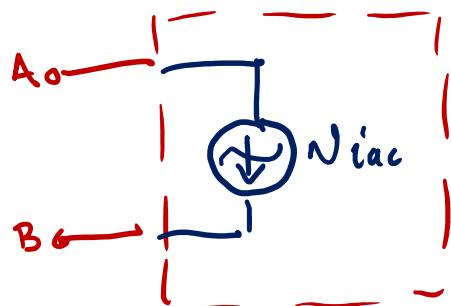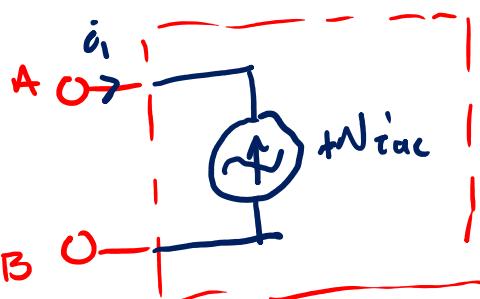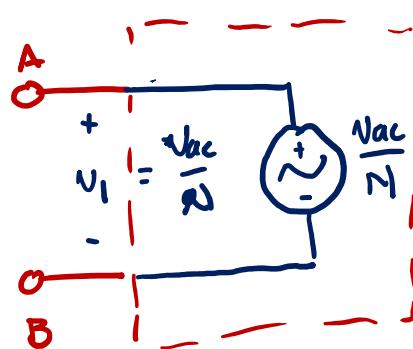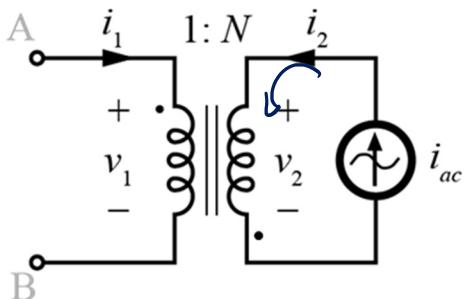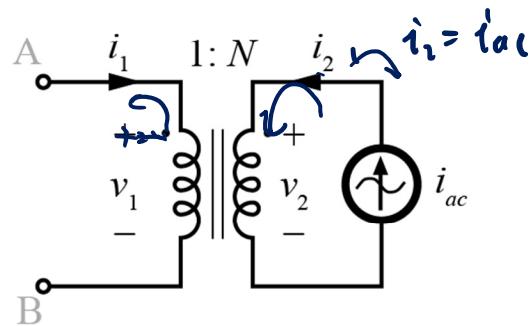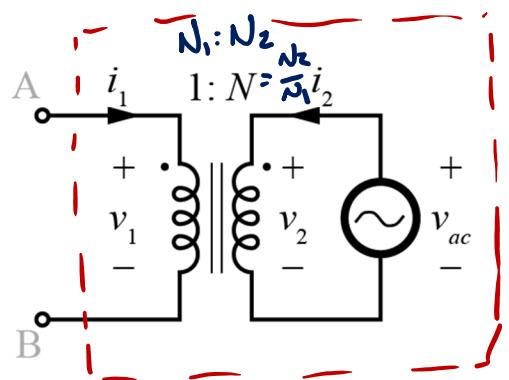

$$\frac{N_1}{N_2} = \frac{N_2}{N_1}$$


$$N_1 i_1 + N_2 i_2 = \phi$$



$$\frac{v_1}{1} = \frac{v_2}{N}$$

$$1 \cdot i_1 + N \cdot i_2 = \phi$$

$$i_1 + N i_2 = \phi$$

$$i_1 = -N i_2$$

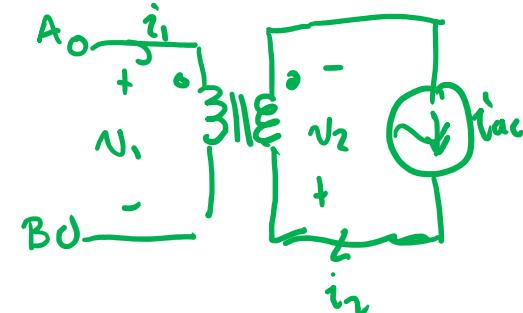

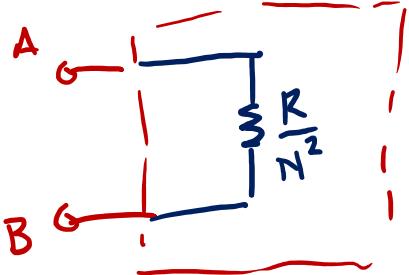
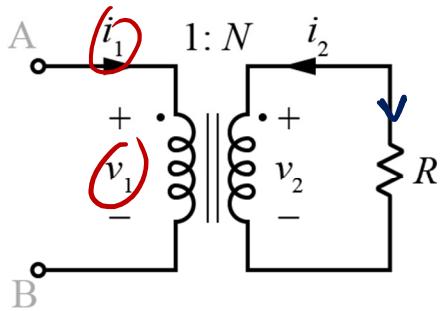


$$v_1 = \frac{v_2}{N} + i_1 + N i_2 = 0$$

$$v_2 = (-i_2) R$$

$$N v_1 = \left(-\frac{i_1}{N} \right) R$$



$$v_1 = i_1 \frac{R}{N^2}$$

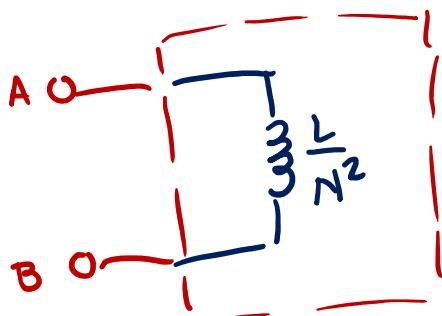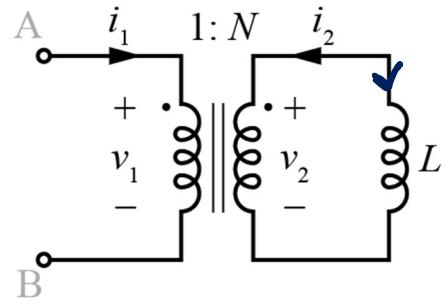

$$v_2 = L \frac{d}{dt} (-i_2)$$

$$N v_1 = L \frac{d}{dt} \left(\frac{i_1}{N} \right)$$

$$v_1 = \frac{L}{N^2} \frac{di_1}{dt}$$

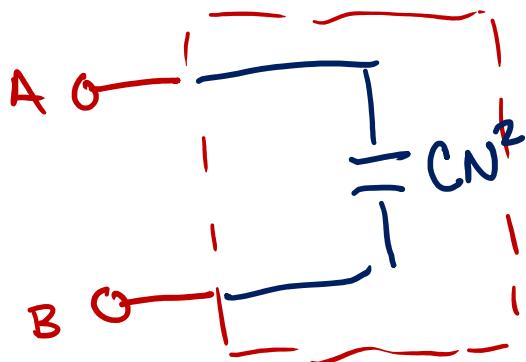
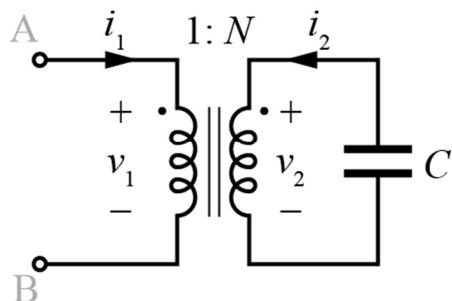


$$-i_2 = C \frac{dNv_2}{dt}$$



$$\frac{i_1}{N} = C \frac{d}{dt} N v_1$$

$$i_1 = N^2 C \frac{dv_1}{dt}$$


Example Circuit Simplification

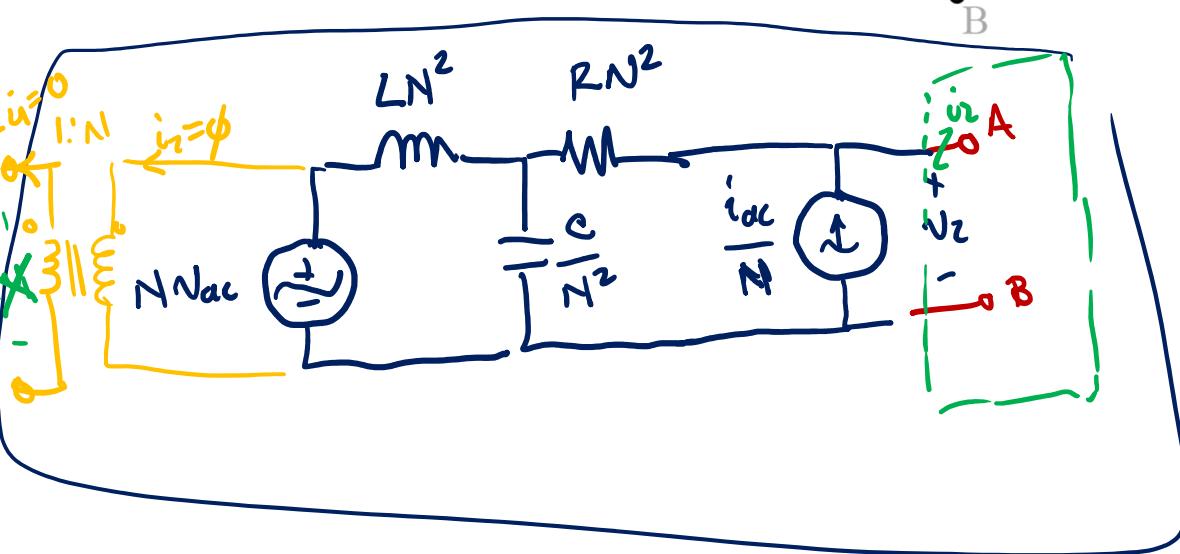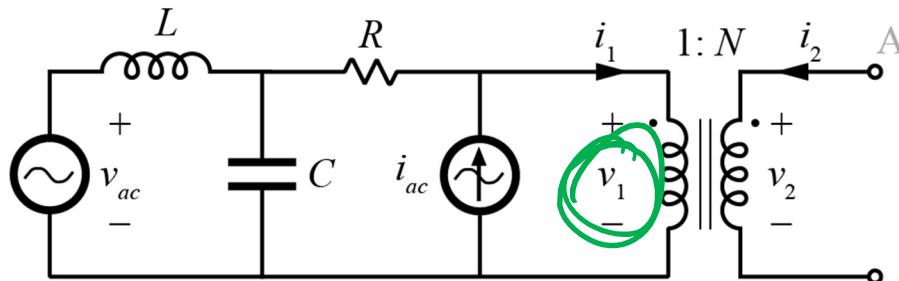


Equivalent Circuits

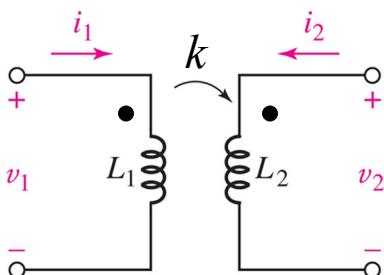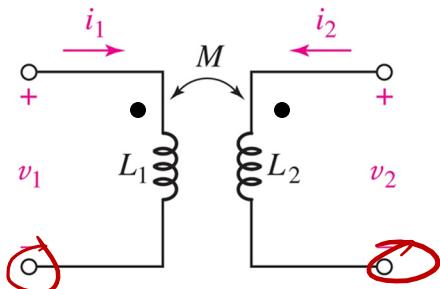
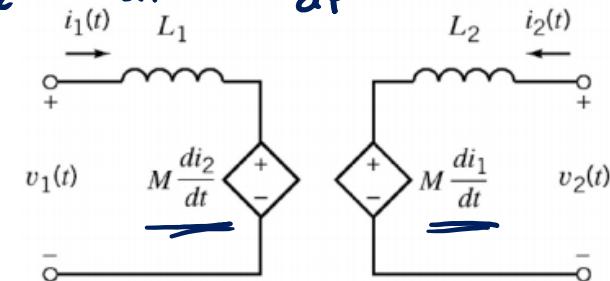
$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$




T-Network

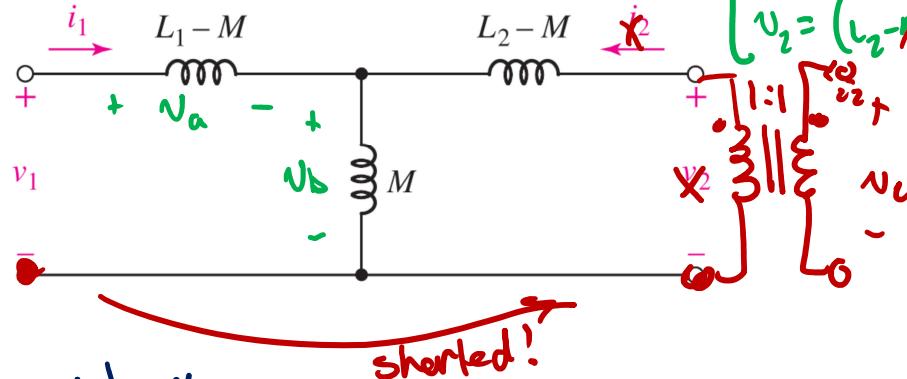

$$\begin{cases} v_1 = (L_1 - M) \frac{di_1}{dt} + M \frac{d}{dt}(i_1 + i_2) \\ v_2 = (L_2 - M) \frac{di_2}{dt} + M \frac{d}{dt}(i_1 + i_2) \end{cases}$$

cantilever model

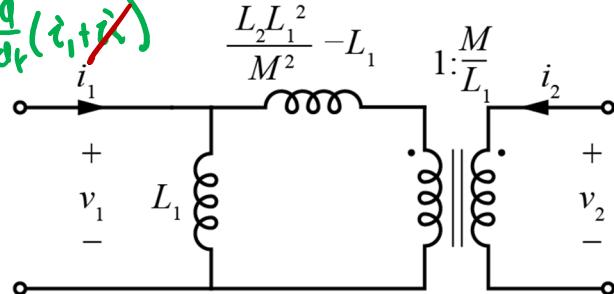

Π -Network

