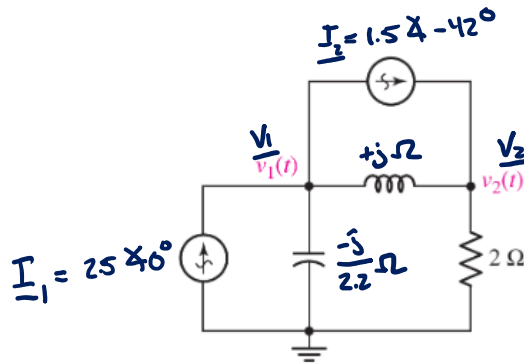


FIGURE 10.59

49. Referring to the circuit of Fig. 10.59, employ phasor-based analysis techniques to determine the two nodal voltages.



By superposition, with \underline{I}_1 on

$$\underline{V}_1 = \left(\underline{I}_1 \cdot \frac{-j}{2.2} \Omega \right) \frac{2 + j \Omega}{2 + j(1 - \frac{1}{2.2}) \Omega} - \left(\underline{I}_2 \cdot \frac{-j}{2.2} \Omega \right) \left(\frac{j \Omega}{2 + j(1 - \frac{1}{2.2}) \Omega} \right)$$

↑ Thevenin equivalent ↑ Voltage divider ↑ Current divider

$$\underline{V}_2 = \left(\underline{I}_1 \cdot \frac{-j}{2.2} \Omega \right) \frac{2 \Omega}{2 + j(1 - \frac{1}{2.2}) \Omega} + \underline{I}_2 \cdot (2 \Omega) \left(\frac{j \Omega}{2 + j(1 - \frac{1}{2.2}) \Omega} \right)$$

$$v_1(t) = 0.27 \cos(10t - 86^\circ)$$

$$v_2(t) = 0.269 \cos(10t - 16.5^\circ)$$