

Circuit Solution Tips

- Order of analysis
 - Series/parallel equivalents
 - Source transformations
 - Transformer reflection
 - KVL/KCL equations + Element Equations
 - Node Voltage / Mesh Current Analysis (if necessary)
- Stay symbolic as long as possible
 - Define new equivalent variables as necessary

Form of the solution

$$\sum_{i=0}^N b_i \frac{d^i}{dt^i} v_o(t) = \sum_{i=0}^M a_i \frac{d^i}{dt^i} v_i(t)$$

In phasor domain $\frac{d}{dt} \rightarrow (j\omega)$

$$\sum_{i=0}^N b_i (j\omega)^i \underline{v}_o = \sum_{i=0}^M a_i (j\omega)^i \underline{v}_i$$

from/ to
any voltage or
current in the
circuit

→

$$\underline{v}_o = \underline{v}_i \left(\frac{\sum_{i=0}^M a_i (j\omega)^i}{\sum_{i=0}^N b_i (j\omega)^i} \right)$$

↑
 $H(\omega)$

Chapter 11

AC CIRCUIT POWER ANALYSIS

LTI Systems (L7)

For a function $f(\cdot)$

Linearity

if: $v_{o,1}(t) = f(v_{i,1}(t))$ $v_{o,2}(t) = f(v_{i,2}(t))$

then: $av_{o,1}(t) + bv_{o,2}(t) = f(av_{i,1}(t) + bv_{i,2}(t))$

superposition applies

Time Invariance

if: $v_o(t) = f(v_i(t))$


then: $v_o(t - T) = f(v_i(t - T))$

LTI: $v_x(t) + v_y(t), \quad \alpha v_x(t), \quad \frac{dv_x(t)}{dt}, \quad \int_0^t v_x(t) dt$ (neglecting ICs)

Not LTI: $v_x(t) \cdot v_y(t), \quad v_x(t)^2, \quad |v_x(t)|$ \rightarrow *power isn't a linear calculation*


LTI

Average Power

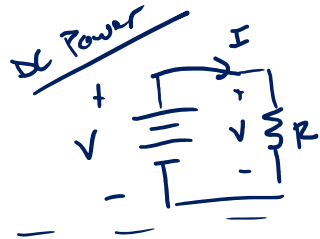

$P_R = V \cdot I \rightarrow$ Generally true for any 2-terminal element

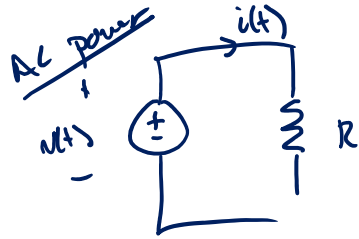for a resistor $V = IR$
 $P_R = I^2 R = \frac{V^2}{R}$



$P_R(t) = v(t) \cdot i(t) \rightarrow$ Generally true of all 2-terminal elements

for a resistor $P_p(t) = i(t)^2 R = \frac{v(t)^2}{R}$

In any case, power calculation is not LTI


Average Power

Average power defined over some time interval $t \in [t_1, t_1 + T]$

capital "P" denotes average $\rightarrow P = \frac{1}{T} \int_{t_1}^{t_1+T} p(t) dt$

Average power over all time
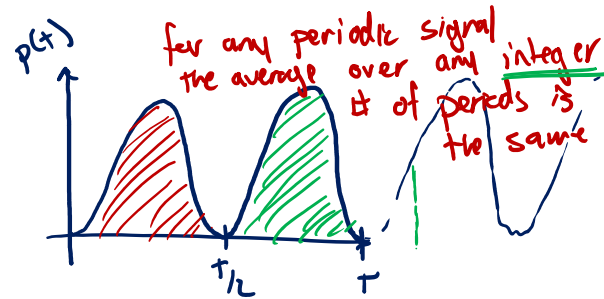
$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$$



Power in a Resistor

Average power in a resistor with periodic (e.g. sinusoidal) sources

$$P_R = \frac{1}{T} \int_0^T P_R(t) dt = \frac{1}{T} \int_0^T i(t)^2 R dt$$
$$= R \frac{1}{T} \int_0^T i(t)^2 dt$$

$$P_R = R \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}^2$$

$$P_R = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

rms is 'root mean squared'

Define rms

$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

Note: Book calls this "effective" instead of rms

$$I_{eff} = I_{rms} \quad V_{eff} = V_{rms}$$

RMS of a sinusoid

$$\omega = 2\pi f \quad T = \frac{1}{f} = \frac{2\pi}{\omega}$$

$$i(t) = I_A \cos(\omega t + \phi)$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T (I_A \cos(\omega t + \phi))^2 dt}$$

$$I_{rms}^2 = \frac{1}{T} \int_0^T I_A^2 \cos^2(\omega t + \phi) dt$$

$$I_{rms}^2 = \frac{1}{T} I_A^2 \frac{1}{2} \int_0^T (1 + \cos(2\omega t + 2\phi)) dt$$

$$I_{rms}^2 = \frac{1}{T} I_A^2 \frac{1}{2} \left[t + \sin(2\omega t + 2\phi) \frac{1}{2\omega} \right] \Big|_0^{T = \frac{2\pi}{\omega}}$$

$$I_{rms}^2 = \frac{1}{T} I_A^2 \frac{1}{2} \left[\left(\frac{2\pi}{\omega} - 0 \right) + \frac{1}{2\omega} \left(\cancel{\sin(4\pi + 2\phi)} - \sin(2\phi) \right) \right]$$

$$I_{rms}^2 = \frac{\cancel{\omega}}{\cancel{2\pi}} I_A^2 \frac{1}{2} \frac{\cancel{2\pi}}{\cancel{\omega}}$$


$$I_{rms}^2 = \frac{I_A^2}{2}$$

$$I_{rms} = \frac{I_A}{\sqrt{2}}$$

for any sinusoidal signal

trig identity
 $\cos^2(\theta) = \frac{1}{2}(1 + \cos 2\theta)$

Power with Sinusoidal Sources

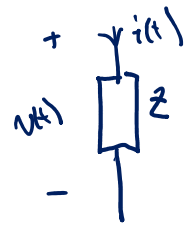

In steady-state with single-frequency sinusoidal sources @ ω

$$\begin{aligned} v(t) &\rightarrow \underline{V} = V_A e^{j\phi_V} \\ i(t) &= \underline{I} = I_A e^{j\phi_I} \end{aligned}$$

$$\underline{V} = \underline{I} Z$$

$$\rightarrow Z = \frac{\underline{V}}{\underline{I}} = \frac{V_A e^{j\phi_V}}{I_A e^{j\phi_I}} = \frac{V_A}{I_A} e^{j(\phi_V - \phi_I)}$$

power: since power is not LTI, we don't know how to calculate power w/ phasors
Not $\underline{V} \cdot \underline{I} \rightarrow$ go back to time domain to calculate

Trig identity: $2 \cos \theta \cos \psi = \cos(\theta + \psi) + \cos(\theta - \psi)$

$$p(t) = i(t) \cdot v(t) = I_A \cos(\omega t + \phi_I) \cdot V_A \cos(\omega t + \phi_V)$$

$$= \frac{I_A V_A}{2} \left(\underbrace{\cos(2\omega t + \phi_I + \phi_V)}_{\text{sinusoid @ } 2\omega} + \underbrace{\cos(\phi_I - \phi_V)}_{\text{constant (not time-varying)}} \right)$$

sinusoid @ 2ω

constant (not time-varying)

Average power

$$P_z = \frac{I_A V_A}{2} \cos(\phi_I - \phi_V) = \frac{I_A V_A}{2} \cos(\phi_Z) = V_{rms} I_{rms} \cos(\phi_Z)$$