



# Average Power

# Power in a Resistor

# RMS of a sinusoid

# Power with Sinusoidal Sources

# Power with Sinusoidal Sources

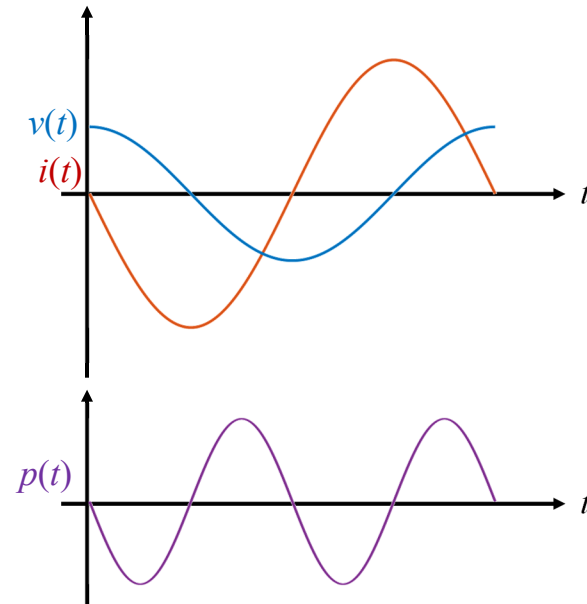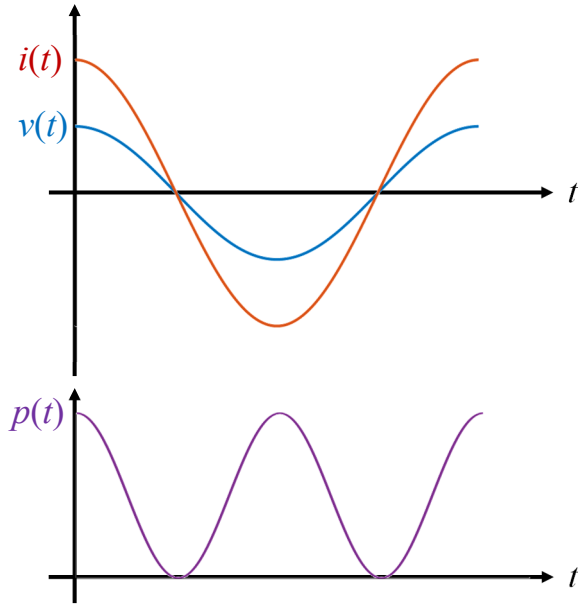

# Complex Power