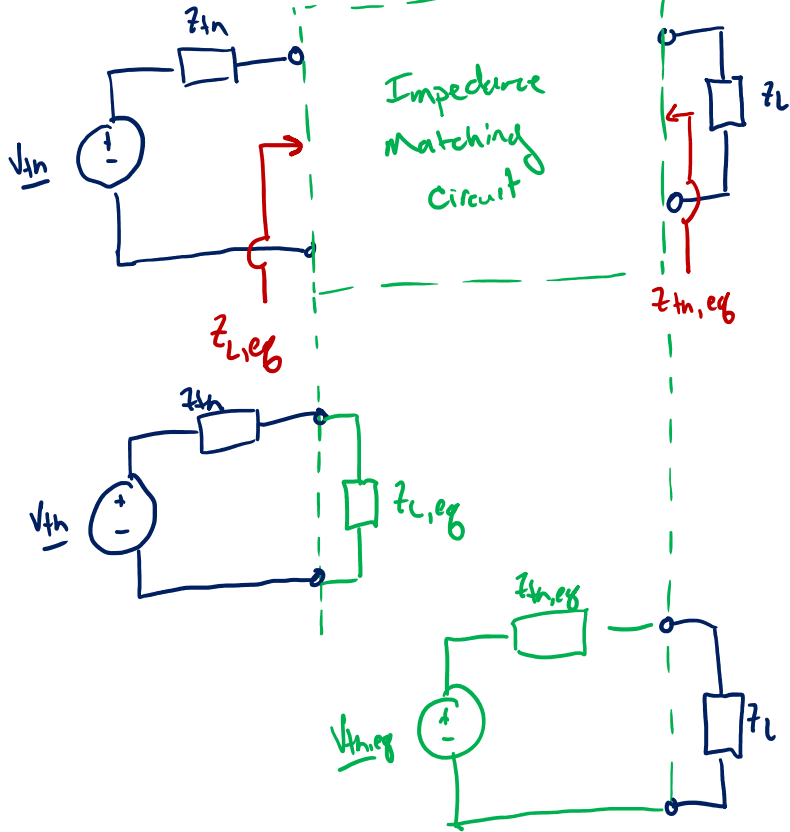




Impedance Matching



Impedance matching goals

- Maximize power transfer $\rightarrow Z_L = Z_{th,eq}^*$
- Minimize distortion $\rightarrow Z_L = Z_{th,eq}$
- Maximize efficiency $\rightarrow \text{Re}\{Z_{th,eq}\} \ll \text{Re}\{Z_L\}$
- Maximize Quality Factor $\rightarrow \text{Im}\{Z_{L,eq}\} = \phi$


Example Matching Circuits

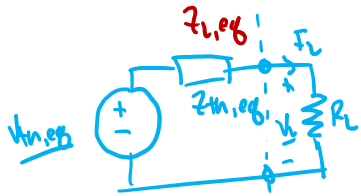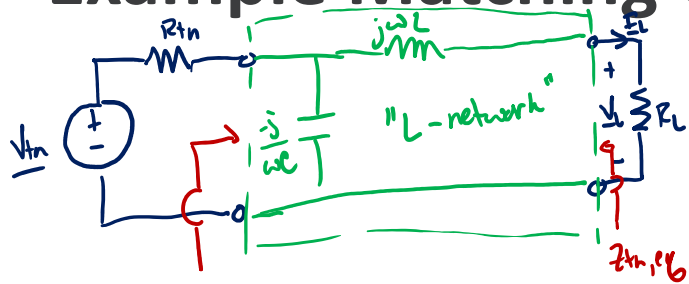

$$V_{th,eq} = \frac{V_{th}}{R_{th}} (R_{th} \parallel -jX_c)$$

$$X_c = \sqrt{\frac{R_L R_{th}^2}{R_{th} - R_L}}$$
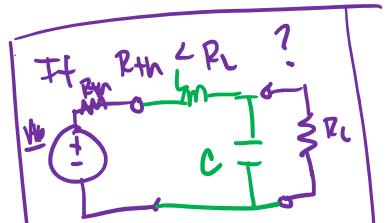
$$X_L = \frac{X_c R_{th}^2}{R_{th}^2 + X_c^2}$$



Just flip the two parts

transformer can be used for scaling

$$Z_{th,eq}$$

$R_{th} > R_L$, but want maximum possible power to R_L

using "L-network" set

$$Z_L = Z_{th,eq} \quad \text{or} \quad Z_{L,eq} = Z_{th}$$

$$Z_L = j\omega L = jX_L, \quad X_L = \omega L \quad \Bigg| \quad Z_C = \frac{j}{\omega C} = -jX_C, \quad X_C = \frac{1}{\omega C}$$

$$Z_{th,eq} = (R_{th} \parallel -jX_C) + jX_L$$

$$= \frac{-jX_C R_{th}}{R_{th} - jX_C} \frac{(R_{th} + jX_C)}{(R_{th} + jX_C)} + jX_L$$

$$= \frac{jX_C R_{th}^2 + X_C^2 R_{th}}{R_{th}^2 + X_C^2} + jX_L$$

$$= \frac{X_C^2 R_{th}}{R_{th}^2 + X_C^2} + j \left[X_L - \frac{X_C R_{th}}{R_{th}^2 + X_C^2} \right]$$


$$\text{Re}\{Z_{th,eq}\} = R_L$$

$$\text{Im}\{Z_{th,eq}\} = 0$$

$X_c \rightarrow \infty \quad \text{Re}\{Z_{th,eq}\} \rightarrow R_{th}$
 $X_c \rightarrow 0 \quad \text{Re}\{Z_{th,eq}\} \rightarrow 0$ } this circuit requires R_{th}

Note: In lecture, the line below was copied incorrectly. R_{th} is squared, not X_c , in the imaginary term

Matching Example

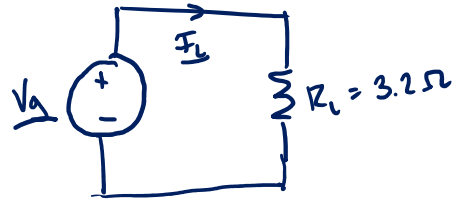

$$\omega = 2\pi 60 \text{ Hz}$$

$$V_g = 170 \angle 0^\circ \text{ V}$$

residential wall outlet is
 $120 \text{ V}_{\text{rms}} = 170 \text{ V}_{\text{pk}} @ 60 \text{ Hz}$

with $R_L = 3.2 \Omega \approx$ equivalent model of plugged-in load

$$\frac{I_L}{L} = \frac{V_g}{R_L} = \frac{170 \angle 0^\circ}{3.2} = 53 \angle 0^\circ \text{ A}$$

$$S_g = \frac{1}{2} V_g I_L = \frac{1}{2} (170 \angle 0^\circ) (53 \angle 0^\circ) = 4.5 \text{ kW} + j0 \text{ VAR} = 4.5 \angle 0^\circ \text{ kVA}$$

