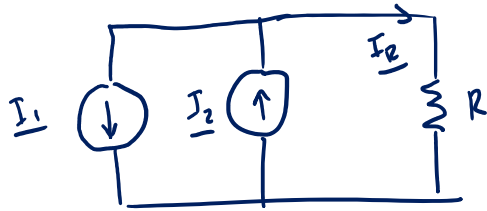


Power Spectrum



$\underline{I}_1 = \underline{I}_2$ By inspection $\underline{I}_R = \phi$
Therefore $P_R = \phi$


Correctly apply superposition:

$$\underline{I}_R = \underline{I}_{R1} + \underline{I}_{R2} = (-\underline{I}_1) + \underline{I}_2 = \phi$$

Incorrect to apply superposition to power (because it's nonlinear)

If I did it anyway = $P_R = P_1 + P_2 = I_{1,rms}^2 R + I_{2,rms}^2 R \neq \phi$ (wrong)

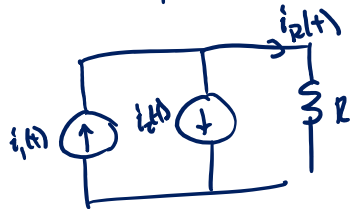However, this will work if I have two sources at different frequencies



$$i_1(t) = I_{A1} \cos(\omega_1 t) \quad i_2(t) = I_{A2} \cos(\omega_2 t), \quad \omega_1 \neq \omega_2$$

$$P_R(t) = i_R(t)^2 R = (i_1(t) - i_2(t))^2 R$$

$$P_R = \frac{1}{T} \int_0^T i_R(t)^2 R dt = \frac{1}{T} \int_0^T (I_{A1} \cos(\omega_1 t) + I_{A2} \cos(\omega_2 t))^2 R dt$$

$$= \frac{R}{T} \int_0^T I_{A1}^2 \cos^2(\omega_1 t) + I_{A2}^2 \cos^2(\omega_2 t) + 2 I_{A1} I_{A2} \cos(\omega_1 t) \cos(\omega_2 t) dt$$

$$= I_{1,rms}^2 R + I_{2,rms}^2 R$$

(only for $\omega_1 \neq \omega_2$)

$\cancel{I_{A1} I_{A2} (\cos(\omega_1 t + \omega_2 t) + \cos(\omega_1 t - \omega_2 t))}$ due to averaging

Limitations of Phasor Analysis

- ① single frequency
- ② sinusoids only
- ③ only steady-state response
- ④ LTI systems only

Reminder at the course: develop techniques to address ①-③

Approaches:

① use superposition in the time-domain
→ Ch 15 on Frequency Response

② Express arbitrary signal as a sum of (infinite) sinusoids
→ Ch 17 Fourier Series / Transform

③ Include exponentials with our sinusoids
→ Ch 14 Laplace Transform

Limitations of Phasor Analysis

Frequency Response

phasor Analysis:

$$\underline{V}_O = \underline{V}_I \frac{z_c}{z_c + z_R} = \underline{V}_I \frac{-j/\omega C}{-j/\omega C + R} = \underline{V}_I \left(\frac{1}{1 - j\omega CR} \right)$$


$$\underline{V}_O = \underline{V}_I \left(\frac{1}{1 - j\omega CR} \right) = \underline{V}_I \underbrace{H(j\omega)}$$

→ tells us, at any ω , how does circuit alter input at the output

Any LTI circuit has $\underline{V}_O = \underline{V}_I H(j\omega)$

In polar form


$$\begin{aligned} V_{OA} \angle \phi_{Vo} &= (V_{IA} \angle \phi_{Vi}) \cdot |H(j\omega)| \angle \phi(H(j\omega)) \\ &= \underbrace{(V_{IA} |H(j\omega)|)}_{\text{Magnitudes multiply}} \angle \underbrace{\phi_{Vi} + \phi(H(j\omega))}_{\text{Phases add}} \end{aligned}$$

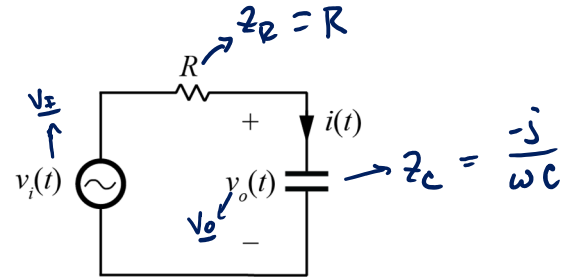

$$H(j\omega) = \frac{1}{1 - j\omega RC}$$

$$\text{Gain: } |H(j\omega)| = \frac{1}{\sqrt{1^2 + (\omega RC)^2}}$$
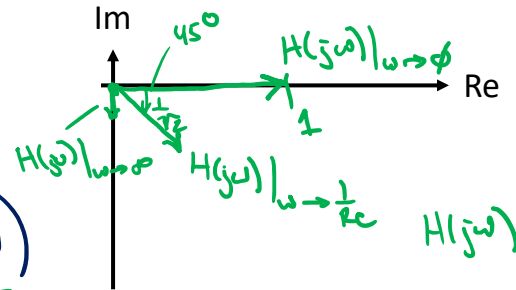
$$\text{Phase: } \angle H(j\omega) = 0 - \tan^{-1}\left(\frac{\omega RC}{1}\right) = -\tan^{-1}(\omega RC)$$



Frequency Response


example

$$R = 10$$


$$C = 10\text{nF}$$

$$\frac{1}{RC} = 10\text{ k rad/sec} = 1.6\text{ kHz}$$

Gain

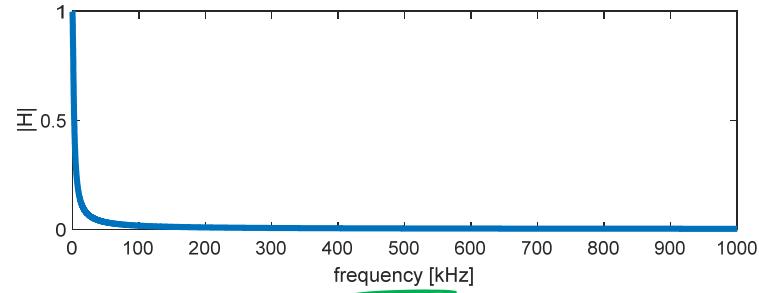

Phase

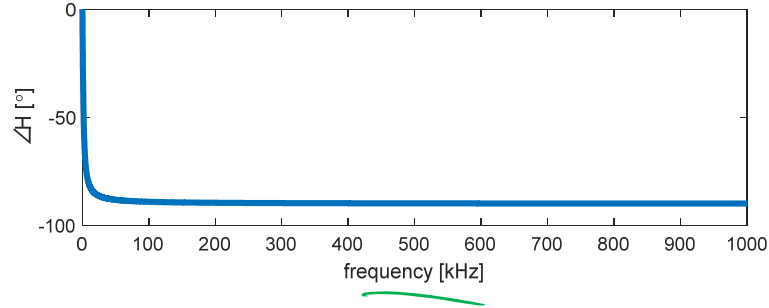

Bode Plot – Frequency Response

