


# Symmetry in Fourier Series

Even functions

$$f(t) = f(-t)$$

Typo in the book  
in table 17.1

$$b_n = 0$$

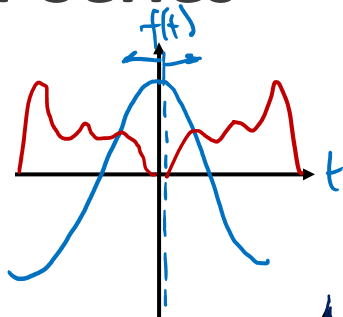


All apply with  
the DC component  
removed

Odd functions

$$f(t) = -f(-t)$$


$$a_n = 0$$

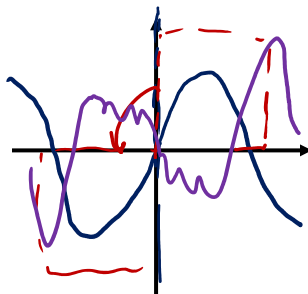

Half-wave symmetric functions


$$f(t + \frac{T}{2}) = -f(t)$$

$$a_n, b_n = 0 \text{ for even } n$$

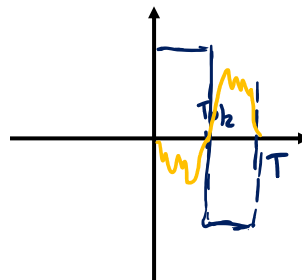


# Application: Digital Communication

Low Pass Filter

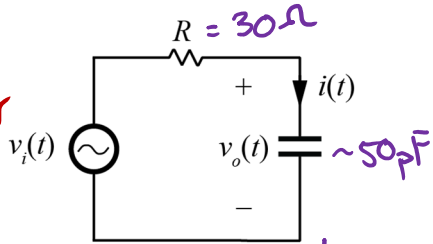


$$H(j\omega) = \frac{V_o}{V_i}$$



Gain

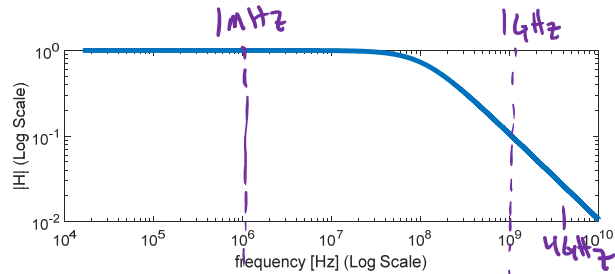

Phase

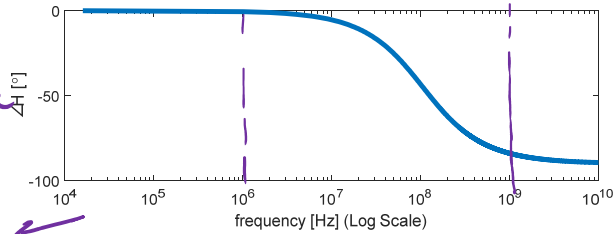

DC ←

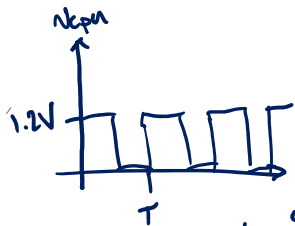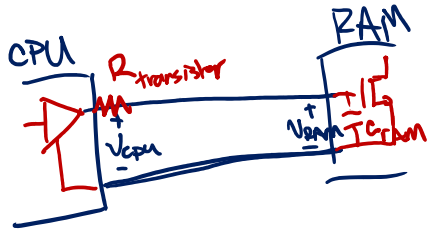




$$\omega_0 = \frac{2\pi}{T} = 2\pi f, \quad f = 4\text{GHz}$$

$$a_0 = 0.6\text{V}$$


$$a_n = 0$$

$$b_n = \begin{cases} 0, & n \text{ even} \\ \frac{2}{n\pi}(1.2), & n \text{ odd} \end{cases}$$

# Application: Digital Communication

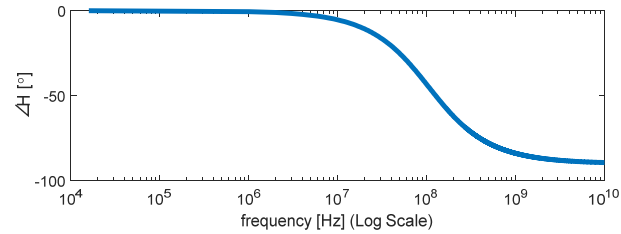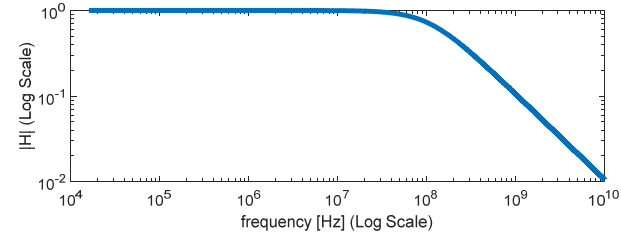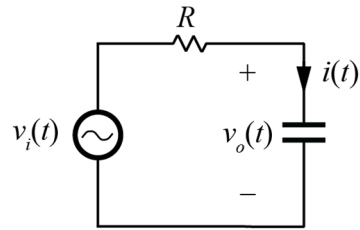

# Applying Superposition

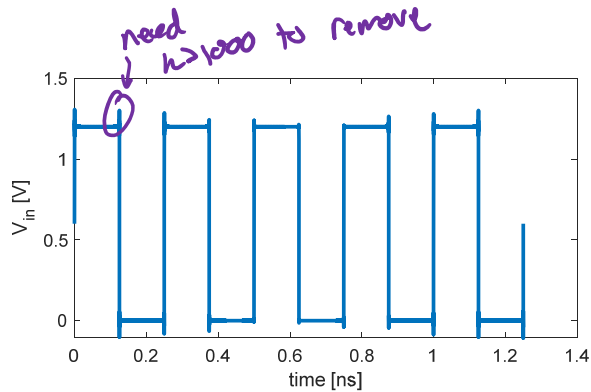

$$V_i(t) = f(t) = a_0 + \sum_{k=1,3,5,\dots}^{\infty} b_k \sin(k\omega_0 t)$$


← first 1000 indices of summation

$$H(j\omega) = \frac{1}{1 - j\omega RC}$$




$$V_o(t) = a_0 |H(j\omega \rightarrow 0)| + \sum_{k=1}^{\infty} |H(jk\omega_0)| b_k \sin(k\omega_0 t - \angle H(jk\omega_0))$$



# Calculated Output Voltage

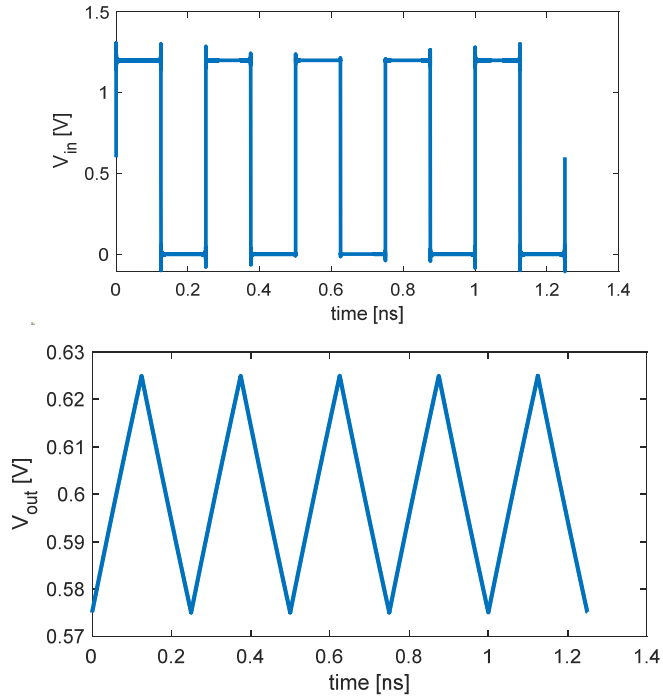

# Simulation Verification

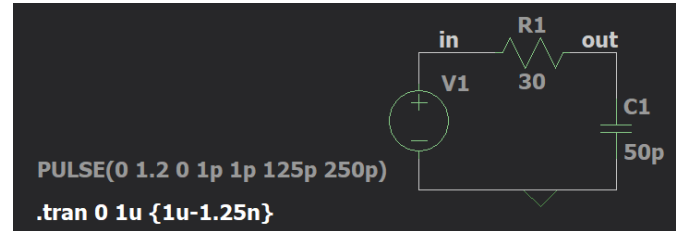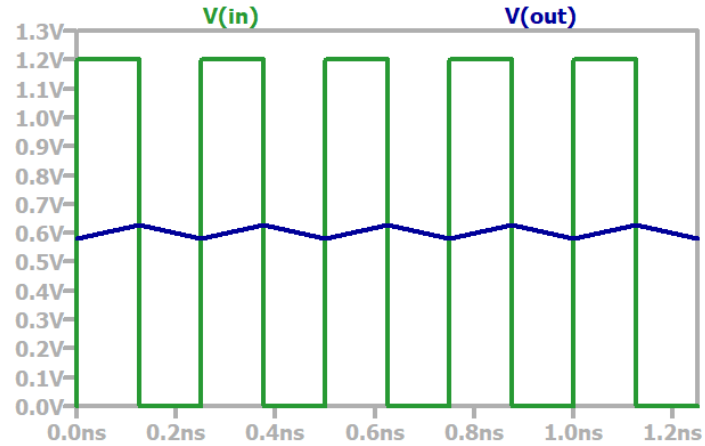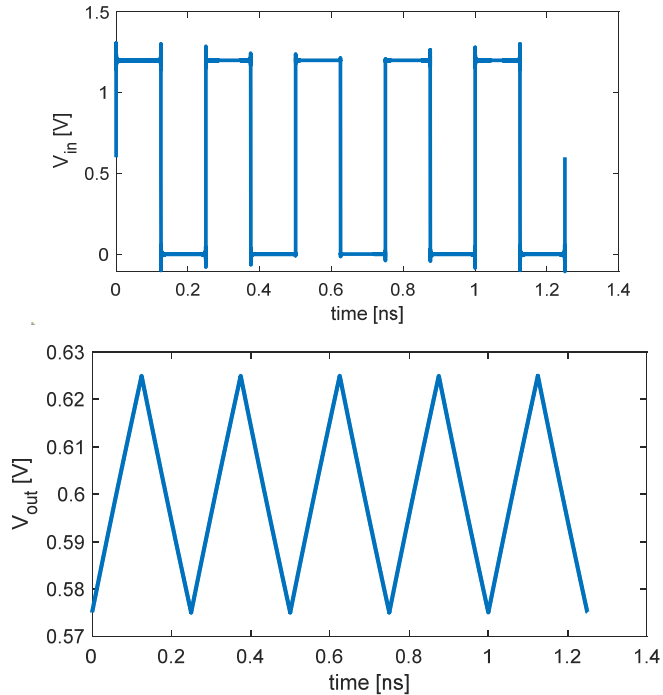

# Frequency Domain Interpretation

