

Initial and Final Value Theorems

Initial Value Theorem

$$\begin{aligned} \mathcal{L} \left\{ \frac{df}{dt} \right\} &= \lim_{s \rightarrow \infty} \int_{0^-}^{\infty} e^{-st} \frac{df}{dt} dt = sF(s) - f(0^-) \\ \lim_{s \rightarrow \infty} \left[\int_{0^-}^{0^+} e^{-st} \frac{df}{dt} dt + \int_{0^+}^{\infty} e^{-st} \frac{df}{dt} dt \right] &= \lim_{s \rightarrow \infty} [sF(s) - f(0^-)] \\ = f(0^+) - f(0^-) &= \lim_{s \rightarrow \infty} [sF(s)] - f(0^-) \end{aligned}$$

$$= \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} [sF(s)]$$

↑ fastest part of response ↑ highest frequencies

$$\begin{aligned} \text{Final Value Theorem} : \lim_{s \rightarrow 0} \left[\int_{0^-}^{\infty} e^{-st} \frac{df}{dt} dt \right] &= \lim_{s \rightarrow 0} [sF(s) - f(0^-)] \\ f(t \rightarrow \infty) - f(0^-) &= \lim_{s \rightarrow 0} [sF(s)] - f(0^-) \end{aligned}$$

$$= \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} [sF(s)]$$


All poles in LHP
(Final value is defined)

TABLE 14.2 Laplace Transform Operations


Operation	$f(t)$	$\mathbf{F}(s)$
Addition	$f_1(t) \pm f_2(t)$	$\mathbf{F}_1(s) \pm \mathbf{F}_2(s)$
Scalar multiplication	$kf(t)$	$k\mathbf{F}(s)$
Time differentiation	$\frac{df}{dt}$	$s\mathbf{F}(s) - f(0^-)$
	$\frac{d^2f}{dt^2}$	$s^2\mathbf{F}(s) - sf(0^-) - f'(0^-)$
	$\frac{d^3f}{dt^3}$	$s^3\mathbf{F}(s) - s^2f(0^-) - sf'(0^-) - f''(0^-)$
Time integration	$\int_{0^-}^t f(t) dt$	$\frac{1}{s}\mathbf{F}(s)$
	$\int_{-\infty}^t f(t) dt$	$\frac{1}{s}\mathbf{F}(s) + \frac{1}{s} \int_{-\infty}^{0^-} f(t) dt$
Convolution	$f_1(t) * f_2(t)$	$\mathbf{F}_1(s)\mathbf{F}_2(s)$
Time shift	$f(t-a)u(t-a), a \geq 0$	$e^{-as}\mathbf{F}(s)$
Frequency shift	$f(t)e^{-at}$	$\mathbf{F}(s+a)$
Frequency differentiation	$tf(t)$	$-\frac{d\mathbf{F}(s)}{ds}$
Frequency integration	$\frac{f(t)}{t}$	$\int_s^\infty \mathbf{F}(s) ds$
Scaling	$f(at), a \geq 0$	$\frac{1}{a}\mathbf{F}\left(\frac{s}{a}\right)$
Initial value	$f(0^+)$	$\lim_{s \rightarrow \infty} s\mathbf{F}(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} s\mathbf{F}(s)$, all poles of $s\mathbf{F}(s)$ in LHP
Time periodicity	$f(t) = f(t + nT), n = 1, 2, \dots$	$\frac{1}{1 - e^{-Ts}} \mathbf{F}_1(s),$ where $\mathbf{F}_1(s) = \int_{0^-}^T f(t) e^{-st} dt$

Circuit Laplace Transform


Time Domain

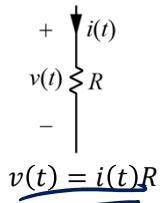

Phasor Domain

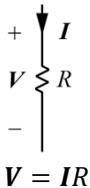




s-Domain

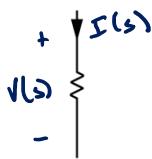

$$\mathcal{L}\{v(t)\} = \mathcal{L}\{i(t) R\}$$

$$V(s) = R I(s)$$


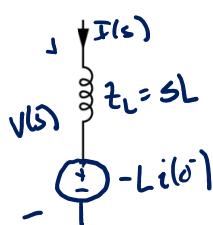
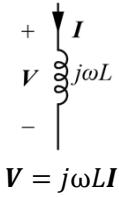
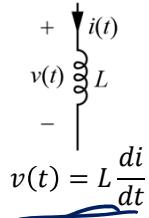
$z_R = R \rightarrow$ still called "Impedance"



$$\mathcal{L}\{v(t)\} = \mathcal{L}\left\{\int L \frac{di(t)}{dt}\right\}$$

$$V(s) = sL I(s) - L i(0^-)$$

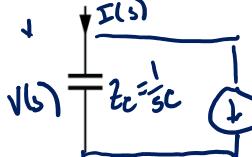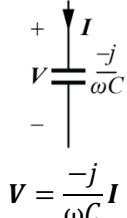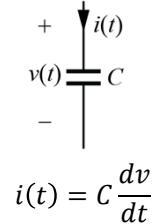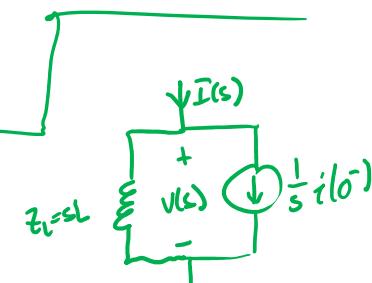
$$I(s) = \frac{V(s)}{sL} + \frac{1}{s} i(0^-)$$




$$\mathcal{L}\{i(t)\} = \mathcal{L}\left\{C \frac{dv(t)}{dt}\right\}$$

$$I(s) = sC V(s) - C v(0^-)$$
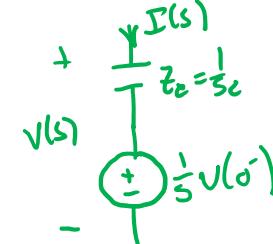
$$V(s) = \frac{1}{sC} I(s) + \frac{1}{s} v(0^-)$$




Time Domain

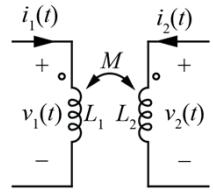

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$


Phasor Domain

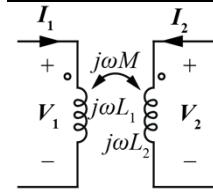

$$\mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M \mathbf{I}_2$$


$$\mathbf{V}_2 = j\omega M \mathbf{I}_1 + j\omega L_2 \mathbf{I}_2$$

s-Domain

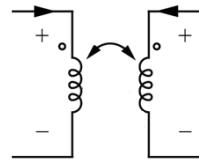


$$V_1(s) = sL_1 I_1(s) - L_1 i_1(0^-) + sM I_2(s) - M i_2(0^-)$$
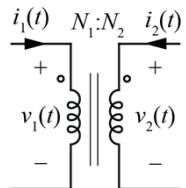
$$V_2(s) = sM I_1(s) - M i_1(0^-) + sL_2 I_2(s) - L_2 i_2(0^-)$$




$$\frac{v_1(t)}{N_1} = \frac{v_2(t)}{N_2}$$

$$N_1 i_1(t) + N_2 i_2(t) = 0$$

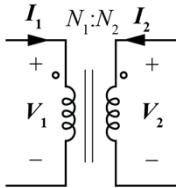

$$\frac{\mathbf{V}_1}{N_1} = \frac{\mathbf{V}_2}{N_2}$$
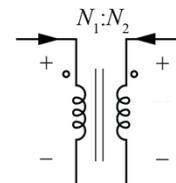
$$N_1 \mathbf{I}_1 + N_2 \mathbf{I}_2 = 0$$



$$\frac{V_1(s)}{N_1} = \frac{V_2(s)}{N_2}$$

$$N_1 I_1(s) + N_2 I_2(s) = 0$$

Laplace Transform of Diff EQs

N^{th} order circuit with sinusoidal input described by ($M \leq N$ for causality)

$$b_N \frac{d^N}{dt^N} v_o(t) + \cdots + b_1 \frac{d}{dt} v_o(t) + b_0 v_o(t) = a_M \frac{d^M}{dt^M} v_i(t) + \cdots + a_1 \frac{d}{dt} v_i(t) + a_0 v_i(t)$$

$$\sum_{i=0}^N b_i \frac{d^i}{dt^i} v_o(t) = \sum_{i=0}^M a_i \frac{d^i}{dt^i} v_i(t)$$

Then the Laplace transform of the circuit, neglecting initial conditions, is

$$\mathcal{L} \left\{ \sum_{i=0}^N b_i \frac{d^i}{dt^i} v_o(t) \right\} = \mathcal{L} \left\{ \sum_{i=0}^M a_i \frac{d^i}{dt^i} v_i(t) \right\}$$

$$\sum_{i=0}^N b_i s^i V_o(s) = \sum_{i=0}^M a_i s^i V_i(s)$$

Rearranging:

Transfer
function

$$\boxed{\frac{V_o(s)}{V_i(s)} = H(s) = \frac{\sum_{i=0}^M a_i s^i}{\sum_{i=0}^N b_i s^i}}$$

if we replace $s \rightarrow j\omega$
in $H(s)$
we get $H(j\omega)$, the
frequency response



Laplace Circuit Solution Algorithm

1. Transform all sources, signals into Laplace Domain
2. Transform circuit components (including initial conditions) into Laplace Domain
3. Solve the circuit using 201 techniques


$$V_o(s) = H(s)V_i(s) = \frac{\sum_{i=0}^M a_i s^i}{\sum_{i=0}^N b_i s^i}$$

4. Inverse Laplace Transform to get back to time domain

Example Laplace Circuit Analysis

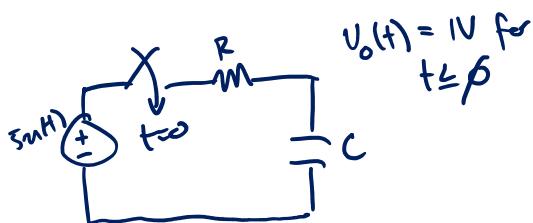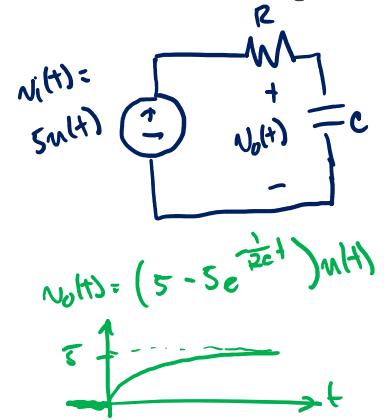

$v_o(t) @ t=0$ is zero

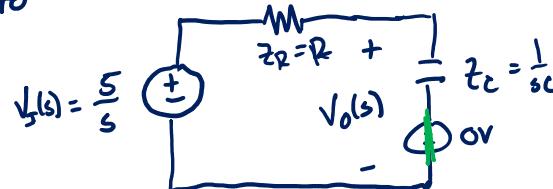


$$v_o(s) = V_I(s) \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{5}{s} \frac{\frac{1}{sC}}{\frac{1}{sC} + R} \rightarrow \frac{5}{s} \frac{\frac{1}{RC}}{\frac{1}{RC} + s}$$

$$v_o(t) = L^{-1}\{v_o(s)\} = L^{-1}\left\{\frac{A}{s} + \frac{B}{\frac{1}{RC} + s}\right\} \rightarrow L^{-1}\left\{\frac{5}{s} + \frac{-5}{\frac{1}{RC} + s}\right\}$$

PFE (more review coming)
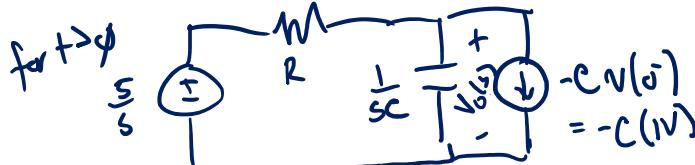
$$v(t) = L^{-1}\left\{\frac{5}{s}\right\} + L^{-1}\left\{\frac{-5}{\frac{1}{RC} + s}\right\} = \boxed{5u(t) - 5e^{-\frac{t}{RC}}u(t)}$$



$$v_o(s) = V_I(s) \frac{\frac{1}{sC}}{\frac{1}{sC} + R} + C(V) \left[R \parallel \frac{1}{sC} \right]$$