

Approximate Graphical Analysis

- $\| H_1(s) \cdot H_2(s) \|_{dB} = \| H_1(s) \|_{dB} + \| H_2(s) \|_{dB}$

multiplication \rightarrow addition

- $\| \omega^n \|_{dB} \rightarrow 20(n) \log(\omega) \rightarrow 20(n) \text{ dB/dec line}$

exponentiation \rightarrow mult.


- $\| 1 + jX \|_{dB} = \begin{cases} 1 & X \ll 1 \\ \sqrt{2} & X = 1 \\ \| X \|_{dB} & X \gg 1 \end{cases}$

addition \rightarrow max()



$$z_{eq} = z_1 + z_2$$

$$\| z_{eq} \|_{dB} = \| z_1 + z_2 \|_{dB} = \begin{cases} \| z_1 \|_{dB}, & |z_1| \gg |z_2| \\ ? & |z_1| = |z_2| \\ \| z_2 \|_{dB}, & |z_2| \gg |z_1| \end{cases}$$

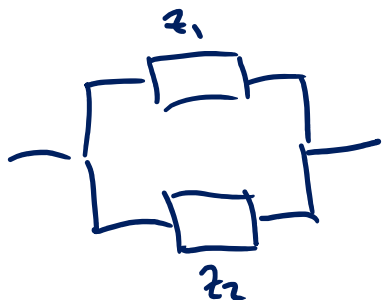


$$z_{eq} = z_1 || z_2$$

$$\| z_{eq} \|_{dB} = \left\| \frac{z_1 \cdot z_2}{z_1 + z_2} \right\|_{dB} = \begin{cases} \| z_2 \|_{dB}, & |z_1| \gg |z_2| \\ ? & |z_1| = |z_2| \\ \| z_1 \|_{dB}, & |z_2| \gg |z_1| \end{cases}$$

Reactance Paper


$z_c = \frac{1}{s}$
 $\|z_c\| = \frac{1}{|j\omega c|} = \frac{1}{\omega c}$

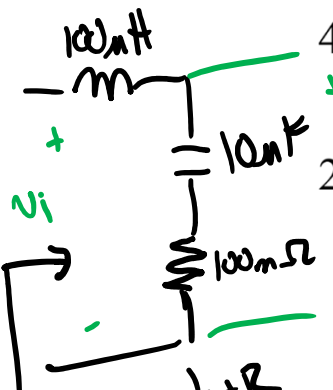

$z_{in} = sL + \frac{1}{sC} + R$

$z_{in} = \frac{100nH}{s} \left(\left(\frac{s}{\omega_0} \right)^2 + \frac{s}{Q\omega_0} + 1 \right)$

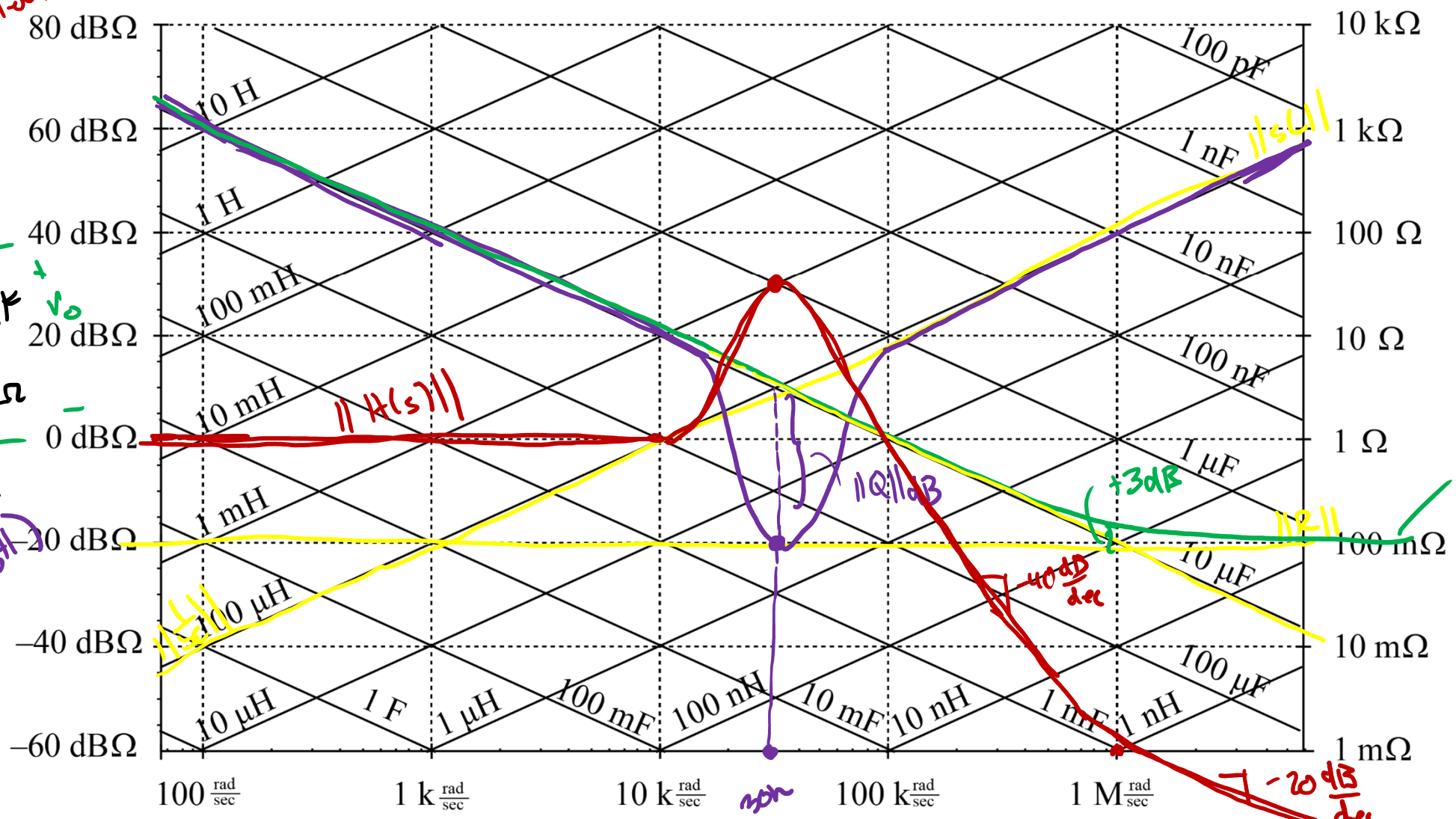
$\omega_0 \approx 30 \text{ krad/sec}$
 $Q \approx 30 \text{ dB} \approx 31$





$H(s) = \frac{v_o}{v_i}$
 $= \frac{R + \frac{1}{sC}}{R + \frac{1}{sC} + sL}$
 $= \frac{R + \frac{1}{sC}}{z_{in}}$

$\|R + \frac{1}{sC}\|$


Reactance Paper

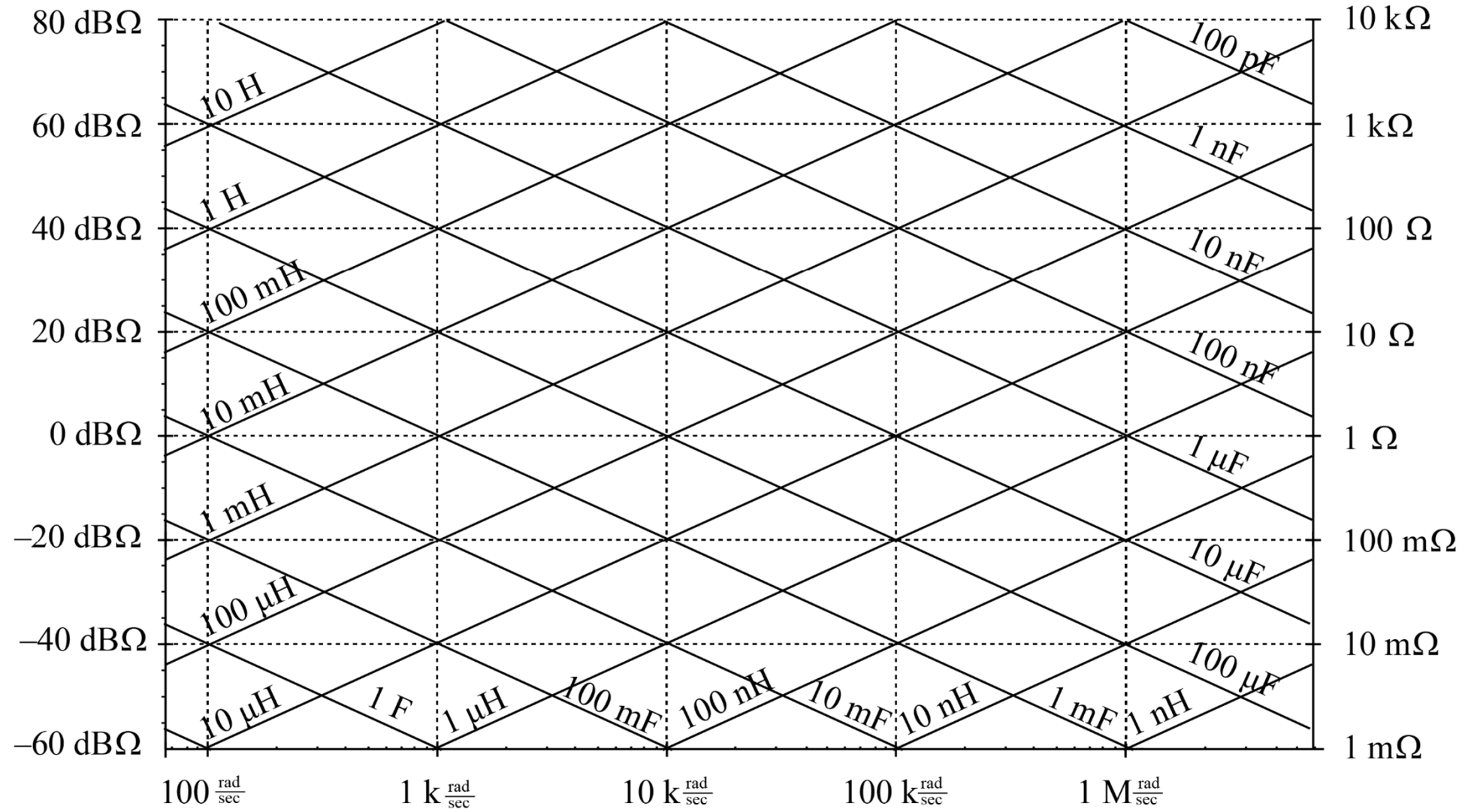

Graphical Analysis

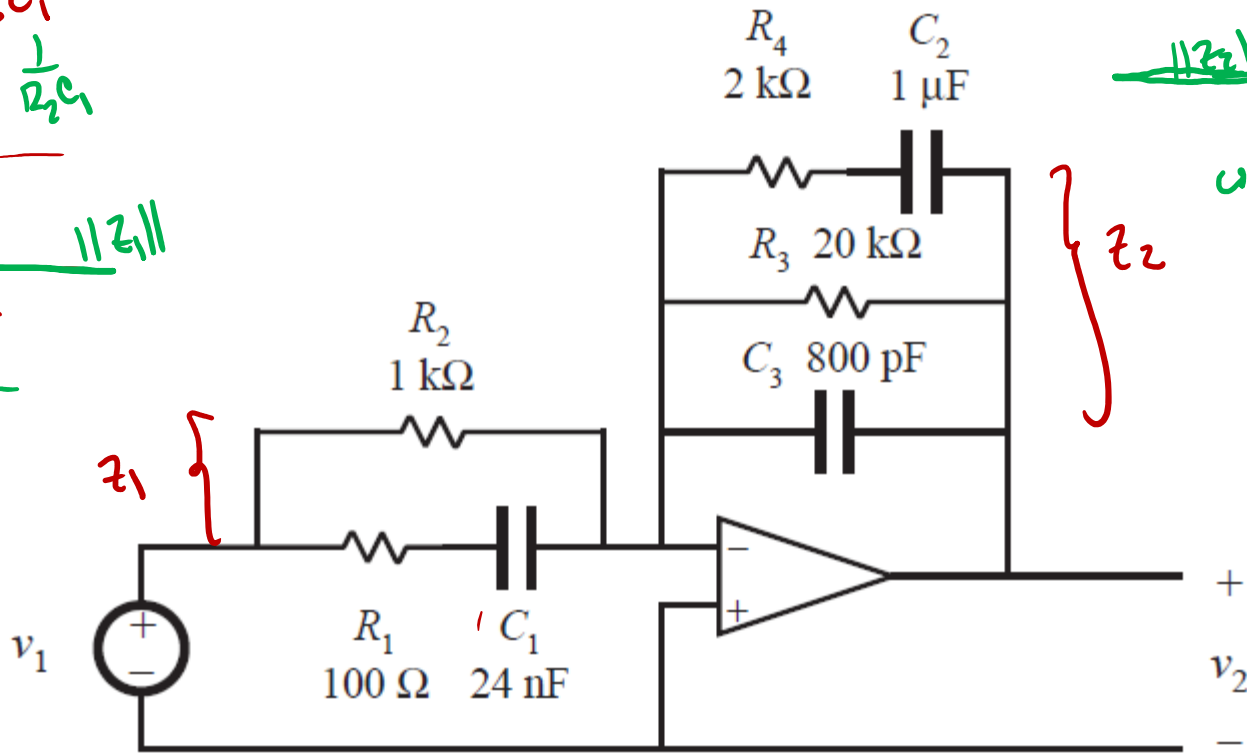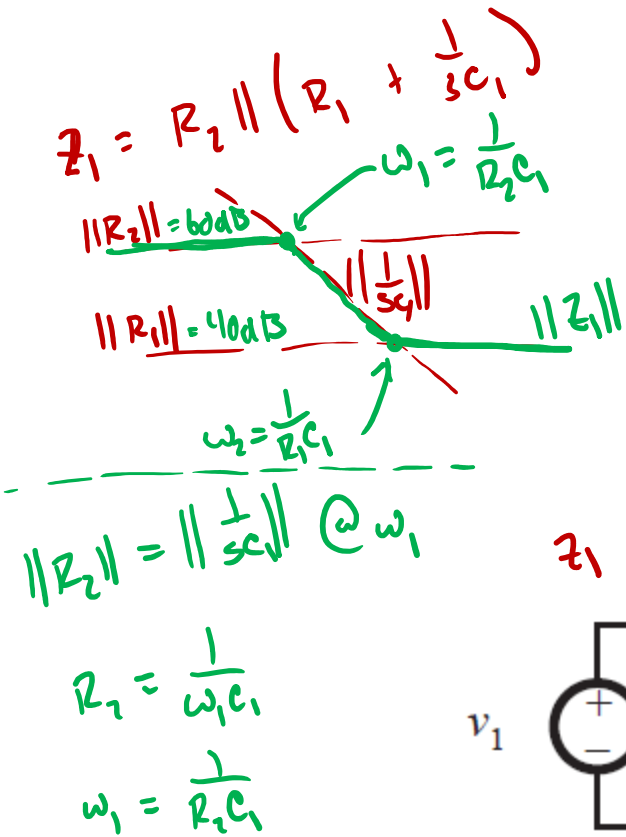
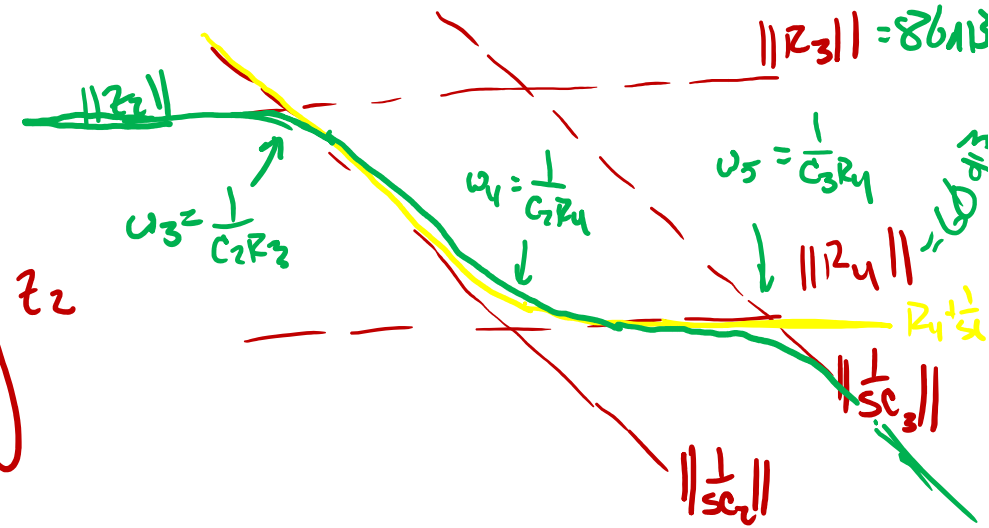
$$Z_2 = \frac{1}{sC_3} \parallel R_3 \parallel \left(R_4 + \frac{1}{sC_2} \right)$$



$$H(s) = \frac{V_2}{V_1} = -\frac{Z_2}{Z_1}$$



86dB Impedance/Reactance Paper

