
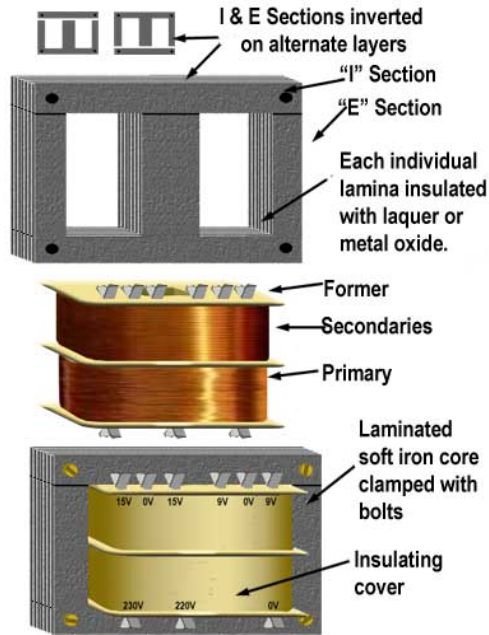



# Example Transformer

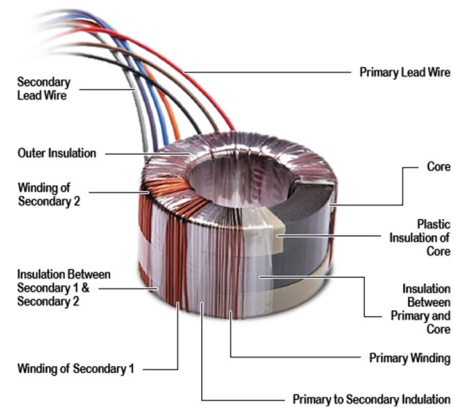




[http://www.learnabout-electronics.org/ac\\_theory/transformers03.php](http://www.learnabout-electronics.org/ac_theory/transformers03.php)





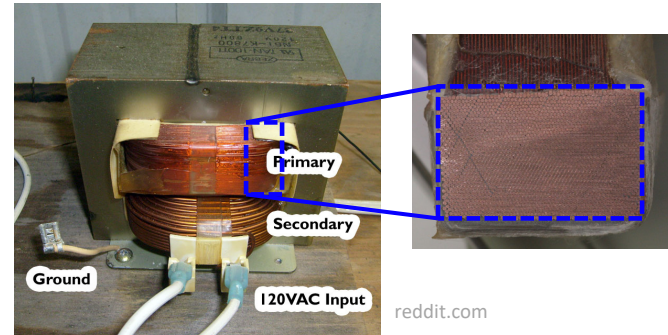
<https://www.altrancorp.com/products/toroidal-power-transformers/>




# Transformer Reflection

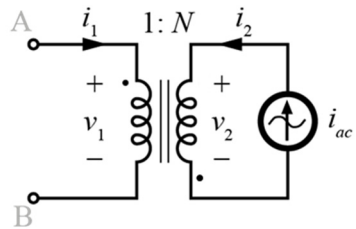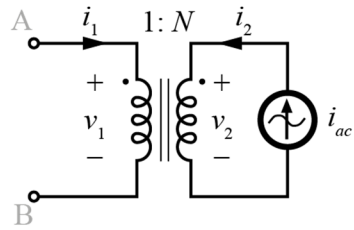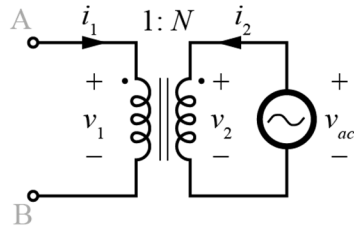

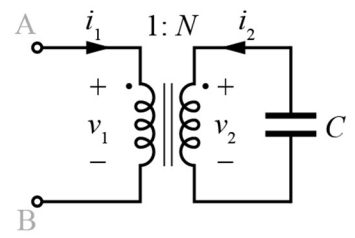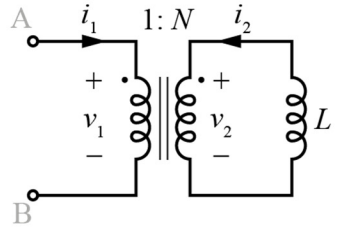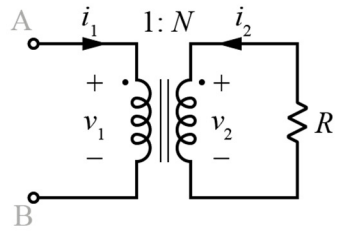

# Example Circuit Simplification

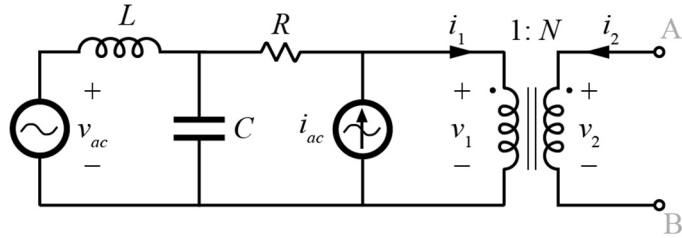



# Ideal Transformer Example

