
Lecture 10: Isolated Converters II & DCM Introduction

ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville

Fall 2013

Announcements

- Midterm exam due Thursday, start of class
- Hw #3 returned today
- Missing HW assignments

3. [30 pts] Design of a Boost Converter

The boost converter in Fig. 3 connects a lead-acid battery to a 48 V DC bus. The converter input is the battery voltage, which has characteristics:

- Maximum V_{bat} : 15 V
- Minimum V_{bat} : 10 V

The maximum output power is 100 W, and the switching frequency is 100 kHz. The inductance L is chosen to be 10 μ H, and the capacitance may be assumed to be very large for parts (a)-(c).

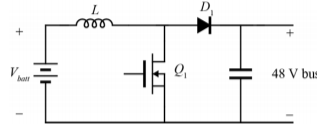


Figure 3: Boost converter

- a) [10 pts] A number of parts are available for both the MOSFET and diode. Important characteristics of each device are shown in Tables I and II. The rated maximum currents and voltages are the maximum *instantaneous* values which the devices can handle.

TABLE I: MOSFET DEVICES

| Device | Rated max V_{DS} | Rated max I_{DS} | R_{on} |
|--------|--------------------|--------------------|---------------|
| I | 40 V | 30 A | 5 m Ω |
| II | 100 V | 15 A | 15 m Ω |
| III | 100 V | 20 A | 50 m Ω |
| IV | 150 V | 15 A | 30 m Ω |
| V | 150 V | 20 A | 75 m Ω |


TABLE II: DIODE DEVICES

| Device | Rated max V_R | Rated max I_F | V_F |
|--------|-----------------|-----------------|-------|
| VI | 40 V | 20 A | 0.5 V |
| VII | 100 V | 15 A | 1.0 V |
| VIII | 150 V | 5 A | 0.7 V |
| IX | 200 V | 20 A | 1.5 V |


Select one MOSFET and one diode which will work best in this converter. Explain why you

6.3.1. Full-bridge and half-bridge isolated buck converters


Full-bridge isolated buck converter

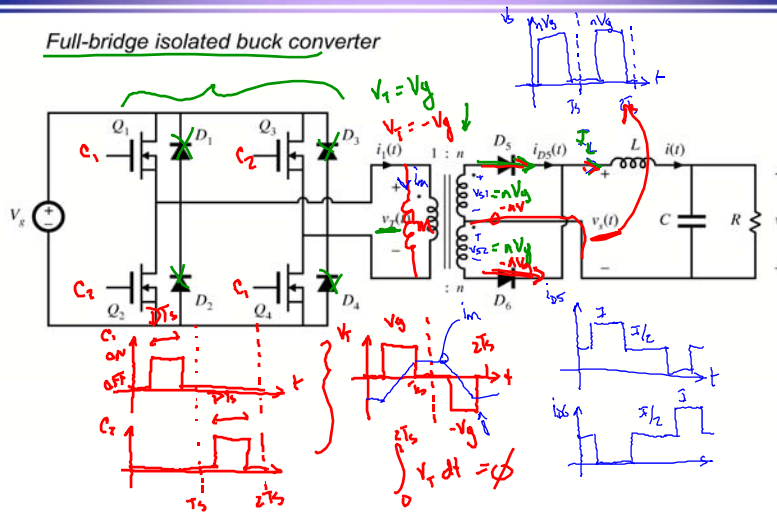

Full Bridge Switch Structure

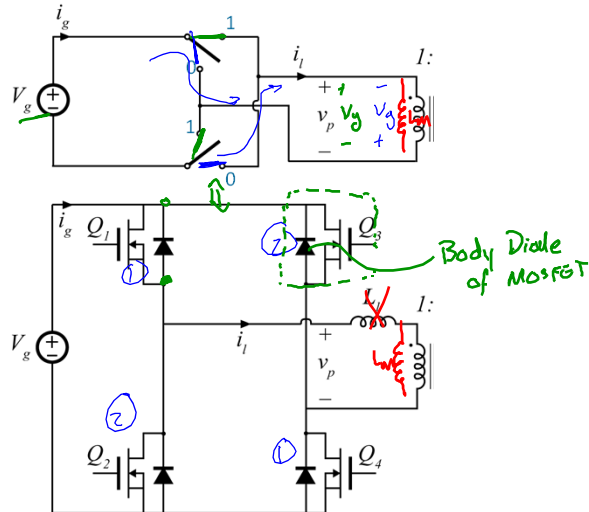

Full-bridge: waveforms

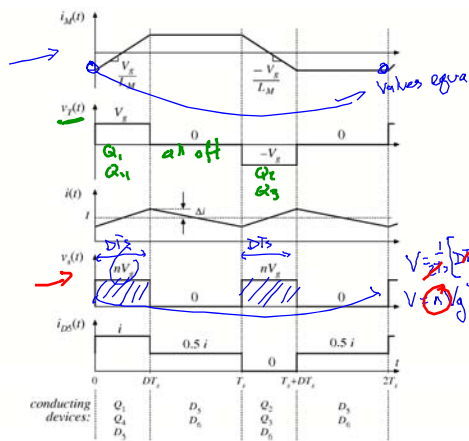

- During first switching period: transistors Q_1 and Q_4 conduct for time DT_s , applying volt-seconds $V_g DT_s$ to primary winding
- During next switching period: transistors Q_2 and Q_3 conduct for time DT_s , applying volt-seconds $-V_g DT_s$ to primary winding
- Transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities?

Effect of nonidealities on transformer volt-second balance

Volt-seconds applied to primary winding during first switching period:

$$(V_g - (Q_1 \text{ and } Q_4 \text{ forward voltage drops})) (\underbrace{Q_1 \text{ and } Q_4}_{\text{Different sum of } Q_1 \text{ \& } Q_4} \text{ conduction time})$$

Volt-seconds applied to primary winding during next switching period:

$$- (V_g - (Q_2 \text{ and } Q_3 \text{ forward voltage drops})) (\underbrace{Q_2 \text{ and } Q_3}_{\text{conduction time}})$$

These volt-seconds never add to exactly zero.


Net volt-seconds are applied to primary winding

Magnetizing current slowly increases in magnitude

Saturation can be prevented by placing a capacitor in series with primary, or by use of current programmed mode (Chapter 12)


Operation of secondary-side diodes

Center-tapped rectifier

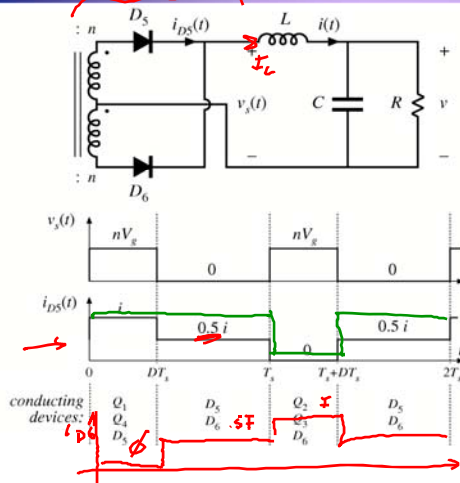


- During second (D') subinterval, both secondary-side diodes conduct
- Output filter inductor current divides approximately equally between diodes
- Secondary amp-turns add to approximately zero
- Essentially no net magnetization of transformer core by secondary winding currents

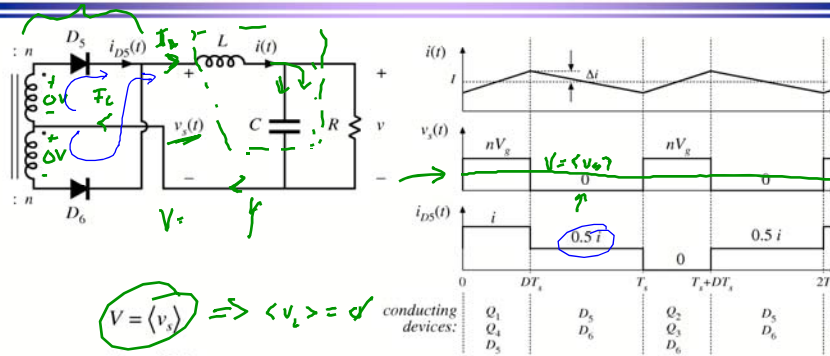Volt-second balance on output filter inductor




$V = \langle v_s \rangle \Rightarrow \langle v_s \rangle = \checkmark$ conducting devices: Q_1, Q_4, D_5, D_6
 $V = nDV_g$
 $M(D) = nD$ buck converter with turns ratio

Half-bridge isolated buck converter

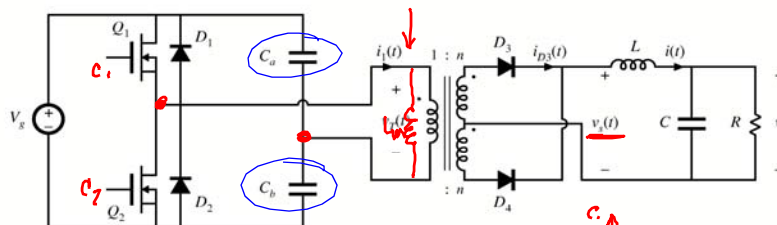


- Replace transistors Q_3 and Q_4 with large capacitors
- Voltage at capacitor centerpoint is $0.5V_g$
- $v_s(t)$ is reduced by a factor of two
- $M = 0.5 nD$

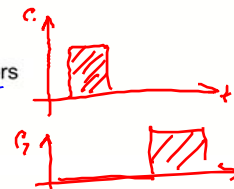
$\langle v_{in} \rangle = D(V_g - V_{cb}) + D(0.5V_g - V_{cb})$



6.3.3. Push-pull isolated buck converter

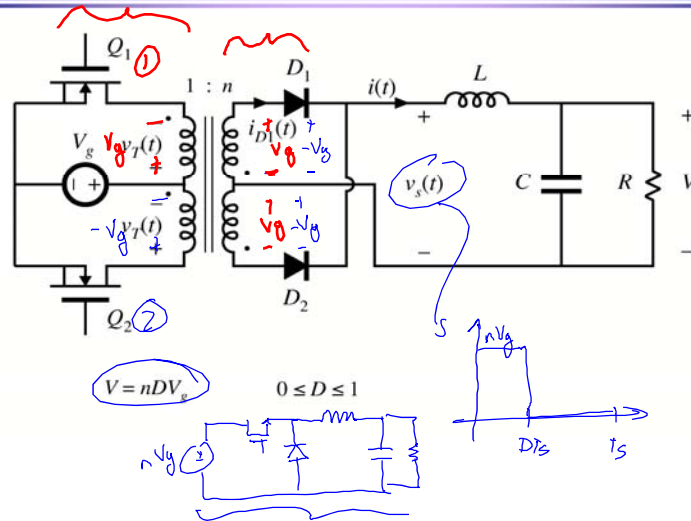


Waveforms: push-pull

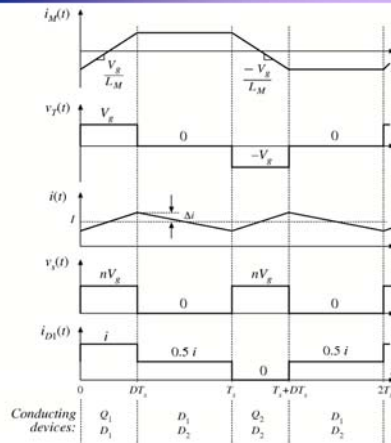


- Used with low-voltage inputs
- Secondary-side circuit identical to full bridge
- As in full bridge, transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities on transformer volt-second balance?
- Current programmed control can be used to mitigate transformer saturation problems. Duty cycle control not recommended.

6.3.2. Forward converter

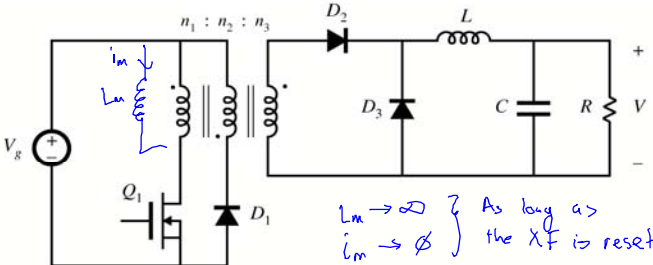


- Buck-derived transformer-isolated converter
- Single-transistor and two-transistor versions
- Maximum duty cycle is limited
- Transformer is reset while transistor is off

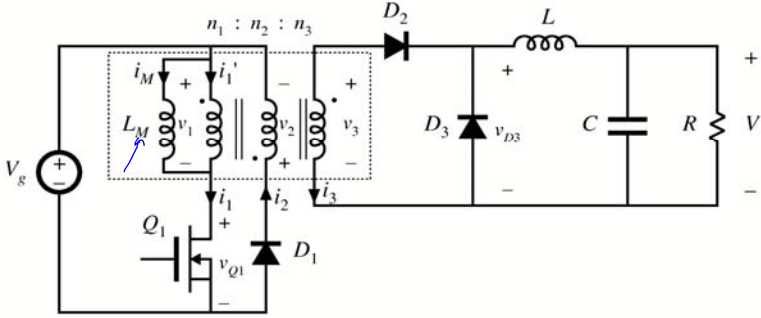Forward converter with transformer equivalent circuit



Forward converter: waveforms

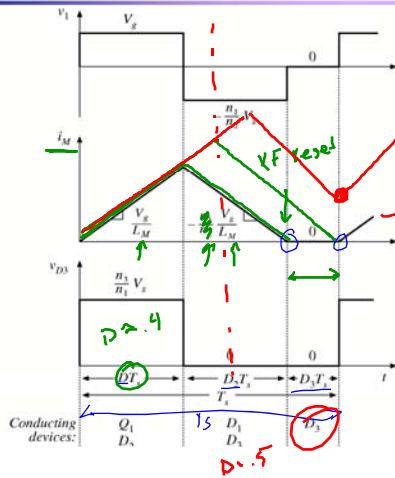


• Magnetizing current, in conjunction with diode D_1 , operates in discontinuous conduction mode


• Output filter inductor, in conjunction with diode D_3 , may operate in either CCM or DCM

if $n_1 = n_2$
 \rightarrow DC-S for transformer reset


Subinterval 1: transistor conducts

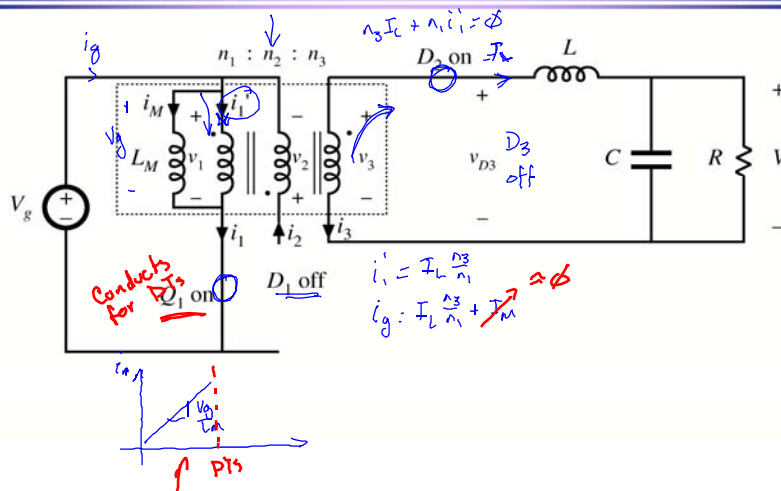


Subinterval 2: transformer reset

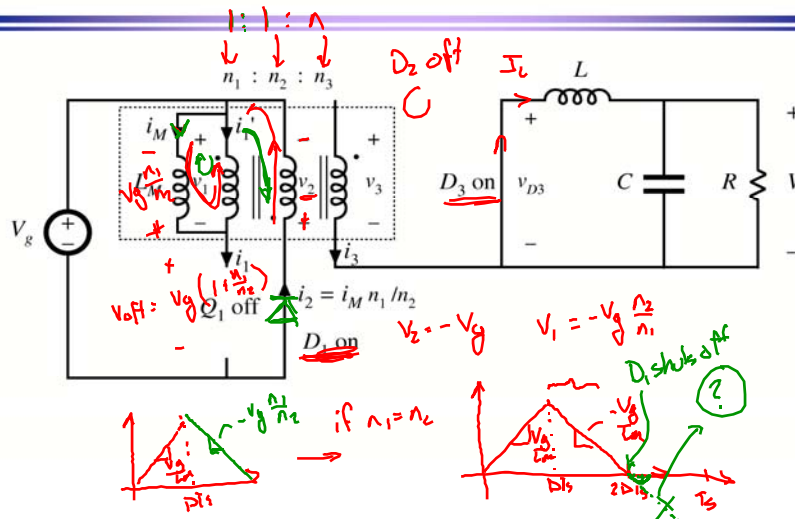

Subinterval 3

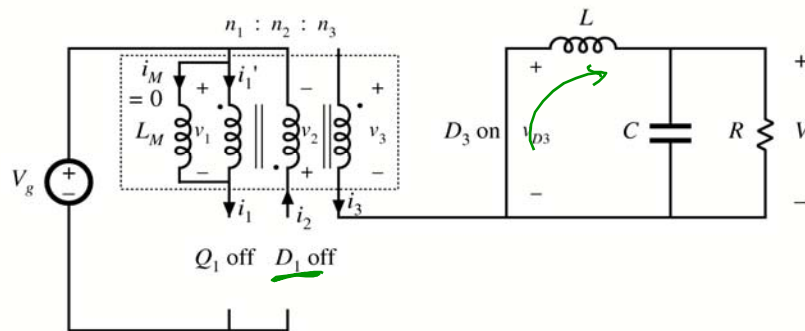

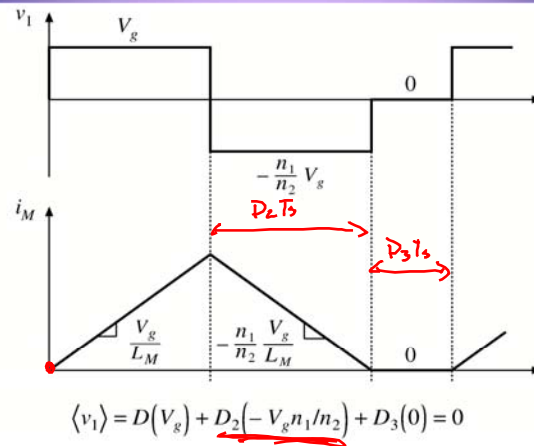Magnetizing inductance volt-second balance



Transformer reset

From magnetizing current volt-second balance:

$$\langle v_1 \rangle = D(V_g) + D_2(-V_g n_1/n_2) + D_3(0) = 0$$

Solve for D_2 :

$$D_2 = \frac{n_2}{n_1} D$$

D_3 cannot be negative. But $D_3 = 1 - D - D_2$. Hence

$$D_3 = 1 - D - D_2 \geq 0$$

$$D_3 = 1 - D \left(1 + \frac{n_2}{n_1} \right) \geq 0$$


Solve for D

$$D \leq \frac{1}{1 + \frac{n_2}{n_1}}$$


for $n_1 = n_2$: $D \leq \frac{1}{2}$

What happens when $D > 0.5$

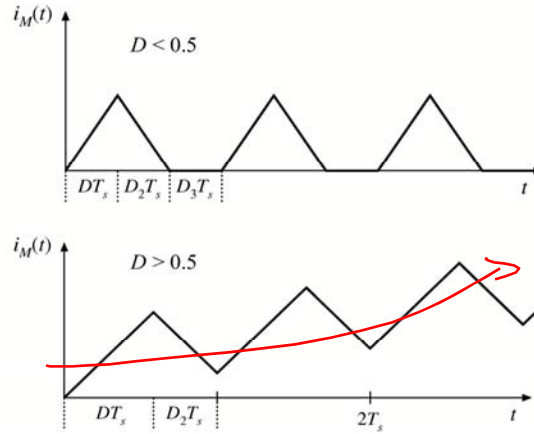magnetizing current waveforms, for $n_1 = n_2$



Conversion ratio $M(D)$

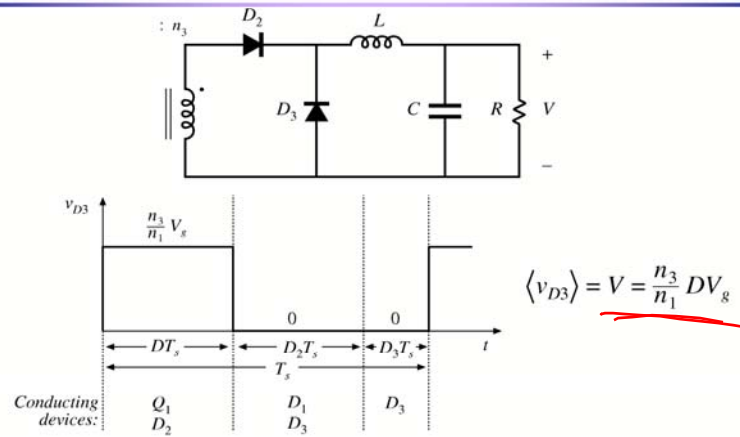

Maximum duty cycle vs. transistor voltage stress

Maximum duty cycle limited to

$$D \leq \frac{1}{1 + \frac{n_2}{n_1}}$$


which can be increased by increasing the turns ratio n_2/n_1 . But this increases the peak transistor voltage:

$$\max(v_{Q1}) = V_g \left(1 + \frac{n_1}{n_2} \right)$$

For $n_1 = n_2$

$$D \leq \frac{1}{2} \quad \text{and} \quad \max(v_{Q1}) = 2V_g$$

The two-transistor forward converter

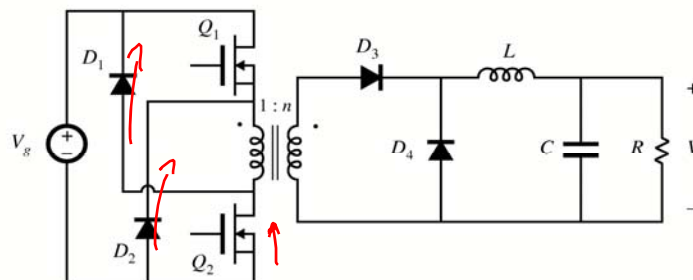

$$V = nDV_g \quad D \leq \frac{1}{2} \quad \max(v_{Q1}) = \max(v_{Q2}) = V_g$$

Chapter 5. The Discontinuous Conduction Mode


- 5.1. Origin of the discontinuous conduction mode, and mode boundary
- 5.2. Analysis of the conversion ratio $M(D,K)$
- 5.3. Boost converter example
- 5.4. Summary of results and key points

Introduction to Discontinuous Conduction Mode (DCM)

- Occurs because switching ripple in inductor current or capacitor voltage causes polarity of applied switch current or voltage to reverse, such that the current- or voltage-unidirectional assumptions made in realizing the switch are violated.
- Commonly occurs in dc-dc converters and rectifiers, having single-quadrant switches. May also occur in converters having two-quadrant switches.
- Typical example: dc-dc converter operating at light load (small load current). Sometimes, dc-dc converters and rectifiers are purposely designed to operate in DCM at all loads.
- Properties of converters change radically when DCM is entered:
 - M becomes load-dependent
 - Output impedance is increased
 - Dynamics are altered
 - Control of output voltage may be lost when load is removed

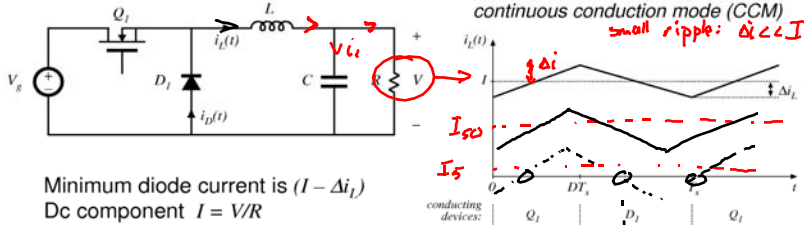5.1. Origin of the discontinuous conduction mode, and mode boundary

Buck converter example, with single-quadrant switches



Minimum diode current is $(I - \Delta i_L)$
 Dc component $I = V/R$
 Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD T_s}{2L}$$


Note that I depends on load, but Δi_L does not.
 if $\angle i_c = \phi$

$$I_L = \frac{V}{R}$$

DCM operation $\Delta i > I_S$ small ripple does not apply

Reduction of load current

Increase R , until $I = \Delta i_L$

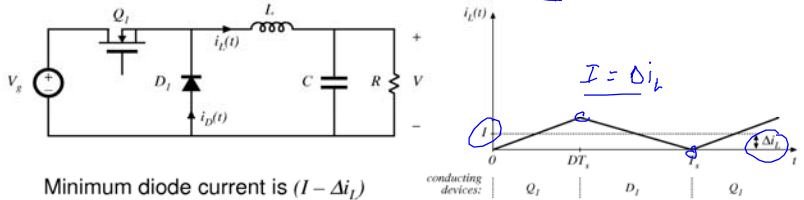

Minimum diode current is $(I - \Delta i_L)$
 Dc component $I = V/R$
 Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD T_s}{2L}$$


Note that I depends on load, but Δi_L does not.

"Continuous Cond. Mode"
 CCM-DCM boundary
 $I = \Delta i_L$

Further reduce load current

Increase R some more, such that $I < \Delta i_L$


Discontinuous conduction mode

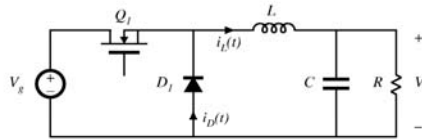

Minimum diode current is $(I - \Delta i_L)$
 Dc component $I = V/R$
 Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD'T_s}{2L}$$

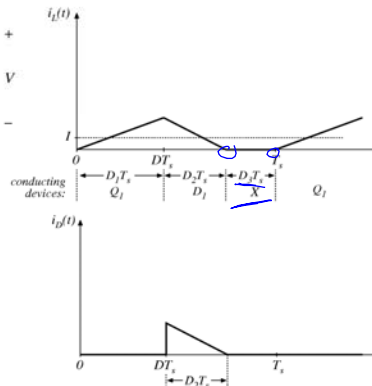Note that I depends on load, but Δi_L does not.
 The load current continues to be positive and non-zero.



Mode boundary

Boundary
 @ $I = 0$

$$\begin{aligned} I > \Delta i_L & \text{ for CCM} \\ I < \Delta i_L & \text{ for DCM} \end{aligned}$$

Insert buck converter expressions for I and Δi_L :

$$\frac{DV_g}{R} < \frac{DD'T_s V_g}{2L} \quad \leftarrow \quad \begin{aligned} v &= DV_g \\ I_L &= \frac{v}{R} = \frac{DV_g}{R} \end{aligned}$$

Simplify:

$$\frac{2L}{RT_s} < D' \quad \leftarrow \quad \text{for buck } K_{crit}(D) = D'$$


This expression is of the form

$$\text{where } K < K_{crit}(D) \text{ for DCM} \\ K = \frac{2L}{RT_s} \text{ and } K_{crit}(D) = D'$$

↪ unitless parameter

as $L \downarrow$ $D_{crit} \uparrow$
 ↪ closer to DCM
 as $T_s \downarrow$ $D_{crit} \downarrow$
 ↪ farther from DCM
 as $R \downarrow$ $I_L \uparrow$
 ↪ farther from DCM

K and K_{crit} vs. D

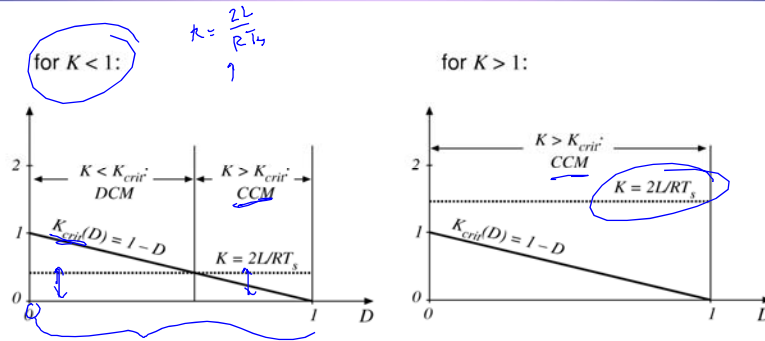

Critical load resistance R_{crit}

Solve K_{crit} equation for load resistance R :

$$\begin{aligned}
 & R < R_{crit}(D) \quad \text{for CCM} \\
 & R > R_{crit}(D) \quad \text{for DCM}
 \end{aligned}$$

where

$$R_{crit}(D) = \frac{2L}{D^2 T_s}$$

Summary: mode boundary

$$\begin{aligned}
 &K > K_{crit}(D) \quad \text{or} \quad R < R_{crit}(D) \quad \text{for CCM} \\
 &K < K_{crit}(D) \quad \text{or} \quad R > R_{crit}(D) \quad \text{for DCM}
 \end{aligned}$$

Table 5.1. CCM-DCM mode boundaries for the buck, boost, and buck-boost converters

| Converter | $K_{crit}(D)$ | $\max_{0 \leq D \leq 1} (K_{crit})$ | $R_{crit}(D)$ | $\min_{0 \leq D \leq 1} (R_{crit})$ |
|------------|---------------|-------------------------------------|-----------------------------|-------------------------------------|
| Buck | $(1 - D)$ | 1 | $\frac{2L}{(1-D)T_s}$ | $2 \frac{L}{T_s}$ |
| Boost | $D(1 - D)^2$ | $\frac{4}{27}$ | $\frac{2L}{D(1 - D)^2 T_s}$ | $\frac{27}{2} \frac{L}{T_s}$ |
| Buck-boost | $(1 - D)^2$ | 1 | $\frac{2L}{(1 - D)^2 T_s}$ | $2 \frac{L}{T_s}$ |

5.2. Analysis of the conversion ratio $M(D,K)$

Analysis techniques for the discontinuous conduction mode:

Inductor volt-second balance

$$\langle v_L \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = 0$$

Capacitor charge balance

$$\langle i_C \rangle = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = 0$$

Small ripple approximation sometimes applies:

$v(t) \approx V$ because $\Delta v \ll V$ Assuming operating as DC voltage regulator
 $i(t) \approx I$ is a poor approximation when $\Delta i > I$

No small ripple in i

Converter steady-state equations obtained via charge balance on each capacitor and volt-second balance on each inductor. Use care in applying small ripple approximation.

Example: Analysis of DCM buck converter $M(D,K)$

