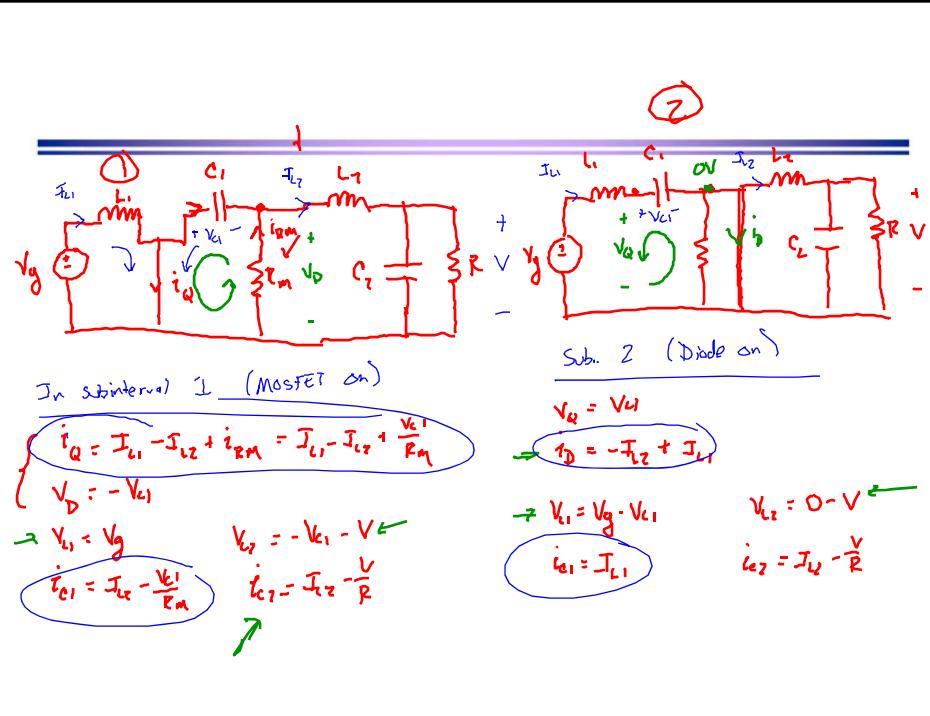



Lecture 13: Midterm, Dynamics and Control (cont.)

ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science
University of Tennessee Knoxville
Fall 2013



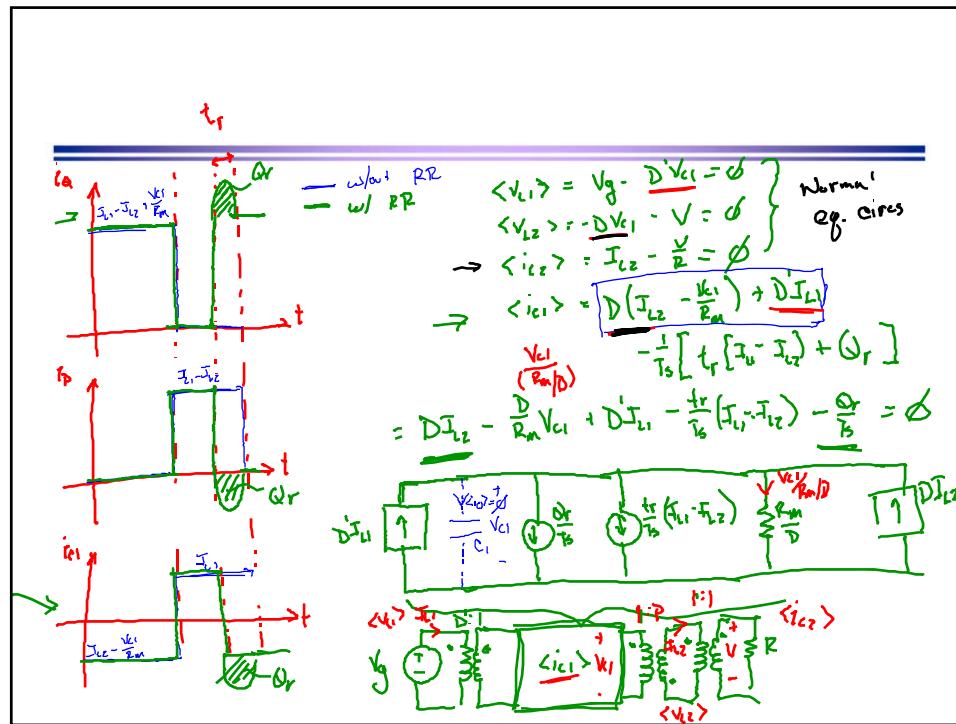

Chapter 7. AC Equivalent Circuit Modeling



- 7.1 Introduction
- 7.2 The basic AC modeling approach**
- 7.3 State-space averaging
- 7.4 Circuit averaging and averaged switch modeling
- 7.5 The canonical circuit model
- 7.6 Modeling the pulse-width modulator
- 7.7 Summary of key points

AC, small signal variation


$i_t(t) = \bar{i}_t + \hat{i}_t$

$|\hat{i}_t| \ll \bar{i}_t$ (small ripple)

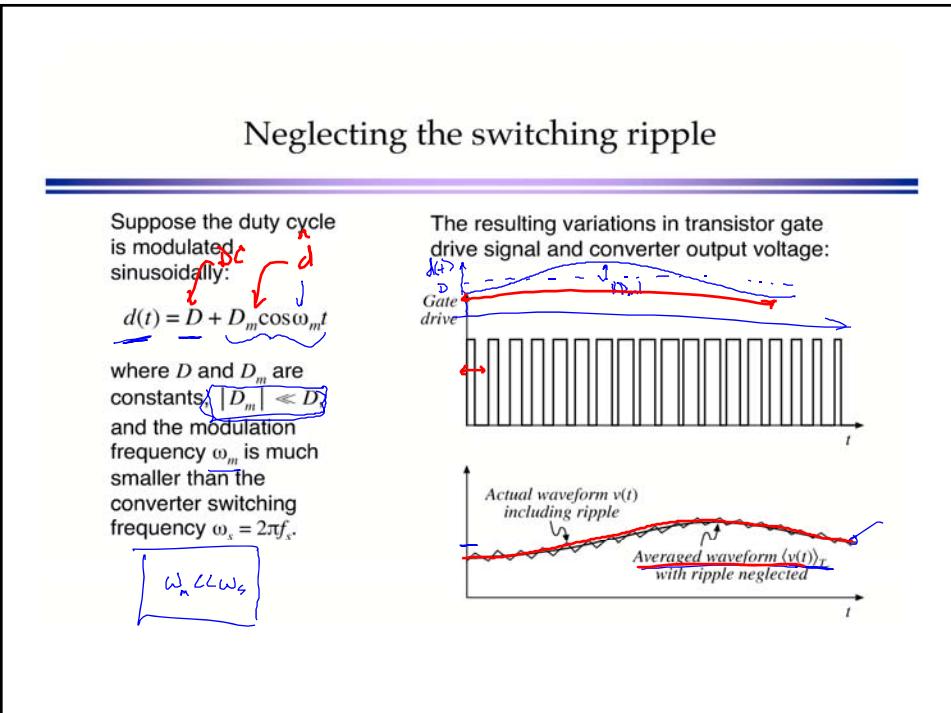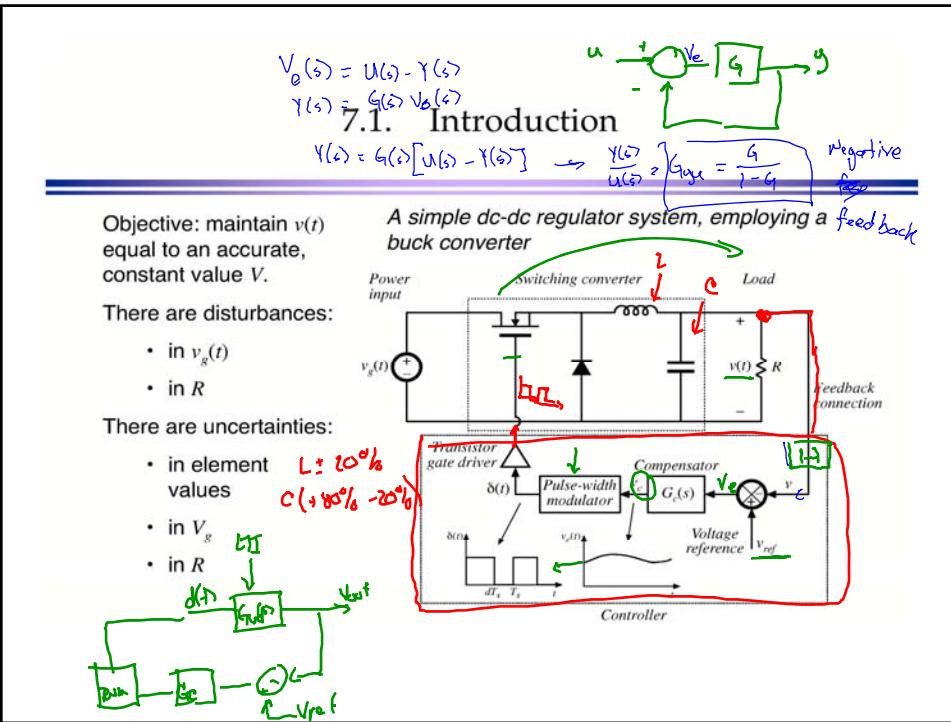
$\omega_m \ll \omega_s$ switching freq of AC



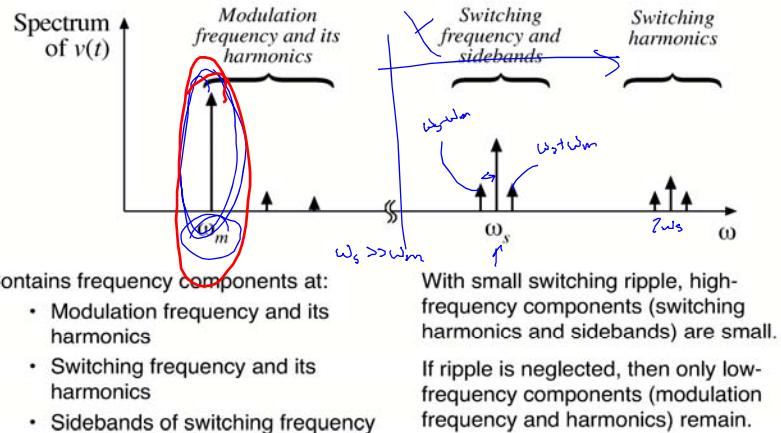Output voltage spectrum with sinusoidal modulation of duty cycle



Transient Volt-Second Balance

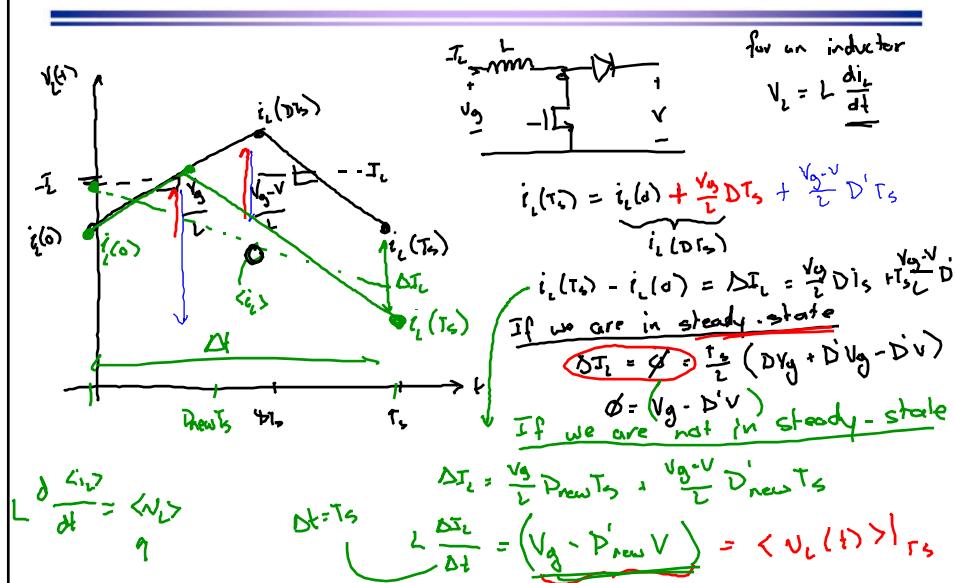

Averaging to remove switching ripple

Average over one switching period to remove switching ripple:

$$\begin{aligned} L \frac{d\langle i_L(t) \rangle_{T_s}}{dt} &= \langle v_L(t) \rangle_{T_s} \\ C \frac{d\langle v_C(t) \rangle_{T_s}}{dt} &= \langle i_C(t) \rangle_{T_s} \end{aligned}$$

where

Note that, in steady-state,

$$\begin{aligned} \langle v_L(t) \rangle_{T_s} &= 0 \\ \langle i_C(t) \rangle_{T_s} &= 0 \end{aligned}$$

by inductor volt-second balance and capacitor charge balance.

$$\langle v_L \rangle = \emptyset = V_g - D'V$$



e.g. Boost

$$L \frac{di_L}{dt} = V_g - D'v$$

$v(t)$

$(1-D)v(t)$

\hat{i} is a small-signal value $i = I_m \cos(\omega_m t)$
 $I_m \ll I$


Small-signal modeling of the diode

Nonlinear diode, driven by current source having a DC and small AC component


DC from Quiescent

Small-signal AC model


$$\hat{i} = \frac{1}{r_D} \hat{v}$$

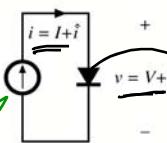

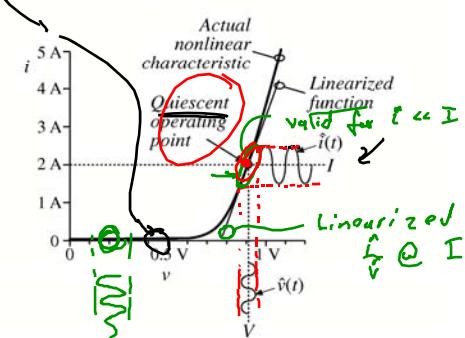
Linearization of the diode $i-v$ characteristic about a quiescent operating point




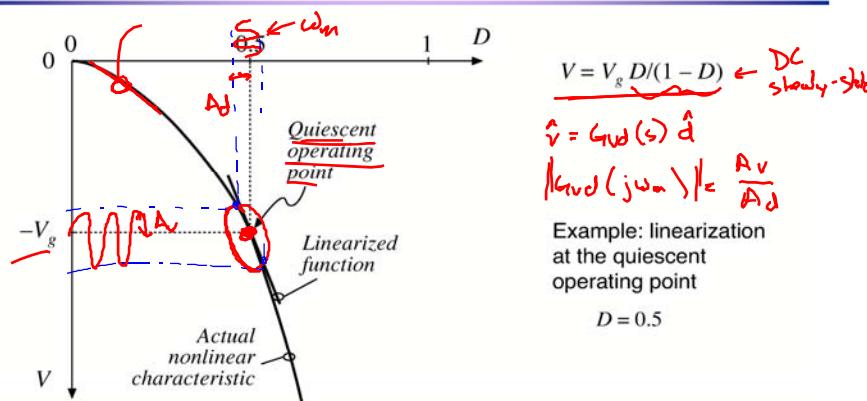Buck-boost converter: nonlinear static control-to-output characteristic



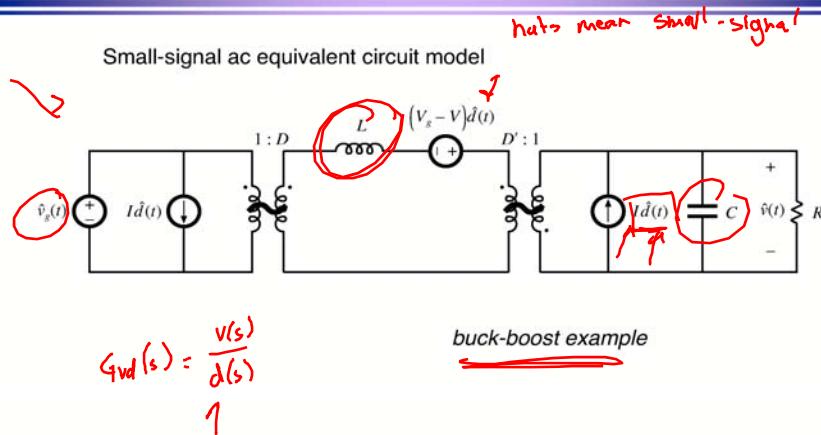Result of averaged small-signal ac modeling




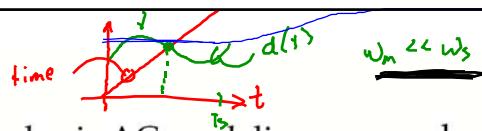

7.2. The basic AC modeling approach

$$0 < \frac{1}{2} d(t) T_S \quad \frac{d(t) T_S}{2} \leq t \leq T_S$$

Buck-boost converter example

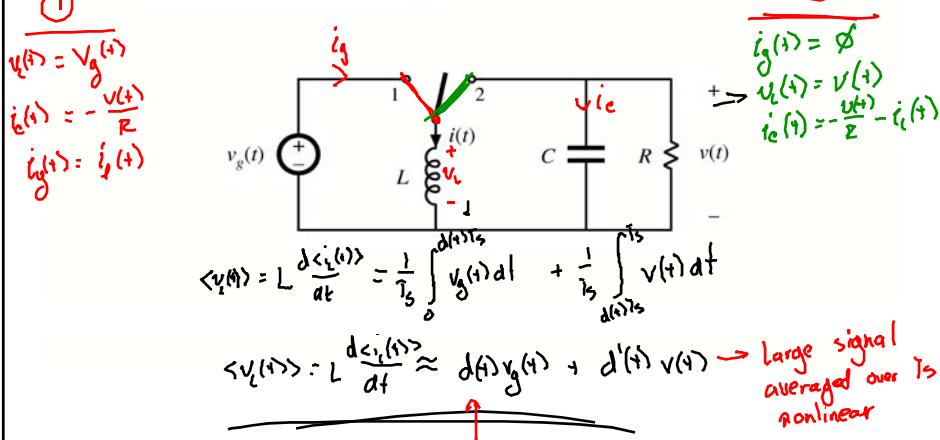

$$\langle v_L(t) \rangle = L \frac{d \langle i_L(t) \rangle}{dt} = d(t) v_g(t) + d'(t) v(t)$$

$$d(t) = D + \hat{d}$$

$$v_g(t) = V_g + \hat{v}_g$$

$$v(t) = V + \hat{v}$$