
Lecture 18: Z_{out} , Closed Loop Converters

ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville

Fall 2013


Announcements

-
- No office hours this afternoon
 - HW#7 due, solutions and HW#8 this afternoon

ECE 482: Power Electronic Circuits

Course reformatted for Spring 2014

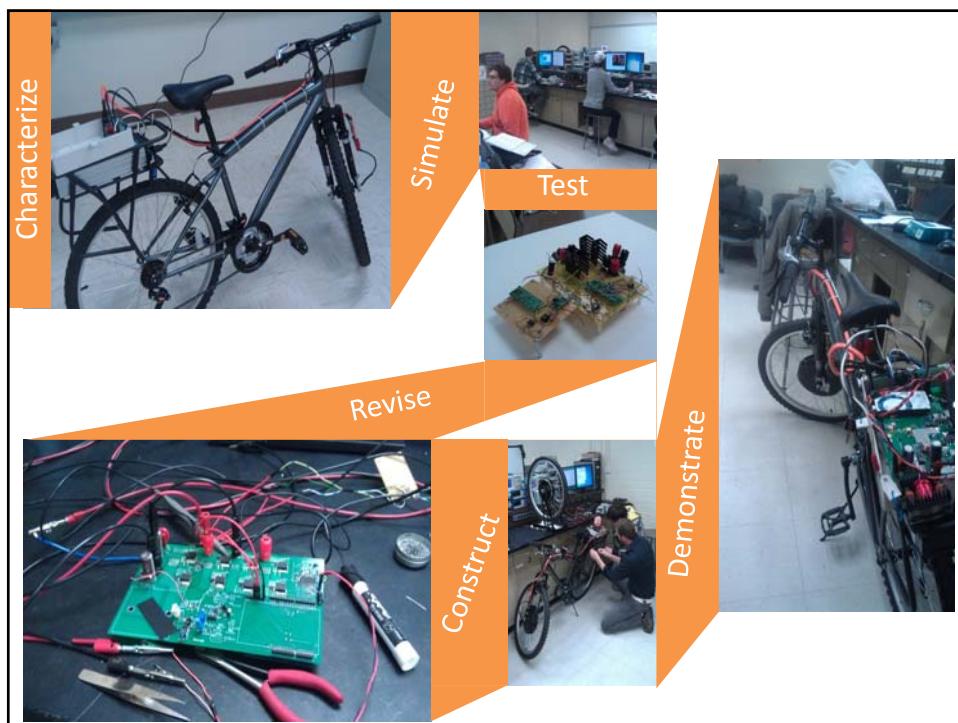- Design-oriented introduction to the analysis, modeling, and testing of power electronics
- Fabrication of the multiple switched-mode power converters
 - Analog and digital control systems
 - Realize a functioning, sub-kW electric vehicle
 - Compete to achieve best performance of EV drive train



ECE482 Schedule

	Monday	Tuesday	Wednesday	Thursday	Friday	Saturday
9am	ECE 482-001 29437 Class 9:05 am-9:55 am MINKAO 406		ECE 482-001 29437 Class 9:05 am-9:55 am MINKAO 406	9-11		ECE 482-001 29437 Class 9:05 am-9:55 am MINKAO 406

? ECE 433 @ 9:00 ?


Deviation of exact curve from magnitude asymptotes

$$\|G(j\omega)\| = \sqrt{\frac{1}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2} + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0}\right)^2}$$


At $\omega = \omega_0$, the exact magnitude is

$$\|G(j\omega_0)\| = Q \quad \text{or, in dB:} \quad \|G(j\omega_0)\|_{\text{dB}} = |Q|_{\text{dB}}$$


The exact curve has magnitude Q at $f = f_0$. The deviation of the exact curve from the asymptotes is $|Q|_{\text{dB}}$

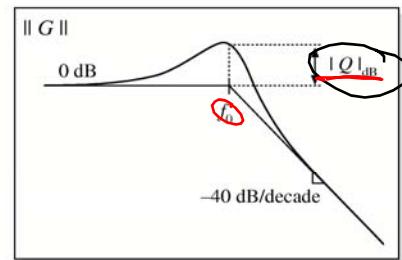


The Low-Q Approximation

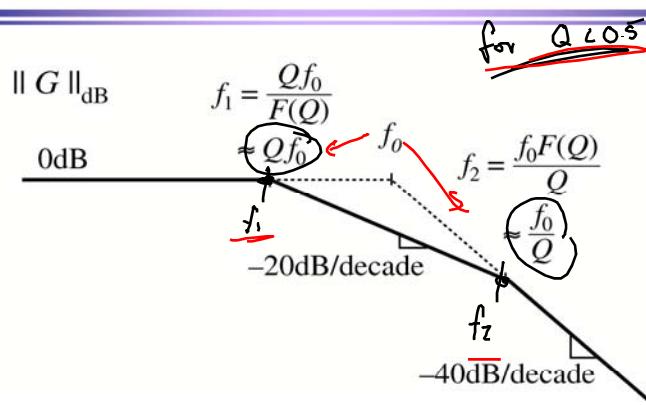


Summary: Asymptotes for Complex Poles

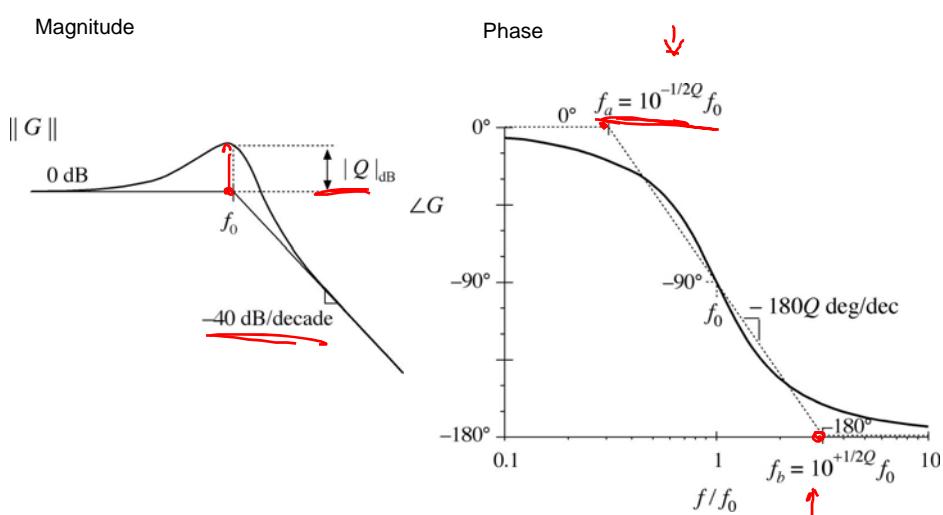

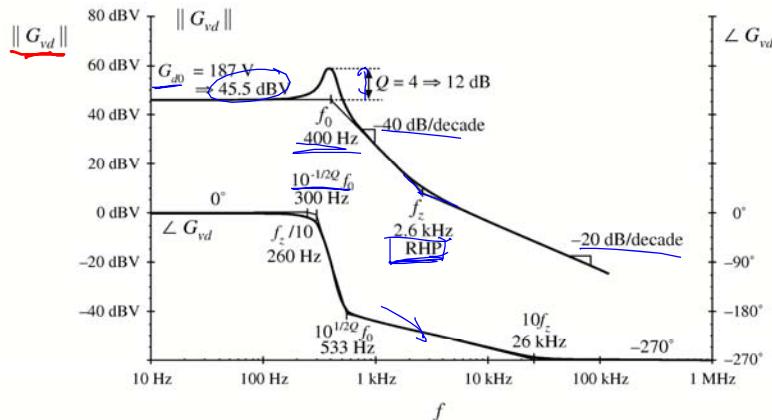
Bode plot: control-to-output transfer function



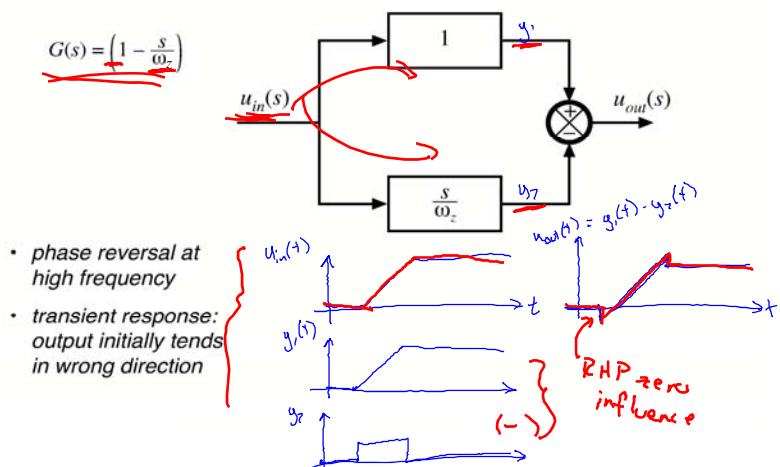
8.2.3. Physical origins of the right half-plane zero




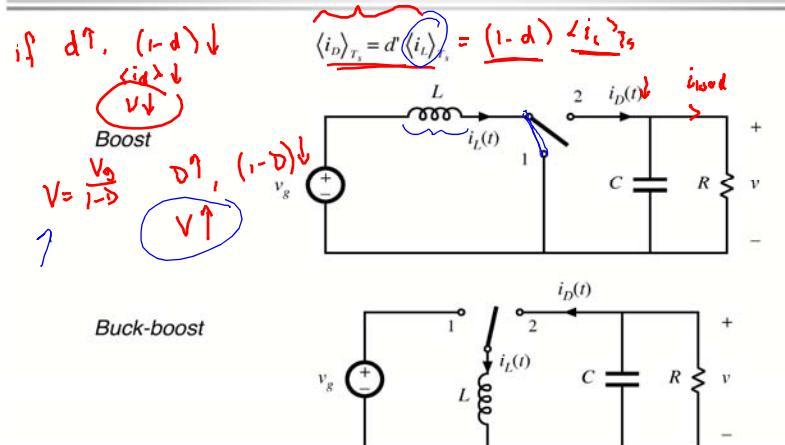
Two converters whose CCM control-to-output transfer functions exhibit RHP zeroes




Waveforms, step increase in duty cycle

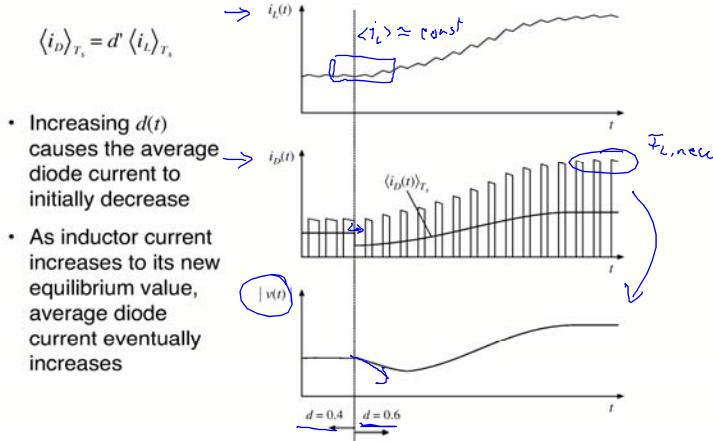

Buck-Boost Output Impedance

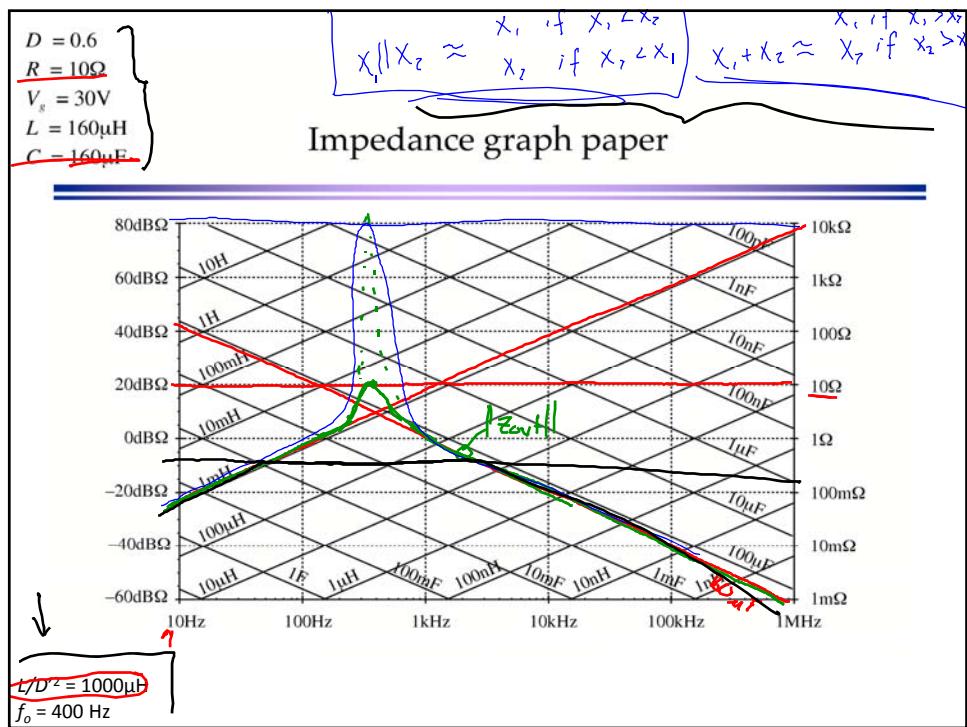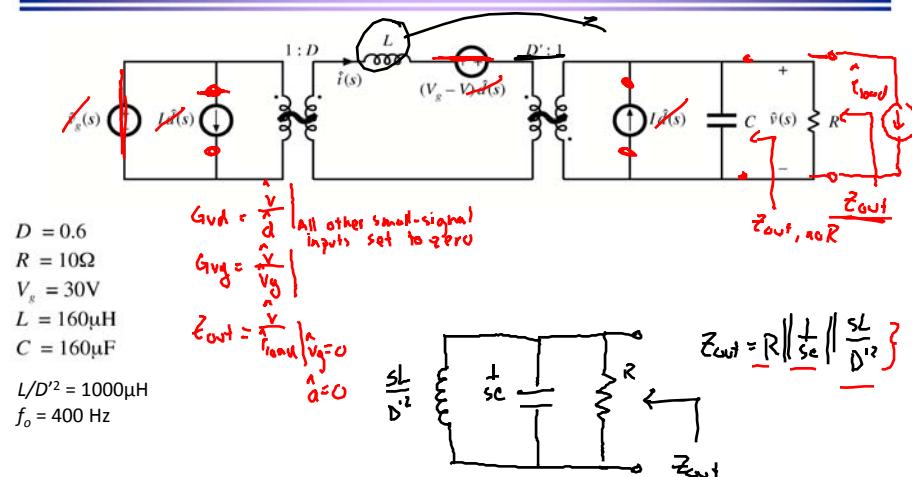

Nonideal Output Impedance

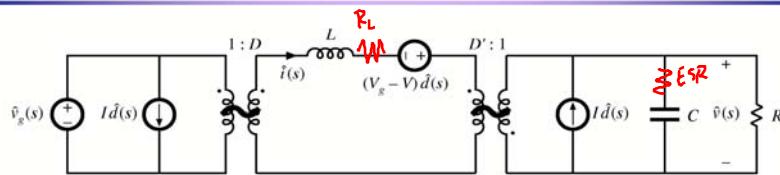

$$D = 0.6$$

$$R = 10\Omega$$

$$V_g = 30V$$

$$L = 160\mu H$$

$$C = 160\mu F$$

$$L/D'^2 = 1000\mu H$$

$$f_o = 400 \text{ Hz}$$

$$R_L = 316m\Omega = -10dB\Omega$$

$$\text{ESR} = 10m\Omega = -40dB\Omega$$

Nonideal Output Impedance


$$D = 0.6$$

$$R = 10\Omega$$

$$V_g = 30V$$

$$L = 160\mu H$$

$$C = 160\mu F$$

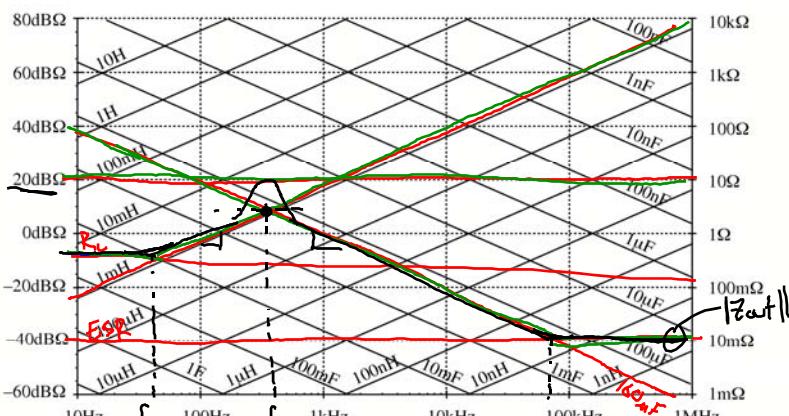

$$L/D'^2 = 1000\mu H$$


$$f_o = 400 \text{ Hz}$$

$$R_L = 316m\Omega = 10dB\Omega$$


$$\text{ESR} = 10m\Omega = -40dB\Omega$$

$$|Z_{out}| = \sqrt{\frac{j\omega L}{D^2}} \rightarrow \omega_L = \frac{RL}{L}, D^2 = \omega C, \omega_o = \frac{1}{\sqrt{LC}}$$

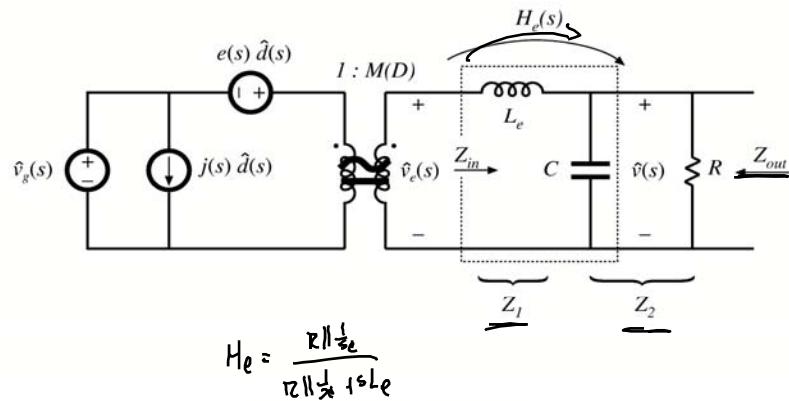Transfer functions predicted by canonical model




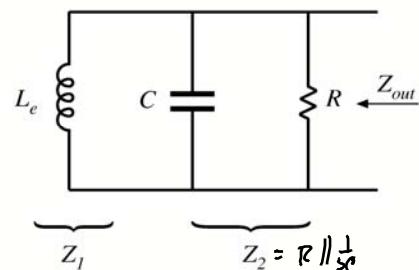Output impedance Z_{out} : set sources to zero




~~$$Z_{out} = Z_1 \parallel Z_2$$~~

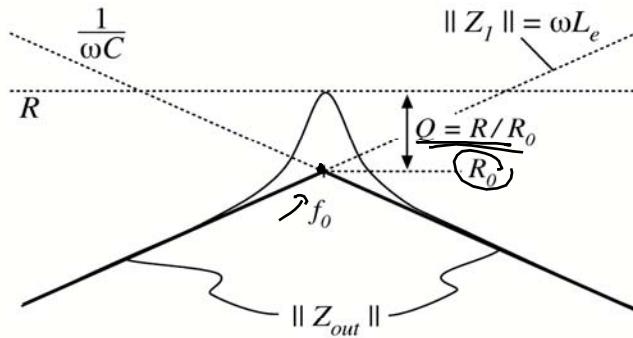
Graphical construction of output impedance



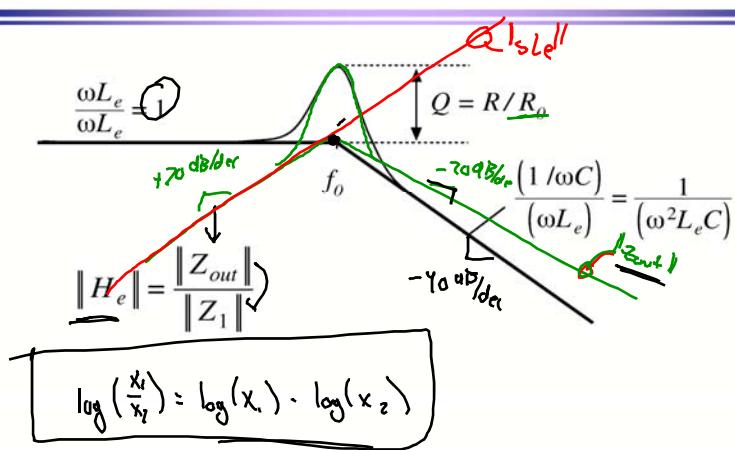Graphical construction of filter effective transfer function



Boost and buck-boost converters: $L_e = L / D'^2$

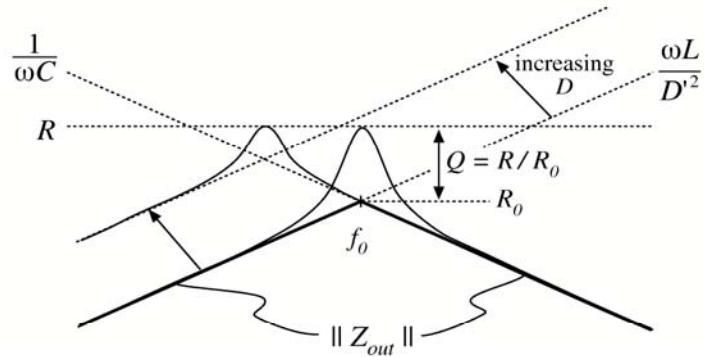

Chapter 9. Controller Design

9.1. Introduction

9.2. Effect of negative feedback on the network transfer functions

9.2.1. Feedback reduces the transfer function from disturbances to the output

9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop

9.3. Construction of the important quantities $1/(1+T)$ and $\underline{T/(1+T)}$ and the closed-loop transfer functions

Controller design

→ 9.4. Stability

- 9.4.1. The phase margin test
- 9.4.2. The relation between phase margin and closed-loop damping factor
- 9.4.3. Transient response vs. damping factor

9.5. Regulator design

- { 9.5.1. Lead (PD) compensator
- 9.5.2. Lag (PI) compensator
- 9.5.3. Combined (PID) compensator
- 9.5.4. Design example



Controller design

9.6. Measurement of loop gains




- 9.6.1. Voltage injection
- 9.6.2. Current injection
- 9.6.3. Measurement of unstable systems

9.7. Summary of key points

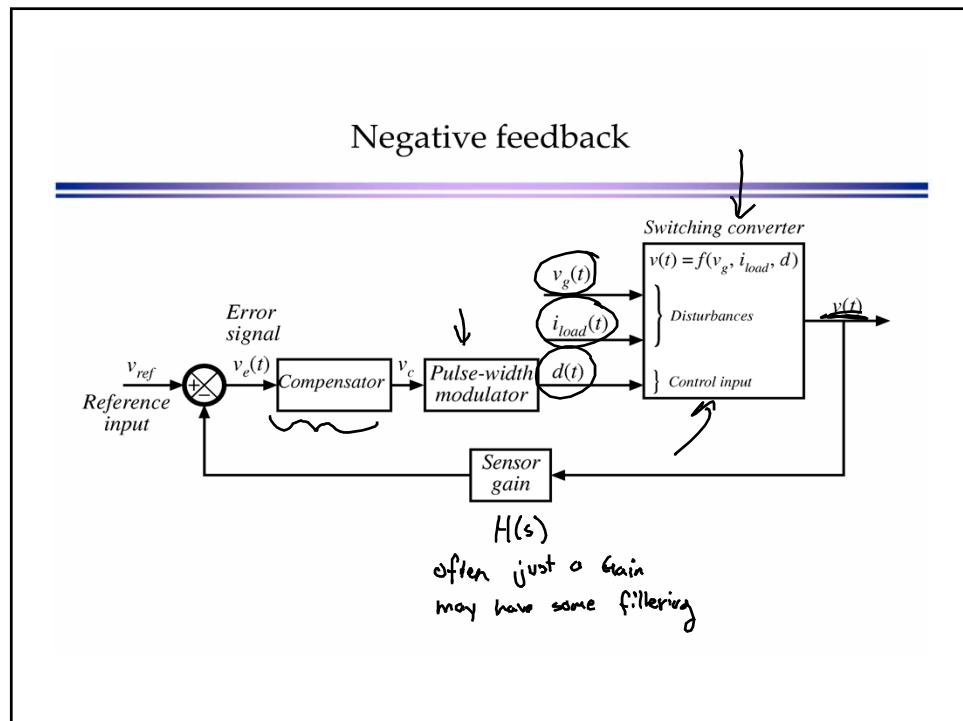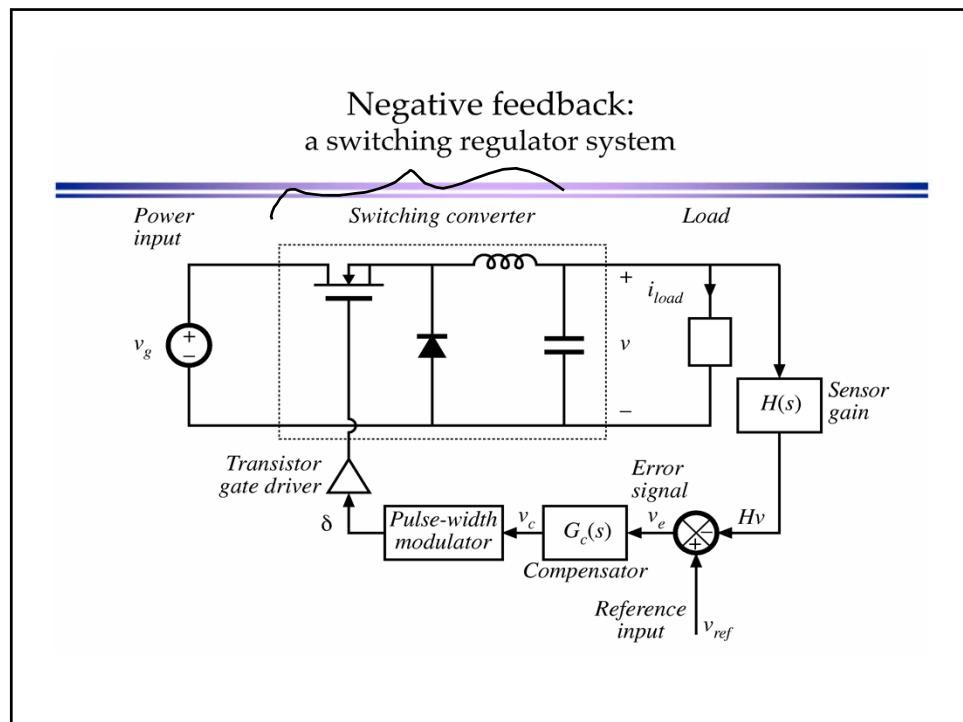

9.2. Effect of negative feedback on the network transfer functions

Small signal model: open-loop converter

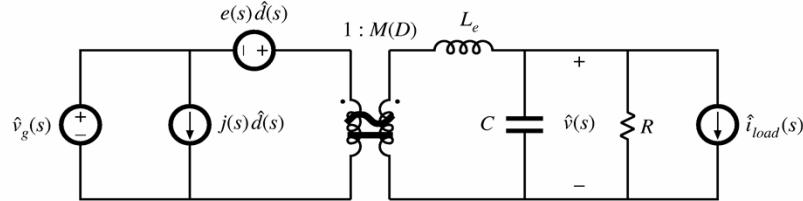

Output voltage can be expressed as

$$\hat{v}(s) = G_{vd}(s) \hat{d}(s) + G_{vg}(s) \hat{v}_g(s) - Z_{out}(s) \hat{i}_{load}(s)$$

where

$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\begin{subarray}{l} \hat{v}_g = 0 \\ \hat{i}_{load} = 0 \end{subarray}} \quad G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\begin{subarray}{l} \hat{d} = 0 \\ \hat{i}_{load} = 0 \end{subarray}} \quad Z_{out}(s) = - \left. \frac{\hat{v}(s)}{\hat{i}_{load}(s)} \right|_{\begin{subarray}{l} \hat{d} = 0 \\ \hat{v}_g = 0 \end{subarray}}$$


Voltage regulator system small-signal model

- Use small-signal converter model
- Perturb and linearize remainder of feedback loop:

$$v_{ref}(t) = V_{ref} + \hat{v}_{ref}(t)$$


$$v_e(t) = V_e + \hat{v}_e(t)$$

etc.

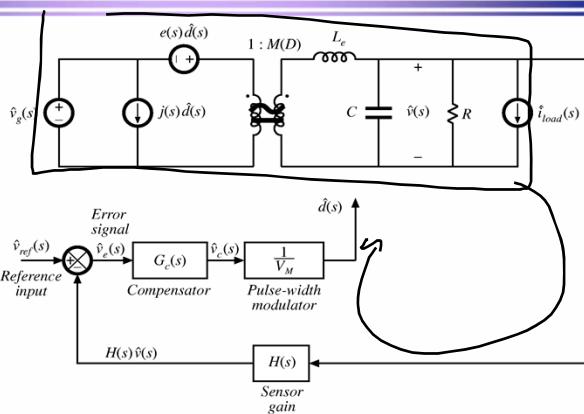


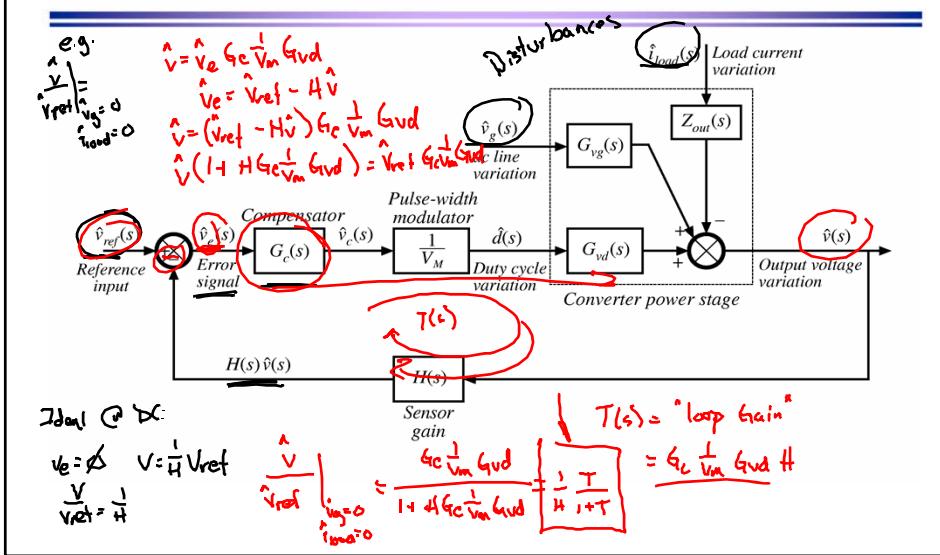(1) Very large DC gain gives


Regulator system small-signal block diagram



Closed Loop Reference-to-Output

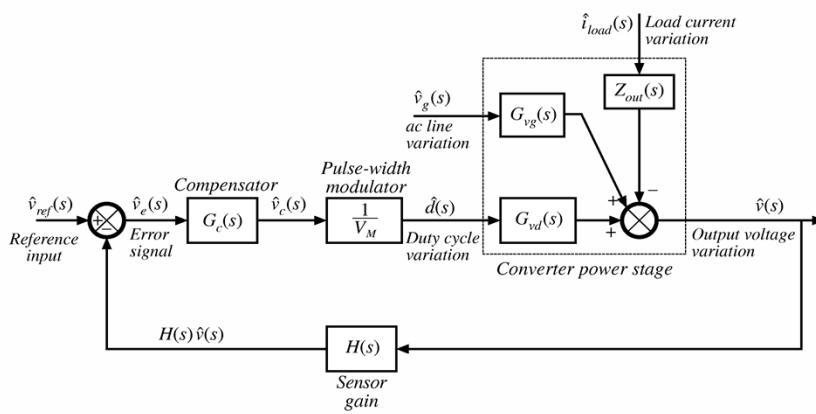

Closed Loop Disturbance-to-Output

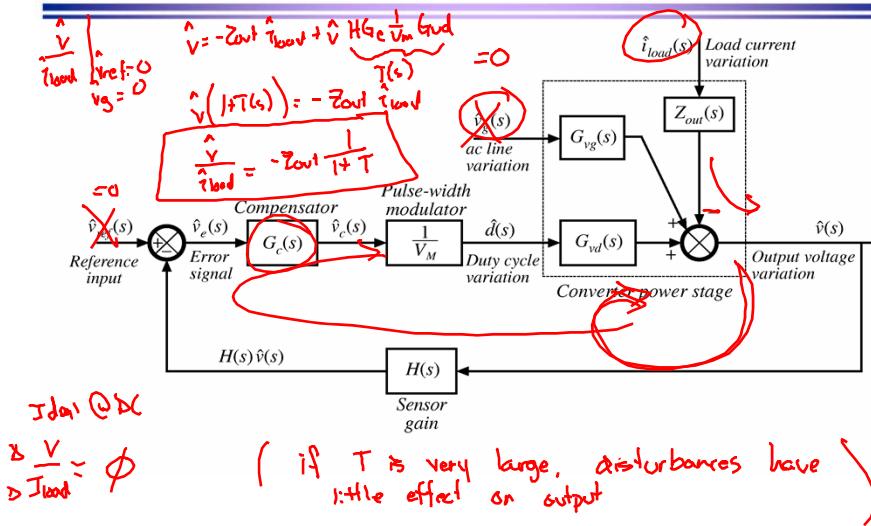

Solution of block diagram

Manipulate block diagram to solve for $\hat{v}(s)$. Result is

$$\hat{v} = \hat{v}_{ref} \frac{G_c G_{vd} / V_M}{1 + H G_c G_{vd} / V_M} + \hat{v}_e \frac{G_{vg}}{1 + H G_c G_{vd} / V_M} - \hat{i}_{load} \frac{Z_{out}}{1 + H G_c G_{vd} / V_M}$$

which is of the form

$$\hat{v} = \hat{v}_{ref} \frac{1}{H} \frac{T}{1+T} + \hat{v}_e \frac{G_{vg}}{1+T} - \hat{i}_{load} \frac{Z_{out}}{1+T}$$

such that T is "very large"

with $T(s) = H(s) G_c(s) G_{vd}(s) / V_M$ = "loop gain"

$$\hat{v} \approx \hat{v}_{ref} \frac{1}{H}$$

Loop gain $T(s)$ = products of the gains around the negative feedback loop.

9.2.1. Feedback reduces the transfer functions from disturbances to the output

Original (open-loop) line-to-output transfer function:

$$G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} \Big|_{\begin{subarray}{l} \hat{d}=0 \\ i_{load}=0 \end{subarray}}$$

With addition of negative feedback, the line-to-output transfer function becomes:

$$\frac{\hat{v}(s)}{\hat{v}_g(s)} \Big|_{\begin{subarray}{l} v_{ref}=0 \\ i_{load}=0 \end{subarray}} = \frac{G_{vg}(s)}{1 + T(s)}$$

Feedback reduces the line-to-output transfer function by a factor of

$$\frac{1}{1 + T(s)}$$

If $T(s)$ is large in magnitude, then the line-to-output transfer function becomes small.

Closed-loop output impedance

Original (open-loop) output impedance:

$$Z_{out}(s) = -\frac{\hat{v}(s)}{\hat{i}_{load}(s)} \Big|_{\begin{subarray}{l} \hat{d}=0 \\ v_g=0 \end{subarray}}$$

With addition of negative feedback, the output impedance becomes:

$$-\frac{\hat{v}(s)}{\hat{i}_{load}(s)} \Big|_{\begin{subarray}{l} v_{ref}=0 \\ v_g=0 \end{subarray}} = \frac{Z_{out}(s)}{1 + T(s)}$$

Feedback reduces the output impedance by a factor of

$$\frac{1}{1 + T(s)}$$

If $T(s)$ is large in magnitude, then the output impedance is greatly reduced in magnitude.

9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop

Closed-loop transfer function from \hat{v}_{ref} to $\hat{v}(s)$ is:

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \Big|_{\begin{subarray}{l} v_g = 0 \\ i_{load} = 0 \end{subarray}} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)}$$

If the loop gain is large in magnitude, i.e., $\|T\| \gg 1$, then $(1+T) \approx T$ and $T/(1+T) \approx T/T = 1$. The transfer function then becomes


$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \approx \frac{1}{H(s)}$$

which is independent of the gains in the forward path of the loop.

This result applies equally well to dc values:

$$\frac{V}{V_{ref}} = \frac{1}{H(0)} \frac{T(0)}{1 + T(0)} \approx \frac{1}{H(0)}$$

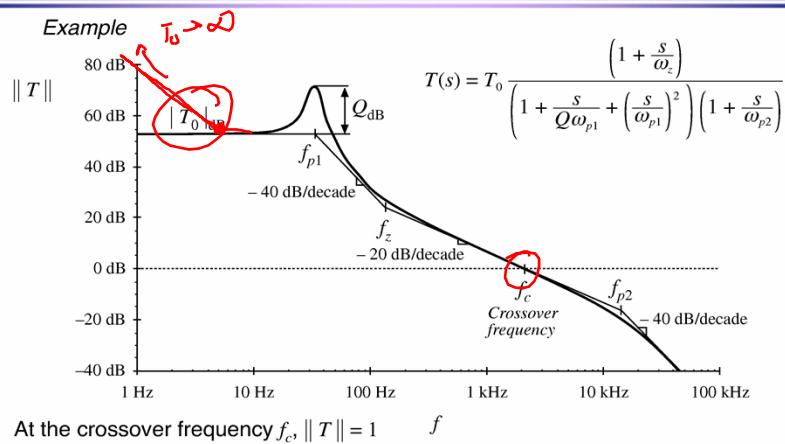9.3. Construction of the important quantities $1/(1+T)$ and $T/(1+T)$




Approximating $1/(1+T)$ and $T/(1+T)$

$$\rightarrow \frac{T}{1+T} \approx \begin{cases} 1 & \text{for } \|T\| \gg 1 \\ T & \text{for } \|T\| \ll 1 \end{cases}$$

$$\rightarrow \frac{1}{1+T(s)} \approx \begin{cases} \frac{1}{T(s)} & \text{for } \|T\| \gg 1 \\ 1 & \text{for } \|T\| \ll 1 \end{cases}$$

Example: construction of $T/(1+T)$

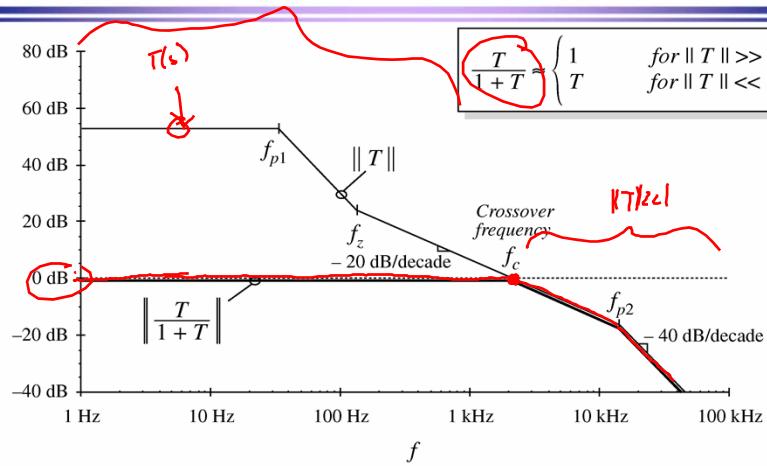

Example: analytical expressions for approximate reference to output transfer function

At frequencies sufficiently less than the crossover frequency, the loop gain $T(s)$ has large magnitude. The transfer function from the reference to the output becomes

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)} \approx \frac{1}{H(s)}$$

This is the desired behavior: the output follows the reference according to the ideal gain $1/H(s)$. The feedback loop works well at frequencies where the loop gain $T(s)$ has large magnitude.

At frequencies above the crossover frequency, $\| T \| < 1$. The quantity $T/(1+T)$ then has magnitude approximately equal to 1, and we obtain

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)} \approx \frac{T(s)}{H(s)} = \frac{G_c(s)G_{vd}(s)}{V_M}$$

This coincides with the open-loop transfer function from the reference to the output. At frequencies where $\| T \| < 1$, the loop has essentially no effect on the transfer function from the reference to the output.

Same example: construction of $1/(1+T)$

